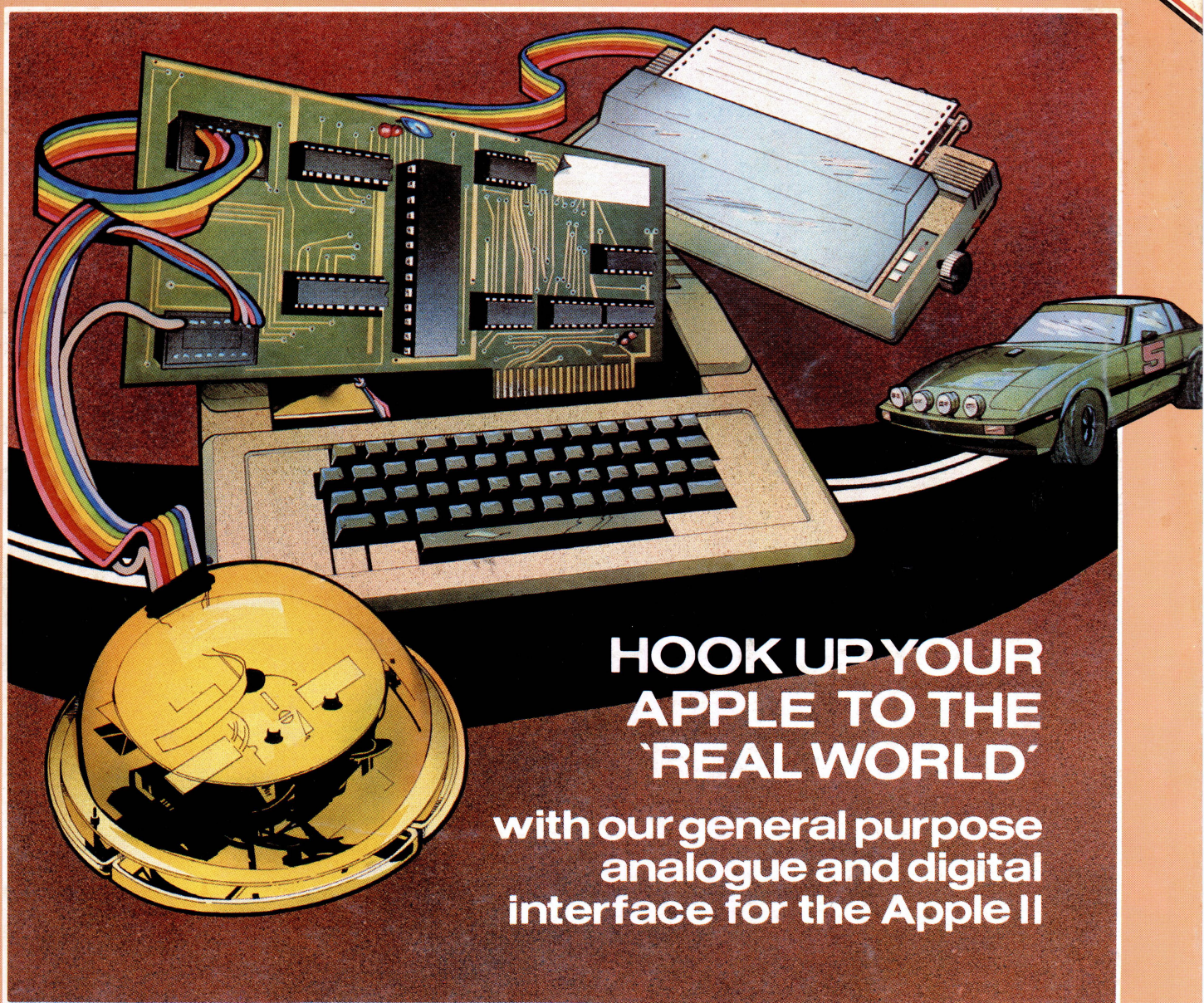


\$2.35\* NZ \$2.75 MARCH 1983



# ELECTRONICS TODAY INTERNATIONAL

**COMPONENT WALLCHART**  
from Jaycar  
**CHECK INSIDE**



## HOOK UP YOUR APPLE TO THE 'REAL WORLD'

with our general purpose  
analogue and digital  
interface for the Apple II

**PUSHBUTTON-OPERATED  
WINDSCREEN WIPER  
CONTROLLER**

**SCRs, triacs & power control**

**'Float' charger for  
NiCad batteries**

**Shure VI5 Type 5  
cartridge reviewed**

# Power you can taste.




Sony's new TA-AX5 amplifier with memory is a high fidelity feast.

Its multiple memory lets you create your own acoustic "flavours." Bass and treble tone settings, turnover frequencies, high and low filter are all programmable.

At a touch you can instantly recall the recipe for bittersweet country, hot 'n' spicy rock, or a well-seasoned Stravinsky. And electronic displays graphically show you everything the amp is cooking up.

Sony's Audio Signal Processor means that every function is touch controlled. This knifes through the usual maze of audio circuitry for a streamlined design of the future. Pure and simple, it sounds delicious.

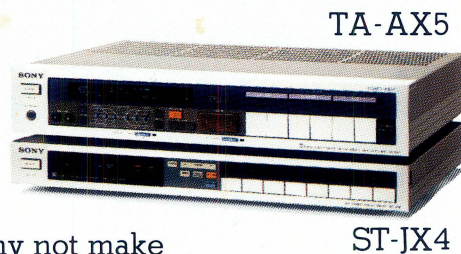The ideal companion for this tasty new amplifier is Sony's ST-JX4 synthesizer tuner. Why not make a reservation for two?



TA-AX5

ST-JX4

**SONY**  
THE ONE AND ONLY  
SON 0118

## advertisers

Adaptive Electronics	94
Applied Technology	85, 86, 87, 88
Altronics	6, 7, 29, 44, 45
AED	94
Audio Engineers	96
A & R Soanar	12
Convoy	102
Dick Smith	76, 77
Diggerman	42
Daneva Control	89
Elmeasco	33
Emona	64
Essex Laboratories	66
Ferguson	64
G.F.S.	60
Imark	42
Imark	42
Jaycar	14, 15, 22, 23, 34, 35, 49, 61, 62, 63
Kalex	65
K-Nar	79
Moss	50
Magraths	4
Magnetic Media	81
National Panasonic	99
Nicholas Kiwi	110
Pioneer	OBC
Pre-Pak	47
Q.T. Computers	92
Rose Music	115
Rod Irving Zip Out	67-74
Scientific Devices	12
Scientific Electronics	28
Sanyo	104
Sony	IFC
Truscotts	50
Vendale	80

# features

- 16 SCRs, Triacs and Power Control** Fundamentals of ac and dc power control  
**82 Robotic Arm Techniques** The fundamental techniques of robot arms

## projects and technical

- 24 335: Pushbutton-operated Windscreen Wiper Controller** Push-wipe, push, wipe-wipe  
**30 268: NiCad 'Float' Charger** Keep your NiCads in trim  
**36 654: General Purpose Interface for the Apple II** Analogue and digital  
**16 Circuit File: SCRs, Triacs and Power Control** Part 1, fundamentals  
**46 Ideas for Experimenters** Motor speed controller, output splitter  
**50 Shoparound** Where to buy kits, components, pc boards & panels for projects

## computing today

- 75 Dazzling Growth for Modems/Interfaces** IBM get 12% stake in Intel  
**36 654: General Purpose Interface for the Apple II** Analogue and digital  
**82 Robotic Arm Techniques** The fundamental techniques of robot arms  
**84 SME Systems Unicorn Reviewed** On the horn of a dilemma  
**90 Time Flies on the TRS-80C** Colour clocks for Tandy's "Coco"  
**92 '660 Software** CHIP 8 character generator and video message maker  
**95 The MicroBee Column** Bee-O-Rhythm reprint, integer accuracy, etc.

## sight & sound

- 97 Ortofon's 'Ortophase' cartridge** RCA plan release of CED in Europe  
**105 Pioneer A-8 Amp Re-tested** Distortion — how low can you go?  
**106 Shure V15 Type V Cartridge Reviewed** The microgroove is not yet dead

## news


- 8 News Digest**  
**10 Equipment News**  
**13 Component News**  
**59 Communications News**  
**78 Printout**  
**100 Sight & Sound News**

## contests and special offers

- 11 Special Offer — LCD Multimeter**  
 Super new Univolt DMM — under \$100!  
**48 Idea of the Month Contest**  
 New Prize — \$90 'Work Centre' from Scope
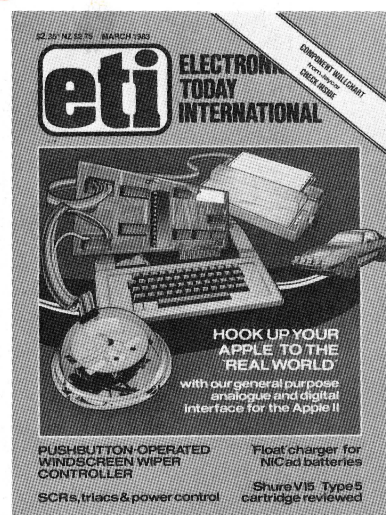
## general

- 51 Eight pages of Mail Order Books**  
**65 Letters**  
**96 Subscriptions, Back Issues, Order Form**  
**111 PCB page**  
**112 Mini-Mart**  
**114 Dregs**



This month's cover features the general purpose interface card for the Apple II, page 36. It shows some of the devices, such as the Tasman Turtle robot and slot car, which can be controlled.

Cover design: by Ali White

Registered by Australia Post —  
 Publication No. NBP0407  
 ISSN No. 0013-5216

SENDATA

BULK TAPE ERASER	BTE-1	\$30.15	Ⓢ
TAPE MAGNETISER	THD-1A	\$19.80	Ⓢ
ELECTRONIC DEMAGNETISER	THD-4	\$22.10	Ⓢ
TV TO STEREO ADAPTOR	TVA-1	\$11.35	Ⓢ
HEADPHONE EXTENSION 8-METRE CURL CORD FITTED WITH STEREO PLUG & SOCKET		\$5.65	Ⓢ

14-Way <b>98¢</b> per mtr.	36-Way <b>\$2.15</b> per mtr.
16-Way <b>\$1.12</b> per mtr.	40-Way <b>\$2.40</b> per mtr.
25-Way <b>\$1.75</b> per mtr.	50-Way <b>\$3.00</b> per mtr.

75 ohm Co-Ax. Air-Core	50¢ per mtr.
5 Core Shielded	\$1.40 per mtr.
Fig. 8 Shielded	40¢ per mtr.
2 x Fig. 8 Shielded	80¢ per mtr.
2 Core Shielded SC6	60¢ per mtr.
5 Core Unshielded MC7-5	40¢ per mtr.
8 Core Unshielded MC7-8	95¢ per mtr.

MANY MORE TYPES AVAILABLE. ALL CABLES TAX CODE(C)

## Great Value!

47,000 $\mu$ F 16 VOLT	\$8.20
100,000 $\mu$ F 16 VOLT	\$14.31
2,200 $\mu$ F 25 VOLT	\$6.60
10,000 $\mu$ F 25 VOLT	\$4.40
22,000 $\mu$ F 25 VOLT	\$7.29
47,000 $\mu$ F 25 VOLT	\$10.70
4,700 $\mu$ F 40 VOLT	\$4.30
10,000 $\mu$ F 40 VOLT	\$6.60
22,000 $\mu$ F 40 VOLT	\$9.18

PLUS TAX  
CODE C

- Reliable 300 BPS Full Duplex operation.
- High degree of ambient noise immunity.
- Power can be supplied from the terminal device or from a 9V plug pack.
- Provide either RS232 or TTL compatible signals.
- 25-way interface cable provided as standard.
- Unique design allows use with most modern handsets.

data integrity when both ends are acoustically coupled.

HM6116P-3	\$5.99	250 ns
MB2716	\$2.95	450 ns 16K EPROM
MB2764-30	\$10.96	300 ns 64K EPROM
MB8118	\$3.95	120 ns 16384 X 1 RAM
MM2708Q	\$2.80	450 ns 8K EPROM
MB8114 NLC	\$4.00	300 ns CERAMIC
HN462532G	\$7.00	450 ns 32K EPROM
S6834	\$13.30	512 x 8 EPROM
S6810	\$4.70	128 x 10 RAM 450 NS
MC68000-L8	\$99.95	8MHZ C.P.U.

PLUS TAX CODE C

For the first time, a microcomputer system desk with all the features you would look for is available at a **HOME COMPUTERIST TYPE PRICE!**

**\$174.69**  
Inc. tax/20% (B)

- Metal crush proof body.
- Replaceable nozzle – slim profile for high density PCB's.
- Self cleaning – plunger extends and ejects solder particles.
- Replaceable plunger washer

**\$15.50**  
+ B tax

**FERGUSON TRANSFORMERS**

PL15/5VA	\$5.85	PL18/40VA	\$12.15
PL24/5VA	\$5.85	PL24/40VA	\$12.15
PL30/20VA	\$10.80	PL24/60VA	\$15.75
PL12/20VA	\$10.80		

PLUS TAX CODE©

**Adjustable power  
and heat.**  
20 – 140 Watts  
**Fast heating**  
200°C  
– 500°C.



**SCOPE  
MINI  
SUPER  
SPEED  
SOLDERING  
IRON.**

Variable temperature  
10-75 WATTS.  
5 second heating.  
3.3 to 6 VOLT  
operation

Model MSB  
**\$26.60**  
+ B. tax.

**CUTS** holes  
any shape, any size over  $\frac{7}{16}$ "

**TRIMS**  
undersized holes to fit

**NOTCHES**  
clearance for plugs  
and wiring.

**\$14.60**  
+ B tax.

Model SSB  
24.00

TAX CODE

☐ (A) - EXEMPT      ☐ (C) - 20%  
☐ (B) - 7.5%      ☐ (D) - 32.5%

ELIZABETH ST

A BECKETT ST

LATROBE ST

SWANSTON ST

R.M.I.T.

N

**55 A'BECKETT STREET  
MELBOURNE, 3000.  
Tel (03) 347 1122  
Telex:AA31001**



**SUPER  
BARGAINS AT  
MAGRATHS**

# eti

## Editor

Roger Harrison VK2ZTB

## Technical Editor

David Tilbrook VK2YMI

## Assistant Editor

Jennifer Whyte B. App. Sc.

## Editorial Staff

Geoff Nicholls B.Sc./B.E.

Jonathan Scott

B.Sc./B.E. (Hons) VK2YBN

Jan Vernon B.A.

## Draughting

David Currie

## Advertising Production

John Gerrie

## Advertising Sales

Bob Taylor (Group Manager)

John Whalen (National)

## Art Staff

Ali White B.A.

Bill Crump

Githa Pilbrow

## Typesetting

Julie Hewlett

## Reader Services

Jane Nicholls

## Managing Editor

Collyn Rivers

## Acoustical Consultants

Louis Challis & Associates

## Editorial and Sales Office

140 Joynton Ave, Waterloo NSW 2017  
Ph: (02)663-9999; Tlx FEDPUB AA74488

**Melbourne:** Virginia Salmon and Mel Godfrey,  
150 Lonsdale St, Melbourne Vic. 3000.  
Ph: 662-1222; Tlx AA34340.

**Adelaide:** Admedia Group, 24 Kensington Rd,  
Rose Park SA 5067. Ph: 332-8144;  
Tlx AA82182.

**Brisbane:** Geoff Horne Agencies, 16 Bellbowrie  
Centre, Bellbowrie Qld 4070. Ph: 202-6813.

**Perth:** C. Thomas, Adrep Advertising  
WA 6000. Ph: 325-6395; Tlx ADREP PERTH.

**New Zealand:** Frank Hargreaves, Circulation  
Marketing Manager, c/- ACP, 4th Floor, Sun  
Alliance House, 42-44 Shortland St, Auckland.  
Ph: (9)30311.

**United Kingdom:** Australian Consolidated  
Press, Ludgate House, 107 Fleet St, London  
EC4A 2AL. Ph: 353-1040; Tlx: 267163.

**Japan:** Genzo Uchida, Bancho Media  
Services, 15 Sanyocho, Shinjuku-Ku, Tokyo  
160. Ph: 359-8866; Cable: Elbanchorito;  
Tlx: BMSINC J25472 Tokyo.


**USA:** Australian Consolidated Press, 21 East  
40th Street, (Floor 23), New York NY 10016.  
Phone: (212)685-9570.

Electronics Today International is published  
by The Federal Publishing Company Proprietary  
Limited, 140 Joynton Avenue, Waterloo NSW  
2017. (02)663-9999. Telex AA74488  
'FEDPUB'. This issue was printed by ESN,  
The Litho Centre of 140 Joynton Avenue,  
Waterloo NSW 2017. (02)662-8888. Distributed  
by Network Distribution Company.

\* Recommended retail price only
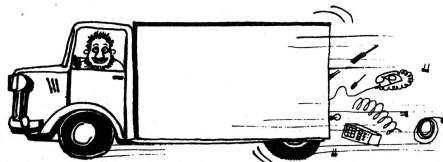
# WE'RE ON THE MOVE!

ETI is now owned and published by  
**The Federal Publishing Co.**  
and our new offices are located at  
**140 Joynton Ave, Waterloo NSW 2017.**  
Our new phone number, for all enquiries, is  
**(02)663-9999**  
Ask for Electronics Today Magazine.



## services

**Technical enquiries:** We can only answer readers' technical enquiries by **telephone after 4.30 pm Mondays to Thursdays**. The technical enquiry number is **(02)663-9999**. Technical enquiries by mail must be accompanied by a stamped, self-addressed envelope. There is no charge. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. We try to answer letters as soon as possible. Difficult questions may take some time to answer.

**General enquiries:** For enquiries about back issues, photostats of articles, artwork or submitting articles, call **(02)663-9999** or write to the address on this page.

**The publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.**


**COPYRIGHT:** The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, The Federal Publishing Company, or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

## next month

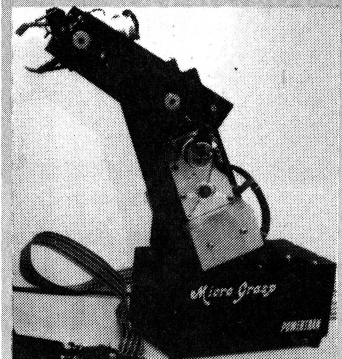

## BUILD A ROBOT ARM!

Last year we brought you the Tasman Turtle robot — this year, it's the Micro-Grasp robot arm! The next logical step (pardon the pun...) for hobby computerists is robotics. Next month's feature project is a robot arm that is jointed at the shoulder, elbow and wrist and includes a gripper. It can be interfaced to most computers. GET and PUT commands will never be the same again!

## THE WORLD OF SCANNING

There's a whole other world of communications beyond 'the shortwaves'. There are thousands of communications channels in the very high and ultra high frequency bands (VHF and UHF). Aircraft, carphones, customs, taxis etc. What's it all about? This article explains it in straightforward terms and looks at some of the equipment available for exploring the world beyond the shortwaves.

## RTTY CONVERTER FOR THE MICROBEE

This simple project allows you to hook up the MicroBee to a receiver and print radioteletype messages on the VDU screen. A simple bit of software (included in the article) does the decoding.

## HOW TO USE DVM MODULES

Part 1 of a two-part series giving dozens of applications and circuits for the popular liquid crystal display digital volt-meter modules like the DPM-05 and ETI-161 (from Aug. '82). Circuits include: ratiometric measurement techniques, thermometers, ohmmeters, voltmeters of all varieties, capacitance meters, frequency meters, etc.

## LIGHTWEIGHT HEADPHONES REVIEWED

Lightweight headphones are in big demand — especially for use with 'hip' stereo players and receivers. Louis Challis has reviewed seven models from the well-known European and Japanese manufacturers — and makes some interesting observations.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.

## Cat K6000 . . . . . \$39.50


★★★★★

## ★ ★ ★ ★ ★

- |                 |          |
|-----------------|----------|
| K6750 . . . . . | \$199.50 |
|-----------------|----------|

**\$10 DELIVERY ANYWHERE  
IN AUSTRALIA!**

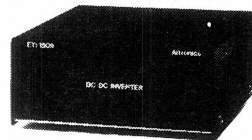K 6509 includes metal case . . . . . **\$39.50**



K 6505 Includes Metal Case . . . . . **\$37.50**

K6300 . . . . . \$4.95



K9653.....	\$44.50
------------	---------

K9668	\$48.50
-------	---------

K9760	\$17.50
-------	---------



K 9644 . . . . . (See ETI Oct 82) . . . . . **\$169.50**

K 9645 Modem Option I . . . . . **ONLY \$30.00**

**For Universal Brush Type Motors  
Drawing up to 3 amps.**



K 6005 . . . . . VALUE \$13.95

Combination Colour Organ and Light Chaser. Four channel colour organ. Internal microphone or connect to speakers for colour organ operation. (The lights connected to each channel pulse in beat to the music proportional to portion of frequency spectrum concerned.) Four chaser modes forward and reverse. Output lamp load capacity a massive 2400 watts — that's 100 party globes. Full instructions and every last nut and bolt included. Great for parties, shop signs, display windows etc.

K5800.....\$89.50

**et-160**

**POWER SUPPLY**

**OVERLOAD**

13.8 Volts

7.5 Amps Continuous

10 Amps Intermittent

**OUTPUT**

**POWER**

(See ETI JULY 1982)

- \* Output voltage — 13.8 Vdc.
  - \* Output current — 7.5A continuous  
10A intermittent
  - \* Regulation — 0 to 7.5A : 50mV
- Save the expense of a mains powered rig.  
Kit complete in every way.*

K3250. . . . .	\$84.00
----------------	---------

+ 5 Volts @ 3 Amps, + 12 Volts @ 2 Amps,  
- 12 Volts @ 200 mA



- + 5 Volts for memory, CPU all Micro's.
- + 12 Volts for RS232 interfaces etc.
- 12 Volts handy for additional hardware using OP Amps.
- ★ Uses TO-3 Regulators + 5 V and + 12 V.
- ★ Heavy Duty Fan Type Heatsink.
- ★ Complete Boxed Kit with Delux Front Panel.

**NOTE:** This unit has enough grunt to power most small disk drives.

K 3350	\$59.50
--------	---------

**The Altronics Kit includes all components for the modifications, detailed by Electronics Australia Feb. 1983.**

Yes, it's bad enough paying \$2.00 a gallon for petrol without wasting a fortune on an out of tune engine. Fit this transistor assisted ignition kit in minutes and start saving money from the very next petrol stop. Easy to build!

K 4010 .....\$35.00

*Protect Your Valuable Car and Contents*

Circuit detects minutest voltage drop across vehicle's battery earth strap, tripping the alarm ★ uses Milspec LM394 ★ Quality diecast box ★ genuine fujitsu relay ★ automatic reset after pre set time period ★ installs in minutes ★ includes dash mounting LED-flashes to deter thieves.

K 4330 ..... \$29.50

A staggering number of cars are stolen each year. Install an Altronics Alarm Kit and yours won't be one of them.

Circuit operates by detection of voltage drops in the electrical system and features a flashing LED for dash mounting as a deterrent to would be vandals and thieves.


K 4084 . . . . . \$12.00

### Ingeniously simple circuit indicates battery low-okay-overcharging, ETI Kit



K4320.....	\$4.95
------------	--------

## HAS MANY APPLICATIONS

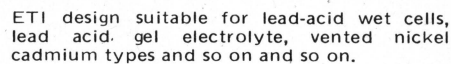

Unit covers range of 10.5v to 15v

### Determine battery condition instantly

### Easy to Build!

K4326. . . . . \$9.50

Handy little test gadget will enable you to check voltage drops, on/off battery charge voltages and resistances in any vehicle electric systems.

**Unit indicates:** reversed polarity ★ voltage drops of 0.5V or less ★ voltage between 12V and 13.5V ★ voltages above 13.5V ★ resistance below 150R ★ resistance 10K or above ★ resistance 50K or above.

### Polarity and Overvoltage Protection Complete Boxed Kit

K4334.....\$14.50

Unit suitable for 1, 2, 3, 4, 6 and 8 cylinder vehicles, 2 stroke or 4 stroke ★ fully compatible with conventional, CDI and transistorized ignition systems ★ includes protection circuitry to prevent noise and high voltage spikes from the points and coil circuit damaging the electronics. ★

**Display flashes when over-revving occurs**  
**\* only 3 connections required to electrical system.**

*Check The Performance of Your Vehicle  
At A Glance!*

K 4324	\$24.50
--------	---------

**For address, phone number  
and despatch details see our  
advertisement on page 45.**

# Australian laser is really hot stuff

The brightest laser in the world can be found at the Australian National University. The laser research group, within the Research School of Physical Sciences, is using the laser for probing the behaviour of matter under extremely hot and energetic conditions.

The laser can deliver radiation of unparalleled intensity to a target, vaporising it, stripping electrons from atoms, transforming it instantly to a superhot cloud of ionised atoms and free electrons known as plasma.


When laser light was first produced from a ruby crystal about 20 years ago no one was quite sure how to make the best use of it. Laser light has some unique characteristics, including extreme purity of colour and the property known as 'coherence', which means, among other things, that a beam of laser light is precisely aligned. It doesn't spread out and can be focussed down to a very fine point.

At the ANU the laser light (actually infra-red radiation) is produced by rods of silicate glass doped with the rare element neodymium. When the beam is focussed through a high quality lens system it forms a spot with a

diameter of only two microns and a power density of more than  $10^{18}$  watts/sq cm. This is comparable to all the sunlight falling on the earth's surface being funnelled onto one square centimetre.

The laser research group, which is part of the Department of Engineering Physics, has been studying the behaviour of high temperature plasmas. At very high intensities the stream of photons in the laser beam exerts a pressure on the plasma, stretching it out of shape. The ANU team has taken holograms which show the remarkable effects of 'light pressure'.

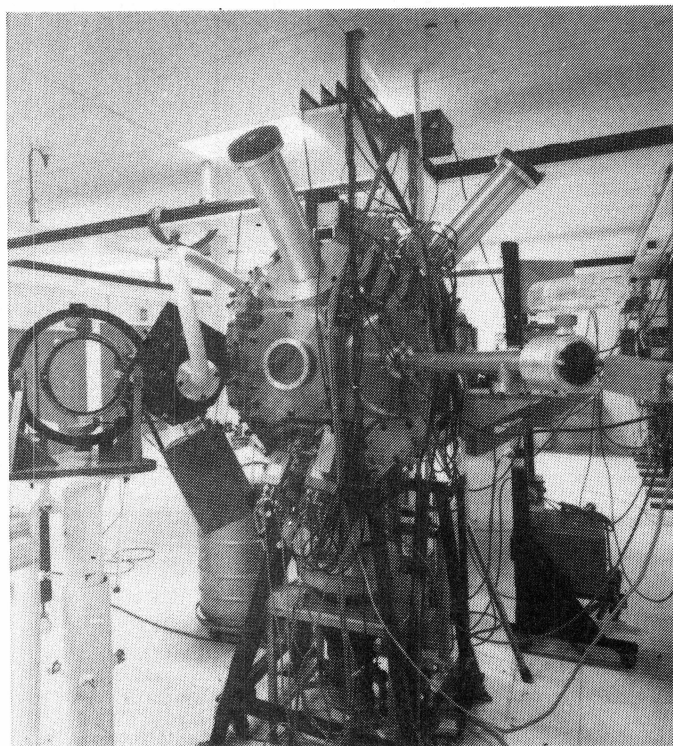The fact that the hot though very shortlived plasma emits x-rays leads to the possibility of studying very fast chemical reactions by irradiating the reacting chemicals with the very short pulses of x-rays. The ANU team is currently engaged in a joint study of this method with



Chamber pot. Target chamber for studying plasma reactions.

chemists from the University of Sydney.

The next step for the laser group will be the substitution of phosphate glass for the silicate glass now used in the laser. This would produce a laser with a power density of about two and a half times what they are achieving at present, with the possibility of transforming the energy of the plasma into matter through 'pair-production'. So there's more excitement to come.


## High-res contact film

**Allmakes Micrographics, suppliers of duplicating films for the micrographics industry, has introduced to their line of products a complete range of Teledyne Post's new Ultra-Fi non-silver diazo duplicating film.**

Ultra-Fi is a high resolution diazo contact film for use in graphic arts, litho duplicating and ideally suited for printed circuit photo tooling. Because Ultra-Fi is an organic dye based emulsion rather than the usual silver emulsion, the film can be for all practical purposes considered grainless, giving extremely high resolution in the order of 500 lines/mm.

Ultra-Fi has a tough, scratch resistant surface on a polyester base which is available in a range of thicknesses. Unexposed Ultra-Fi can be safely handled in normal room lighting so a darkroom is not necessary nor does Ultra-Fi require darkroom chemicals.

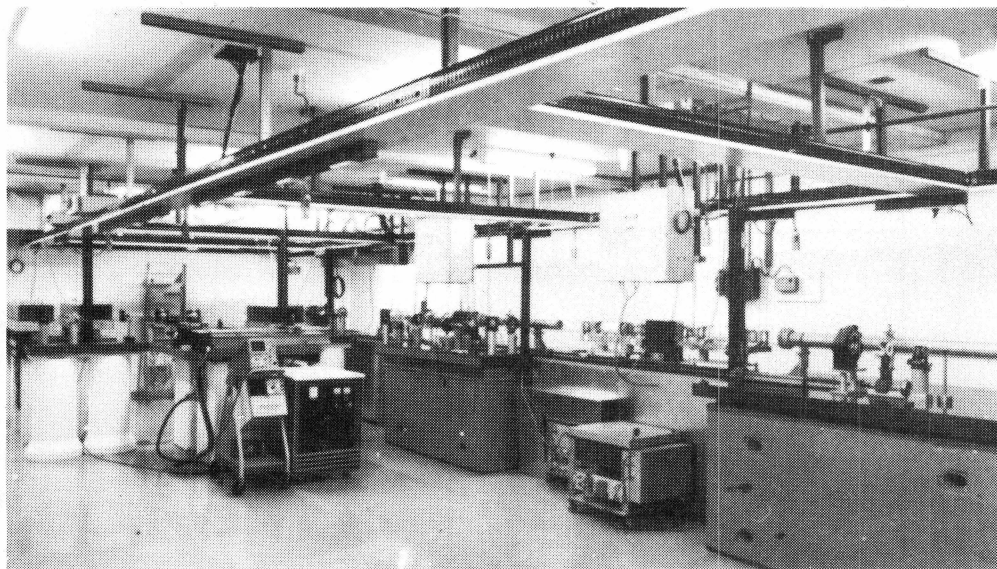For more information contact **Allmakes Micrographics Pty Ltd, 34 Balcombe Rd, Mentone Vic. 3194. (03)584-7811.**



Hot shot! Overview of the ANU's powerful infra-red laser system.

## Graphical symbols for electrotechnology

The Standards Association of Australia has published new editions of three parts of its standard dealing with graphical symbols for electrotechnology.

They are AS 1102.3 — resistors, capacitors and inductors, AS 1102.5 — semiconductor devices and AS 1102.8 — location symbols, power and communication installations for buildings and sites. These incorporate amendments to their previous editions, new symbols, the updating of cross references to other Australian standards

and the re-numbering of symbols in accordance with the current IEC method.

Copies of AS 1102.3 and AS 1102.8 can be purchased from any SAA office at a cost of \$9.80 plus a \$1.50 postage and handling charge. AS 1102.5 costs \$8 plus a \$1.50 postage and handling charge.

## Precision pliers

Two pliers in the Channellock Little Champ range are the 43G needle nose and the 41G diagonal cutters.

These general purpose precision pliers are drop forged from high grade steel and polished to a bright finish. Handles are of dipped blue plastic cushion grip.

The complete range of Channellock electronics pliers includes extra long needle nose, flush cutting sharp nose diagonal spring pliers, end cutting nippers, flat nose and round nose pliers, needle nose with side cutters, transverse end cutters and curved needle nose pliers. They are available from Selectronic Components Pty Ltd, 25 Holloway Drive, Bayswater



Vic. 3153. (03)762-4822.



## Put it there, mate!

If you put your mind to it, there are a lot of humorous, and somewhat dubious, uses for 'Locoman'. But even though it works with great precision it is an industrial robot, so it can't be expected to cope with all the strange quirks of one's imagination.

Locoman, the second robot from the British company Pendar Robotics Ltd, is controlled by a standard microprocessor. The carbon fibre double pantograph arm is powered by three electric stepping motors which move it in x, y and z axes at speeds up to one metre per second. It can carry loads up to four kilos and return to any taught or programmed position with an accuracy of  $\pm 0.05$  mm.

Designed by Birmingham University, the robot can store up to 200 instructions and can operate either continuously or begin each cycle in response to an external command, such as the arrival of the next part in an assembly process.

## New address for Australian School of Electronics

The Australian School of Electronics Pty Ltd has moved to 219 Balaclava Rd, Caulfield Vic. 3161.

The new numbers are (03) 523-5622 or (03)523-7544. The address for correspondence has not been changed. P.O. Box 108, Glen Iris Vic. 3146.

## Singapore electronic equipment on display

Four Singapore manufacturers of electrical and electronic equipment will display products at the ASEAN Trade Fair in Perth in April.

Portable radios, mono and stereophonic cassette recorders and clock radios will be exhibited by Advanced Concept Technology.

Leo Electronics, which specialises in electronic motor car accessories, will display a full range of its products, including an auto-scanner, multifunction digital clocks, monitoring gauges for battery, headlights, fluid and brakes and wiper control systems.

A compact instant water heater will be exhibited by Prime Electrical Products.

Teco Electric and Machinery, a well-established motor manufacturer and supplier, will exhibit industrial induction



motors, such as the single and three-phase squirrel cage induction motors, and an ac/dc magnetic brake motor, a kiln vibration motor, a helical brake geared motor and an air curtain.

For more information contact John Yarwood, 21 Clontarf St, Sorrento WA 6020. (09)447-1642.



## Blind electronics enthusiasts

Blind people interested in electronics can now check their own projects and equipment.

The students of the Footscray Institute of Technology, assisted by staff lecturer Mr. Michael Fawcner, have developed a multimeter and a standing wave ratio meter which measure with

audible signals rather than the conventional needles and lights.

Members of the Radio Enthusiasts Club of the Blind are now using the multimeter which features positive and negative overload sensing. The standing wave ratio meter alerts the user to faults within a transmission line or antenna.

## Intelligent logic troubleshooting system

Hewlett-Packard's new logic troubleshooting system, the HP 55005A, uses 'built-in intelligence' to guide manufacturing and service personnel quickly through sophisticated checkout procedures.

A specialised software package runs on an HP-85 personal computer which controls an HP 5005B programmable signature multimeter. The HP-85, acting through the signature analyser, learns about the product under development by probing the circuit. A nodal map is created and the circuit connections of the product under test are recorded before it is handed over to manufacturing.

The HP 55005A also allows the engineer to specify critical verification nodes (V-nodes) which can be used later by the system to prompt the manufacturing technician to measure the V-nodes first in the checkout procedure.

Since the troubleshooting system learns the circuit through probing, a new program is not needed for each product. Also, no IC-device libraries must be maintained because the system needs only the IC-pin interconnections.

There are two probing modes of the troubleshooting system. The signature-dictionary mode

permits a technician to do free-hand probing through the pc board or backplane under test, searching for incorrect or unstable signatures. The user doesn't need to look at the display of the computer or signature analyser as cues come from a series of beep tones generated by the HP-85. In the backtrace mode the user is prompted to probe a set of points in sequence, tracing a trail of bad signatures back to the bad circuit node.

HP 55005A output documentation of both the circuit database and the checkout process comes almost automatically. A report is printed of the product's signatures by node, by IC and pin number or by troubleshooting tree.

The HP 5005B signature multimeter can also be used for analogue troubleshooting to measure and report frequencies, time intervals, peak voltages, dc voltages, differential voltages and resistance.

For more information on this product contact **Hewlett-Packard Australia Ltd, 31-41 Joseph St, Blackburn Vic. 3130. (03)890-6351.**




## Semi universal insulation displacement connector press

Scope Laboratories has released a termination station Model DILP, complete with tooling, that can handle any insulation displacement plug, socket and 'D' connectors with flat tops and 0.3" or 0.6" pitch top inserted pins (max. 50 pin).

Aimed at the medium sized firm who requires the security of multi-sourcing without the cost and inflexibility of acquiring several custom tooled terminating presses.

The Scope Model DILP, complete with tooling, sells for under \$200 through all major electronic trade distributors. Weighing under 3 kg, the press is bench mounted and can be quickly converted to a 225 kg Arbour Press.

For further information contact

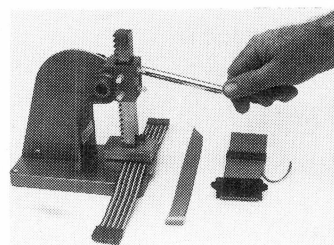

**Scope Laboratories, 3 Walton St, Airport West NSW 3042. (03)338-1566.**

## What's new from Emona?

**Two frequency counters, a digital LCR meter, a triggering oscilloscope and two function generators are now available from Emona Enterprises.**

The frequency counter GFC-8010F has a frequency range from 1 Hz to 120 MHz with a sensitivity of less than 20 mV from 10 Hz to 100 MHz and less than 30 mV in the 100 MHz to 120 MHz range.

The frequency counter GFC-8100F has a range of 1 Hz to 1 GHz with sensitivities from less than 10 mV at the low end of the range to less than 50 mV at the high end. Both frequency counters have a 8-digit LED display.



The digital LCR meter LCR-2430 has a 5-digit display for LCR and 4-digit for D and Q. The test range is R: 1M —


99.999M, L: 0.2 mH — 9999.9 H, C: 0.1 pF — 99999 UF, D: 0.0001 — 9.999, Q: 0.01 — 999.9.

The triggering oscilloscope GOS-2310 has a sensitivity of 5 mV to 5 V/div, a bandwidth of dc or 2 Hz to 10 MHz and a sweep rate of 10 ms to 0.1 us/div.



The function generator GFG-8015F and the digital display function generator

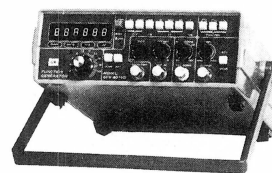GFG-8016D have a frequency range of 0.2 Hz to 2 MHz, an output level of greater than 20 V<sub>p-p</sub> open circuit and greater than 10 V<sub>p-p</sub> into 50 ohm and a VCF of 0 — 10 V.



These instruments can be obtained from **Emona Enterprises Pty Ltd, 661 George St, Haymarket, Sydney NSW 2000. (02)212-4815.**

# 3½-DIGIT LCD DIGITAL MULTIMETER

by Univolt

- 8 FUNCTIONS 23 RANGES
- PUSHBUTTON OPERATION
- DC VOLTS TO 1 kV, AC VOLTS TO 750 V
- RESISTANCE FROM 200 OHMS TO 20M
- AUTO-RANGING ON AC/DC VOLTS & RESISTANCE
- AC & DC CURRENT TO TEN AMPS
- FINGER-GUARDS ON PROBES & SHROUDED PLUGS FOR MAXIMUM SAFETY
- TRANSISTOR GAIN MEASUREMENT
- TRANSISTOR CLIP LEAD INCLUDED
- PROTECTIVE CARRY CASE INCLUDED

Here is an opportunity to buy a versatile, top-line multimeter at a very good price, complete with carry case, special probes, leads and spare fuse.

**OFFER PRICE**  
**\$97.50 tax paid**  
**\$84.38 tax exempt**



**SPECIAL  
ETI READER  
OFFER**

This instrument would normally sell for about \$130 retail.

This is an entirely new multimeter from Univolt and this offer is being made as a special promotion for the Model DT-860 which has only just been released here. It is a 3½-digit liquid crystal display instrument featuring 23 ranges in eight functions, three functions being auto-ranging. It is a handheld instrument but comes with a tilt stand to prop it up from the bench. The display features 12 mm high digits, plus value and function indicators (volts, ohms, ac, low battery, -ve, etc). The front panel is functional and well laid out. The test probes supplied have shrouded plugs to prevent accidental finger contact for safety when using the instrument on high voltage circuits, plus the probes have finger guards for further safety and convenience. A strong, synthetic leather carry case is included. The instrument is powered by two 1.5 V 'AA' cells. We have tested a sample DT-860 in the ETI Lab and found it met specifications, functioned well and was generally easy to use. It appears to be a robust, well-made device. Any technician, engineer, serviceman or hobbyist would find it a very useful instrument.

This offer is made by BENELEC PTY LTD (Incorporated in NSW). ETI is acting as a clearing house for orders. All mail orders will be despatched by certified post. Please allow up to four weeks for delivery. Offer closes 31 March 1983.

## INSPECTION

You can inspect one of these multimeters during office hours at ETI's Sydney and Melbourne offices:

Sydney: \_\_\_\_\_ Melbourne: \_\_\_\_\_  
4th Floor, 15 Boundary St 23rd Floor, 150 Lonsdale St  
Rushcutters Bay Melbourne

## HOW TO ORDER YOUR MULTIMETER

Fill out the coupon below and enclose a cheque, bank cheque or money order for the amount required made out to BENELEC PTY LTD.

If you are not paying sales tax, please quote your sales tax number on the coupon, where indicated, or for schools, colleges or other educational institutions, enclose a sales tax declaration on your letterhead.

SEND completed coupon to:

UNIVOLT MULTIMETER OFFER  
c/o ETI MAGAZINE, 140 Joynton Ave, Waterloo NSW 2017.

## DT-860 UNIVOLT LCD DIGITAL MULTIMETER

### SPECIFICATIONS

- **3½-digit** liquid crystal display; 12 mm high digits.
- **dc volts** 200 mV-1000 V (max) **auto-ranging**; resolution: 0.1 mV @ 200 mV, 100 mV @ 200 V.
- **ac volts** 2 V-750 V (max.) **auto-ranging**; resolution: 1 mV @ 2V, 100 mV @ 200 V.
- **resistance** 200 ohms-20 M **auto-ranging**; resolution: 0R1 @ 200R, 10k @ 20M.
- **ac/dc current** 2000 uA/200 mA/10 A; overload protected; resolution: 1 uA/100 uA/10 mA.
- **hFE** 0-1999 ( $\pm 10\%$ ) with  $V_{ce} = 1.2 V$ ,  $I_b = 1 uA$ .
- **continuity** buzzer sounds at resistances under 20 ohms ( $\pm 10R$ ).
- **diode check** reads forward drop in millivolts at 0.6 mA test current; 1 mV resolution.
- **warranty** three months normal parts and labour warranty.
- **miscellaneous** input impedance 10M minimum; input capacitance less than 50 pF; polarity: '-' indicated automatically; overrange indicated by '1' or '-1'; size: 145(D)x82(W)x28(H) mm; weight: 180 g excluding batteries; protection provided by 0.2 A, 250 V fast blow fuse.

### ACCURACY

- **dc volts** 200 mV;  $\pm (0.5\% \text{ of rdg} + 2)$   
2 V/20 V;  $\pm (0.5\% \text{ of rdg} + 1)$   
200 V/1 kV;  $\pm (0.7\% \text{ of rdg} + 1)$
- **ac volts** 2 V/20 V;  $\pm (0.5\% \text{ of rdg} + 5)$   
200 V/750 V;  $\pm (1.0\% \text{ of rdg} + 5)$
- **dc current** 2 mA/200 mA;  $\pm (1.0\% \text{ of rdg} + 1)$   
10 A;  $\pm (1.2\% \text{ of rdg} + 1)$
- **ac current** 2 mA/200 mA;  $\pm (1.2\% \text{ of rdg} + 5)$   
10 A;  $\pm (2.0\% \text{ of rdg} + 5)$
- **ohms** 200R;  $\pm (0.75\% \text{ of rdg} + 3)$   
2k/20k/200k;  $\pm (0.5\% \text{ of rdg} + 2)$   
2M;  $\pm (1.0\% \text{ of rdg} + 2)$   
20M;  $\pm (2.0\% \text{ of rdg} + 3)$

max. open circuit voltage = 1.5 V on 200R range  
max. open circuit voltage on other ranges = 0.65 V

## STOP PRESS

We will be moving premises sometime in February. Please phone 662-8888 if you want to inspect a DT-860 in Sydney to check which address we'll be at.

PLEASE SEND ME . . . . . Univolt Model DT-860 multimeter(s) @ \$84.38 each, excl. tax or \$97.50 each, inc. tax.

Post and handling \$2.50

Sales Tax No . . . . . (if applicable)

Offer closes 31 March 1983


I enclose \$ . . . . . total Cheque or Money Order No. . . . . Signature . . . . .

Name . . . . .

Address . . . . . Postcode . . . . .

# SOANAR

## LEADS WITH FIBRE OPTICS

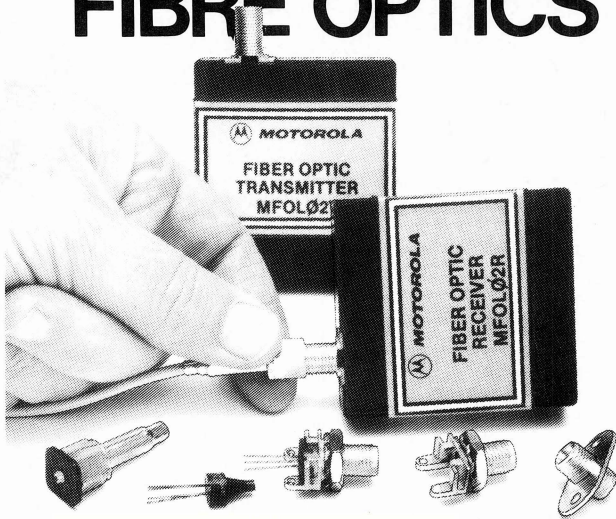


### OPTICAL FIBRE CABLES

Are now available in continuous lengths in multiples of one metre to a maximum of 1 kilometre. The 125 Micron Fibre in 2.7mm diameter cable is designed for high flexibility and tensile strength and can be supplied plain or fitted with connectors at the factory.
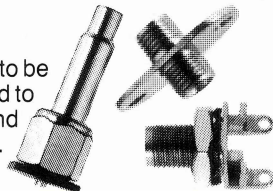
### CONNECTORS

Enable fibre optic cables to be joined together or coupled to transmitters, receivers and other active components.



### CUTTING & STRIPPING TOOLS

**S311S** — Cuts optical fibre squarely for a mirror-like surface.

**S211** — Removes covering from optical fibre.



### ACTIVE COMPONENTS

Emitters, Detector/Preamplifiers, Transmitting and Receiving Modules suitable for medical electronics, industrial controls, security, computer and peripheral systems.



Technical Information Available on Request

# SOANAR


**SOANAR ELECTRONICS PTY. LTD.**  
INCORPORATED IN VICTORIA

**30-32 Lexton Road, Box Hill, Vic., 3128, Australia.**  
VICTORIA: 840 1222 QUEENSLAND: 52 1131  
N.S.W.: 789 6733 WEST AUST: 381 9522  
Sth. AUST: 42 8918 TASMANIA: 31 6533



# National

## A NEW WAVE IS ON THE HORIZON

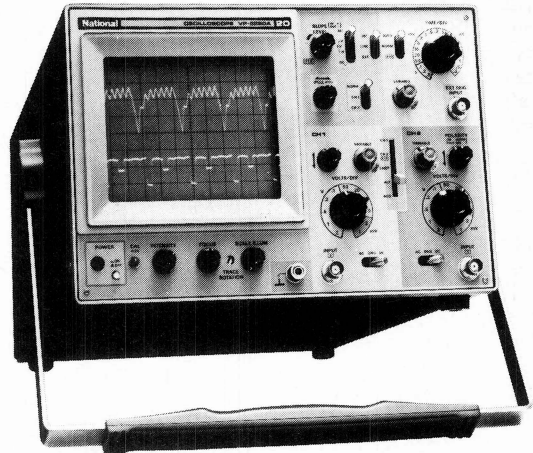

### Available in four models these low cost oscilloscopes feature:

- 15-20-30 MHZ.
- 1mV/Div sensitivity
- Stable automatic trigger 'AUTO FIX'
- Full range of triggering mode
- Bright and sharp CRT with Auto Fix
- TV(V) and TV(H) sync separator circuit
- Rectangular tube, illuminated internal graticule (VP-5220A and VP-5231A)
- Built-in delay line for observation of pulse transient (VP-5231A only)
- High reliability—MTBF 15,000 hours

**National have a wide range of scopes—to 300 MHz. Please call or write for further information**

**...FROM \$399.00 (NOT INC. S.T.)**

Probes supplied as standard accessory



**bankcard**  
welcome here

**SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.**

2 JACKS ROAD, SOUTH OAKLEIGH, VICTORIA, 3167.

TELEPHONE: 579 3622

P.O. BOX 63, SOUTH OAKLEIGH, VICTORIA, 3167. TELEX: AA32742

CABLES: DEVICES MELBOURNE

31 HALSEY ROAD, ELIZABETH EAST, S.A., 5112.

TELEPHONE: (08) 255 6575

35-37 HUME STREET, CROWS NEST, N.S.W., 2065.

TELEPHONE: (02) 43 5015

## Rotary switch — in a DIL package!


A new rotary switch in a dual-in-line package has been released by The New Ohto Co, represented here by Associated Controls.

The switch incorporates a well-proven contact construction, utilising 'knife edge high pressure' contacts to ensure reliable operation and long life, according to the makers.

The high pressure edge contact, it is claimed, will break any film formed by oxidation or sulfuration. Life expectancy is quoted as 20 000 cycles or more.

The miniaturised switch allows high density packing on a pc board. Pin spacing is standard 2.54 mm (0.1") and the switch can be inserted in a standard IC socket, if necessary.

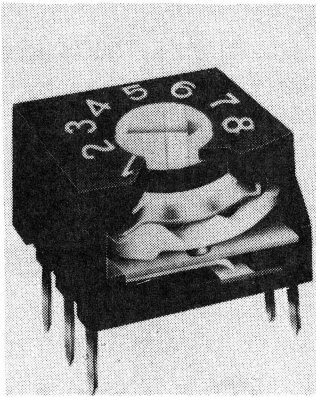The terminals are all moulded into the fully-sealed housing which prevents ingress of moisture, solder flux or other contaminants. The switch can be flow-soldered and is immersion washable.



Associated Controls has also released the 'K' series DIL switches from The New Ohto Co, having similar features.


Further details from Associated Controls Pty Ltd, P.O. Box 21, Padstow NSW 2211. (02)709-5700.

## Crimp versions of F161 connectors

Crimp versions have been added to Philips F161 range of subminiature rack and panel connectors.

These new versions accept AWG20 to AWG30 solid or stranded wire, are internationally standardised and are suitable for all areas of industry, especially telecommunications and data processing applications.

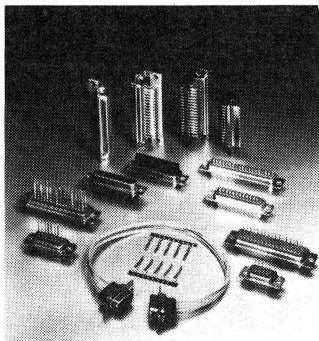Each connector consists of a glass-fibre filled thermoplastic insulating block into which crimpable pins and sockets are inserted. The contact pins and sockets are made of copper alloy and are selectively gold plated on



a nickel layer.

A modern, semiautomatic electric stripping/crimping machine (speed approx. 2000 crimps/h) is available.

For further information contact Elcoma, 67 Mars Rd, Lane Cove NSW 2066. (02)427-0888.


## Probe case and hardware

The GSC — CTP1 probe case, complete with associated hardware, is ideal for housing signal injectors, logic probes, small counters, voltage and resistance probes and continuity checkers.

The moulded grey plastic case measures 147 x 25 x 18 mm and is supplied with a one meter long two wire lead with a moulded strain reliever and alligator clips attached and a nickel plated screw-in probe tip. Also included

are a mating tapped hex probe tip connector, assembly screws and a blank pc board pre-cut to size.

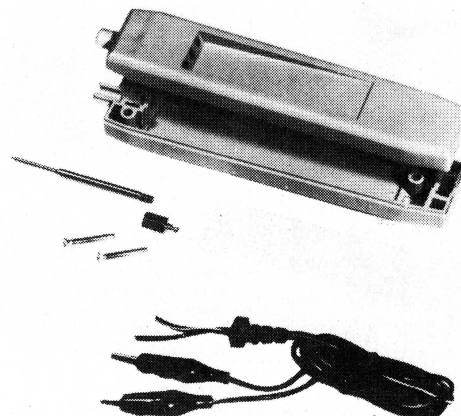These are available from Commquip Pty Ltd, Unit 2, 9 Douglas St, West Perth WA 6005. (09)328-9451.



## 3½ digit voltmeter IC

A 3½ digit voltmeter IC with the facility to remove the zero errors of external signal conditioning circuits is now available from Ferranti Electronics, Fields New Rd, Chadderton, Oldham UK.

Called the ZN451, the chip does not include auto-zero switches, but two logic outputs are provided to control external auto-zero switches. Op-amps and other signal conditioning circuits can thus be included inside the auto-zero loop and have their errors removed by the ZN451 digital auto-zero system. This allows the chip's basic  $\pm 199.9$  mV full-range scale to be reduced to as low as  $\pm 1.999$  (one microvolt resolution) while still retaining the auto-zero facility by using a low cost op-amp with a gain of 100.

In addition, the combination of charge-balancing measurement

technique and digital auto-zero offers good linearity, a well-defined conversion time and freedom from the layout-dependent stray capacitance problems sometimes associated with dual-slope designs.

Other features of the ZN451 include on-chip clock and precision bandgap reference, under-range/over-range, display hold facility and direct drive of liquid crystal display.


For further information contact the British High Commission, Commonwealth Avenue, Canberra ACT 2600. (062) 73-0422.

## Slotted optocoupler/ interrupter modules

Motorola has a series of six slotted optocoupler/interrupter devices which represent drop-in replacements for the G.E.H21 and H22 series.

These devices consist of a gallium arsenide infrared emitting diode facing a silicon NPN photo transistor, encapsulated in a molded plastic housing. A slot in the housing between the emitter and the detector provides a means of interrupting the optically coupled signal by means of an externally introduced opaque material such as a card, tape or disk.

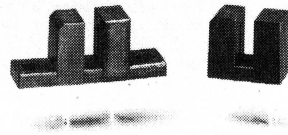The slotted optocouplers are widely used in video games,



copy machines, keyboards, card readers, garage door openers, tape drives and floppy and hard disk drives. Other applications include position and motion indicators, digital pressure sensors, scales, industrial machine controls, limit switches etc.

These devices are available from Motorola Semiconductor Products, 250 Pacific Hwy, Crows Nest NSW 2065. (02) 438-1955.

# MARCH MAD


▶▶▶▶▶▶▶▶▶▶ JAYCAR'S FIRST "MARCH MADNESS" SALE. EVERYONE HAS HAD ONE.

MORE HAVE BEEN FOUND!!

Last month we did not advertise the GE Smoke and Burglar Alarms. This is because our stocks were getting very low and we did not expect to have any left by February.

We were more surprised than anyone when we found another consignment arrive on our front door! This is great news as we have never seen a greater bargain then these products — as thousands of you will already testify! The Smoke Detector was a flop at \$49.50 (see story below) BUT at \$14.50 its the bargain of the century. So too the Burglar Alarm — at about ½ THE PRICE of its closest competitor!!
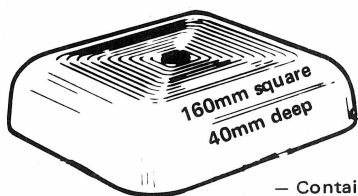
## final runout of GE Consumer Products Burglar Alarm



Cat. LA5006

FROM \$12.50

- Contains Americium 241 Ionization Chamber
- Contains very loud solid state buzzer
- 12 month factory warranty.


One of the greatest consumer flops of the last decade was the Ionization Chamber Smoke Detector. Even though it is a brilliant product (reliable compact, easy installation, fail-safe etc) it just did not sell. Human nature being what it is finds safety-oriented products just not worth the investment. We all know that accidents and fires never happen to US!! As smoke is the greatest killer in a fire, the market research gurus thought that such a product would have a wide appeal. When they were \$49.50 no-one wanted them. The price fell to a very reasonable \$29.50 and still they stayed on the shelf. We have now been instructed to clear them for less than ½ of \$29.50.

QUANTITY PRICES

1-\$14.50: 2-5 \$13.50ea: 6-10 \$13.00ea: 10 up \$12.50ea

GENERAL  ELECTRIC

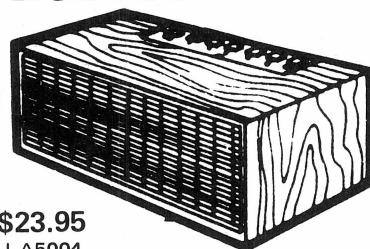BURGLAR ALARM SLASHED!!!  
HUGE SCOOP PURCHASE —  
ONCE SOLD FOR OVER \$100




FROM \$23.95

Cat. LA5004

Amazingly low price for a full feature ultrasonic proximity/burglar alarm. + Completely self contained + 12 month manufacturer guarantee + Instant or delayed alarm + Handsome imitation woodgrain + Cabinet measures 180(w)x85(h)x100(d)mm + Programmable multi-code disable switch + Single 9V Alkaline battery\* lasts one year + unit beeps when battery gets low + Contains receiver element designed for greater sensitivity without false triggering + Uses state-of-the-art LSI circuitry + Worth the money in parts alone + Comprehensive 24 page manual included + Comes complete with 4 window deterrent stickers + Absolutely no installation needed \* Battery extra.

1-\$29.50: 2-5 \$25ea: 6-10 \$24.50ea: 10up \$23.95ea

### BACK TO TECH BREADBOARDS

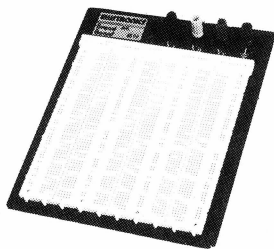

Many of the Tech Colleges and CAE's are specifying plug-in bread boards as training aids in their Electronics and Radio courses. At around March Breadboards get VERY scarce as thousands of students buy all available stocks. Jaycar has stocked up especially this year but we may be out of stock later in March if you don't act quickly.

Cat. PB8810	WB-DN	100 holes
		\$2.95
Cat. PB8812	WB-TN	640 holes
		\$8.95
Cat. PB8814	WB-2N	840 holes
		\$12.95
Cat. PB8816	WB-4N	1680 holes
		\$24.95
Cat. PB8818	WB-6N	2420 holes
		\$39.95

### FABULOUS SENNHEISER HD-40



\$29.95

PRE-SALES TAX INCREASE  
PRICE

Sennheiser — the name that means the ultimate in Headphone technology. These are high quality West German made units that are now available at a bargain basement price. As used in the 1st class section of the TAA Airbus and all Qantas 747's (1st class). Naturally the frequency response is a flat 20-20KHz. Impedance is 8 ohms.  
Cat. AA2010

### LIQUID CRYSTAL DISPLAY



We have a small number of specific liquid crystal displays in stock. Each unit described below is supplied with a specific data sheet for that product as well as application notes re: drive requirements, multiplexing etc.

TYPE 5301A-51 This is a 3" high Starburst display which enables you to display all letters of the alphabet and 0-9 digits. Each segment is addressable. A large, high contrast display can be achieved. Normally around \$25 each a small quantity available at \$10 each  
ONLY \$10 EACH — Cat. ZM9010

TYPE H5545-54 This is a 4 digit x 0.5" high display with "plus", "minus" and "arrow" annunciators, with 4 decimal point locations. Normally \$20 each — ONLY \$7.50 each Cat. ZM9011

TYPE L-5640 — 51 & 54 This is basically identical to the H-5545 except that the digits are 0.6" high with a colon as well as the decimal point. Normally \$22 each ZM9012(51) & ZM9013(54) \$9.50 ea

TYPE L-563A-51 A 3 ½ digit 0.6" high 12 hour clock display with AM/PM annunciator and colon.  
Normally \$15 EACH — NOW ONLY \$7 EACH Cat. ZM9014


# NESS SALE!

NOW IT'S YOUR TURN TO SAVE!!

## MARCH IS ALSO WELLER MONTH

Weller

Buy The  
Best!

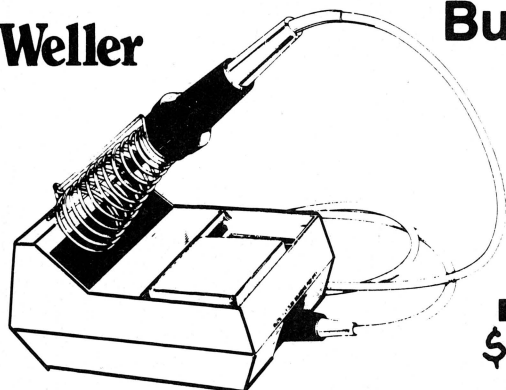

PRE-TAX

**\$74<sup>50</sup>**

### Controlled Output Soldering Station

What better way to start off the New Year than with a brand new Soldering Station!

Jaycar is one of the few resellers left who have stuck with Weller soldering equipment. Why? Because it is still simply far and away the best Temperature-Controlled soldering equipment available. Weller is consistent with Jaycar's philosophy of only selling quality merchandise. You may save around \$10-\$15 if you buy an Asian made "Electronic" Soldering Station. But remember this MOST "Electronic" Soldering Stations get out of calibration. OK if you have a thermocouple probe temperature meter to recalibrate it every 6 weeks or so.

But if you don't have a thermocouple, consider the WTCPN. The WTCPN Station uses an exclusive world-patented principle which guarantees that the temperature of your iron will not drift once you have set it up.

But the best news is the price. 7½% sales tax went on this equipment on January 1 this year. Jaycar still has stock at the pre-sales tax price. This stock will not last and the price of the Weller Station MUST GO UP.

Cat. TS1000

### TRANSISTOR BARGAIN

3 AMP HIGH SPEED TO-5 POWER TRANSISTOR Type 2SC799.

Normally \$1.95 each.

March Madness!! \$0.75 each or \$5 for 10! — has exclusive slide-on flange to convert to chassis mount for greater power dissipation!

SPECS: NPN Silicon

— Vce 40V, Vcb 80V,

Vbe 5V — Ic 3A,

hFE 50-90 —

Ft 150MHz. Cat. ZT2600



### JUMBO SPEAKER CABLE

Now you can have super-quality cable without breaking the bank! Each conductor contains a MASSIVE 259 strands of 0.12mm wire!! It could carry 30 amps! Great for Hi Fi or high power amps.

Only \$2.50/m

100m \$2.00/m

Cat. WB1732



Fully  
Guaranteed

**\$12<sup>50</sup>**

» INTRIGUING «

~~\$36.50~~

For years and years 240V mains powered strobes have been selling for between \$30 and \$40. Even kits are around \$36. So why is it that Jaycar can sell a 240V strobe — guaranteed — for \$12.50?

We can tell you for a start that we're not selling them below cost. Even at \$12.50 we're doing OK.

Why so cheap?

Well they were made for a well known electronics chain. Their Q.C. (Quality Control) Department rejected them on the grounds that around 5% of them were faulty. That was an unacceptable figure considering the very good name that the chain has in this country. All goods were rejected (even the 95% good ones) and sent back to the importer.

The importer came to us with his problem. We said that we would sell them PROVIDED we could offer a 90 day guarantee on the item.

Whilst all stock has been checked and the duds weeded out we STILL feel that even at \$12.50 you deserve a comeback if we sell you faulty goods.

So that's it. You get a 240V strobe that is perfectly OK for \$12.50. Compare THAT with the \$36.50 that you will pay elsewhere.

It's almost too good to be true except for one thing. It's true.

FULL 90 DAY WARRANTY — Cat. XM7005

### 4116 RAMs 150nS — GOING CHEAP

We have secured a quantity of 4116 (150nS) RAMs at a price which means great savings to you. Why are they cheap? Well they don't actually have '4116' branded on them. They have '9016 FPC' on their little backs. They are used in a well known TV-game computer and this is the 'House Number' for their 4116. If you have ever had to buy a non-standard replacement part you will know that the 'House Number' part can be VERY expensive. We don't want to sell them as 9016 FPC's we want to sell them as 4116's — and at a great price. The normal (i.e. lower than most) price for our 250nS 4116 is \$2.50. You can grab a 9016 FPC (150nS) 1-off for only \$1.95!!!

For larger quantities see below:

Cat. ZZ8419

This price includes sales tax!!



1-9 pcs \$1.95  
10-24 pcs \$1.85  
25-99 pcs \$1.75  
100+ \$1.65

## Jaycar NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000

PHONE: 264 6688 TELEX: 72293

"NEVILLES CORNER"

Cnr. CARLINGFORD & PENNANT HILLS ROAD,

CARLINGFORD

PHONE: 872 4444

MAIL ORDERS TO: BOX K 39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES

\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)

\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)

\$100 up (\$8.00)

NEW SHOP HOURS

Mon - Fri 8.30 to 5.30pm

Sat 8.30 to 12.00pm

Thurs night to 8.30pm

Mail Order By **BANKCARD**  
Via Your Phone



# SCRs, triacs and power control

SCRs and triacs are high speed solid state switches specifically intended for use in ac and dc power control applications. Ray Marston explains their basic principles in this edition of Circuit File, to be followed next edition with a stack of application circuits.

## Ray Marston

FOR ELECTRONIC switching applications in dc and ac circuits, SCRs and triacs have no equals and wide application. The SCR is like a diode you can turn on and off while the triac is like two back-to-back diodes you can turn on and off (back-to-back SCRs!). That's the easiest way to think of these two very useful, related, devices. But to be able to appreciate their characteristics and how to use them, you need to know about them in somewhat more depth. So, let's look at some basic theory and circuits first.

### The SCR: basic theory

The SCR, or silicon controlled rectifier, is a four-layer pnpn semiconductor switching device. It is represented by the symbol shown in Figure 1a. Figure 1b shows the transistor equivalent circuit of the SCR, which takes the form of a complementary regenerative switch in which the base current of Q1 is derived from the collector of Q2 and the base current of Q2 is derived from the collector of Q1. Figure 1c shows the basic connections for using the SCR as a switch in dc power control circuitry. The basic characteristics of the SCR can readily be understood with the aid of Figures 1b and 1c, and are as follows.

(1) When power is first applied to the SCR (by closing SW1 in Figure 1c) the SCR is 'blocked' and acts like an open-circuit switch. This action can be understood by looking at Figure 1b, where it can be seen that, since Q1 base is shorted to the cathode via R1-R2, Q1 is cut off; through lack of base current and thus feeds no base drive to Q2, which is also cut off. As both transistors are cut off under this condition only a small leakage current flows between the anode and cathode of the device.

(2) The SCR can be turned on and made to act like a closed switch (or forward-biased silicon rectifier) by simply applying positive gate current by closing SW2 in Figure 1c. This gate current causes the

SCR to switch on very rapidly.

If the externally-applied gate current is sufficiently large it will apply base drive to Q1, causing Q1 to start to turn on. As Q1 starts to turn on, its collector current feeds base drive to Q2, causing Q2 to turn on and feed increased base drive into Q1, etc. A fast regenerative action thus takes place, with both transistors switching rapidly into saturation, the total saturation voltage typically being in the range one to two volts.

(3) Once the SCR has been turned on and is conducting significant forward current, the gate loses control and the SCR remains latched on even if the gate drive is subsequently removed. Thus, only

a brief pulse of gate current is needed to latch the SCR on. Note from Figure 1b that, because of the presence of R1 and R2, the SCR can *not* be turned off by shorting or reverse-biasing the gate-cathode terminals of the device.

(4) Once the SCR has latched into the on state it can only be turned off again by momentarily reducing its anode current below a value known as the 'minimum holding current'. Since turn-off occurs whenever the current is reduced below this critical value, it follows that turn-off occurs automatically in ac circuits near the zero-crossing point at the end of each half-cycle.

(5) Internal capacitance inevitably


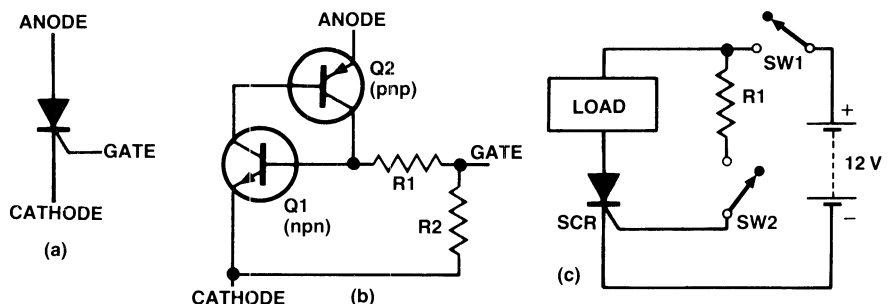


Figure 1. (a) SCR symbol (b) transistor equivalent circuit of the SCR and (c) basic connection for using the SCR as a dc power-control switch.

DATA FILE 7		TOTAL CURRENT		$V_{GT} \text{ (max)}$	$I_{GT} \text{ (max)}$	$I_H \text{ (max)}$
DEVICE TYPE NO.	PIV RATING	RATING, RMS/average				
TAG 1/100	100 V	1 A/0.64 A	2.5 V	10 mA	25 mA	
TAG 1/600	600 V	1 A/0.64 A	2.5 V	10 mA	25 mA	
C106D	400 V	4 A/2.5 A	0.8 V	0.2 mA	3 mA	
2N3525	400 V	5 A/3.2 A	2 V	15 mA	20 mA	
BT109	500 V	6.5 A/4 A	2 V	15 mA	3 mA	
IR122A	100 V	8 A/5 A	1.5 V	25 mA	30 mA	
IR122D	400 V	8 A/5 A	1.5 V	25 mA	30 mA	
C116D	400 V	8 A/5 A	1.5 V	20 mA	35 mA	
C126M	600 V	12 A/7.5 A	1.5 V	30 mA	35 mA	

Figure 2. Basic details of some of the most popular SCRs.

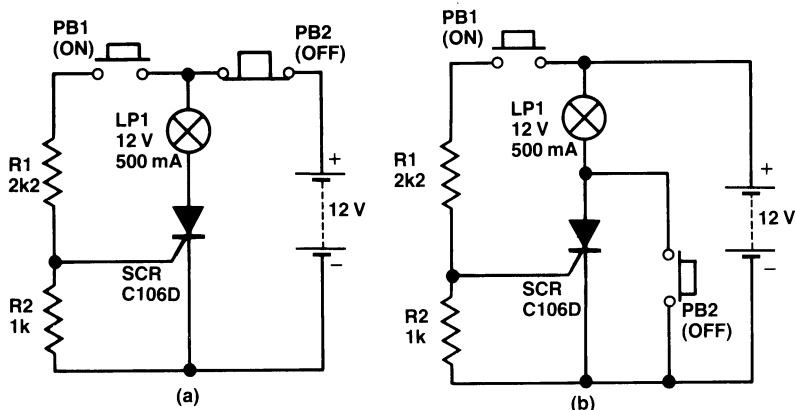

**Figure 3.** (a) Simple dc on/off circuit and (b) alternative dc on/off circuit.

exists between the anode and gate of the SCR. Consequently, if a sharply rising voltage is applied to the SCR anode this internal capacitance can cause part of the rising voltage to break through to the gate and thus trigger the SCR on. This 'rate-effect' turn-on can be caused by supply-line transients, and sometimes occurs at the moment that supplies are switch-connected to the SCR anode. Rate-effect problems can usually be overcome by wiring a simple RC 'snubber' network between the anode and cathode of the SCR, to limit the rate-of-rise to a safe value.

These then, are the basic characteristics of the SCR. As you can see, it's a pretty simple device. If you ever need to select an SCR for a particular application, you'll usually find that the most significant parameters are the main voltage and current ratings, plus the gate sensitivity rating and (occasionally) the device's 'minimum holding current' value. The list of Figure 2 gives basic details of a few of the most popular SCRs.

## The SCR: basic dc circuits

SCRs have applications in both dc and ac power control circuitry. Let's look first at some basic dc circuits. Figures 3a and 3b show alternative ways of using the SCR as a pushbutton-controlled on/off power switch feeding a 12 volt, 500 mA lamp. In both circuits the lamp and SCR can be latched on by momentarily closing PB1, thereby feeding gate drive to the SCR via R1. Note that the gate is tied to the cathode via R2, to give improved stability. Once the SCR has latched on, it can only be turned off again by momentarily reducing the anode current below the device's  $I_H$  value; in Figure 3a this is achieved by momentarily opening PB2; in Figure 3b the turn-off action is achieved by using PB2 to place a momentary short between the anode and cathode of the SCR.

Figure 4 shows another way of achieving SCR turn-off. Here, once the SCR has turned on, C1 charges up to almost the full supply voltage via R3 and the SCR anode, with the R3 end going positive. When PB2 is subsequently closed it clamps the positive end of C1 to ground, and the C1 charge forces the

SCR anode to momentarily swing negative, thereby reverse-biasing the SCR and causing it to turn off. The capacitor charge bleeds away rapidly under this condition, but has to hold the SCR anode negative for only a few microseconds to ensure complete turn-off. Note that C1 must be a non-polarised component.


A variation of the capacitor turn-off circuit is shown in Figure 5. A slave SCR is used to replace PB2 of Figure 4 and capacitive turn-off of SCR1 is achieved by briefly driving SCR2 on via PB2. SCR2 turns-off once PB2 is released, since the anode current provided by R3 is lower than the SCR2 holding current.

Figure 6 shows how the above circuit can


be modified so that it acts as an SCR bistable or flip-flop driving two independent lamp loads. Assume that SCR1 is on and SCR2 is off, so that C1 is fully charged with its LP2 end positive. The state of the circuit can be changed by briefly operating PB2. SCR2 is then driven on via its gate, and as it goes on it drives SCR1 off capacitively via its anode. C1 then recharges in the reverse direction. The state of the circuit can then again be changed by briefly operating PB1, thus driving SCR1 on via its gate and driving SCR2 off capacitively via its anode. The flip-flop process is repeated ad infinitum.

The dc circuits that we have looked at so far have all used simple resistive 'lamp' loads and have inevitably produced a self-latching

**Figure 4.** Capacitor turn-off circuit.

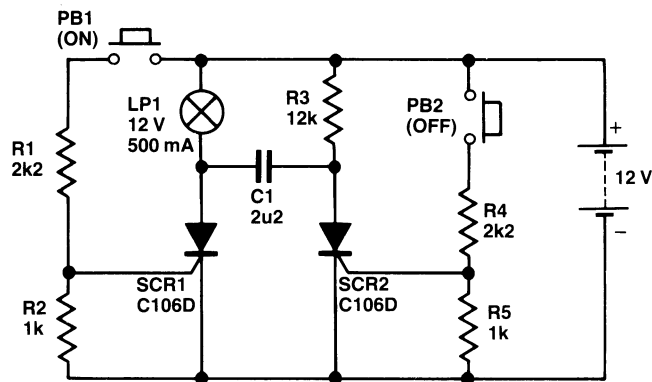

**Figure 5.** Capacitor turn-off with SCR slaving.

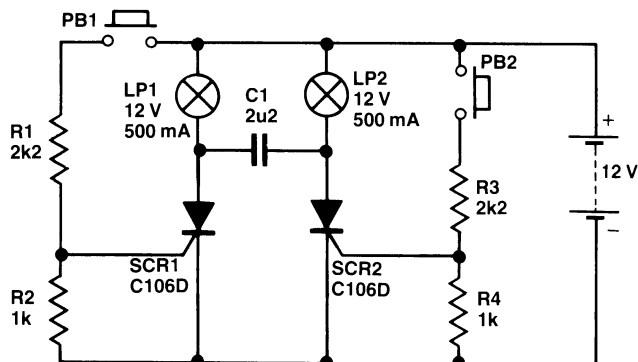

**Figure 6.** SCR bistable or flip-flop.

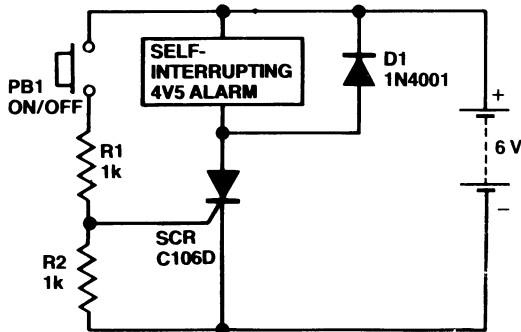


Figure 7. Simple non-latching alarm circuit.

action in the SCRs. Figure 7 however, shows a simple dc alarm circuit driving a self-interrupting load such as a bell or buzzer, and gives a non-latching action.

When self-interrupting devices such as bells or buzzers are connected across a supply, a current flows through a built-in solenoid via a pair of contacts. This current induces a magnetic field in the solenoid and causes a striker to fly outwards and open the contacts, causing the current to fall to zero and making the magnetic field collapse. Once the field has collapsed the striker falls back again and the contacts close, so current is again applied to the solenoid and the action repeats. Consequently, this type of load acts like a switch that repeatedly opens and closes rather rapidly.

When such loads are connected in the Figure 7 circuit therefore, the circuit does not self-latch in the normal way and the alarm operates only so long as PB1 is closed. Because of the inductive nature of such loads, a damping diode must be wired across them when they are used in SCR circuits, as shown in the diagram.

The Figure 7 alarm circuit can be modified to give a self-latching action if required by simply wiring a 470R (or lower) resistor in parallel with the alarm, as shown in Figure 8. In this case, the anode current of the SCR does not fall to zero when the alarm self-interrupts, but falls to a value determined by R3. If this value is in excess of the SCR's 'holding' value, the SCR self-latches. The circuit can be unlatched by briefly operating PB2, enabling the anode current to fall to zero when the alarm self-interrupts.

Finally, to complete this section, Figure 9 shows a circuit that can be used to demonstrate the rate-effect turn-on of the SCR, and a method that can be used for rate-effect suppression. Here, the SCR uses a 3 V lamp as its anode load, and is connected across the 4V5 battery supply via SW1. A 4V5 domestic door bell can be connected across the supply via PB1, and enables transient modulation to be applied to the supply line and thus to the anode of the SCR. This modulation can cause rate-effect turn-on of the C106D SCR, which has a critical slew rate of 20 V/us. The network R2 and C1 form a 'snubber' or rate-effect suppression network and can be

connected to the SCR via SW2.

To demonstrate the rate-effect, open SW2, close SW1, and then close PB1 so that the bell rings. The resulting supply line transients should be enough to trigger the SCR and turn the lamp on; if not, wire a one ohm resistor in series with the battery. Once the SCR and lamp have been triggered on, they can be turned off again by briefly opening SW1.

Once the turn-on rate-effect has been demonstrated, the effect of the suppressor network can be demonstrated by closing SW2 and SW1 and then operating the bell via PB1. The lamp resistance (plus R2) acts with C1 as a smoothing network that reduces the rate of rise of the anode modulation signal, thereby protecting the SCR against false triggering. R2 is wired in series with C1 to limit the capacitor's discharge currents to safe values when the SCR is triggered on via legitimate signals.

### The SCR: basic ac circuits

Figure 10 shows a basic halfwave on/off circuit driving a 100 W lamp from a 120 or 240 Vac power line. With SW1 open, zero gate drive is applied to the circuit, so the lamp and SCR are off. Suppose however, that SW1 is closed. On negative half-cycles, the SCR is reverse biased and gate signals are inhibited by D1, so the SCR is off. On positive half-cycles, the SCR is initially off at the start of each half-cycle, so the full available line voltage is applied to the gate via the lamp and D1-R1; shortly after the start of the

half-cycle sufficient voltage is available to trigger the SCR, which turns on. As the SCR goes on its anode voltage falls to near zero, thus removing the gate drive but the SCR remains self-latched for the duration of the half-cycle. The SCR automatically turns off again when the half-cycle ends and the anode current falls to zero.

The Figure 10 circuit gives halfwave operation only. Figures 11 and 12 show alternative ways of obtaining fullwave operation. In these circuits, the ac is converted to rough (unsmoothed) dc via a bridge rectifier and the rough dc is applied to the SCR. With SW1 open the SCR is off, so zero current flows through the bridge and the load. When SW1 is closed the SCR is driven on shortly after the start of each half-cycle of rough dc, so fullwave power is applied to the load. As the SCR goes on in each half-cycle, the gate drive is automatically removed but the SCR stays latched on for the duration of the half-cycle. The SCR switches off at the end of each half-cycle as its anode current falls to zero, so power is removed from the load when SW1 is opened.

Note in the Figure 11 circuit that the load is connected to the dc side of the bridge. A fuse must be placed on the ac side of the bridge, to give protection in the event of a short in the bridge rectifier. In the Figure 12 circuit the load is placed in the ac side of the bridge, which does not need fuse protection since the load itself will limit currents to a safe value in the event of a bridge failure.

A pair of SCRs can easily be wired in

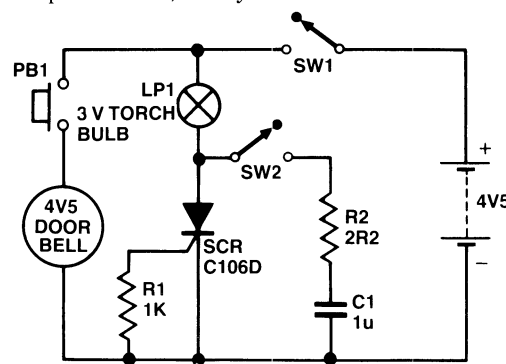


Figure 9. Rate-effect demonstration circuit.

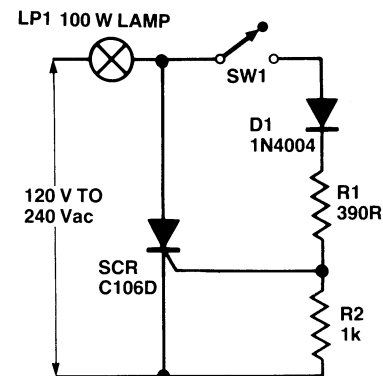


Figure 10. Line driven halfwave on/off circuit.

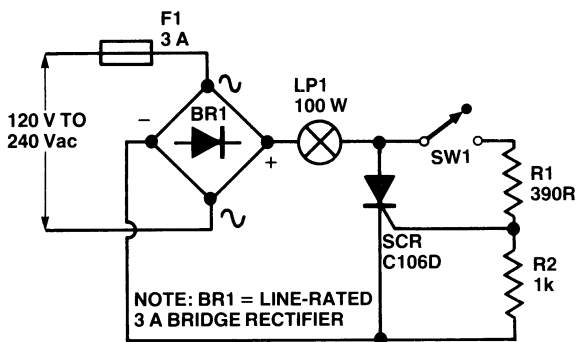


Figure 11. Fullwave on/off circuit.

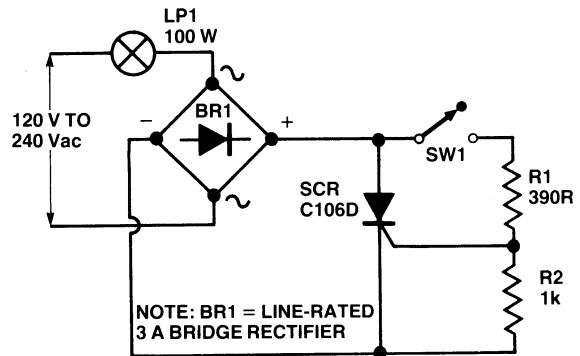


Figure 12. Alternative connection for fullwave on/off circuit.

inverse parallel and used to give fullwave power control without the use of additional rectification. In reality, however, a far more effective way of obtaining fullwave power control is to use a triac in place of the SCRs. Let's now look at triac basics.

## The triac: basic theory

A triac can be regarded as being equal to two conventional SCRs connected in inverse parallel within a single three-terminal package, but so arranged that they share a single gate terminal. The triac acts as a solid state power switch that can conduct current in either direction and can be switched from the off to the on state by a gate signal of either polarity.

Figure 13a shows the triac symbol and Figure 13b shows a basic connection for using the device as an ac power switch. The load is wired in series with the triac's main terminals, the combination being wired directly across the ac power line. By closing SW1 dc gate drive can be applied to the triac. Referring to Figure 13b, the basic characteristics of the triac are as follows:


(1) Normally, with no gate signal applied, the triac is off and acts (between MT1 and MT2) like an open circuit switch.

(2) If MT2 is appreciably positive or negative relative to MT1 the triac can be turned on (so that it acts like a closed switch) by applying a gate signal via SW1. The device takes only a few microseconds to turn on. A saturation potential of one or two volts is developed across the triac in the on mode. Once the triac has turned on it self-latches and remains on so long as main-terminal current continues to flow. Only a brief pulse of gate current is thus needed to turn the triac on.


(3) Once the triac has self-latched the gate loses control and the triac can only be turned off again by reducing its main-terminal current below a minimum holding value. When the triac is used as an ac power switch therefore, turn-off occurs automatically near the zero-crossing point at the end of each half-cycle as the main-terminal currents fall to zero.

(4) The triac can be turned on by either a positive or negative gate signal,

MT2 (MAIN TERMINAL 2)

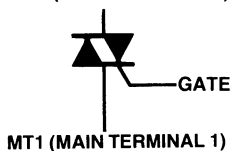

(a)

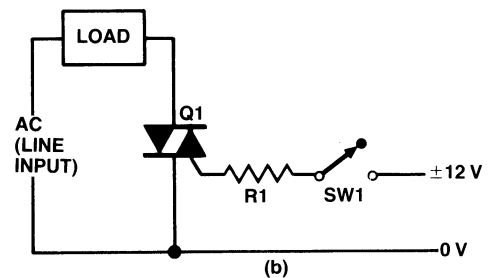

(b)

Figure 13. (a) Triac symbol and (b) basic triac circuit with dc gate drive.

irrespective of the polarities of the main-terminal voltages. The device thus has four possible triggering modes or 'quadrants', signified as follows:

- I+ Mode, MT2 current = +ve,  $I_{gate} = +ve$ .
- I- Mode, MT2 current = +ve,  $I_{gate} = -ve$ .
- III+ Mode, MT2 current = -ve,  $I_{gate} = +ve$ .
- III- Mode, MT2 current = -ve,  $I_{gate} = -ve$ .

Gate sensitivities in the I+ and III- modes are approximately equal and about twice as high as in the I- and III+ modes.

(5) Triacs can handle very high surge or non-repetitive currents. Typically, a device with a 10 A RMS rating may be

able to handle a single-cycle, non-repetitive 50 Hz surge current of 100 amps!

Figure 14 shows basic details of a limited range of popular triacs. In most applications this limited information is sufficient for user needs. Let's now move on and look at some basic ways of using the triac.

## The triac: basic circuits

Figure 15 shows the practical circuit of a simple dc-triggered triac power switch in which the dc supply is derived via step-down transformer T1. When SW1 is open, no current flows to the gate of the triac, which is thus off. When SW1 is closed, gate drive is

DEVICE TYPE NO.	PIV RATING	TOTAL CURRENT RATING RMS	$V_{GT} (max)$	$I_{GT} (max)$	$I_H (max)$
C206D	400 V	3 A	2 V	5 mA	30 mA
2N6073	400 V	4 A	2.5 V	30 mA	70 mA
C226D	400 V	8 A	2.5 V	50 mA	60 mA
SC146D	400 V	10 A	2.5 V	50 mA	75 mA
TIC246D	400 V	15 A	2.5 V	50 mA	50 mA

Figure 14. Basic details of some popular triacs.

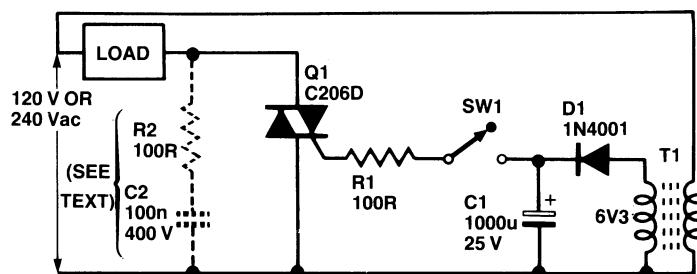


Figure 15. Simple ac power switch with dc gate triggering.

applied to the triac so it and the load are driven on. If an inductive load, such as a motor, is used in this circuit the R2-C2 'snubber' network must be wired in place as indicated to prevent false-triggering by rate-effects.

Note in the Figure 15 circuit that the dc side of the circuit is connected directly to one side of the mains and is thus 'live'. This snag is overcome in the UJT-triggered isolated-input circuit of Figure 16. Here, the UJT (unijunction transistor) operates at several kilohertz and thus delivers roughly 50 trigger pulses to the gate of the triac — via isolation pulse transformer T1 — during each half-cycle of the ac power line waveform. Consequently, the triac is fired by the first trigger pulse occurring in each mains half-cycle, and this pulse occurs within a few degrees of the start of the half-cycle. The triac is thus turned on almost permanently when SW1 is closed and virtually full power is applied to the ac load. The trigger circuit is, however, fully isolated from the mains by transformer T2 and pulse transformer T1.

Figure 17 shows how the triac can be used as a simple line switch with line-derived triggering. With SW1 open, zero gate drive is applied so the triac and lamp are off. Suppose however, that SW1 is closed. At the start of each half-cycle the triac is off, so the full line voltage is applied to the gate via the lamp and R1. Shortly after the start of the half-cycle, enough drive is available to trigger the triac and the triac and lamp go on. As the

triac goes on and self-latches it saturates and automatically removes the gate drive until the start of the next half-cycle, thus minimising the dissipation in R1.

Finally, Figure 18 shows how the above circuit can be modified to give either half-wave or fullwave operation. In the halfwave mode, the gate drive is applied via D1, so the triac triggers on positive half-cycles only. In the fullwave mode the triac triggers on both positive and negative half-cycles, as in the case of the Figure 17 circuit.

### Phase-triggered power control

The SCR and triac circuits that we have looked at so far have all been designed to give a simple on-off form of power control. These devices can easily be used to give fully-variable power control in ac circuits and are widely used in lamp dimmers and electric motor speed controllers, etc. The most widely used system of ac variable power control is known as the 'phase triggering' system.

Figure 19 illustrates the principle of phase-triggering using a triac as the power control element. Here, instead of the triac being triggered 'directly' from the ac power line, it is triggered via a variable phase-delay network that is interposed between the power line and the triac gate. Thus, if the triac is triggered 10° after the start of each half-cycle, almost the full available line power is fed to the load. If the triac is triggered 90° after the start of each half-cycle,

only half of the available line power is fed to the load. Finally, if the triac is triggered 170° after the start of each half-cycle, only a very small part of the available power is fed to the load.

The three most popular methods of obtaining variable phase-delay triggering are to use either a line-synchronised UJT, a special-purpose IC, or to use a diac plus RC network in the basic configuration shown in Figure 20.

The diac can be regarded as a bilateral threshold switch. When connected across a voltage source, it acts like a high impedance until the applied voltage rises to about 35 volts, at which point it switches into a low impedance state and remains there until the applied voltage falls to about 30 volts, at which point it reverts to the high impedance mode. It then stays in this state until the applied voltage rises back to 35 volts, at which point the process repeats.

In the Figure 20 circuit, in each mains half-cycle the R1C1 network applies a variable phase-delayed version of the mains waveform to the triac gate via the diac, and

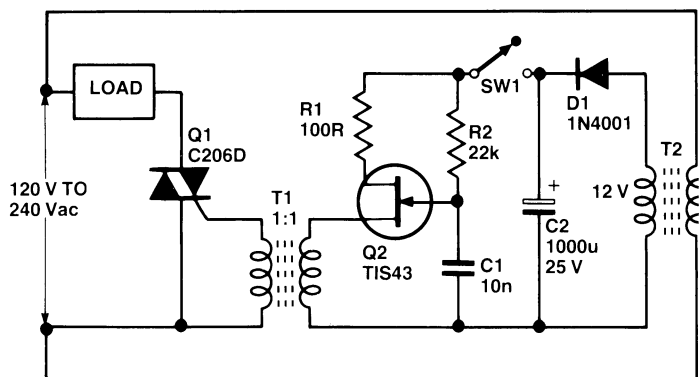


Figure 16. UJT-triggered isolated-input ac power switch.

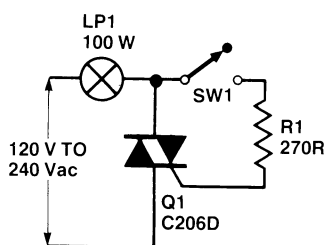


Figure 17. Line-triggered triac switch.

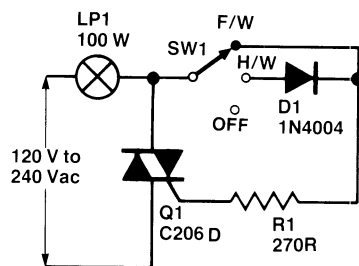


Figure 18. Three-way line switch.

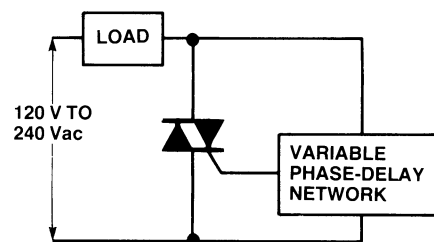


Figure 19a. Variable phase-delay 'switch'.


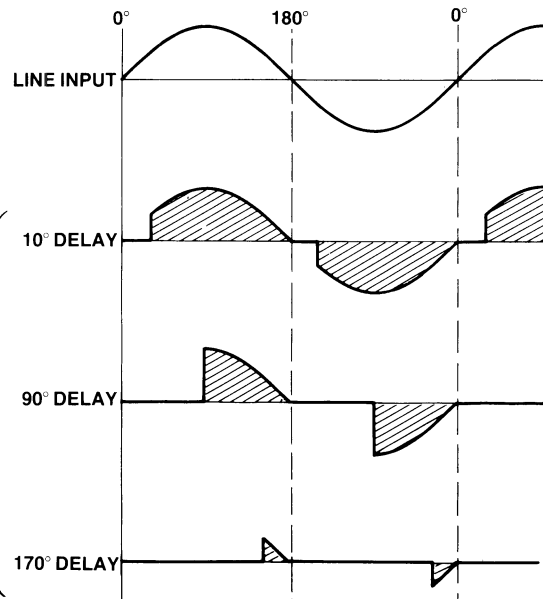


Figure 19b. Variable phase-delay waveforms.

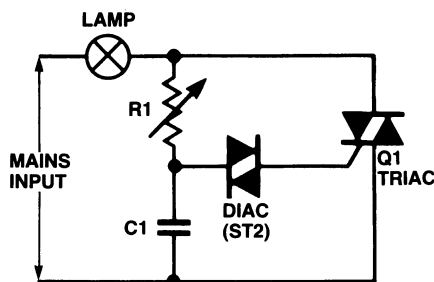

**Figure 20.** Basic 'diac-type' variable phase-delay lamp dimmer circuit.

each time the C1 voltage rises to 35 volts the diac fires and delivers a trigger pulse to the triac gate, thus turning the triac on, simultaneously applying power to the lamp load and removing the drive from the RC network. The mean power to the load (integrated over a full half-cycle period) is thus fully variable from near-zero to maximum, via R1.

## Radio frequency interference (RFI)


You can see from the Figure 19 waveforms that, each time the triac is gated on, the load current changes abruptly (in a few microseconds) from zero to a value determined by the load resistance and the instantaneous mains voltage. This action generates radio frequency interference (RFI). The RFI is greatest when the triac is triggered at 90°, and is least when the triac is triggered close to the 0° and 180° 'zero-crossing' points of the mains waveform.

In lamp dimmer circuits, where there may be considerable lengths of mains cable between the triac and the lamp load, this RFI may be offensive as it will be widely radiated, interfering with radio and television receivers and other appliances. In practical lamp dimmers the circuit is usually provided with an LC RFI suppression network, as shown in Figure 21, to overcome this problem. (Note: in Figure 21 the values in brackets are applicable to 120 V mains operation.)


## Zero-crossing techniques

When high power loads, such as electric heaters, are driven from triac circuitry special techniques must be used to minimise RFI. Even if the triac is used as a simple on-off switch in such applications, a 'spurt' of RFI will be generated each time the switch is turned on, and will be of maximum amplitude if the instantaneous phase delay happens to be 90° at the moment of turn-on. RFI problems can be eliminated in high-power applications by using the synchronous or 'zero-crossing' gating technique illustrated in Figure 22.

Here, a low power 12 volt dc supply is generated directly from the mains via R1-D1-ZD1 and C1. A simple zero-crossing detector network (a couple of transistors) is

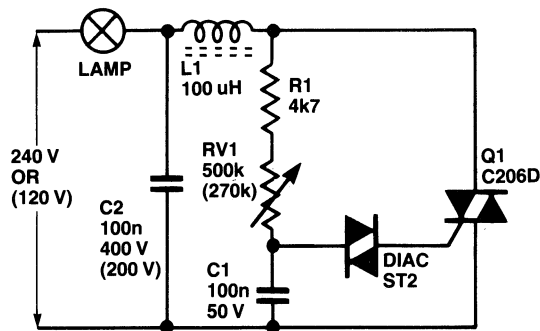

**Figure 21.** Practical lamp dimmer with RFI-suppression.

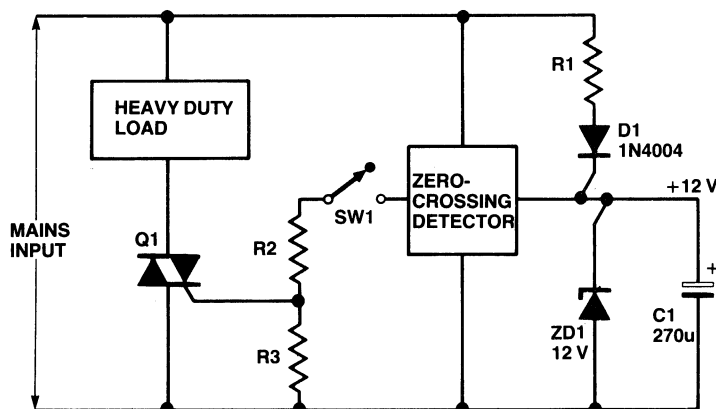

**Figure 22.** Basic synchronous or 'zero-crossing' mains power switch.


connected directly across the mains and controls the passage of current from C1 to SW1 in such a way that the C1 current is made available for only 5° or so on either side of each zero-crossing point of the mains waveform. Thus, if SW1 is closed, a pulse of gate current is fed to the triac at the start of each half-cycle of mains voltage, at which point the mains voltage is close to zero, so the triac always generates minimal RFI as it turns on.

The 'zero-crossing' technique can be used to provide RFI-free variable power control in high-power loads, such as electric heaters, by replacing SW1 of Figure 22 with a variable mark/space-ratio waveform generator so that a variable integral number of complete

mains power cycles are alternately fed or not fed to the load.

Figure 23 illustrates the basic principle, in which the total integral period is equal to eight mains cycles. Thus, if the power is alternately switched on for four cycles and off for four cycles, the mean load power is equal to half of the total available power, and if the power is on for one cycle and off for seven cycles, the mean power is equal to only one eighth of the total available power.

In the next edition of 'Circuit File' we'll look at some practical 'zero-crossing' and integral-cycle power controllers, together with a variety of lamp dimmers and motor-speed controllers.

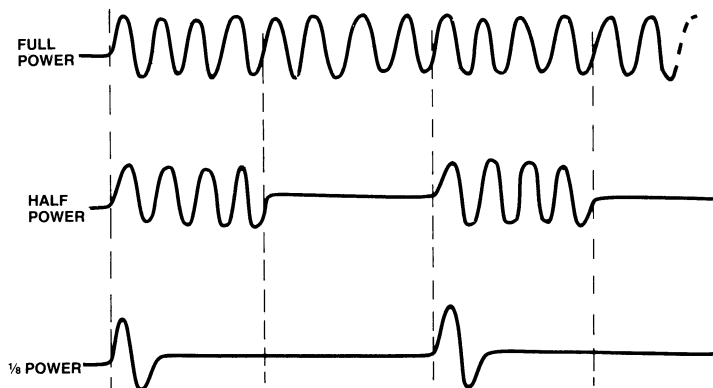


**Figure 23.** Integral-cycle power control waveforms.
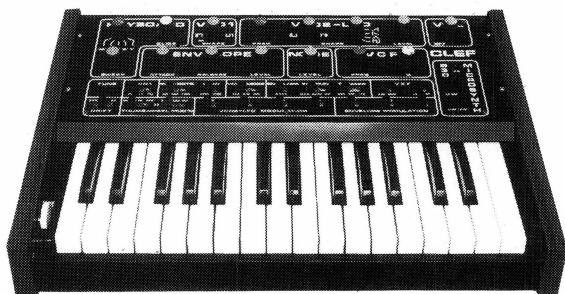
# GREAT NEW PROD

CLEF  
ELECTRONIC  
MUSIC

MICROSYNTH  
COMPACT MUSIC SYNTHESIZER



Equally suited to home, studio or stage use, the Microsynth has resulted from an extensive re-think of what is required from a synthesiser. Its compact and economic design achieves high performance at low cost without sacrificing versatility or musical stability.

A highly efficient switched routing system for signals and/or control voltages is capable of rapid operation for live work, yet unlike other small synthesizers does not restrict the possibilities for complex sound creation. Despite its small size, the Microsynth can produce startlingly rich sounds owing to the number of waveforms available, together with the sub-octave voices. It is capable of advanced effects such as Ring Modulation as well as rhythmic "staircase" or random patterns.

Operates in two modes depending on the configuration of the second oscillator (VCO2), which can either run at audio frequencies or as a voltage controlled low frequency oscillator (LFO). In audio mode, VCO2 will track VCO1 perfectly over its entire range. A Thumbwheel allows manual control of oscillator pitch or filter cut-off frequency, depth of LFO modulation, etc., and internal power amplification will drive headphones or a monitor loudspeaker.

#### SPECIFICATIONS (BRIEF)

\* Keyboard - 2½ octaves (30 notes) may be stepped through 5 octave range from 16' to 1' using the "Range" switch  
\* VCO1 - 10Hz to 10kHz, triangle output to VCA, ramp and square outputs to VCF \* VCO2/LFO - VCO mode 10Hz to 10kHz, LFO mode 0.1Hz to 30Hz. \* Sub octaves - 2 divide-by-2 \* Noise - white noise source with level control. \* Envelope - attack and release times variable 0 to 10 seconds \* Retrigger - causes the envelope shaper to retrigger itself with a repeat time equal to the sum of the attack and release times. "Sustain" operates in 3 modes, manual, auto and hold. \* VCF - state variable filter with manual control of roll-off frequency. \* VCA - controls output volume of synthesiser  
\* Sample and Hold - analogue memory samples instantaneous output voltage from VCO2/LFO each time envelope ends. \* Sweep \* Thumbwheel - Manual level control \* Power amp - output 2 watts into 8 ohms plus headphone socket \* Sequencer socket \* Size: 19½" x 14" x 5½". Weight: 10lb. Power: 240V AC 5W.

**\$399** *kit*  
Cat. KJ6002

## BAND-BOX *kit*

**LIVE PERFORMANCE** - Feed in, store, and play complete Music Pad of around 60-100 Backing Scores up to a total of approximately 3,000 Chord changes, each up to eight Beats in length, on more than 120 different chords.

**Program Intros, Chorus Repeats, Codas, Key changes and modulations** on single or multi-tune sequences. Use simple Playback procedures for live performance, including optional foot operated controls.

**PRACTICE SOLOISTS** - Instrumental or Vocal Soloists grow to full four piece BAND performance played in any Key, Tempo, and Rhythm style for demanding practice sessions with unlimited, but controlled, Chorus repeats.

**ELECTRO-MUSIC RECORDING/COMPOSITION** - Full Chord sequence and Rhythm programmability for three instrumentalists enables creative Composing and Arranging for both Professional and Amateur applications.

#### SPECIFICATIONS (BRIEF)


\* Music simulation capacity - three backing instrumentalists. Over 3,000 programmable stored chord changes. 132 different chords plus additional inversions. \* Chord instrumentalist - four note chords, four waveform options, four envelope options sixteen permutations for piano, organ etc, twenty four programmable rhythm patterns. \* Bass instrumentalist - four voice/envelope combinations, eight rhythmic figures \* Drums - twenty four programmable patterns, eight tracks selecting eleven instrument sounds, Sticks, brushes & Latin American. Sequence operation up to 16 bar repetition. \* Playback facilities - Keyboard selection of score, display of selected score, variable tempo, switched selection of any key, in-play changes to key, tempo and all instrument voices, rhythmic patterns and levels, bar down beat indicator, all-beat indicator, unlimited chorus repeats, Coda key to cancel repeats, automatic stop, manual instant stop, automatic reset to beginning of selected score, measures/beat selectable to match 4 drumming styles. \* Composition facilities \* Composition instructions \* Pre-recorded scores \* Musical compass - Tuning range - one semitone, use alternative key for gross pitch change, Bass compass - 16 notes, F1 to G2 44Hz to 104Hz, chord instruments - 18 notes E3 to A4 165Hz to 440Hz, automatic chord inversion to fit compass \* Percussion instruments - Bass drum, low & high tom toms, snare, drum, rim-shot, cymbal, long & short brushes, high bongo, claves, and accent for dynamics. \* Operator interfaces - numerous \* External socket: - numerous \* Size: 19" x 11" x 4½" overall. Weight 11lb. Power requirements: 240V 6W.

(MASTER RYTHM KIT EXTRA)


Cat. KJ6600

**\$699**

Cat. KJ6604

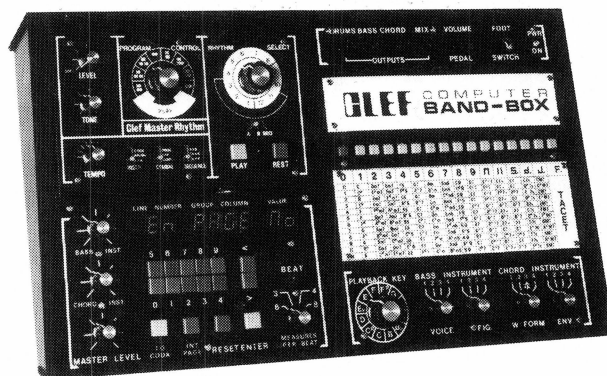
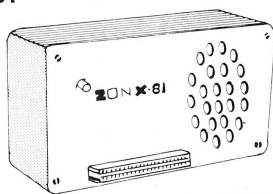
## SINCLAIR ZX-81 COMPUTER SOUND GENERATOR



Cat. KJ6620

**\$69.50**

Make amazing sound effects with your Sinclair Computer.

- The ZON X-81 SOUND UNIT is completely self contained and especially designed for use with the ZX 81. It just plugs in - no dismantling or soldering.
- No power pack, batteries, leads or other extras.
- Manual Volume Control on panel - ample volume from built-in loudspeaker.
- Standard ZX 81 - 16K RAM pack or printer can be plugged into ZON X-81 Sound Unit without affecting normal ZX 81 operation.
- Huge range of possible sounds for games or: Music, Helicopters, Sci-Fi, Space Invaders, Explosions, Gun Shots, Drums, Planes, Lasers, Organs, Bells, Tunes, Chords etc., or whatever you devise!
- Uses 3-channel sound chip giving programme control of pitch, volume of tones and noise, all with envelope control.
- Easily added to existing games or programmes using a few simple "BASIC" lines.
- FULL instructions with many examples of how to obtain effects and the programmes, supplied.
- Extension card at base of unit allows further use of Sinclair Expansion Card.

## SOMETIMES THINGS AREN'T WHAT THEY SEEM. ....

OK so you have had that high quality cassette deck for some time now. You were thinking of updating to one of those fancy 3-head microprocessor decks but - well they ARE expensive!

Why not give your current deck a new lease on life?

If your deck is more than 3 years old and has had a bit of work its quite possible that the record/replay head is worn. This can lead to poor H.F. performance. Or it may have never been any good in the first place. Or you may want better performance than the head in your car cassette player can give.

Jaycar now stocks replacement very high quality cassette deck heads to suit most machines - especially Japanese. They are made in the U.K. by MONOLITH.

Amazingly most cassette deck heads are standard fittings (EIAJ). So even if you want to just refurbish that cheap player that you use to load programs into your computer Jaycar has the replacement head.

C21RPS18	Mono record/playback	\$14.95
B24-02	Stereo record/playback	\$17.95
B24-07	Stereo record/playback for use with Dolby	\$24.95
C42RPH04	Stereo record/playback glass ferrite faced	\$36.50
C21ES18	Mono or stereo erase	\$7.95

(All record/playback have mounting hole centres on 17mm pitch and 12.5mm from face of head)




# UCTS-LOW PRICES COMPUTER SENSATION!!

You may have wondered why Jaycar did not (until now) sell home computers. We had many reasons but our main one was that we were not entirely "happy" with any of the units currently on the market. The closest we came to what we thought was a pretty good computer was the Apple. We thought that it was, quite frankly expensive. However it was sold and serviced throughout Australia by a reputable sales network — so there was no need for Jaycar!

That's why we got so excited when we saw the "Micro Professor MkII". It is the closest thing that we have seen to be software compatible with the Apple. Yes, we know what you're thinking. It's NOT one of those cheap Taiwanese "Apple" copies which infringe Apples' copyright. The Micro Professor MkII is a completely new and unique design in its own right. It just so happens that most of the widely distributed Apple software will run on this machine. O.K. But why so excited? LOOK AT THE PRICE! Check out the STANDARD FEATURES of this unit. Sit down. Think about it and COMPARE what you get with the Micro Professor MkII as STANDARD that are options on other machines!!

6 Colours

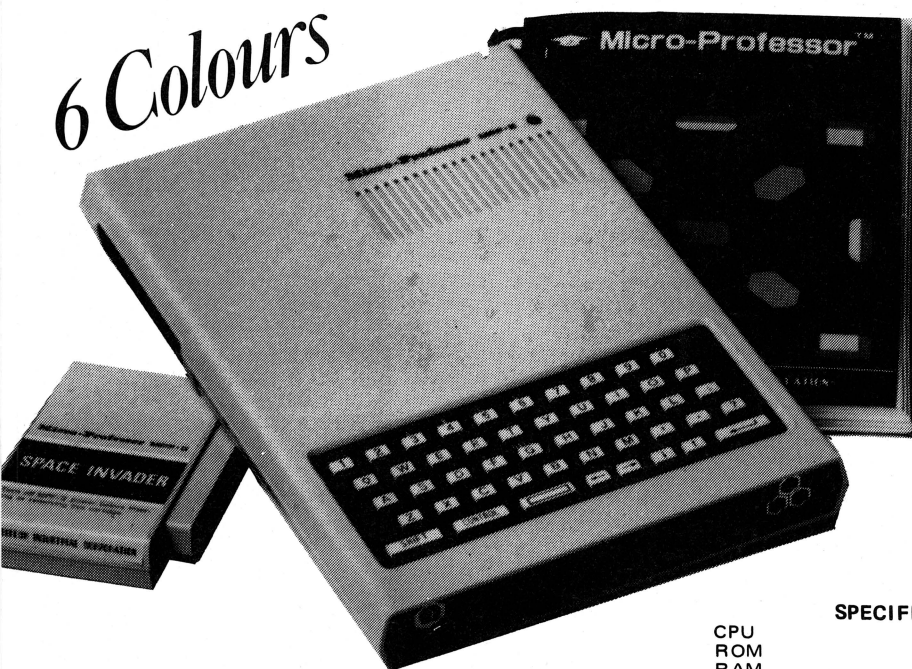

Cat. YC1300

Only  
**\$598**

- \* 64K OF RAM SUPPLIED STANDARD all that you are ever likely to need.
- \* Text, Lo and Hi resolution graphics STANDARD
- \* Video AND TV (RF) output STANDARD
- \* Easy-to-use manual included in the price (over 248 pages)
- \* Power supply included as STANDARD
- \* Centronics printer interface STANDARD
- \* Multitech BASIC is compatible with APPLE II BASIC. Most APPLE software will run on the Micro Professor MkII

## SPECIFICATIONS

CPU  
ROM  
RAM  
BASIC

Interpreter

Video  
Display

Type  
Mode

Screen Format  
Character Set  
Character Type  
Graphics Capacity

Keyboard  
Cassette  
Software  
Printer  
Display  
Remote  
Speaker  
Power

Number of Colors

Interface  
Cartridge Interface  
Interface  
Control Paddle

Dimensions

R6502  
16K Bytes  
64K Bytes  
More than 90 instructions stronger than those for Apple II  
Memory mapped into system RAM  
Text, low-resolution graphics, high resolution graphics (3 modes are mixed)  
960 characters (24 lines, 40 columns)  
Upper case ASCII, 64 characters  
5 x 7 dot matrix  
1920 blocks (low resolution) in 40 x 48 array, 53760 dots (high resolution) in 280 x 192 array  
6 colors  
49 alphanumeric and function keys  
Use various cassette tapes and cartridges as data storage units  
Connects to printers with Centronics I/F  
Connects to color TV or video display  
Used for education & entertainment  
8 ohm, 55mm, 0.25W  
A switching power supply is provided to convert AC power to required power supply  
241 x 175 x 30mm

## COOLING FANS 240VAC


Quality Ball Race construction, now you pay no more for quieter, much longer lasting and more efficient ball-bearing fans from Jaycar!

TWO POPULAR SIZES:  
12 WATTS — 80x80x42(d)

**\$24.95** Cat. YX2510

13.5 WATTS — 119x119x25(d)

**\$27.50** Cat. YX2514

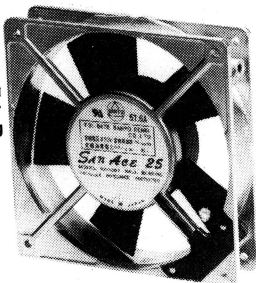


## MAGAZINE BINDER

Keep your precious (and expensive) magazines in order for easy reference. Smart blue colour with gold lettering. Heavy gauge and richly chromed metal fittings.  
**LOW IMPORT PRICE ONLY \$4.95**  
4 up \$4.50 each

FROM  
**\$4.50**

Cat. BB7000

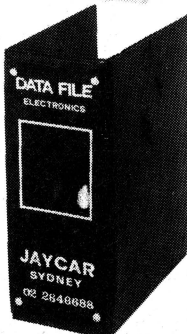


## Jaycar NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000  
PHONE: 264 6688 TELEX: 72293  
"NEVILLES CORNER"  
Cnr. CARLINGFORD & PENNANT HILLS ROAD,  
CARLINGFORD  
PHONE: 872 4444  
MAIL ORDERS TO: BOX K 39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 up (\$8.00)

NEW SHOP HOURS  
Mon. 8.30 to 5.30pm  
Sat. 8.30 to 12.00pm  
Thurs night to 8.30pm

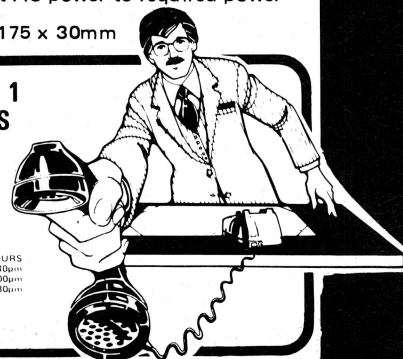Mail Order By **BANKCARD**  
Via Your Phone



# Pushbutton-operated windscreen wiper controller

Windscreen wipers always wipe either too frequently or not frequently enough. This is a corollary of Murphy's law. Vehicle engineers have spent much creative thought and effort on solving this problem since vehicles had windscreens and covered cabins. Knobs and switches abound. This one simply requires a push or two on some buttons and gives you the exact wiping frequency you need.

**Geoff Nicholls  
Roger Harrison**

THE CIRCUIT for this project won the 'Idea of the Month' contest, sponsored by Scope Laboratories, for the September 1982 issue. A reader from Herston in Queensland, who only wished to be identified as J.D.W., submitted the circuit. It is probably one of the most intriguing circuits ever submitted for the contest. Not only that, it solved a practical problem in an elegant and intriguing way.

As the introduction says, windscreen wipers either wipe too frequently, or not frequently enough. As most late-model cars are fitted with dual-speed wipers, at high speed they're making setting-teeth-on-edge noises after half a dozen wipes in the high speed position or not getting rid of the water fast enough in the slow speed position, in any given downpour.

Vehicle manufacturers, in our opinion (and experience), have never adequately addressed themselves to the problem. Two-speed wiper systems are legion. And what driver of a vehicle with a two-speed wiper has *not* mentally labelled the two speeds 'too slow' and 'too fast'.

A 'fully variable' system has long been considered the best solution. With these a rotary control provides a variation in wiper speed from a wipe every few seconds to a few wipes per second (maximum motor speed). That's fine, but you have to mentally 'calibrate' the control. At slow wiping speeds, this is a difficult task and you spend some considerable time fiddling with the control. Inevitably, you give up and take the 'that'll do' line of least resistance.

Let us examine what happens when you're driving along and it starts to rain. First thing, the windscreen gets wet. When it gets wet enough, you want it wiped. You start the wiper and it does its job. Some interval later, the windscreen gets wet enough that you want it wiped again. *That's* the interval at which the wipers should operate. How on earth does one design a control that does that? The answer is, you don't. What you need is a controller with a 'memory'. Press a button to wipe the windscreen when it first gets too wet for you, then press it again when the windscreen next gets too wet, and have the controller repeat the wipes at the same interval. That's what the memory does — remembers the interval between the first two wipes.

What to do when the rain increases? Simply press the button again between wipes, setting a new interval. How do you stop it when the rain stops? — simple, have a stop button!

What to do when the rain decreases? Aahh — thought you'd ask that. Hit the stop button, but keep the memory going, then start the wipers again when the windscreen gets too wet, repeating the wipes at the interval between the last wipe and the new one.

That's exactly what this project does.

There's one final question to resolve, however. How long should the 'memory' be? Our correspondent set it at about 40 seconds. From observation, this seems about right. Driving in intermittent rain, we observed that the maximum interval between successive 'too wet' windscreens was about

30 seconds. During the latter half of 1982, Sydney turned on some very Melbourne-like weather — intermittent rain and shine, very light, 'patchy' rain, etc. The Editor cursed his dual-speed wiper and yearned for something better. Hence, this project.

The circuit employs half a dozen ICs, two transistors, a handful of capacitors and around 30 resistors. A relay is used to control the operation of the wiper motors.

Before going on with the construction, let us take a look at the wiper systems in modern vehicles.

## Wiper systems

With rare exceptions, windscreen wipers on modern vehicles are driven by an electric motor. Two motor types are employed — permanent magnet motors and wound field motors. The wiper systems are generally arranged so that the wipers are 'parked' out of the field of view when they're not in use. A cam-operated switch effects this, turning off the wiper motor only when the wipers are in the appropriate position and the supply to the motors is cut. However, the two different motor types have different braking characteristics when the motor supply is cut, so different switch schemes are used for parking.

Wound field motors simply have the supply cut when the wipers are in the appropriate position. A set of cam-operated contacts on the drive shaft effects this. Figure 1 shows how the arrangement works. The cam opens the contacts when the wipers are in the parked position. The wiper switch parallels the cam contacts. When you turn the wiper switch to the off position, the motor will continue until the cam contacts open.

Permanent magnet motors have 'dynamic braking' applied. A short circuit is connected across the motor armature when the wipers reach the parked position. The circuit is shown in Figure 2. Cam-operated changeover contacts are connected such that, when the wiper switch is set to the off position, the cam contacts short the armature. When power to the motor is cut, it becomes a generator, ►

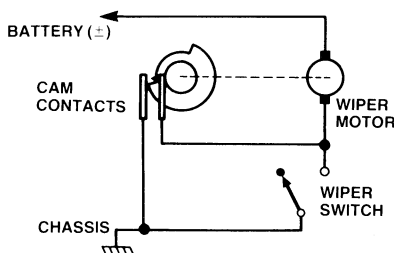


Figure 1. Self-parking arrangement for a wound field wiper motor.

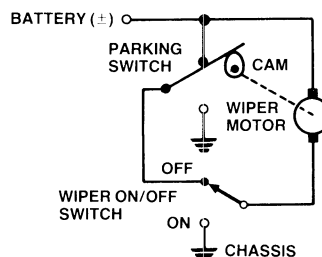


Figure 2. Self-parking arrangement for a permanent magnet wiper motor.

## HOW IT WORKS — ETI-335

The best way to understand how this circuit works is to first look at the various circuit elements employed, then the step-by-step operation.

IC1 is a one-second monostable multivibrator that drives Q1. This operates the relay, RL1, the contacts of which operate the windscreen wiper motor.

IC1 is triggered via IC3d. Initially, pin 1 of this gate will be low (0 V), held down via R4 and R5. Pin 2 of IC3d will also be low initially. This is connected to the output of IC5 (pin 6) which will be at 0 V as its two inputs will initially be at 0 V.

IC2 has pins 2 (trigger) and 6 (threshold) tied together. Initially, they'll be low (below threshold), and the output (pin 3) will appear as an open circuit.

IC3a and IC3b form a flip-flop. This controls IC4, an astable multivibrator. The flip-flop inputs are pin 8 of IC3a and pin 13 of IC3b. Initially, both will be low and the flip-flop output will be low. Thus IC4 is disabled.

The output of IC4 drives the input of IC6, a dual binary counter with its two sections cascaded. Each counter has a 4-bit output. These outputs are connected to a resistor ladder network, making a 'stair step' generator. Thus, the voltage on pin 3 of IC5 rises in small 'steps' as IC4 oscillates, stopping on the last step when IC4 ceases to oscillate, providing a voltage 'memory'.

Now, let us see what happens when the WIPE button is pressed for the first time.

Operating PB1 puts a voltage pulse across R1. As C1 is discharged, this pulse appears across R4 and thus a logical high ('1') appears on pin 1 of IC3d. The output of IC3d (pin 3) will initially be high, going low (0 V) when pin 1 goes high. This triggers IC1 and its output, pin 3, goes high for a period of one second.

This turns Q1 on and the relay will be held operated for one second, causing the wiper motor to operate. The wiper will complete one wipe and, as it takes longer than one second, the relay will have dropped out by the time the wiper returns to the start position and the wiper motor will thus 'park'.

When Q1 turns on, its collector goes low and Q2 will be biased on via R15-R16. Thus, C7 will charge rapidly via R23. It can only charge to a maximum of 6.2 volts, limited by the zener diode ZD2.

After IC1 has completed its one second timing cycle and Q1 turns off, Q2 will turn off and C7 will discharge slowly via R9-R10, taking about 40 seconds. The voltage across R10 provides a small voltage which is applied to the 'control' pin (5) of IC2, which affects the threshold level at which IC2 can be triggered.


The flip-flop, IC3a-b, remains unchanged when PB1 is first pressed. Both flip-flop inputs (pins 8 and 13 of IC3) go high immediately PB1 is pressed, and thus the flip-flop output will remain low and IC4 will remain disabled.

When C7 is charged, and while it remains sufficiently charged, IC2's trigger-threshold pins (2 and 6) will be above the threshold and pin 3 will pull the cathode of D2 low (almost to 0 V). At the same time, the inverting input of IC5 (pin 2) will be held at the same voltage as is on C7 and its output will be driven to 0 V.

If the WIPE button is pressed again within 40 seconds of the first press, a voltage pulse will appear across R1 and R4, as before, but this time pin 1 of IC3d is held low by the output (pin 3) of IC2, via D2. Thus, IC1 won't trigger via this means.

However, as pin 8 of IC3a (one flip-flop input) is held low via R11-R13, the voltage pulse across R4 will appear on the other input of the flip-flop, pin 13, changing its output (pin 10/12) from low to high. Thus, IC4 is enabled and will commence to oscillate.

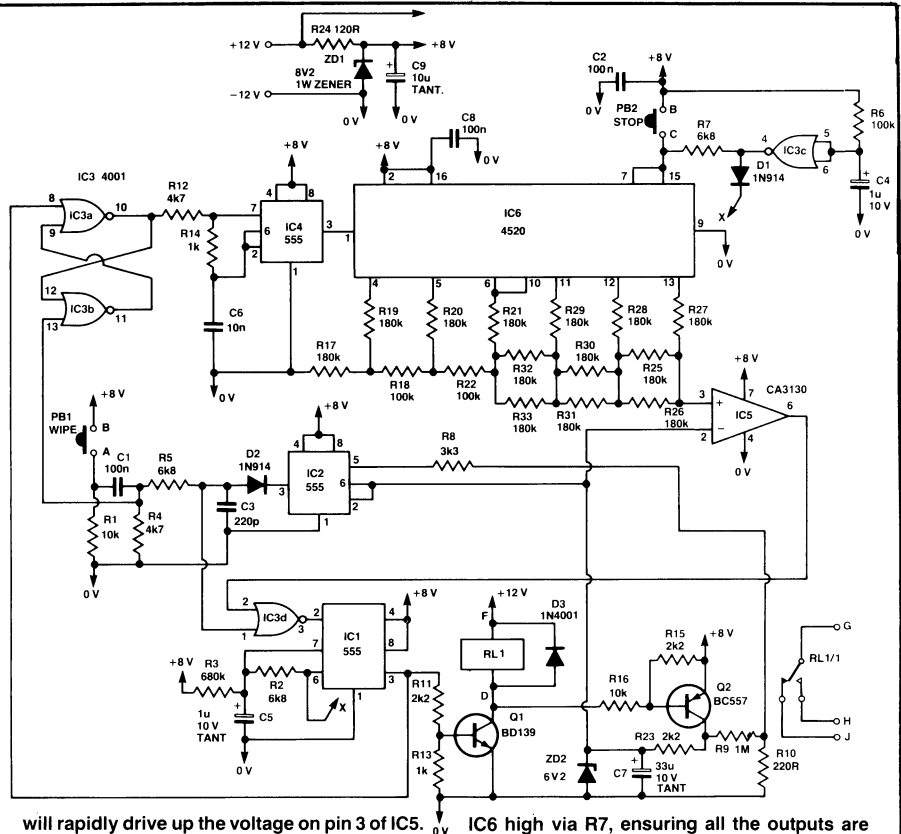As IC4 oscillates, the stair step generator



will rapidly drive up the voltage on pin 3 of IC5. When it reaches the same voltage as that on pin 2, the output of IC5 will immediately go high (jump to +8 V), driving pin 2 of IC3d high. Pin 3 of IC3d will then go low, triggering IC1. Thus, Q1 operates the relay once again and the wiper wipes.

When IC1 triggers this time, pin 5 of IC3a will go high and the flip-flop output will go low, disabling IC4 and stopping the count in the 4520. The output voltage of the stair step generator will thus stop at that point — providing a 'memory' of the voltage left on C7 after it discharged for the period between the first and second presses of PB1.

When Q1 turns on again, Q2 will turn on again, charging C7, raising the voltage on pin 2 of IC5 above that on pin 3. This will now drive the output of IC5 to 0 V once more, setting pin 3 of IC3d high once again, restoring the initial conditions.

After IC1 completes its timing period, Q1 and Q2 will turn off and C7 will begin to discharge again. When the voltage on C7, and thus the voltage on pin 2 of IC5, drops to that held on pin 3 by the stair step generator, the output of IC5 will go high, triggering IC1 via IC3d, as before, and the whole cycle will repeat at that interval it takes for C7 to discharge to the voltage 'remembered' by the stair step generator.

You can shorten the interval at any time by pressing PB2 between wipes.

To stop the wipe sequence, press PB2. This puts a momentary high on the 'master reset' inputs of both counters in IC6 (pins 7 and 15). All outputs are then reset low. This drops the voltage on pin 3 of IC5 to 0 V, its output then going to 0 V, setting IC3d to the initial conditions.

IC3c provides a 'power-on reset'. This ensures that the controller does not operate the wipers when the ignition is turned on and power is applied to the unit. It works like this: Capacitor C4 will be initially discharged, holding the inputs of IC3c low. When power is applied to the unit, pin 4 of IC3c will immediately go high. This drives the master reset inputs of

IC6 high via R7, ensuring all the outputs are low, and also drives the threshold input of IC1 (pin 6) high via D1, preventing IC1 from operating and holding its output (pin 3) low. Thus Q1 and RL1 cannot operate.

Capacitor C4 will slowly charge via R6 and when the voltage across it reaches the high threshold (about 4 V,  $\pm 1$  V) of the IC3c inputs (pins 5, 6) the output, pin 4, will go low, readying IC6 for counting. Diode D1 will now be reverse biased and IC1 will be ready for operation.

That covers the general operation, but there are a few more details you'll need to know for better understanding of its operation.

Firstly, the period of IC1 is determined by R3 and C5. The actual period is not critical, so close tolerance components are not necessary here.

The frequency at which IC4 oscillates is determined by R12, R14 and C6. This is about 2 kHz. Here too, the exact frequency is not important, it simply means that at that rough frequency, the stair step generator output steps up to the required level very rapidly.

The RC network consisting of R1-C1-R4 is there simply to provide a pulse. When PB1 is pressed, C1 will initially be discharged, so the voltage across R4 will rise instantly to 8 V. But C1 will charge fairly rapidly and the voltage across R4 will die away quickly. The RC network of R5-C3 is an integrator which 'cleans up' the pulse from PB1. Contact bounce in PB1 may prevent reliable operation of IC3d and thus IC1.

Diode D3 shorts out the back-emf of the relay coil when Q1 turns off, protecting Q1 from collector-emitter reverse voltage breakdown.

The +8 V supply is provided by a simple zener regulator consisting of R24 and ZD1. Capacitor C9 provides supply rail bypassing, as do capacitors C8 and C2.

The 'memory' interval is determined by C7 and R9. We do not recommend you vary R9 if you want to vary the memory interval. Vary the value of C7 instead.

## Project 335

current through the short circuit sets up a field in the armature which reacts with the permanent magnet field so as to produce a force opposing the rotation of the armature.

Connection of the wiper controller relay contact to the wiper system differs for each scheme, and this is covered later in the article.

### Construction

Assembly of the project is quite straightforward. We recommend you use our pc board design. This avoids wiring errors and provides a robust mount for the parts. You can make your own pc board or buy one ready made (see the 'Shoparound' page in this issue). We'll assume you're using our pc board.

All the electronic parts are mounted on the board. The relay and two pushbuttons are mounted elsewhere, in convenient places in the vehicle. Tackle the pc board assembly first. Before commencing assembly, go over the board looking for broken tracks, small 'bridges' between tracks — particularly where they run close together and between IC pins. Also look for holes that haven't been drilled. If, or when, all is well you can tackle the assembly.

There are a total of 11 links on the board. We did this to avoid the expense of a double-sided pc board. Nine of the links are simply straight 'straps' using 22 gauge tinned copper wire (identified by dotted lines on the overlay). The other two are 'flying wire' links — one on the top side of the board (the black, snaky line on the overlay), the other underneath IC6 (shown in the accompanying photograph). Install the tinned copper wire links first. Note that one runs beneath IC5 and another beneath IC6. The flying wire links use insulated hookup wire and are installed later.


With the links in position, all the resistors can be soldered in place. The overlay has been laid out so that component placement is easily identified. Component numbers start in the top left hand corner of the board and go down, then across the board in increasing number. The last resistor (R33) is at the bottom right of the board.

Solder the capacitors in place next. Follow with the two 1N914 diodes, ZD1 (8V2), ZD2 (6V2), Q1 (BD139) and Q2 (BC557). The diodes and transistors have to be correctly oriented. Check which way round they go by looking at the component pinouts and the board overlay.

Now solder IC1, IC2, IC4 and IC5 in place. These are all in 8-pin packages. ICs 1, 2 and 4 are all 555s, while IC5 is a CA3130. Note that all ICs are oriented the same way, with pin 1 toward the 'top' of the board. Last of all, solder IC3 and IC6 in place. These are both CMOS ICs. Only handle them with your thumb and forefinger, holding the package by the ends so as to avoid touching the pins. If you're new to project assembly, a metal IC insertion tool is a great help. Solder pins 7 and 14 of IC3 first, then the other pins. With IC6, solder pins 9 and 16 first, then all the other pins. Do not use IC sockets as vibration in a vehicle can 'jog' the ICs out of the sockets.

Now you can install the flying wire links.

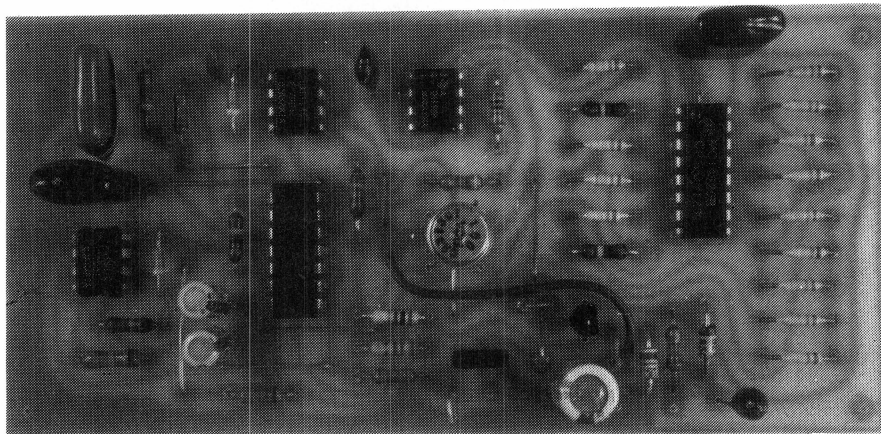Connection between the board and the external components, the relay and pushbuttons, is made via a six-way terminal



**Circuit board.** The completed pc board. Note that some resistors are stood on end. The pc board pattern is reproduced on page 111.

block. At this stage, you're going to have to work out where everything is to fit in your vehicle. You've probably already done that, anyway. You could temporarily hook things up and try it out (without connecting the relay contacts), just to see if it works and to sort out any possible troubles before finally installing the unit.

When testing it out, check that it works as described and see that the between-wipers 'memory' is at least 30 seconds. This will vary somewhat from unit to unit, because of the tolerance range of C7 and R9. That doesn't really matter, just so long as the maximum interval is about 30 seconds.


We mounted the pc board in a conveniently sized jiffy box and tucked it away under the dash. A 50 x 90 x 150 mm box will comfortably accommodate the board. Mount the six-way terminal block on the outside and inscribe the box with the A-B-C-etc terminal designations. The WIPE and STOP buttons can be mounted in any convenient position on the dash — either by drilling holes in the dash or mounting them to a box or bracket which is then affixed to the dash.

For the pushbuttons, you'll find the larger variety better to use, not the miniature ones. Both PB1 and PB2 are momentary-contact (SPST) types. Dick Smith Electronics stocks a suitable type, catalogue S-1199, as do Altronics (catalogue no. S 1080) and Electronic Agencies (catalogue no. SE0252). All these have a 15 mm square button (you can have any colour you like, so long as it's red) and require a 12 mm mounting hole.

The relay, as originally suggested by J.D.W., can be mounted in the engine compartment. This means you don't hear it going 'click-click' all the time when the wipers are in use. Any standard 12 V relay with a set of changeover (SPDT) contacts rated at 5A at least can be used. If you can find one with lugs that take automotive-type slip-on spade connectors, so much the better.

Don't forget to wire D3 across the relay coil. You could, if you like, mount D3 on the six-way terminal block. (No, we didn't forget to include this on the board. It's just that, as the board was getting pretty cramped, it was more convenient to mount D3 off the board.)

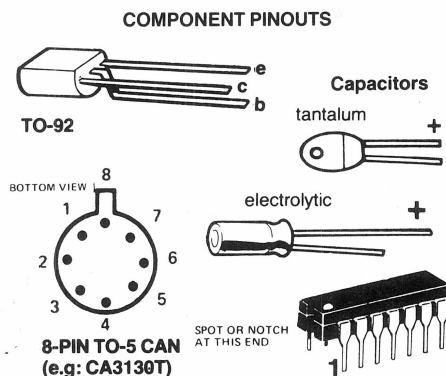
Secure the relay firmly with a bracket. Use medium or heavy duty hookup wire (10 x 0.2 mm or 24 x 0.2 mm) to wire in the relay and pushbuttons.



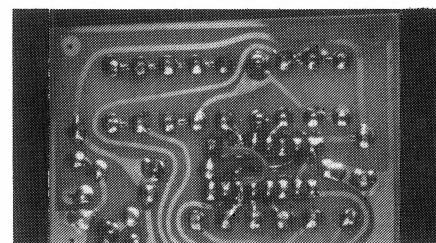
### Wiring it to the wiper system

The general wiring schematics for single- and dual-speed wiper systems employing wound-field motors are shown in Figures 3 and 4. In each case, the *normally open* relay contacts of the controller are wired in parallel with the parking switch. Trace the wiring between the wiper motor and the switch. For the type of system shown in Figure 3, the switch will have two wires running between it and the wiper motor. It should be an easy matter to sort out which wire is which and to connect the relay contacts accordingly.


The dual-speed system shown in Figure 4 will have three wires running from the wiper switch to the motor. Grounding lead 1 should set the wipers going in 'high speed', grounding leads 2 or 3 should set the wipers going in 'low speed'. You can connect the normally open relay contacts (G and H) from 2 or 3 to chassis, or from 1 to chassis. In the latter case, you can operate the wipers right up to maximum speed.



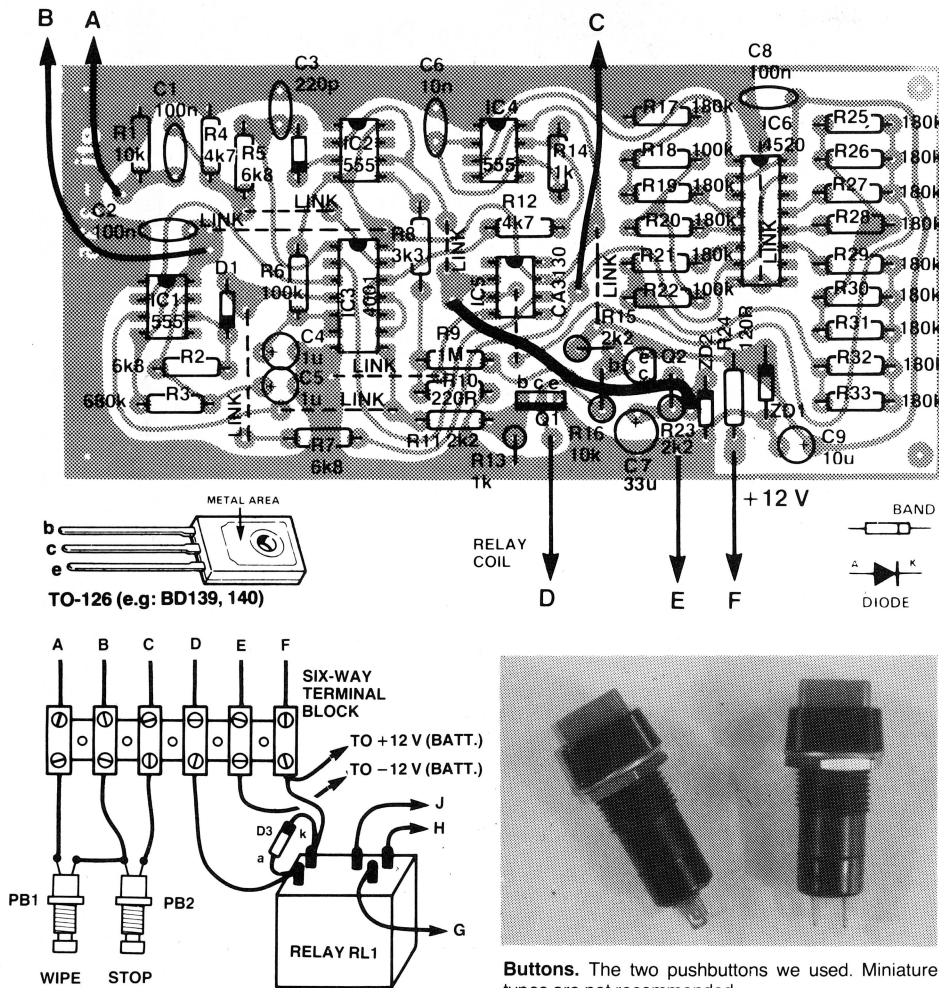**Underside link.** Rear view (copper side) of the board showing the link between pins 6 and 10 of IC6.



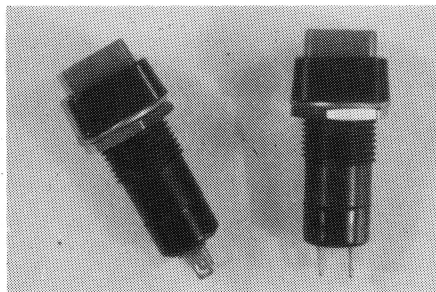**Buttons.** The two pushbuttons we used. Miniature types are not recommended.



The two pushbuttons we used. Miniature types are not recommended.


A dual-speed permanent magnet system is illustrated in Figure 5. Here, the wire from the wiper switch to the parking contacts (3) is cut at X-Y and the wiper controller's *normally closed* contacts (J and G) connected across the cut. The normally open contact (H) is connected to chassis. If you need maximum wiper speed when using this system, simply use the wiper switch as you normally would.

In most instances, the chassis (earth) contact for the wiper switch is made through the body of the switch. Those systems which include a washer system where the washer is activated by pushing the wiper switch will have an extra wire for the washer. Some systems, usually found on British cars, are arranged to operate independently of an earth (i.e. do not use the vehicle chassis as a


PARTS LIST — ETI-335	
<b>Resistors</b>	all 5%, 1/2W unless noted
R1	10k
R2, 5, 7	6k8
R3	680k
R4, R12	4k7
R6, 18, 22	100k
R8	3k3
R9	1M
R10	220R
R11, 15, 23	2k2
R13, R14	1k
R16	10k
R17, 19, 20, 21	180k
25-33	180k
R24	120R
R17	180k
R18	100k
R19	180k
R20	180k
R21	180k
R22	100k
R25	180k
R26	180k
R27	180k
R28	180k
R29	180k
R30	180k
R31	180k
R32	180k
R33	180k
<b>Capacitors</b>	
C1, 2, 8	100n ceramic
C3	220p ceramic
C4	1u/10 V axial electro.
C5	1u/10 V tant.
C6	10n ceramic
C7	33u/10 V tant.
C9	10u/10 V tant.
<b>Semiconductors</b>	
IC1, 2, 4	555
IC3	4001
IC5	CA3130
IC6	4520
ZD1	8V2 1 W zener
ZD2	6V2 1 W zener
Q1	BD139
Q2	BC557
D1, D2	1N914, 1N4148
D3	1N4001, 1N4002 etc.
<b>Miscellaneous</b>	
ETI-335 pc board; RL1 — SPDT relay with 5 A contacts and 180 ohm (or greater) coil (e.g. Dick Smith S-7125, or similar); PB1, PB2 — momentary contact pushbuttons (e.g. Dick Smith S-1199, or similar); 6-way terminal block; box to suit — 50 x 90 x 150 mm (if necessary); hookup wire, nuts, bolts etc.	

return lead) so that they may be fitted to either positive or negative earthed electrical systems. In such cases, you'll find a fifth wire extended from the wiper switch to the wiper motor, as indicated in Figure 5.


The installation of this wiper controller in no way alters normal operation of the wipers via the wiper switch installed in the vehicle.

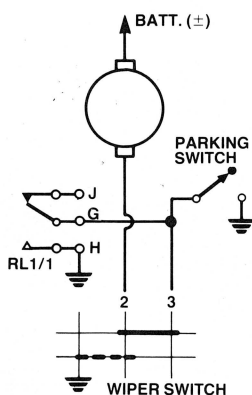

**Figure 3.** Wiring the relay contacts to a single-speed wound field wiper system.

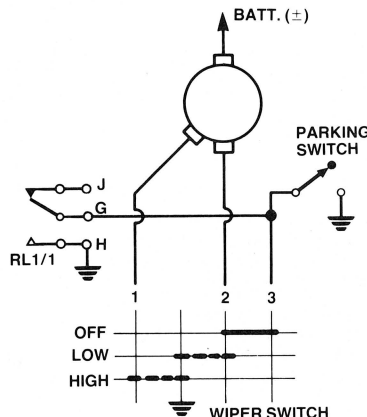

**Figure 4.** Wiring the relay contacts to a dual-speed wound field wiper system.

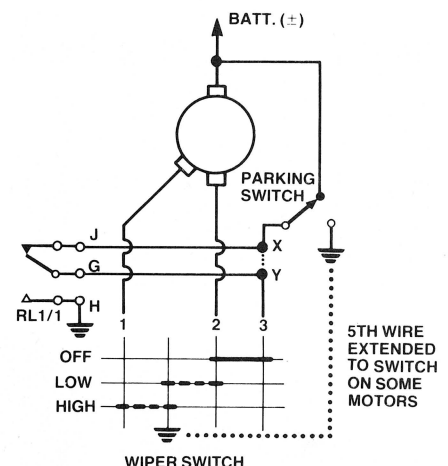

**Figure 5.** Wiring the relay contacts to a dual-speed permanent magnet wiper system.

# MULTIRAIL SWITCHING POWER SUPPLIES



**More choice, more performance, more efficiency, more back up and support — at a truly competitive price.**

- ☐ Single, three & four rail outputs
- ☐ 240V/120V AC input
- ☐ 3.5kV isolation
- ☐ 50KHz switching
- ☐ Standard models
- ☐ Custom design available

- ☐ Output overvoltage shutdown
- ☐ Australian design & manufacture
- ☐ 5 year guarantee
- ☐ Short circuit protected
- ☐ Full local technical back up & service
- ☐ DCLO signal
- ☐ Convenient plug in connectors
- ☐ High efficiency
- ☐ Fan output
- ☐ Compact, rugged, reliable

For complete data, call Scientific Electronics or the distributor in your state.

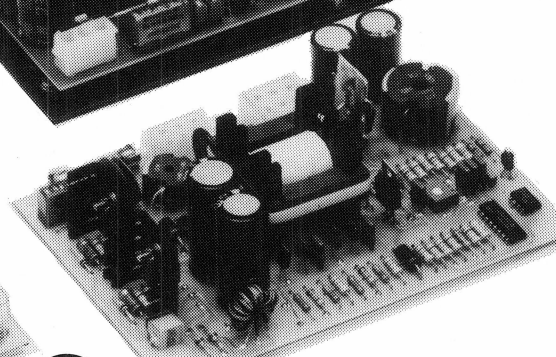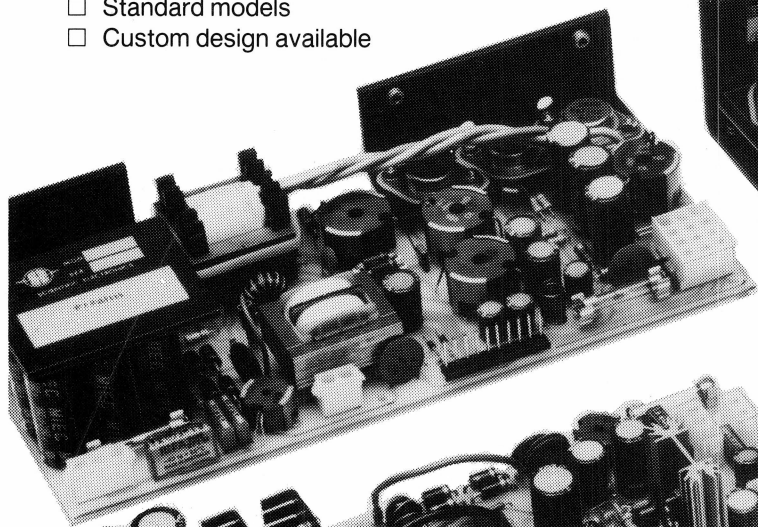**Scientific Electronics  
The Power Supply  
Specialists.**



**MADE IN AUSTRALIA**

**Distributors:** Victoria, Electro Technics 699 2716. N.S.W., Electronic Developments 438 2500.  
S.A., Graphic Electronic Industries 42 6655. QLD., Fred Hoe & Sons 277 4311. W.A., W.J. Moncrieff Pty. Ltd., 325 5722



**Scientific Electronics**

6 Holloway Drive, Bayswater,  
Victoria, 3153

Tel. (03) 762 5777 Telex AA 36308



**ALTRONICS .. ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS**

# A 'float' charger for NiCad batteries

This NiCad battery charger provides a happy medium between fast chargers and constant-current chargers. It's cheap, simple to build and will bring a battery to full charge from complete discharge in 12 hours — then keep it there. And your NiCads are safe from overcharging damage.


Jonathan Scott

AS YOU MIGHT INFER from the great range of chargers available and the number of projects describing them appearing in this and other magazines (should you ever read one, accidentally) there is more to charging NiCads than meets the eye. NiCads are rather finicky things to deal with in that they basically require fairly continuous attention. The very best conditions are simply *use*: if you discharge and charge a set of NiCads once a week or so, they deliver hundreds of cycles quite happily.

However, this is not the case in many typical applications. They may be unused for weeks or months in the flashgun of your camera or as battery backup in instruments. They may, on the other hand, be left trickle-charging endlessly and never discharged more than 10%, as is the case in a torch used for two minutes every week. Neither form of disuse is good. You can get fast chargers, such as the ETI-563, or the recommended controlled current source type which will charge at the ten-hour rate, or very low current trickle charge types such as are incorporated in some electric toothbrushes or small torches. Trickle chargers are safe in that the NiCads are not actively harmed no matter how long you leave them connected, but the cells take three days to recover a full charge. The controlled current sort are able to charge a cell right up in about 14 or 15 hours, but will upset the cells in about 24 hours if left on. Fast chargers are damn quick, and fairly safe if they are the type which turn off and you set them for the correct time, but are more costly and bulky.

Hence we present yet another alternative. This project will bring a set of cells up to full charge from complete discharge in about 12 hours and then automatically drop to a trickle whenever the charging is done. This means full recovery in half a day with safety from overcharging damage. Hence the title, 'Float Charger'.

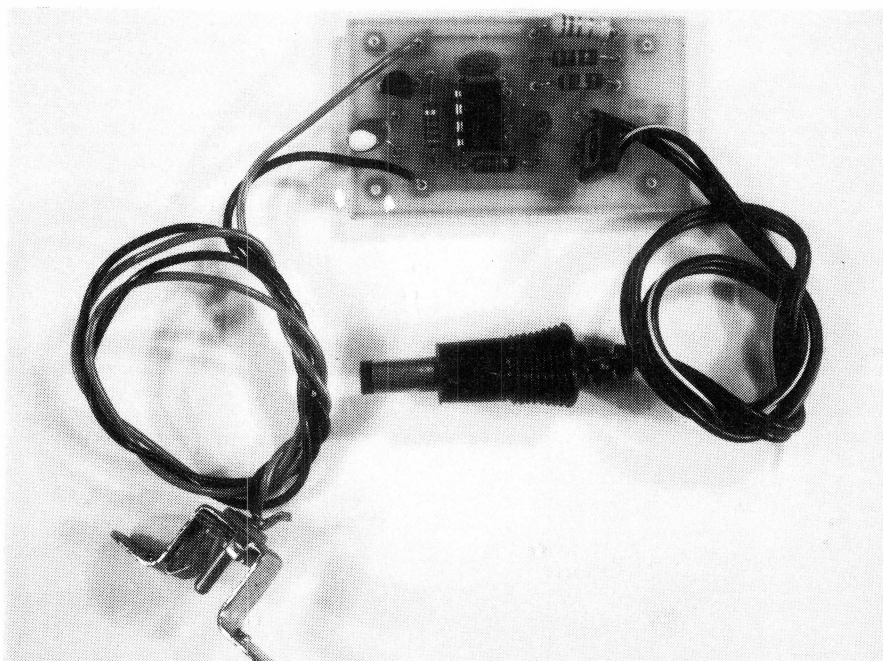The circuit presented here is specifically designed for penlight size batteries ('AA') and is arranged to charge four cells in series, which is the number generally found in portable cassette players, etc. You're not locked-in to this set of circumstances however. You can charge different numbers of cells of amp-hour capacities between 250 mAh ( $\frac{1}{4}$  Ah) and 1 Ah



**Simplicity plus!** A handful of components, a 30 x 50 mm pc board . . . and no complications.

simply by selecting the values of three resistors according to Table 1. The project will charge up to four cells from a 10 volt supply. For each additional cell, the supply needs to be increased by 1.5 V. i.e: six cells need 13 volts supply.

Although the project will charge cells of up to 4 Ah capacity it will work at full rate only on cells up to 1 Ah, but this is not a serious problem as most small appliances and backup systems use quarter or half amp-hour types.

The project can be incorporated inside a piece of equipment or it can be built into some dedicated charger at very little cost (under \$10) and will run off any power supply of 10 to 22 volts (according to what's required). e.g: a plugpack, car battery, power supply, etc. In addition, there are no controls or presets to adjust at all. Some chargers of this type require calibration against a digital meter or similar, but this one is born calibrated. It may be fabricated on its own pc board or incorporated in the power supply of something you are building.

## Construction

Construction of this project is largely left up to you as far as boxes and connectors go because of the many possibilities you have open. The prototype was left unencapsulated, and has been fitted with a plugpack receptacle on the input end and a similar plug on the output as it has been designed to go between a small cassette player and a plugpack originally provided to charge the cells inside the player. A car cigarette lighter plug could just as easily be fitted to allow use in a car. If you do not intend to use a carefully polarised input connector, a diode in series with the input is a good idea as the unit will be damaged if exposed to reverse polarity.


The first thing to do before constructing the project is to select values for the three resistors  $R_A$ ,  $R_B$  and  $R_C$  according to Table 1, given the size (Ah capacity) and number of the cells to be charged. If your application has a number of cells not covered in the table, use the formulae given there to find values. ►

# HOW IT WORKS — ETI-268

The 'ideal' charger for NiCad batteries is a precision voltage source in series with a fixed resistance — where the voltage source is a little above the battery terminal voltage when fully charged. Thus, when a discharged battery is connected, the charge current is maximum, reducing to a 'trickle' when the battery is fully charged. That's what this project has been designed to do. It makes use of a low cost precision reference element, an LM336, and a comparator driving a series-pass transistor to control the charge current applied to the batteries.

The precision voltage reference, IC1, looks to 'the outside world' as a zener diode. The 'adj.' terminal permits adjustment of either the terminal voltage (over a very small range) or the temperature coefficient (how the terminal voltage drifts with variation in temperature). The 8k2 resistor, R1, provides current for IC1 which produces a fixed potential of between 2.390 V and 2.590 V below the positive supply rail at its anode. This is fed to pin 2, the inverting input, of the 308 (IC2) which is here arranged as a comparator.

The non-inverting input of IC2 (pin 3) is fed by a voltage that depends on the sum of the terminal voltage of the cells being charged and the current fed to them. Three resistors —  $R_A$ ,  $R_B$  and  $R_C$  — sample the cell terminal voltage and charging current, providing a fixed sum of these variables. The output of IC2 drives the base of Q1 via LED1. Q1 controls the charging current fed to the cells. The sum of the voltage drops across  $R_C$  and  $R_B$  is maintained at the same voltage as that across IC1. As the terminal voltage of the cells rises with charging, the voltage drop across  $R_C$  will

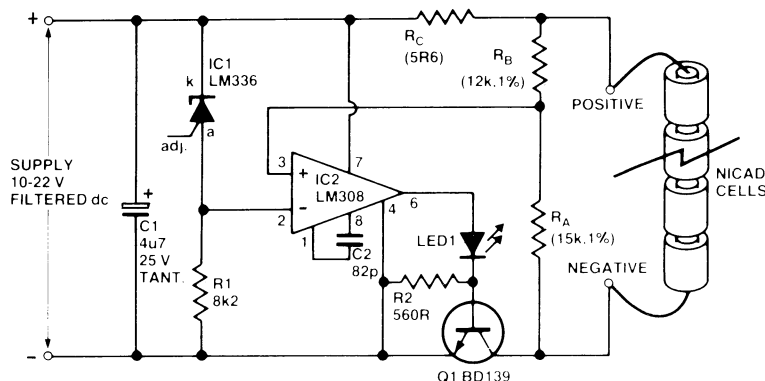

decrease, but the voltage drop across  $R_A/R_B$  will increase. The ratios have been set so that the drive to the base of Q1 decreases as cell voltage rises.

The LED between the base of Q1 and the output of IC2 serves two purposes. It provides the voltage offset required between the IC's output and the negative supply rail as the 308 cannot drive its output right down to the negative rail; and secondly, it gives an indication that the charger is operating. (You can check that the load is correctly connected by looking for an increase in intensity when connection to the cells is made). Resistor R2 keeps Q2 turned off when required and ensures that there is some current flowing in LED1 even when the load draws no current. Capacitor C1 removes any hash from the supply which might upset the 308 in a noisy environment. Capacitor C2 provides compensation for IC2.

Neither capacitor is critical in value, but C1 should be a tantalum type if you intend to run the charger in harsh electrical environments such as a car or near RF equipment. A 308 was chosen for IC2 as it has a very low offset voltage and a high input impedance.


The output of the 308 is current-limited internally and since the load current is equal to the beta of Q1 times the current sourced to its base, the output is current-limited to a value of around 300 mA or so. If the charger output is likely to be shorted (or if the possibility exists), Q1 should be placed on a small heatsink, for safety's sake. Under normal operating conditions charging penlight (AA) cells, Q1 does not require a heatsink. Should you wish to upgrade the unit for higher charging currents, a Darlington-pair device should be substituted for Q1, with suitable heatsinking attached.

## THE NICKEL-CADMIUM CELL (NiCad)


NiCad cells use a potassium hydroxide electrolyte. In a typical unit the positive and negative plates are both perforated steel. The positive plate is filled with nickel hydroxide, the negative plate with finely divided cadmium mixed with a little iron to prevent it flaking and losing porosity. The electrolyte has a specific gravity of 1.15-1.2, depending on the type of service. It does not undergo any chemical change during discharge. Very little electrolyte is needed and the positive and negative plates are very closely spaced.

NiCad batteries are made in a wide variety of sizes and amp-hour capacities. Miniature ones for use in cameras, calculators etc up to large heavy duty types similar to car batteries. They may be operated over a wide temperature range — similar to that of lead-acid batteries. At low temperatures, the amp-hour capacity does not diminish as much as with lead-acid batteries. However, the electrolyte may freeze.

As NiCad batteries may be sealed, they can be used in any position. The no-load terminal voltage of a nickel-cadmium cell is typically 1.3-1.4 volts. This drops to about 1.2 volts under load, and to about 1.1 volts when discharged. As the electrolyte does not change during discharge (as it does in lead-acid batteries); the number of amp-hours obtained from a NiCad battery is much less affected by the discharge rate than are lead-acid batteries.

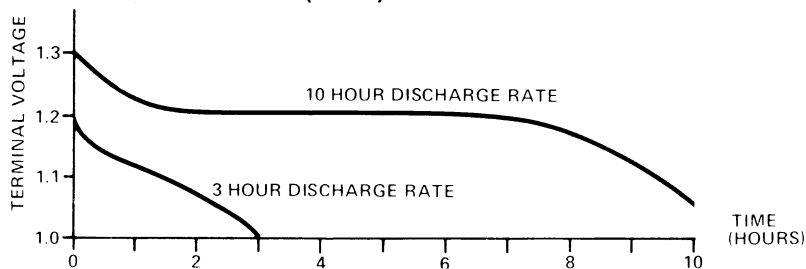

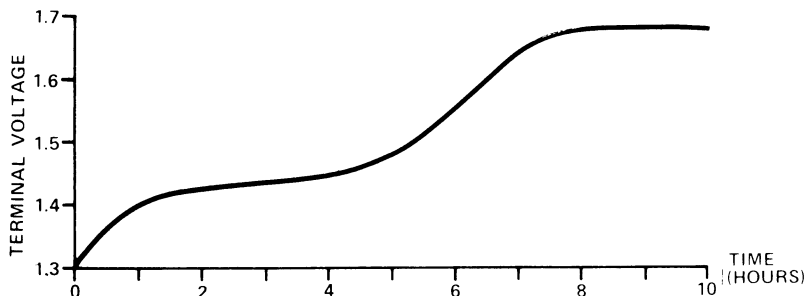Going down. Typical discharge characteristics of NiCad cells.



Juicing up. Typical charging characteristics of NiCad cells.

As NiCad batteries can be made quite small, and can be recharged, they are eminently suitable for use in portable electronic equipment such as calculators, tape recorders, hand-held transceivers, camera flash units etc. They can withstand considerable vibration, are free from sulphating or similar problems, and can be

left in any state of charge without ill effect.

Charging should be done with a constant-current charger. The charging rate for the quickest charge should be no more than 1.5 times the 10 hour discharge rate. Most manufacturers recommend a charge rate and a trickle or 'float' charge rate and this is best adhered to.

## PARTS LIST — ETI-268

**Resistors** ..... all  $\frac{1}{2}W$ , 5% unless noted

R1 ..... 8k2

R2 ..... 560R

R<sub>A</sub> ..... 15k,  $\frac{1}{4}W$ , 1% see Table 1

R<sub>B</sub> ..... 12k,  $\frac{1}{4}W$ , 1% see Table 1

R<sub>C</sub> ..... 5R6 see Table 1

## Capacitors

C1 .....	4u7 or 10u 25 V tantalum
C2 .....	82p ceramic


## Semiconductors

IC2	LM336
IC3	LM308, uA308 (or /A)
LED1	RL209R miniature red LED, or similar
Q1	BD139


### Miscellaneous

ETI-268 pc board; supply input and charger output connectors to suit (see text); small heatsink (see text) if necessary; hookup wire etc.

**Price estimate**  
**\$7 — \$8**

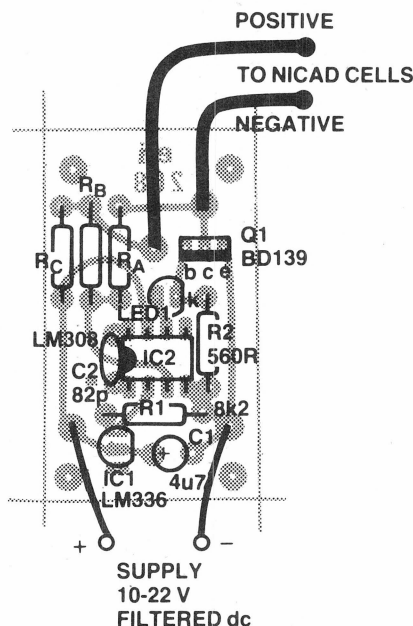

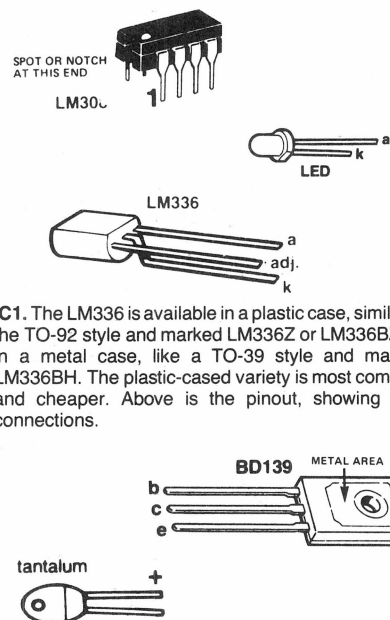**Overlay.** Showing component positioning on the pc board. Components are placed on the non-copper side of the board. Watch the orientation of C1, IC1, IC2, Q1 and LED1. Check these with the component pinouts.



**IC1.** The LM336 is available in a plastic case, similar to the TO-92 style and marked LM336Z or LM336BZ, or in a metal case, like a TO-39 style and marked LM336BH. The plastic-cased variety is most common and cheaper. Above is the pinout, showing lead connections.

Next, fit the components to the pc board according to the overlay, being sure to get the ICs, LED, transistor and tantalum capacitor the correct way around in each case. If you intend to charge cells larger than penlight size, or there is a possibility of more than momentary shorting of the output, leave enough length in the leads of Q1 and fit a small heatsink, about 2 cm<sup>2</sup> in area.

Mounting holes have been marked on the pc board if needed so it can be attached to a chassis.

Once assembled, fit the wires and connectors. A small clear or amber plastic pill bottle makes an excellent case for this project if no particular location is necessary. The wires can be knotted and slipped through two small holes in either end.

## Turn on

Apply power and see that LED1 illuminates. If not, switch off and check the LED orientation and the supply polarity. Fix any faults

and start again. Then connect the cells. A small increase in brightness of the LED should be noticeable as you make the circuit.

Note that you cannot normally judge correct operation by inserting a current meter in series with the batteries as this upsets the sensing by virtue of the slight voltage drop across the meter terminals. Instead, measure the voltage across  $R_C$ , and divide by the resistance to determine current flowing. ●

### TABLE 1

(A)			
Cell capacity	$R_C$		
250 mAh	12R		
500 mAh	5R6		
1000 mAh	3R3		

(B)			
No. of cells	$R_A$	$R_B$	Supply (min.)
2	1k5	10k	10 V
4	15k	12k	10 V
6	68k	27k	13 V
10	56k	12k	19 V
	$\frac{1}{4}W, 1\%$	$\frac{1}{4}W, 1\%$	

### CALCULATION OF VALUES

Make  $R_B$  a convenient value below 100k


$$\text{then, } R_A = R_B \left( \frac{C}{1.754} - 1 \right)$$

where  $C$  is the number of cells.

Go through the routine, reselecting a new value for  $R_B$ , if  $R_A$  does not come out within one or two per cent of a common value.

$$R_C = \frac{3}{I_{nom}}$$

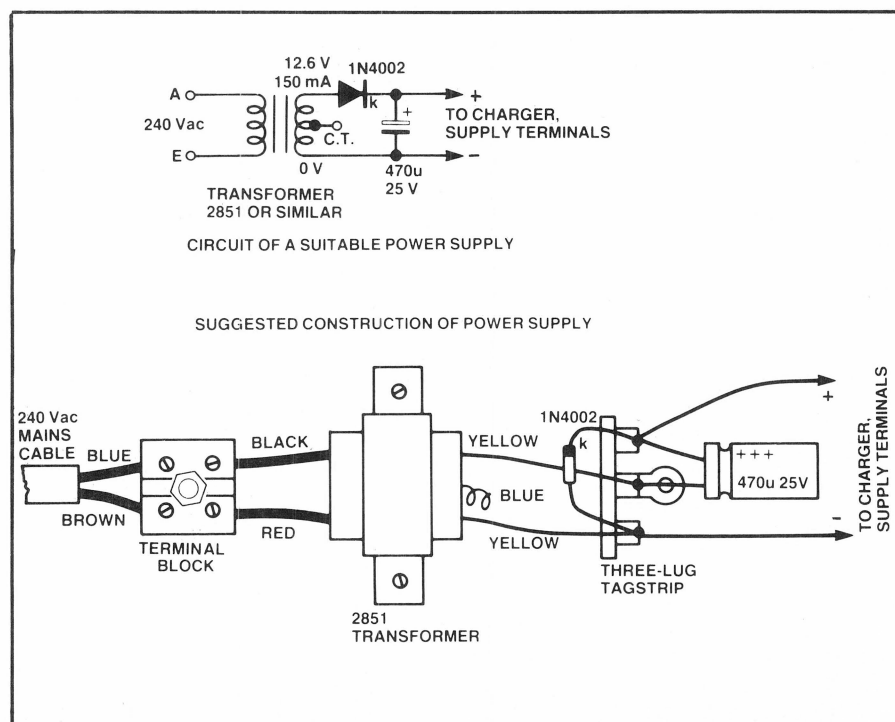
where  $I_{\text{nom}}$  is the nominal 10 hour charge rate.



**THINKING ABOUT  
BUYING A SCOPE?**

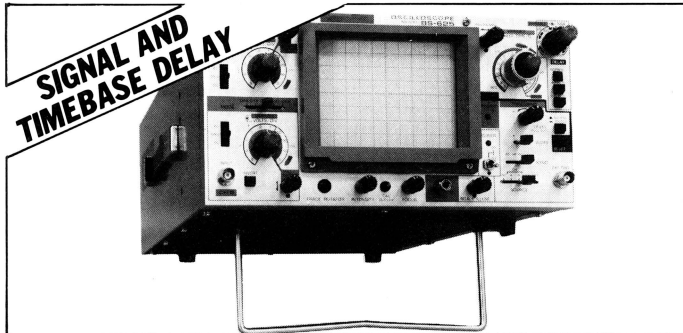
# FOR PERFORMANCE & VALUE AARON HAS TO BE YOUR FIRST SCOPE CHOICE

*All these scopes are dual trace and incorporate  
the latest features such as high brightness rectangular CRTs.*




- 7.7nS risetime
- Single sweep
- Trigger delay
- TV sync
- X-Y, dual, chop, add, subtract etc.

**45MHz/1mV**  
BS625 **\$990.00**

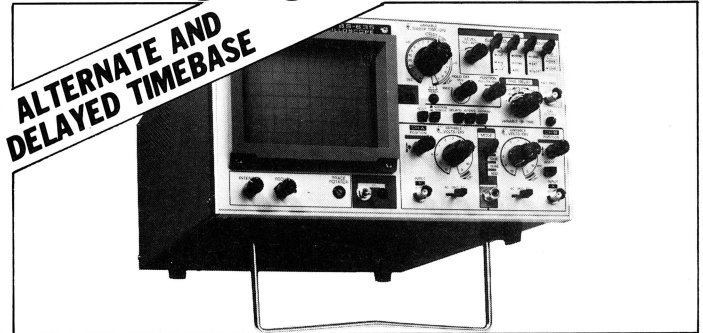

- 21 range timebase
- 100mS-1  $\mu$ S trigger delay
- Front panel trace rotate
- X-Y, dual, chop, add, subtract etc.

**35MHz/1mV**  
BS635 **\$790.00**

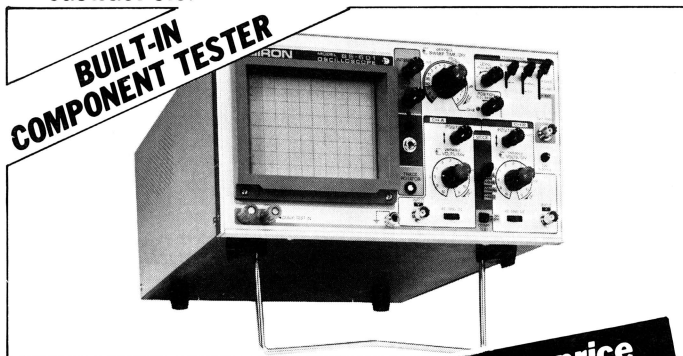


- Check components on screen
- 19 range timebase
- Triggerable to over 30MHz
- 17nS risetime

**New low price  
for popular  
AARON scope**  
**\$485.00**

**20MHz/5mV**  
BS601 **\$550.00**

## QUICK SPEC CHECK

MODEL	B'WIDTH	SENS	SIG DEL	TRIG DEL	SCREEN	T'BASE
625	45MHz	1mV	Y	Y	150mm	0.2 $\mu$ S - 0.5S/div
635	35MHz	1mV	N	Y	150mm	0.1 $\mu$ S - 0.5S/div
601	20MHz	5mV	N	N	150mm	0.5 $\mu$ S - 0.5S/div
310	15MHz	2mV	N	N	95mm	0.5 $\mu$ S - 0.5S/div

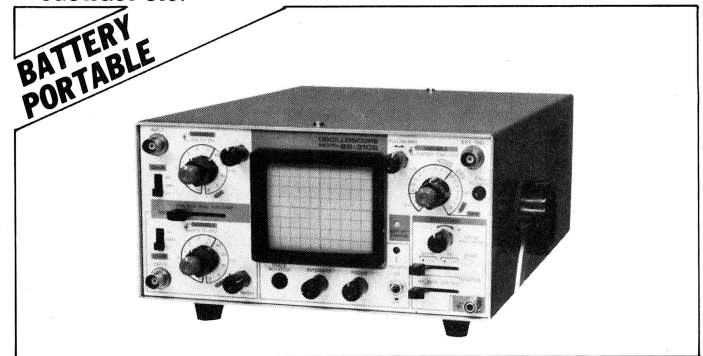

- 2 hour operation from built-in NiCad battery
- Automatic recharging
- Auto trigger free run
- TV sync

**15MHz/2mV**  
BS310 **\$720.00**

## COLINE SP100 PROBE

Professional 100MHz probe offering x1, ref, x10 positions. 1.5m lead with BNC connector and selection of tips. Complete in heavy duty plastic pouch. **\$25.00**



# ELMEASCO

## Instruments Pty. Ltd.

P.O. Box 30, Concord  
N.S.W. 2137  
13-15 McDonald Street,  
Mortlake, N.S.W.  
Telephone (02) 736 2888  
Telex 25887

P.O. Box 107, Mt. Waverley  
Victoria 3149  
21-23 Anthony Drive,  
Mt. Waverley, Victoria  
Telephone (03) 233 4044  
Telex 36206

Adelaide: (08) 271 1839  
Brisbane: (07) 369 8688  
Perth: (09) 398 3362



N.S.W. Ames Agency 699 4524 • George Brown 519 5855 • Davred 29 6601 • DGE Systems (049) 69 1625 • Radio Despatch 211 0191 • Vimcom (042) 28 4400 **VICTORIA** Radio Parts 329 7888 • Browntronic 419 3986 • G.B. Telespares 328 4301 • Elanco 428 4345 • Ellistronics 602 3282 **QUEENSLAND** L.E. Boughen 36 1277 • Colourview Wholesale 275 3188 • Audiotronics 44 7566 • Electronic Shop (075) 32 3632 • Nortek (077) 79 8600 • W.G. Watson (079) 27 1099 **S.A.** Protronics 212 3111 • Trio Electrix 51 6718 **W.A.** Atkins Carlyle 321 0101 • Hincro Eng 381 4477 • Brookades 276 8888 • Protronics 362 1044 **A.C.T.** Actice (062) 80 6576 **N.T.** Thew & McCann (089) 84 4999 **TAS.** G.H.E. Electronics 31 6533 & 34 2233.

## MAIL COUPON FOR FREE GUIDE

Please send me a copy of your shortform oscilloscope guide.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_  
P'CODE \_\_\_\_\_


TELEPHONE \_\_\_\_\_

# ROBOTICS

JAYCAR — FIRST IN AUSTRALIA  
WITH THE VERY LATEST IN THE  
FIELD OF ROBOTICS

Jaycar is the first major electronics company in Australia to stock useful robots in kit and built-up form. Shown below are two models destined to become standards.

## MICRO GRASP

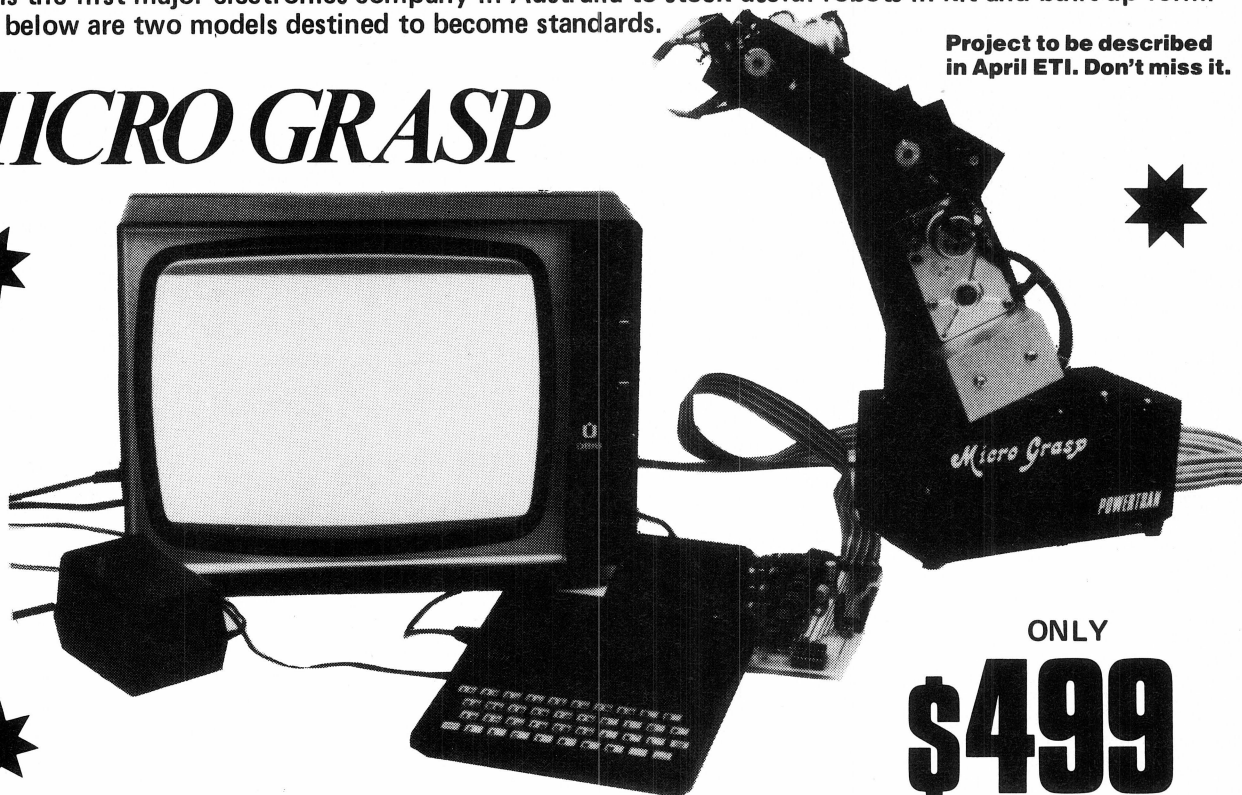

Project to be described  
in April ETI. Don't miss it.

ONLY  
**\$499**

The Micro Grasp is the first low-cost true robot. Basically the unit has an articulated arm jointed at the shoulder, elbow and wrist positions. The entire arm rotates on its base and has a motor driven gripper on the end of the arm. Each of the arm movements is SERVO CONTROLLED i.e. there are position sensors feeding back information to the interface board where it is compared with the programmed in intended position. Any positional error is automatically and continuously corrected. This servo action is independent of the computer, simplifying greatly the software to drive the robot. All programming is carried out with a small number of common BASIC commands. The interface board is memory mapped using only 64 Bytes at any of the 1024 switch selectable locations.

Control of the Micro Grasp as a computer peripheral is accomplished thru the parallel expansion part of most small computers. To keep the cost to an absolute minimum and to increase the learning factor the Micro Grasp is supplied as a self-assembled kit. All components down to the last nut and bolt are included, as is the power supply.

**MICRO GRASP KIT INCLUDING POWER SUPPLY Cat. XR1000 — SPECIAL INTRODUCTORY PRICE \$499.00**


**UNIVERSAL COMPUTER INTERFACE BOARD (in kit form) Cat. XR1010 ONLY \$179.00**

23 + 23 way edge connector at \$9.95

ZX-81 peripheral/RAM pack splitter board \$10.95

**CALL IN TO OUR YORK STREET SHOWROOM AND SEE WORKING!!**

## GENESIS P-102

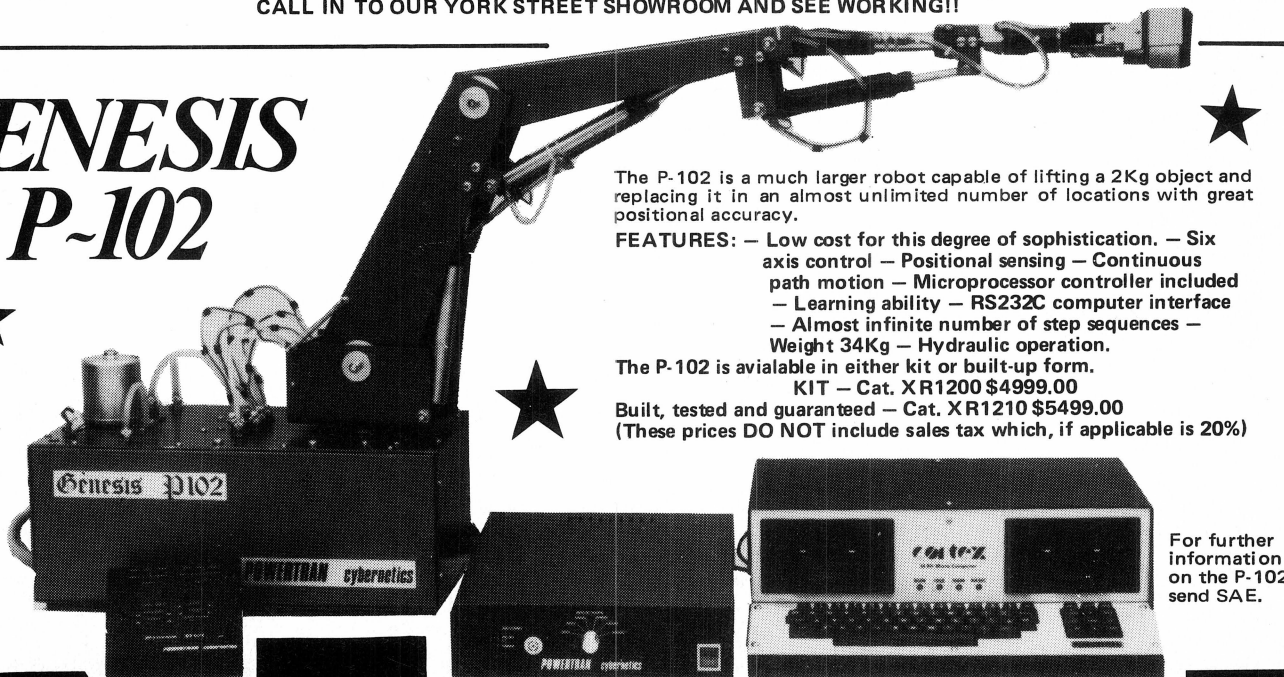

The P-102 is a much larger robot capable of lifting a 2Kg object and replacing it in an almost unlimited number of locations with great positional accuracy.

**FEATURES:** — Low cost for this degree of sophistication. — Six axis control — Positional sensing — Continuous path motion — Microprocessor controller included — Learning ability — RS232C computer interface — Almost infinite number of step sequences — Weight 34Kg — Hydraulic operation.

The P-102 is available in either kit or built-up form.

**KIT — Cat. XR1200 \$4999.00**

**Built, tested and guaranteed — Cat. XR1210 \$5499.00**

(These prices DO NOT include sales tax which, if applicable is 20%)

For further  
information  
on the P-102  
send SAE.

# NEW PRODUCTS




## MICRO CHARTS

Instant Data on the Most Popular Computer and Microprocessor Parts

- Fully decoded data — no need to unscramble numbers
- Instant Access
- Compact 8½" x 11" size
- Durable credit card plastic — lasts a lifetime
- Perfect for programmers and engineers — two-sided and totally comprehensive
- Clear and concise tables for: full instruction set, disassembly, ASCII, base conversion, effect of flags, compare vs. jump, interrupt structure, pinout, cycle times, diagrams, bug notes, and much more...

Cat. BM8500	Z80 CPU	\$12.95
Cat. BM8501	8080A/8085A	\$12.95
Cat. BM8502	6502(65XX)	\$12.95

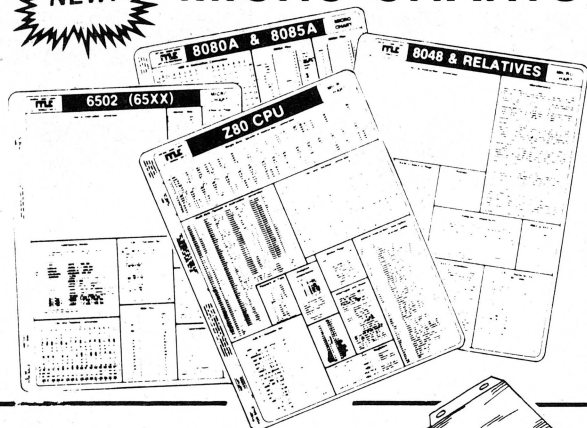

## COMPUTER TRANSFORMER BARGAIN ONLY


**\$29.50**

We have secured a quantity of a power transformer at a never-to-be repeated price. This transformer is ideal as the basis of an S-100 power supply, but can be used for many other computer or general power supplies.


**SPECS:** Primary 240VAC — Secondary 1: 15VAC 2 amp — Secondary 2: 15VAC 2 amp — Secondary 3: 8VAC 8 amp.

A typical DC supply could be ±15VDC @ 1.5A & 5VDC @ 8A or ±12VDC @ 2A & 5VDC @ 8A.

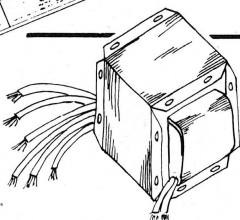This transformer would normally sell for around \$50 but for March only \$29.50. Brand new stock.



## The Probe Case

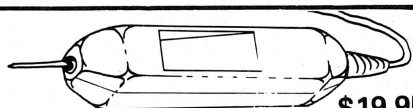


**\$19.95**

AT LAST! WE HAVE A QUALITY PROBE CASE AFTER HUNDREDS OF CUSTOMER REQUESTS.

Includes grey plastic case shell halves; threaded 1.5 inch (38mm) probe tip; hexagonal-barrel female probe tip connector; 36 inch (914 mm) polarised two wire power cord with red, black vinyl jacketed alligator clips attached, molded strain relief feature; pre-cut perf board; mounting screws. Dimensions: 147L x 25W x 18Hmm. Weight 85 grams. Useable PCB area 3.9 x 1.0 inches. Cat. HB6400


## QUALITY REED SWITCH SLASHED!!!

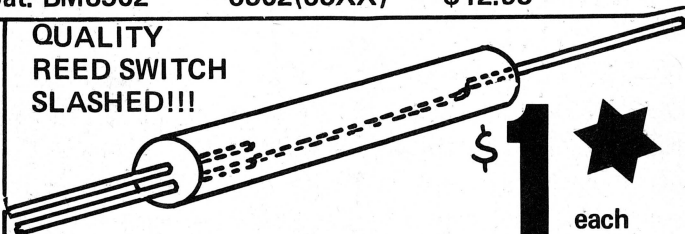

There are reeds and there are reeds. This one is a beauty. Firstly its ALL gold plated with precious metal contacts configured in Single Pole Changeover (i.e SPDT). The glass envelope is inert gas filled. The envelope is 36mm long and 5mm diameter — total overall inc. leads 90mm. This is a three dollar reed normally. But — March only \$1. Cat. SM1050

## SOLAR CELLS NEW LOW PRICE

FROM \$3.45

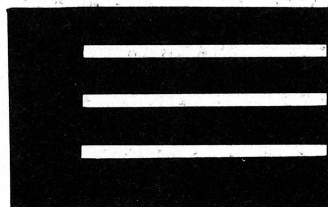

Cat. ZM9000 — 20mm Square unit which gives a whopping 0.4V @ 100mA in bright sunlight! Can be stacked in series or parallel for higher voltage/current combinations. Square cut for efficient packing density.

Only \$3.95 ea or \$3.45 10+ each.

## low cost IC inserters

## AND EXTRACTORS

Up until now these have cost a fortune!!

### Features:

- CMOS SAFE conductive plastic
- Exclusive bent pin alignment guides in handle . 8 to 40 pins.
- Ground strap can be connected.
- One hand operation.

### INSERTERS

CIT820	8—20 pin	ONLY \$5.95
CIT2428	24—28 pin	ONLY \$6.95
CIT3640	36—40 pin	ONLY \$8.95
CIT22	22 pin	\$6.50

### EXTRACTOR

Deceptively simple looking device. One piece metal construction. 8-40 pins ET-840 ONLY \$2.95

**IMPORTANT!!**  
Don't be conned into buying a non conductive inserter/extractor. The possible static damage to your MOS I.C.'s could cost you a fortune!!



**from \$2.95**

## superbright LED

The average 15 cent LED has a light output of 1.8mCd (milli Candelas) at 20mA. Can you imagine a 200mCd LED? (at 20mA)? Well if you can't — buy one and find out. They are ideal for panel illumination or very low current work. (They will still give useful light at 1mA!).

Red with clear lens — 69c each  
10 up only 62c each. . . .

Cat. ZD1790

**69¢**



## Jaycar NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000

PHONE: 264 6688 TELEX: 72293

"NEVILLES CORNER"

Cnr. CARLINGFORD & PENNANT HILLS ROAD,

CARLINGFORD

PHONE: 872 4444

MAIL ORDERS TO: BOX K 39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES

\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)

\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)

\$100 up (\$8.00)


NEW SHOP HOURS

10.30 to 5.30pm

Sat 8.00 to 12.00pm

Thurs night to 8.30pm

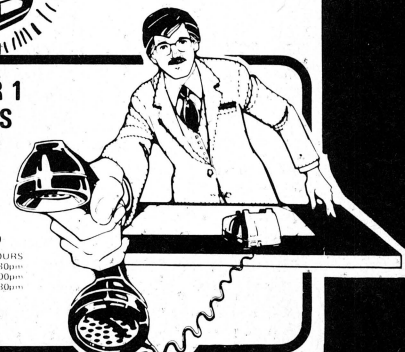Mail Order By **BANKCARD**  
Via Your Phone



# General purpose analogue and digital interface card for the Apple II

Phillip John McKerrow

Lecturer in Computing Science  
University of Wollongong, NSW

Now you can plug in your Apple to the 'real world'. This card has one analogue input and one analogue output plus eight digital inputs and eight digital outputs. With it you can do such things as: controlling a Tasman Turtle robot (or your own!), automatically control a slot car, read a DVM or record the movements of a potentiometer connected to a science experiment.

MORE microprocessors are used in real time process control than in any other application. They are embedded in instruments, motor cars, household appliances, machines and robots. Process control computers use digital and analogue interface circuits to transfer program commands to machinery and to read signals fed back from transducers.

Constructing and using this general purpose interface card will introduce you to the world of real time process control and enable your Apple to interface to 'the real world'. You can use this interface to connect your Apple to computer peripherals, electronic instruments and science experiments. Possible applications include: controlling a Turtle robot, automatic control of a slot car, driving a printer, reading a digital voltmeter, monitoring a weather station or recording the output of a potentiometer connected to a physics experiment.

## Design

The card will interface the computer to eight digital inputs, eight digital outputs, one analogue input, and one analogue output. Detailed specifications are given in Table 1. The interface circuitry is based on a Motorola 6821 peripheral interface adaptor (PIA). The PIA is designed to connect digital signals to a Motorola 6800 microprocessor. The 6502 microprocessor, used in the Apple, has the same external buss structure as the 6800, allowing Motorola peripheral chips to be used in 6502-based systems. The internal architectures of the two microprocessor families differ considerably, however.

Both processor families use memory mapped input/output; that is, all peripheral

interface registers are addressed as if they are memory locations. Memory load and memory store instructions are used to read from and write to interface registers; special input/output instructions are not required. Address decoding for the six internal registers is done by the PIA.

On the peripheral side, the PIA has sixteen bi-directional signal lines, which can be individually selected as input or output lines, and four control lines. The input/output lines are split into two 8-bit bytes, known as the A-side and the B-side.

Timing differences between the clock signals at the processor and the clock signals at the peripheral connector (Figure 1), a result of the unusual design of the Apple II, will cause data loss and must be compensated for. The Apple's master oscillator generates a bi-phase clock signal (C01 and C02 in Figures 1 and 2). Phase two of the master clock is fed to the processor which produces a


second bi-phase clock (P01 and P02) for internal processor timing.

Data is latched into all chips on the falling edge of phase two and ten nanoseconds later data is removed from the buss. The master clock signal (C02), used by the peripheral interface circuits, leads the processor clock signal (P02) by thirty nanoseconds (Figure 2). A direct consequence of this time difference is data loss during read cycles because the PIA starts to remove data from the buss twenty nanoseconds before the processor latches. Data written to interface registers is not affected. Some of the interface control signals have been delayed to minimise this time differential.

Signals from the peripheral connector are buffered (Figure 3) in order to minimise the resistive and capacitive load placed on the peripheral buss by the interface card. The A-side digital outputs are buffered to increase drive capacity.

TABLE 1. SPECIFICATIONS

<b>Normal setup</b>
<ul style="list-style-type: none"><li>• eight digital outputs, TTL level; sink 40 mA, source 10 mA.</li><li>• eight digital inputs, TTL level; maximum load 20 uA.</li><li>• one analogue output (8-bit D-A), 0-10 V, 5 mA maximum.</li><li>• one analogue input (8-bit A-D), 0-10 V, 3k minimum impedance.</li></ul>
<b>Setup variations</b>
<ul style="list-style-type: none"><li>• digital outputs can be used as inputs.</li><li>• maximum analogue output is variable between -10 V and +10 V.</li><li>• analogue input range can be changed to -5 V to +5 V.</li></ul>

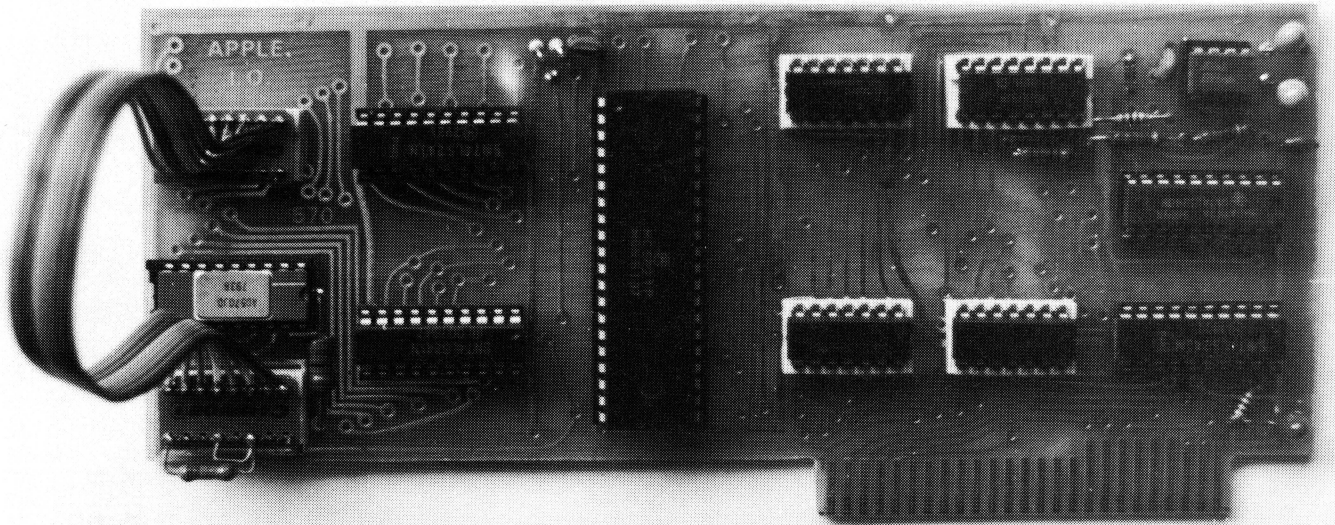


The B-side of the PIA is used for digital and analogue input. A control signal selects which signal, digital or analogue, is on the B-side buss. When analogue input is selected, the digital input buffer is disabled and analogue-to-digital conversion initiated. The analogue-to-digital converter (ADC)


signals that conversion is complete using a second control signal and places the result on the B-side buss. The ADC can be changed from unipolar (+ve voltages) to bipolar (+ve and -ve voltages) operation by removing a link.

A multiplying digital-to-analogue converter


(DAC) is used to produce the analogue output. The DAC data register is addressed independently of the PIA. The magnitude of the analogue output is determined by the product of the digital value stored in the data register and the reference voltage; hence the name *multiplying* DAC.

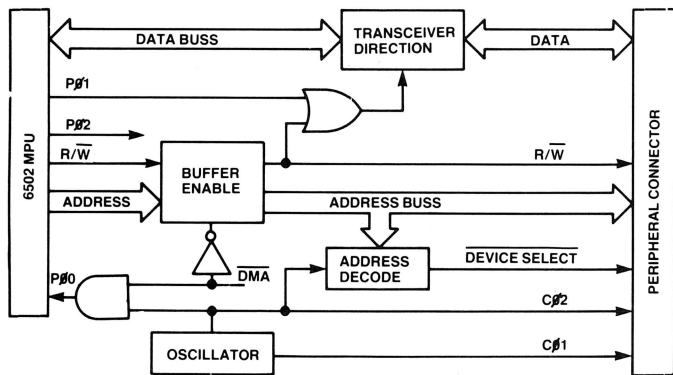

**Figure 1.** Block diagram of Apple II microcomputer showing processor and peripheral clock signals.

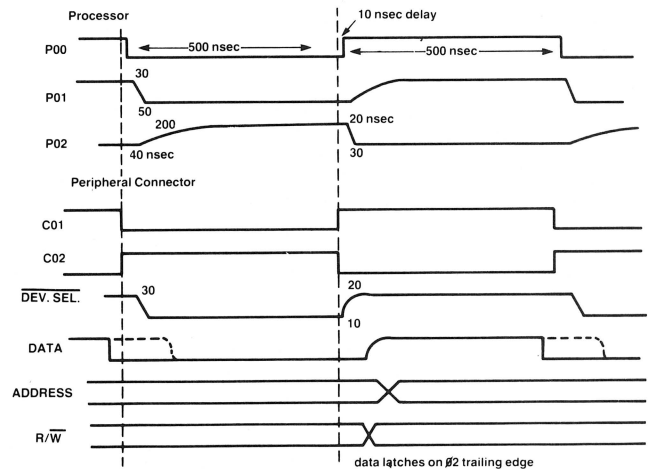

**Figure 2.** Comparison of processor and peripheral connector timing showing 30 nanosecond mismatch between trailing edge of clock 02 at processor and peripheral connector.

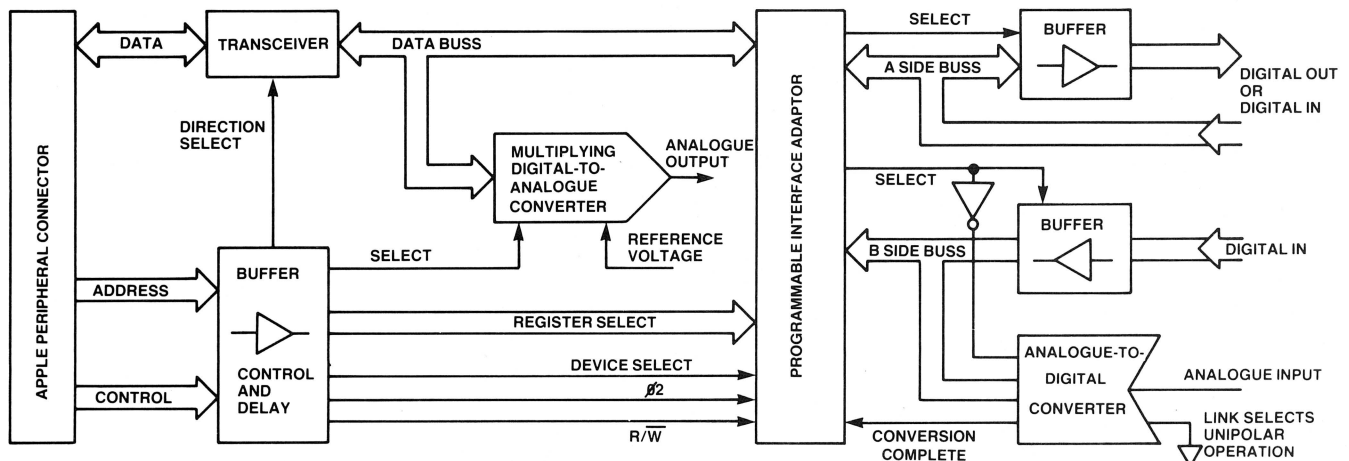



**Figure 3.** Block diagram of the general purpose Apple interface described here.

**Circuit.** All the DIL 'sites' on the pc board are labelled alphabetically, IC1 being site (a), IC2 site (b) etc. I/O connector A is site (f), I/O connector B is site (n). You can match IC numbers with site labels by comparing the naked pc board to the component overlay.

Digital-only operation can be obtained by leaving out IC1, IC2 and IC6.

\*ADJUST THESE RESISTORS TO GET DESIRED OUTPUT VOLTAGE

IC2 AD7524 DAC

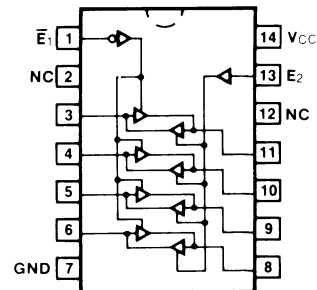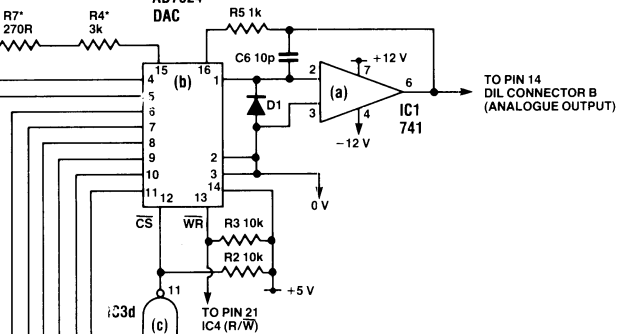


74LS243 PINOUT AND INTERNAL DIAGRAM



INPUTS		OUTPUT	
E1	D	OUTPUT	
L	L	L	
L	H	H	
H	X	Z	
H	X	Z	


INPUTS		OUTPUT	
E2	D	OUTPUT	
L	X	Z	
L	X	Z	
H	L	L	
H	H	H	

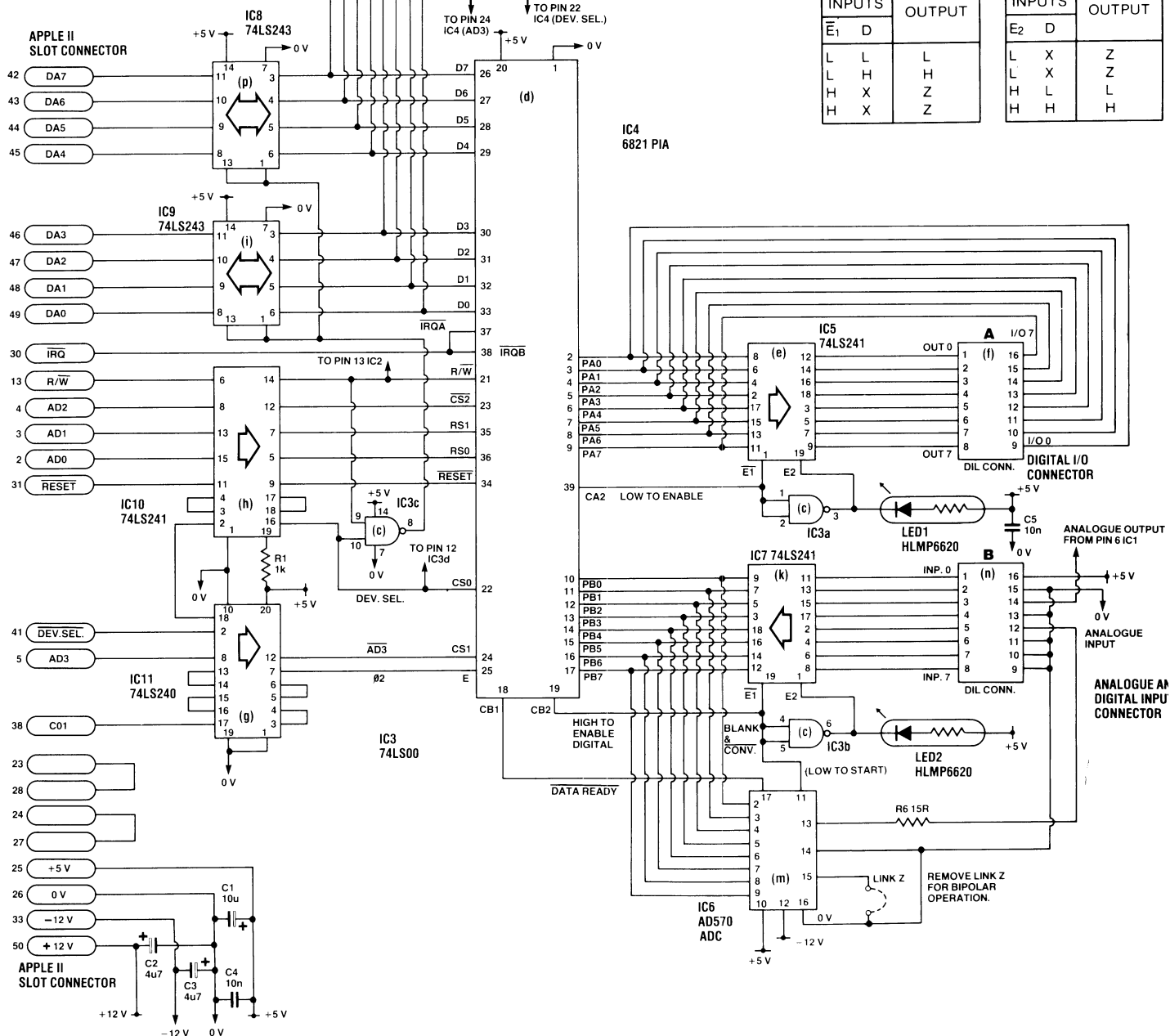

## 6821 PIA INTERNAL DIAGRAM

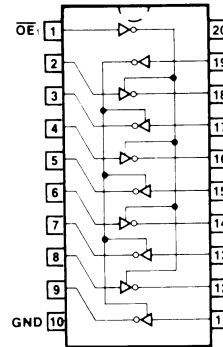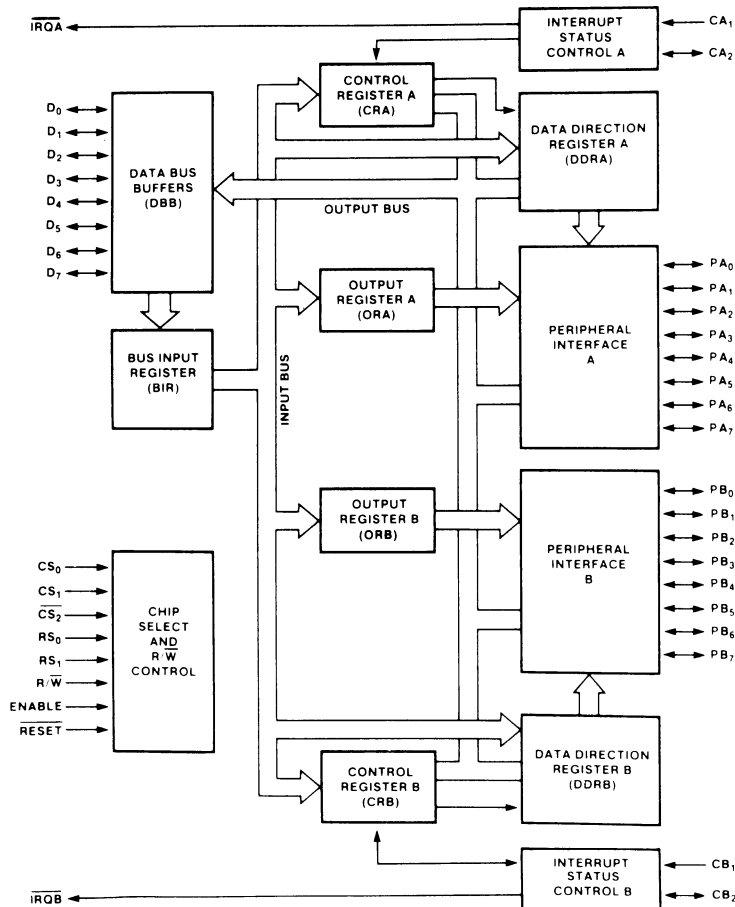

74LS240 PINOUT AND INTERNAL DIAGRAM

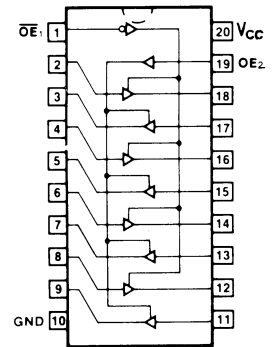

74LS241 PINOUT AND INTERNAL DIAGRAM

## TRUTH TABLES

'S240, 'LS240

INPUTS		OUTPUT	
OE <sub>1</sub>	OE <sub>2</sub>	D	
L	L	H	
L	H	L	
H	X	Z	

'S241, 'LS241

INPUTS		OUTPUT	
OE <sub>1</sub>	OE <sub>2</sub>	D	
L	H	L	
L	H	H	
H	L	X	

H = HIGH Voltage Level L = LOW Voltage Level X = Immaterial  
Z = High Impedance

## HOW IT WORKS — ETI-654

This should be read in conjunction with the text under 'Design'. The object is to transfer signals to and from the Apple's data buss via the peripheral interface adaptor (PIA), a 6821 — IC4. The PIA is controlled by a set of control signals available at the Apple peripheral (or slot) connectors.

Sixteen memory locations are set aside for each peripheral connector. A read or write to one of these locations will assert device-select; this signal is used to enable the address decoding circuits on the interface card. Device-select (pin 41 of slot connector) is delayed by a series of cascaded buffers in IC10 and IC11 to synchronise it with phase two (02) of the processor clock.

Address buss signal three (AD3, pin 5 of slot connector) selects the AD7524 DAC (IC2), and de-selects the PIA when asserted. Thus the analogue output buffer register is at address 8 relative to the base address of the card. The PIA registers are at addresses 0 — 3, and are selected using address buss signals zero and one (AD0 — AD1, pins 2 and 3 of the slot connector), via IC10.

Peripheral connector signal C01 (pin 38, slot) is delayed and inverted by a string of cascaded buffers in IC11 to produce a synchronised enable signal for the PIA (E, pin 25 of IC4). All data latching occurs on the trailing edge of the enable signal (phase two).

The PIA has six internal registers: two control registers, two data registers and two data direction registers. These registers are split into two groups of three: the A-side registers and the B-side registers. As the operation of the two groups is almost identical, only the A-side is discussed.

The direction (input or output) of individual signal lines is selected by setting the corresponding bit in the data direction register (DDR). Setting the DDR bit to one enables data output and clearing it to zero enables data input. Output data is stored in the data register and input data is read from the data register. The data direction register and the data register share the same memory location. The register accessed during a read or write is determined by the value of bit two in the control register — a one selects the data register. The control register is also used to enable the two control lines, CA1 and CA2, and to monitor their status.

The A-side, digital output buffer (IC5) is enabled when CA2 (pin 39, IC4) is low. When CA2 is high the buffer is tri-stated and the A-side can be used for digital input. CA1 is unused.

Control line CB2 (pin 19, IC4) is used to select the B-side digital inputs by enabling IC7 when high, or analogue input by disabling IC7 and requesting analogue-to-digital conversion when low.

The analogue-to-digital converter (IC6, the AD570) used successive approximation to calculate the digital value. When conversion is requested the most significant bit of the internal digital register is set (value: hex 80) to provide the first approximation. This value is converted to analogue using an internal DAC for comparison with the analogue input. The comparator determines whether the DAC output is greater or less than the analogue input. If the output is less the bit is left on, but if it is more the bit is turned off. This process is repeated, bit by bit, until all eight binary-

weighted bits in the internal register have been compared. The final value in the register is the digital equivalent of the analogue signal within plus or minus half of the least significant bit.

When conversion is complete the ADC outputs are enabled onto the B-side buss and CB1 (pin 18, IC4) is asserted low. The converter can be operated either in unipolar mode, by connecting pin 15 to 0 volts, or bipolar mode by removing the link (link Z). CB2 must be raised to reinitialise the chip and to disable the outputs before another conversion can be requested.

Data is latched into the 8-bit multiplying digital-to-analogue converter (IC2, the AD7524) when the chip select line (pin 12) goes high. The voltage reference (pin 15) is connected to outputs 1 and 2 via an internal binary-weighted resistor ladder network.

If a bit in the data register is set, the respective ladder resistor is connected to output 1; if it is cleared, the resistor is connected to output 2. Thus, the current out of output 1, into a low impedance load, is the analogue equivalent of the digital value multiplied by the reference voltage. This current signal is converted to a voltage by the 741 operational amplifier (IC1).

The table here gives the analogue-to-digital and digital-to-analogue conversion values.

Digital Signal (hex)	Analogue Output (volts)	Unipolar Analogue Input	Bipolar Analogue Input
0	0	0	-5
80	-0.5 Vref	+5	0
FF	-Vref	+10	+5

## Construction

A double-sided, through-hole plated pc board has been used for this project, partly to keep the size within bounds so that it fits within the Apple II case. Hence, unless you have access to through-hole plating facilities, you will have to purchase a ready-made pc board from one of the suppliers listed in the Shoparound page in this issue.



Before soldering any components onto the circuit board check that it will plug into a peripheral-connector base in the Apple. If it is oversize, trim the excess width off with a file, being careful to maintain alignment between edge connector tracks and base pins. Then check the board for any shorts between edge connector tracks.

Now you can commence assembly of the board. Install link Z first, followed by the resistors and diodes. Double check the orientation of the diodes before soldering them. If you are using IC sockets put these in next. If not, put the ICs in. Insert them into the board one at a time and solder two diagonally-opposite pins. Check the seating of the socket/IC and that all pins are through the holes before soldering the remaining pins. All ICs except the PIA have the same orientation. Next, put the two DIP connector bases in and finish with the capacitors. The orientation of the tantalum capacitors is important. If you used IC bases plug the ICs in now.

Having completed the construction, visually check the card for missed solder joints, solder bridges (particularly under the DIP connectors), dry joints and incorrectly oriented components. Clean excess flux from the soldering using a little methylated spirits and an old toothbrush.
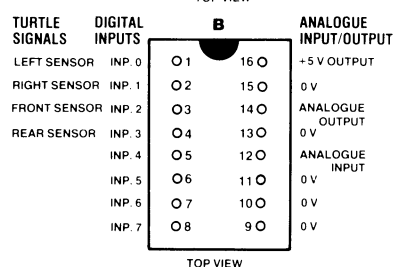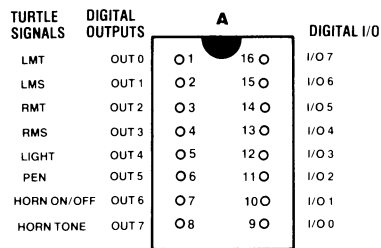
## Installation and testing

The card has been designed for automated testing using the test cable, shown in the



**Connectors.** The A connector pinout has buffered digital outputs on pins 1 to 8 and unbuffered digital I/O on pins 9 to 16 (all PIA A-side I/O). The B connector pinout has buffered digital inputs on pins 1 to 8 (PIA B-side) with the analogue input and output, +5 V supply and 0 V lines on the other side. The 'standard' Turtle control signals are also shown.

drawings, to connect interface outputs to interface inputs. Two test programs are given; one to test digital input/output and one to test analogue input/output. All values printed out by the programs are in decimal, unless otherwise indicated. The analogue test program requires the analogue input range and the analogue output range to be the same; 0 — 10 volts.

Plug the test cable into the input/output connectors and insert the card into peripheral slot 2 of the Apple II. The card will work in any slot, but the test programs are written for slot 2. When facing the keyboard, the components go towards the right, and the input/output connectors towards the keyboard. *Never insert or remove the card while power is on.*

Switch the Apple power supply on. The Apple should come up and display a message on the screen. If it doesn't, turn the power off immediately and recheck the board. If it still fails to come up, use a logic probe to determine which buss signal is pulled permanently high or low.

Once the Apple is up, load and run the digital test program. The two LEDs on the interface card should flash ten times with the Apple's bell ringing every time the lights come on, indicating that the processor can address the PIA's control registers. The invisible character in line 535 of the test program is the bell character, control G. Then, an ascending sequence of numbers will be written out, read in and compared. The error information can be used to diagnose any faults. You may have to convert the numbers to binary, by hand, to see what is happening.

Once the digital section has been checked, the analogue test program can be run. This program writes, reads and displays various analogue values. These can be compared visually to check digital-to-analogue conversion accuracy. Expect differences between input and output of plus or minus one bit due to conversion range and linearity differences. The DAC output can be adjusted to the desired maximum value by changing the reference resistors. No adjustment is available for the ADC. It has been factory trimmed, so its accuracy must be checked with a digital voltmeter.

## Programming

Programming consists of initialising the PIA and transferring data to and from the card. PIA-register contents are read using memory load instructions, and written using memory store instructions. In high level languages like BASIC, PEEK and POKE functions are used. The address of a register is calculated, using the data in Tables 2 and 3, by adding the register address to the interface address.

Slot Number	Hex	Address Decimal
0	C080	-16256
1	C090	-16240
2	C0A0	-16224
3	C0B0	-16208
4	C0C0	-16192
5	C0D0	-16176
6	C0E0	-16160
7	C0F0	-16144

**Table 2.** Interface address (A) — address of DRA for each slot.

Address	Function
A+0	Data Register A or DDRA
A+1	Control Register A
A+2	Data Register B or DDRB
A+3	Control Register B
A+8	Analogue Output

**Table 3.** Register address — address of the interface registers relative to the interface address (A).

When the system is powered up, all PIA registers are cleared and all input/output lines are selected as inputs. Before data can be transferred through the interface the PIA must be initialised. The steps involved are:


1. Select the data direction register by clearing control register bit 2.
2. Write data to the data-direction register to select the direction of the individual signal lines.
3. Select the data register and enable any buffers by writing the desired bit pattern to the control register.

The data register can now be written to and read from. Data written to inputs will be ignored and data read from outputs will be the output value.

Side	Function	Control register bit settings
A	Select data direction register	b2 = 0
	Select data register	b2 = 1
	Enable output buffer	b5 = b4 = 1, b3 = 0
	Disable output buffer	b5 = b4 = b3 = 1
B	Select data direction register	b2 = 0
	Select data register	b2 = 1
	Enable digital input	b5 = b4 = b3 = 1
	Request A/D conversion	b5 = b4 = 1, b3 = 0
	Enable A/D complete interrupt	b1 = 0, b0 = 1
	Disable interrupt	b1 = b0 = 0
	Conversion complete	b7 goes high, reset by reading B-side data register

**Table 4.** Programming the PIA control registers.

TOWARD APPLE KEYBOARD

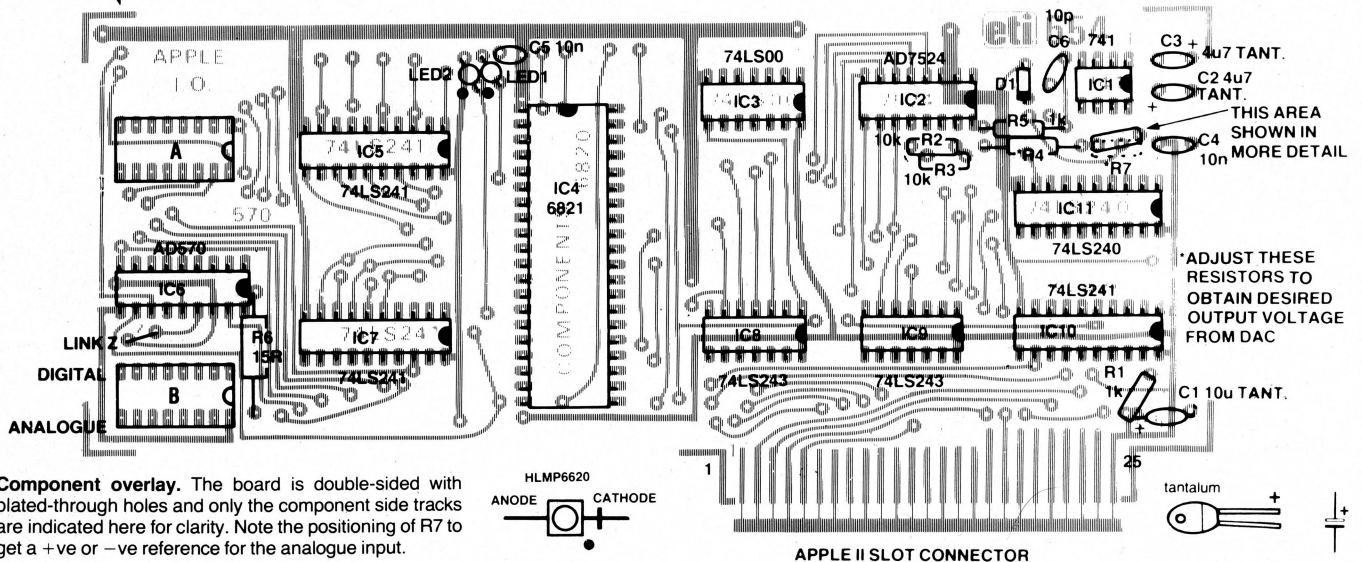

**Component overlay.** The board is double-sided with plated-through holes and only the component side tracks are indicated here for clarity. Note the positioning of R7 to get a +ve or -ve reference for the analogue input.

Details of the effects of control register settings are given in Table 4. On the A-side, bit 2 selects the data register and bits 3, 4 and 5 enable the digital-output buffer. On the B-side, bits 0 and 1 enable the 'analogue-to-digital-conversion-complete' interrupt, bit 2 enables the data register, bits 3, 4 and 5 select analogue or digital input and bit 7 indicates 'conversion complete'.

## Programming digital input/output

The A-side is set up as digital output lines by writing decimal 225 to the data-direction register and setting bits 2, 4 and 5 of the control register.

```
10 REM Initialise A-Side as digital Outputs
20 POKE A+1,0 Select DDR
30 POKE A,225 Select lines as outputs
40 POKE A+1,52 Select DR and Enable Buffer
50 REM Ready for data transfer
60 POKE A,Data Data 0..255 decimal
```

Alternatively the A-side can be set up as 8 digital inputs by writing 0 to the data-direction register, and setting bits 2, 3, 4 and 5 of the control register. The code for initialising the B-side as digital inputs is the same, except the addresses are incremented by two.


```
10 REM Initialise B-side as digital Inputs
20 POKE A+3,0 Select DDR
30 POKE A+2,0 Select lines as inputs
40 POKE A+3,60 Select DR and Enable Buffer
50 REM Ready for data transfer
60 DATA = PEEK (A+2) Data 0..255 decimal
```

## Programming analogue input/output

Analogue outputs are simple; just write to the digital-to-analogue converter.

```
10 POKE A+8,DATA data 0..255 decimal
```

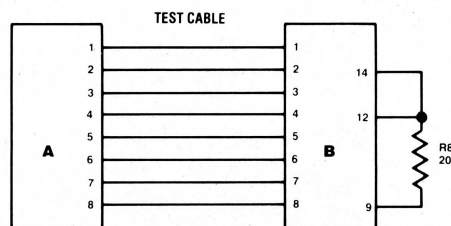Analogue inputs are more complex because you first have to request a conversion, which also disables digital inputs, and then wait for the conversion to complete. Conversion is



## PARTS LIST — ETI-654

**Resistors** ..... all 1/4W, 5% unless noted  
R1, R5 ..... 1k  
R2, R3 ..... 10k  
R4 ..... 3k (see text)  
R6 ..... 15R  
R7 ..... 270R (see text)  
R8 ..... 20k

**Capacitors**  
C1 ..... 10u/25 V TANT.  
C2, C3 ..... 4u7/25 V TANT.  
C4, C5 ..... 10n greencap  
C6 ..... 10p ceramic

**Semiconductors**  
D1 ..... HP5082-2811 Schottky diode  
LED1, 2 ..... HLMP6620 red sub-miniature resistor-LEDs  
IC1 ..... 741  
IC2 ..... AD7524  
IC3 ..... 74LS00  
IC4 ..... 6821  
IC5, 7, 10 ..... 74LS241  
IC6 ..... AD570  
IC8, 9 ..... 74LS243  
IC11 ..... 74LS240


### Miscellaneous

ETI-654 pc board; 3 x 16-pin DIL sockets; 4 x 16-pin DIL plugs; 1 x 40-pin DIL socket; 4 x 20-pin DIL sockets; 1 x 18-pin DIL socket; 3 x 14-pin DIL sockets; 1 x 8-pin DIL socket; ribbon cable.

### Price estimate

**\$45 — \$50** (digital only)

**\$95 — \$100** (complete)

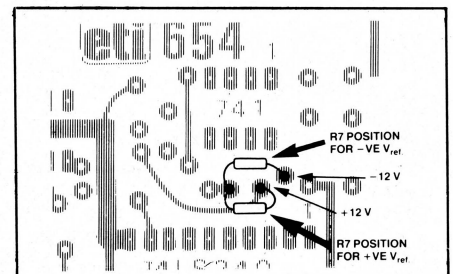

requested by setting bits 4 and 5 and clearing bit 3 of the B-side control register. When the conversion is complete, bit 7 of the control register is set to a one and an interrupt is generated, if interrupts are enabled. The data can be read from the B-side data register. This action also clears bit 7 of the control register. Conversion request must be removed and reapplied to request a second conversion. The program below loops on status, with interrupts disabled, until conversion is complete. Very little time can be gained by using interrupts because the analogue-to-digital conversion only takes 25 microseconds.

```
10 REM Initialise B-side for digital input
20 REM Request A to 0 conversion
30 POKE A+3,52 Request conversion
40 X = PEEK (A+3) Read status
50 IF X < 128 then 40 Test for complete
60 REM Conversion complete
70 Input = PEEK (A+2) Read data, clear status
80 POKE A+3,60 Recycle converter, enable digital inputs
```

## Pascal

The card can be programmed from Pascal using the assembler function PEEK and procedure POKE. These two routines are compiled and linked to the Pascal-code file to form the executable program. The simple Pascal program reproduced in the panel over the page, which can be used to examine and modify memory, illustrates their use. From the viewpoint of the Pascal programmer PEEK and POKE behave like any other function or procedure.

## OLD FASHIONED PRICES

We don't overcharge you  
— we're happy just to make a living.  
8 years with no price rise.

### RESISTORS

Carbon Film 5% 2.2 Ohm  
to 4M7 E12

¼w 70c a 100 same 12c/10 1½c ea  
½w \$1.40 a 100 same 18c/10 2c ea

### POLYESTER FILM CAPS E12 10% 100V

4c



.001 - 4c	.01 - 5c	.1 - 10c
.0012 - 5c	.012 - 6c	.12 - 11c
.0015 - 5c	.015 - 6c	.15 - 12c
.0018 - 5c	.018 - 6c	.18 - 14c
.0022 - 5c	.022 - 6c	.22 - 15c
.0027 - 5c	.027 - 6c	.27 - 16c
.0033 - 5c	.033 - 7c	.33 - 18c
.0039 - 5c	.039 - 7c	.39 - 19c
.0047 - 5c	.047 - 7c	.47 - 20c
.0056 - 5c	.056 - 8c	10%, off 100
.0068 - 5c	.068 - 8c	
.0082 - 5c	.082 - 9c	same uF

### ELECTROS

4c

	16V	25V	50V
0.47uF	4c	5c	6c
1, 2.2, 3.3, 4.7, 10uF	5c	6c	7c
22uF	6c	7c	8c
33uF	7c	8c	9c
47uF	8c	9c	10c
100uF	9c	11c	13c
220uF	11c	13c	22c
470uF	14c	18c	40c
1000uF	18c	28c	65c

(UPRIGHT)

### POTS

35c

LINEAR  
¼" ALUM. SHAFT



TRIMPOTS  
12c (10mm)

### LEDs

specials

\$10

a 100

12c ea



	each	10	100	1000
Red	12c	\$1.10	\$10	\$95
Green	15c	\$1.40	\$13	\$125
Yellow	15c	\$1.40	\$13	\$125
Clips	3c	all quantities		

### 1 Amp. DIODES

	50V	100V	400V	1000V	1N4001 - 5c	1N4002 - 6c	1N4004 - 7c	1N4007 - 9c	1N5408	3 Amp. 1000V - 30c
									IN4148 SIGNAL DIODE	4c each \$3¼ a 100

### CERAMIC

disc capacitors  
50 Volt rating

1pF, 2.2, 3.3, 4.7pF	all 4c each \$3.50 a 100
10pF, 22, 33, 47pF	
100pF, 220, 330, 470pF	
1000pF, 2200, 3300, 4700pF	
.01uF, .022, .033, .047uF — all 5c ea.	\$4 a 100
.1uF @ 8c each,	\$7.50 per 100

### SWITCHES 250V 1½Amp TOGGLE



55c SPST  
65c SPDT




SPST 65c ea.

### MINIATURE TOGGLE

### CROCODILE CLIP JUMPER LEADS

Set of 10 = \$1.90  
5 colour mix

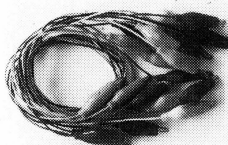

Please add 50c postage to orders.  
Tax exempt available by application.  
Write for full list incl. ICs, transistors, etc.

**DIGGERMAN ELECTRONICS**

P.O. BOX 33, CORAMBA, N.S.W. 2450


## SAWTRON KG103 SERIES

### VHF & UHF HANDY TRANSCEIVERS

THE SAWTRON KG 103  
SERIES FEATURES:-

- THE LATEST THICK FILM HYBRID I.C. TECHNOLOGY.
- MODULAR CONSTRUCTION TECHNIQUES.
- EXCELLENT SENSITIVITY, SELECTIVITY AND BLOCKING.
- RUGGED CONSTRUCTION.

### PERFORMANCE AT A REALISTIC PRICE.

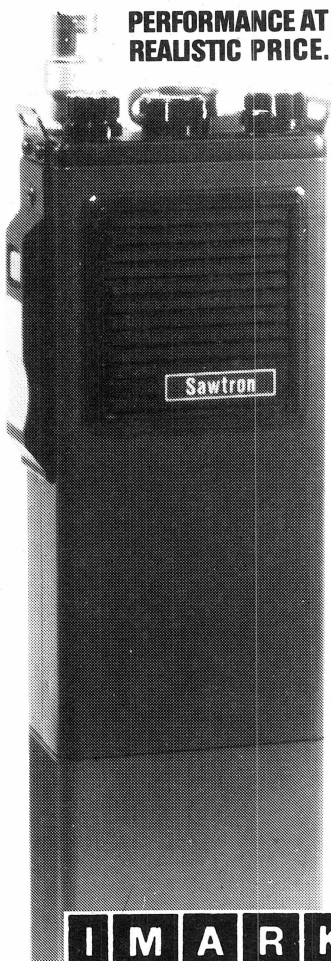

**I M A R K**

167 RODEN STREET,  
WEST MELBOURNE.  
VIC. 3003  
PHONE (03) 329 5433.  
TELEX AA37753

## Project 654

### Applications

Possible applications of this card vary from controlling models to monitoring scientific experiments, as mentioned in the introduction. The following examples illustrate some of the ways the interface can be used.

A number of people use this interface card to control the Tasman Turtle Robot (see ETI project 645, April, May, June 1982). It was originally designed for use with the Terrapin turtle robot, which has the same interface signals. These robots require eight digital outputs to operate motors, lights, pen and horn, and four digital inputs from the touch sensors.

Other digital applications include: reading bar codes with a Hewlett-Packard bar code reader (HEDS 3000), driving a printer and reading a digital voltmeter. Heathkit sell a microcomputer-based weather station (kit ID 4001), which can be interfaced to a computer so that weather data can be collected and analysed (Warburton Franki handle Heathkit equipment in Australia).

The apparatus used in a physics experiment, designed to illustrate Newton's second law, is shown in Figure 4. When the trolley is released, it accelerates along the table until it comes to rest against the buffer. The mass suspended from the pulley provides the accelerating force. A ten-turn potentiometer, connected to the pulley, produces an electrical voltage proportional to the distance the trolley is from the buffer. The signal is read with the analogue input and used to calculate trolley position, velocity and acceleration.

A very interesting application is the control of a slot car. Photodetectors (or in some cases, magnetic reed switches), connected to the digital input/output in a switch matrix configuration, can be used to detect which section of track the car is currently on. The analogue output can be used as a reference signal to an electronic speed controller (see ETI project 825, December 1981). The speed of a manually driven car is measured with the analogue input, recorded for each section of track and stored in a look-up table. When the car is under computer control the computer retrieves the speed for the section of track the car is on and uses it as a speed reference.

### Further reading

1. Analogue Devices, *Data-Acquisition Components and Subsystems Catalogue*, 1980.
2. Apple II, *Hobby/prototyping board-product Specification*.
3. ETI project 645, Allan Branch, *Tasman Turtle*, April 1982 (and subsequent issues).
4. ETI project 825, Jonathan Scott, *Slot Car Controller*, December 1982.
5. McKerrow P.J., *Controlling a 'Turtle' with an 'Apple'*, ACS National Microcomputer Conference, Canberra, July 1980, pages 18.1 — 18.11.
6. McKerrow P.J., *Micro-computers, Slot cars and Education*, IEEE Micro, February 1983.
7. Motorola, *Micro-processors Data Manual*, 1981.

## ANALOGUE TEST PROGRAM

```

5 PRINT
10 PRINT "  APPLE ANALOG I/O TEST"
15 PRINT
17 PRINT "    DATA IS IN DECIMAL"
20 REM P.J.MCKERROW .....3.11.82
80 REM INITIALISE PIA
90 REM SET UP FOR SLOT 2
91 REM A=ADDRESS,V=MAX VOLTS OUT
92 V=10
95 A=-16224
100 POKE A+1,0
110 POKE A,255
120 POKE A+1,52
130 POKE A+3,0
140 POKE A+2,0
150 POKE A+3,60
155 PRINT
160 PRINT "  ANALOG DATA"
170 PRINT "OUT    IN  VOLTS OUT *10"
180 O=1
240 GOSUB 2000
250 GOSUB 1000
260 O=2*O
270 IF O=256 THEN O=255
280 IF O<256 THEN 240
300 O1=1
310 O=255-O1
320 GOSUB 2000
330 GOSUB 1000
340 O1=2*O1
350 IF O1<255 THEN 310
400 END
1000 REM WAIT LOOP
1010 T=0
1020 T=T+1
1030 IF T<500 THEN 1020
1040 RETURN
2000 REM I/O ROUTINE
2010 POKE A+8,0
2020 POKE A+3,52
2030 X= PEEK (A+3)
2040 IF X<128 THEN 2030
2050 I= PEEK (A+2)
2060 POKE A+3,60
2070 V0=10*O*V/255
2080 PRINT O,I,V0
2090 RETURN

```

## DIGITAL TEST PROGRAM

```

5 PRINT
10 PRINT "  APPLE I/O TEST"
15 PRINT
17 PRINT "    DATA IS IN DECIMAL"
20 REM P.J.MCKERROW .....3.11.82
40 C=0
50 W=-16224
60 R=-16222
65 PRINT
66 PRINT "  FLASH LEDS "
67 GOSUB 500
70 REM C=ERROR COUNT,I=TEST COUNT
80 REM W=WRITE ADDRESS,R=READ ADDRESS
90 REM X=DATA OUT,Y=DATA IN,T=TEMP
91 PRINT
92 PRINT "TEST ERROR  DATA"
96 PRINT "NO.    COUNT    OUT  IN"
100 FOR I=1 TO 100
105 GOSUB 300
110 FOR X=1 TO 255
120 POKE W,X
130 Y= PEEK (R)
140 IF Y=X THEN 150
142 C=C+1
144 PRINT I,C,X,Y
150 NEXT X
150 PRINT I,C
170 NEXT I
180 GOTO 400
300 REM INITIALISE PIA
310 POKE W+1,0
320 POKE W,255
330 POKE W+1,52
340 POKE R+1,0
350 POKE R,0
360 POKE R+1,60
370 RETURN
400 END
500 REM FLASH LEDS
505 FOR I=1 TO 10
510 POKE W+1,48
520 POKE R+1,48
530 GOSUB 600
535 PRINT I,""
540 POKE W+1,56
550 POKE R+1,56
560 GOSUB 600
580 NEXT I
585 C=0
590 RETURN
600 REM WAIT LOOP
610 C=0
620 C=C+1
630 IF C<50 THEN 620
640 RETURN

```


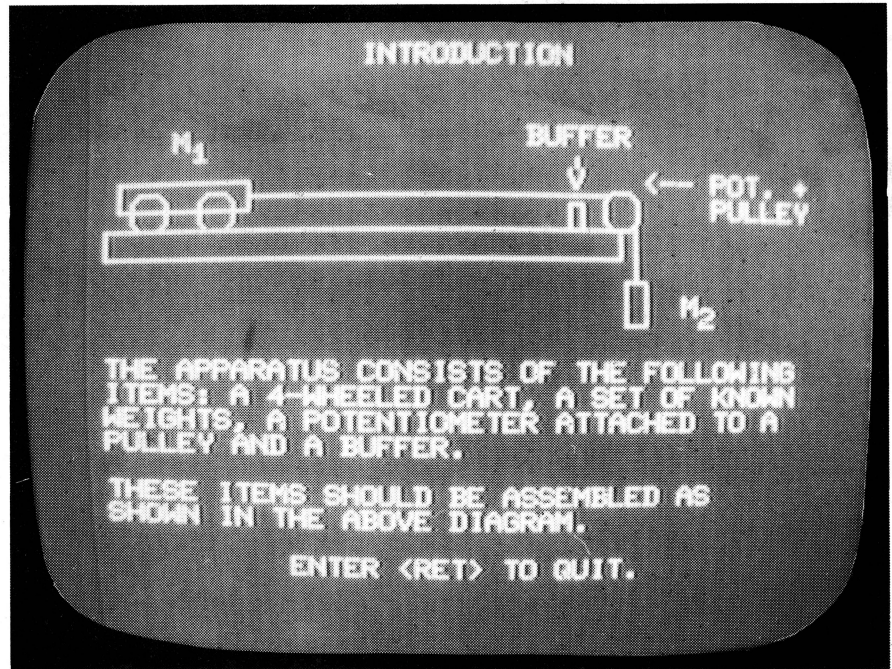


Figure 4. Apparatus for Newton's second law physics experiment. The potentiometer connections to the interface are shown below.

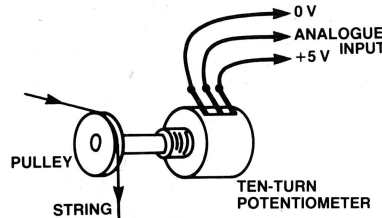

## PASCAL PROGRAM EXAMPLE

```

PROGRAM EXAM;
(*USED TO EXAMINE AND MODIFY MEMORY*)
(*PHILLIP MCKERROW 29.10.82*)
VAR TERM,DATA,DAT1,ADDR:INTEGER;
    REQUEST:CHAR;
PROCEDURE POKE (DATA,ADDR:INTEGER);
EXTERNAL;
FUNCTION PEEK (ADDR:INTEGER):INTEGER;
EXTERNAL;
BEGIN
    WRITELN ('EXAMINE AND MODIFY MEMORY');
    WRITELN (' ALL VALUES ARE DECIMAL');
    WRITELN (' DATA 0-255');
    WRITELN (' ADDRESS -32768 TO 32767');
    WRITELN;
    TERM :=0;
    WHILE TERM=0 DO
        BEGIN
            WRITE ('E:EXAMINE,M:ODIFY,Q:UIT - ');
            READLN (REQUEST);
            CASE REQUEST OF
                'E': BEGIN
                    WRITE ('ADDRESS PLEASE ');
                    READLN (ADDR);
                    DATA := PEEK (ADDR);
                    WRITELN (' ',DATA);
                    END;
                'M': BEGIN
                    WRITE ('DATA,ADDRESS PLEASE ');
                    READLN (DATA,ADDR);
                    POKE (DATA,ADDR);
                    DAT1 :=PEEK (ADDR);
                    IF DAT1<>DATA THEN
                        WRITELN ('ERROR ',DATA,DAT1);
                    END;
                'Q': TERM :=1;
            END;
        END;
    END;
END;
WRITELN ('BYE BYE');
END.

```

## ASSEMBLER PROGRAM EXAMPLE

```

;THE UNIVERSITY OF WOLLONGONG
;PHILLIP MCKERROW 3.11.82
;
; MACRO POP ADDRESS
;POPS 16 BIT ARG FROM STACK TO ADDRESS
;
; .MACRO POP
;PLA ;PULL LS BYTE
;STA %1
;PLA ;PULL MS BYTE
;STA %1+1
;ENDM
;
; MACRO PUSH ADDRESS
;PUSHES 16 BIT ARG TO STACK
;
; .MACRO PUSH
;LDA %1+1
;PHA ;PUT MS BYTE
;LDA %1
;PHA ;PUT LS BYTE
;ENDM
;
; .FUNC PEEK,1
; FUNCTION PEEK (ADDRESS:INTEGER):INTEGER;
;RETURNS CONTENTS OF SPECIFIED ADDRESS
;8 BITS OF DATA RETURNED IN LS BYTE
;MS BYTE SET TO ZERO
;
;RETURN .EQU 0 ;STORAGE FOR RETURN ADDRESS
;ADDR .EQU 2 ;ADDRESS OF DATA
;POP RETURN ;GET RETURN ADDRESS
;PLA ;STACK BIAS
;PLA
;PLA
;PLA
;POP ADDR ;GET ADDRESS
;LDA #0
;PHA ;SET MS BYTE TO 0
;LDY #0
;LDA @ADDR,Y ;GET DATA
;PHA ;RETURN DATA
;PUSH RETURN
;RTS ;GO BACK
;
; .PROC POKE,2
; PROCEDURE POKE (DATA,ADDR:INTEGER)
;PROCEDURE TO WRITE TO ADDRESS
;
;RETURN .EQU 0
;ADDR .EQU 2
;POP RETURN ;SAVE RETURN ADDRESS
;POP ADDR ;MEMORY LOCATION
;LDX #0
;PLA ;GET OUTPUT
;STA @ADDR,X ;POKE
;PLA ;CLEAN UP STACK
;PUSH RETURN
;RTS ;GO BACK
;END

```

# Australia's Most Exciting Personal Computer The Incredible Micro Bee

The Microbee is definitely the most versatile computer now available in Australia. Its ability to run complex software, and its friendliness to the user, have gained the Bee great acceptance, in the home, in small to medium businesses and in schools. In fact the Bee has recently been approved and recommended under contract by the N.S.W. and W.A. Education Departments. Children are growing up with Bee's!

In its basic **16K PLUS** form the Bee is capable of playing music through its built-in speaker, high and low resolution graphics, upper and lower case characters, direct connection to printers and has standard features such as battery backup (keep programs in RAM for months), full size QWERTY keyboard, inbuilt in/out ports and basic contained in ROM.

The all Australian designed and developed "Bee" incorporates the most powerful and comprehensive editing facilities of any micro-computer yet released — editing being the single most important operator/programmer facility. With the Bee it's a dream and, incidentally, attracting attention WORLD WIDE!

## FEATURES OF COMPUTERS COSTING MANY TIMES ITS PRICE

The Bee can be expanded through various stages, (16K-32K, 32K-64K) to a powerful 2.2CP/M Bee with disks capable of word processing and running world class software from machines such as IBM, DEC and HEWLETT PACKARD.

## THE VARIOUS BEES AND HARDWARE

COMPUTER	
D 1016 Microbee 16K Plus	\$ 449.00
D 1032 Microbee 32K Plus	\$ 549.00
D 1064 Microbee 64K Plus	\$ 699.00
D 1216 16K-16K Plus Conversion Pack	\$ 29.95
D 1232 16K-32K Plus Conversion Pack	\$ 125.00
D 1264 32K-64K Plus Conversion Pack	\$ 175.00
D 1270 S-100 Digitalk	\$ 155.00
D 1275 S-100 Romblaster	\$ 165.00
D 1280 S-100 Desk Top Interface	\$ 299.00
D 1285 Parallel Port inc. DB15 Plug and Hood	\$ 19.95

## UPGRADE TO A CP/M2.2 DISK DRIVE SYSTEM

D 1300 Disk Drive with Controller & CP/M2.2	\$ 799.00
D 1305 Add On Disk Drive	\$ 659.00
D 2600 CP/M2.2 Disk	\$ 200.00

## SOFTWARE


The Microbee is supported by an ever increasing range of software cassettes and ROM chips.

CASSETTES	
D 2520 Space Invaders	\$ 14.95
D 2521 Concentration	\$ 9.95
D 2522 Chess	\$ 9.95
D 2523 Typing/Solitaire	\$ 9.95
D 2524 Target	\$ 9.95
D 2525 Lunar Landing/Hurkle	\$ 7.95
D 2626 Star Shoot/Hangman	\$ 7.95
D 2527 Biorhythm/Calendar	\$ 9.95
D 2528 Eliza	\$ 9.95
D 2529 Kids Games	\$ 9.95
D 2530 Master Mind/Nim	\$ 9.95
D 2531 Chase/Wumpus	\$ 9.95
D 2532 Z Trek	\$ 9.95
D 2533 Educational Pack 1	\$ 24.95
D 2534 Educational Pack 2	\$ 24.95
D 2535 Graphic Games	\$ 9.95
D 2536 Missile Wars	\$ 9.95
D 2537 PCG Tutorials	\$ 9.95
D 2538 Microbee Pilot Educational	\$ 14.95
D 2541 "ESC" Key	\$ 9.95
D 2542 Robot Man	\$ 14.95

ROM	
D 2503 Editor/Assembler	\$ 59.50
D 2507 5.1 Basic Upgrade	\$ 20.00
D 2540 Word Bee ROMPack (Word Processor)	\$ 89.50
D 2543 Pascal S+	\$ 299.00



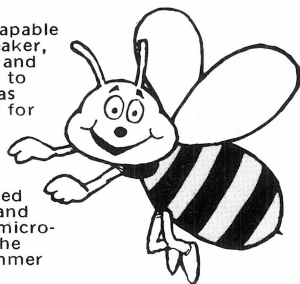CALL IN FOR A DEMO  
AT ALTRONICS NEW  
BEE COMPUTER  
CENTRE




## MICRON 12

Green Phosphor Monitor

Features: 12" screen. Front controls, on/off, contrast/reverse, brightness. Power: 240V/50Hz or 12V DC. Input: RCA type. DC Output Jack: 12V 1.1 Amp — power your Micro direct without a power pack. Bandwidth: 10Hz to 20MHz the resultant definition is truly amazing for a low cost monitor.

Guaranteed by  
**ALTRONICS!**  
Incredible Value.

D 1112 \$199.50

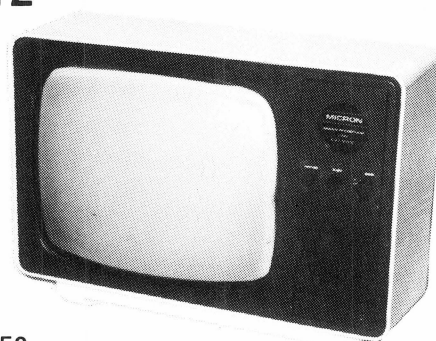


## Adjustable Azimuth DATA CASSETTE

At last a Data Cassette Recorder/Player you can afford. The Micron D 1120 is fully adjustable azimuth (absolutely essential in our opinion) and incorporates tailored audio frequency response audio stage together with low distortion.

Now you can save and load software in your Micro with confidence.

Micron D 1120  
Data Cassette  
ONLY \$49.50

D 1140 C10 Data Cassette	
Tape	\$1.10
D 1141 C20 Data Cassette	
Tape	\$1.20

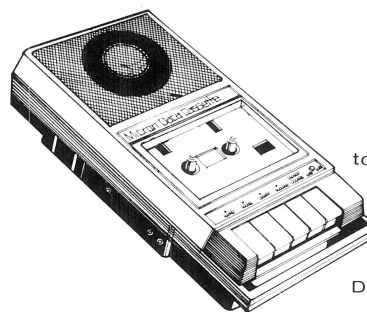

## EPSON MX80/3 DOT MATRIX PRINTER

All serious programmers require hard copy of program listings and every business needs a printer for stock control, invoicing, monthly balances etc.


The economy-priced MX80 has full graphic capabilities (480 x 8, 960 x 8 dots/line, bit image).

**THE QUALITY OF THIS MACHINE'S PRINTING MUST BE SEEN TO BE BELIEVED!**

### Specifications:


**Print Rate:** 80 char. per sec. **Print Direction:** Bidirectional logic seeking. **Character Set:** Full 96 character ASCII with descenders plus 8 international char. sets. **Character Structure:** 9 x 9 text mode. **Character Size:** 3.1 (H) x 2.1 (W)mm. **Total of 32 Printing Styles:** Normal, Normal Enlarged, Condensed, Condensed Enlarged, Emphasized, Programmable. **Paper Feed:** Adjustable sprocket (4"-10") plus Friction Feed. **Interface:** Centronics 8 Bit Parallel.

D 1180 MX80 F/T (No Graphics)	\$1025.00
D 1183 MX80/3 F/T (Graphics)	\$1195.00
D 1188 MX80 Serial Interface Adaptor Board	\$135.00
D 1189 MX80/3 Serial I/Face Board w/- 2K Buffer	\$249
D 1190 Printer Cable Interface Kit	\$49.95

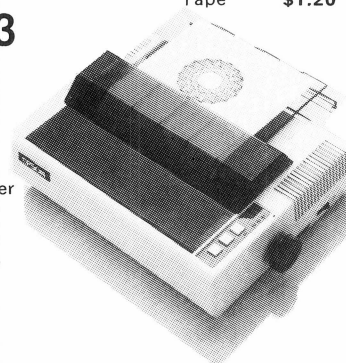
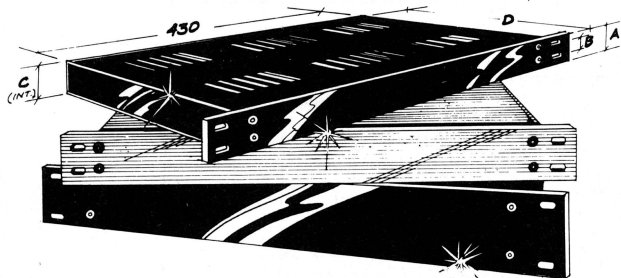
## WILL YOUR BUDGET PROBABLY WON'T STRETCH TO AFFORD OUR PROFESSIONAL SERIES ALL ALUMINIUM RACK CABINETS

NOW YOUR PREAMPS, AMPS, CONTROL MODULES MONITOR PANELS ETC. CAN LOOK EVERY BIT AS GOOD AS TECHNICS, NAKAMICHI AND OTHER TOP MANUFACTURERS



### INTRODUCTORY PRICES

Cat No.	Finish	A	B	C	PRICE	5 or More
H 0401	Natural	44	34	38	\$42.50	\$39.95
H 0402	Natural	88	57	82	49.95	47.50
H 0403	Natural	132	89	126	55.00	49.95
H 0411	Black	44	34	38	42.50	39.95
H 0412	Black	88	57	82	49.95	47.50
H 0413	Black	132	89	126	55.00	49.95

Beware of other rack boxes that do not conform to international rack sizing.

## THE BRILLIANT MARC NR 82 FI

**FEATURING:** Digital frequency Display, SSB CW, FM AM reception, B.F.O., Double Conversion, Double Super-het, crystal controlled (VHF) Local Oscillator, 4 inbuilt antennas and good looks, you will spend hours just learning how to drive it!



See Review in Electronics Australia August 1982

3 Way Power

Digital Tuning

HI FI SOUND

4 Inbuilt Antennae

only \$349 C9484

### SPECIFICATIONS:

Semi-conductors: 1-LSI, 4 - IC's, 7 - FET, 34 - Transistors, 42 - Diodes

### Frequency range:

LW	145-360 KHz	SW3	9-22 MHz	VHF3	88-108 MHz
MW	525-1600 KHz	SW4	22-30 MHz	VHF4	108-136 MHz
SW1	1.6-3.8 MHz	VHF1	30-50 MHz	VHF5	144-176 MHz
SW2	3.8-9 MHz	VHF2	68-86 MHz	UHF	430-470 MHz

Power supply: AC 240V 50Hz, DC 12V (8 x "D" cells), Ext. DC 12V Car/Boat.

Speaker: 12.5cm Permanent Dynamic Speaker (3.2 ohm)

Antenna: Ferrite Bar Antenna for LW, MW and SW1

3 x Telescopic Antenna for SW, VHF and UHF

Controls: Power ON-OFF switch - Digital display ON-OFF switch - Tape-Radio switch, Wide-Narrow band selector switch, AM band selector (LW/MW/SW1/SW2/SW3/SW4), VHF band selector (VHF1/VHF2/VHF3/VHF4/VHF5/UHF), Ant. Selector (Telescopic ANT./EXT. ANT.), Tuning control (direct gear drive), volume control, Bass control, Treble control, Squelch control, BFO pitch control, RF gain control, Antenna adjuster control, Mode switch (USB-NOR-LSB/CW)

Terminals: Ext. Speaker/Headphone Jack, Tape IN-OUT jack, VHF/UHF ANT. connector (coaxial), SW EXT. ANT. terminal (Screw), Ext. battery jack

Meter: Tuning Meter

Digital Frequency Counter Section:

Display: LW/MW/SW-1 KHz SW2-4/VHF1-5 MHz  
Control: SW Calibrator Dimensions: 452mm (W) x 288mm (H) x 130mm (D)

## ALTRONICS RESELLERS

Please note that resellers may not have all the items advertised in stock, and as resellers have to bear the cost of freight, prices may be slightly higher than advertised. ALTRONICS reseller prices should however represent a considerable saving over our competitors' prices.

### NEW SOUTH WALES

CITY  
Radio Despatch ..... 211 0191  
Electronic Agencies ..... 29 2098  
Jaycar ..... 264 6688

### SUBURBAN

LEWISHAM  
PrePak Electronics ..... 569 9770  
CONCORD  
Electronic Agencies ..... 745 3077

### DEE WHY

David Ryall Electronics ..... 982 7500  
WAITARA  
Applied Technology ..... 487 2711  
MATRIVILLE  
Creative Electronics ..... 666 4000

### COUNTRY

BROKEN HILL  
Crystal TV ..... 4803  
COFFS HARBOUR  
Coffs Harbour Electronics ..... 52 5684

### PENRITH

Acorn Electronics ..... 21 2409  
NEWCASTLE  
D.G.E. Systems ..... 69 1625  
WINDANG  
Madjenk Electronics ..... 96 5066

### GOSFORD

Tomorrow Electronics ..... 24 7246  
KURRI KURRI  
Kurri Electronics ..... 37 2141

### SOUTH AUSTRALIA

CITY  
ADN Electronics ..... 212 5505  
SUBURBAN  
PROSPECT  
Jensen Electronics ..... 269 4744

### ELIZABETH GROVE

A.E. Cooling ..... 255 2249  
CHRISTIES BEACH  
Force Electronics ..... 382 3366  
KESWICK  
Freeway Electric Wholesalers ..... 297 2033

### VICTORIA

CITY  
All Electronic Components ..... 662 3506  
Ellistronics ..... 602 3499  
SUBURBAN  
HUNTINGDALE  
Stewart Electronics ..... 543 3733

### SOUTH CROYDON

Truscott Electronics ..... 723 3860  
COUNTRY  
SHEPPARTON  
GV Electronics ..... 21 8866

### MILDURA

Electronic and Digital Services ..... 23 3380

### QUEENSLAND

CITY  
Delsound ..... 229 6155  
SUBURBAN  
SALISBURY  
Colourview Wholesale ..... 275 3188

### FORTITUDE VALLEY

St. Lucia Electronics ..... 52 3547  
BIRKDALE  
Wholesale Sound Accessories ..... 207 2502

### COUNTRY

CAIRNS  
Thompson Instrument Services ..... 51 2404  
TOWNSVILLE  
Solex ..... 72 2015

### ROCKHAMPTON

Purely Electronics ..... 21058  
GLADSTONE  
Purely Electronics ..... 72 4321

### GYMPIE

TV and Appliance Services ..... 82 1671  
IPSWICH  
P & P Electronics ..... 281 8001

### TOOWOOMBA

Hunts Electronics ..... 32 9677  
Down's Radio and TV ..... 32 1044  
NAMBOUR  
Nambour Electronics ..... 41 1604

### NT

DARWIN  
Radio Parts Darwin ..... 81 8508  
Kent Electronics ..... 81 4749  
Ventronics ..... 81 3491

### ALICE SPRINGS

Farmer Electronics ..... 52 2967  
Ascom Electronics ..... 52 1713

### TASMANIA

HOBART  
Beta Electronics ..... 34 8232  
KINGSTON  
Kingston Electronics ..... 29 6802

### AVOCA

Freemans TV ..... 84 2166  
WEST AUSTRALIA  
ALBANY  
BP Electronics ..... 41 2681

### GERALDTON

Geraldton TV and Radio ..... 21 2777  
WYALKATCHEM  
D & J Pease ..... 81 1132  
MANDURAH  
Kentronics ..... 35 3227

### ACT

Scientronics ..... 54 8334  
Electronic Components ..... 80 4654

### RESELLERS WANTED IN ALL AREAS (including WA)

Phone: STEVE WROBLEWSKI (09) 381 7233 for details

### NEW 24 HOUR 7 DAYS P/WEEK PHONE ORDER SERVICE FOR BANKCARD HOLDERS

Take advantage of "off peak" low STD phone rates and phone your order to our new recorded 24 hour order service. Give your name, address with postcode, phone number, bankcard number and expiry date then your order—and presto your order will be processed and back to you in a flash—Please nominate Jetservice if you want overnight delivery.

**\$2.50 DELIVERY AUSTRALIA WIDE** We process your order the day received and despatch via Australia Post. Allow approx. 7 days from day you post order to when you receive goods. Weight limited 10kgs.

**\$4.50 DELIVERY AUSTRALIA WIDE** We process your order day received and despatch via Jetservice for delivery next day.

**BANKCARD HOLDERS CAN PHONE ORDER UP TO 8PM (EST) FOR NEXT DAY DELIVERY - SOUNDS INCREDIBLE DOESN'T IT?** Alright you cynics just try us! Weight limit 3.3kgs. Jetservice cannot deliver to P.O. box numbers (Australia Post would have a fit).

**\$10.00 HEAVY HEAVY SERVICE - AUSTRALIA-WIDE** All orders over 10kgs must travel on the heavy service, that is - road express. Delivery time 7 days average.

**ALTRONICS**  
**105 STIRLING ST., PERTH**  
**FOR INSTANT SERVICE**  
**(09) 328 1599**

**All Mail Orders:**  
**Box 8280 Stirling St.,**  
**Perth WA 6000**

## SCR Motor Speed Controller

H. Nacinovich, Gulgong NSW

Having tried a variety of SCR motor speed controllers, I could never find one to satisfy the requirements of adequate control, good speed regulation and freedom from hunting. The simple phase control circuits so often published utilise the back-emf of the motor as a feedback signal in a manner tending to maintain a constant speed characteristic. Unfortunately, the degree of feedback control obtainable with such a simple circuit is necessarily limited and the speed regulation, as a result, is relatively poor.


The overall performance is a compromise between a combination of factors which determine, on the one hand, the degree of feedback control and on the other, stability (i.e. freedom from hunting, hysteresis etc). The two are inversely related. If you want maximum stability, you sacrifice feedback control, and vice versa.

Phase control over a full 0 to 180 degrees is impossible, in fact, it's considerably less. Component values are critical and dissipation in the control pot is fairly high.

The circuit I devised, after considerable investigation and many trials performs far better than any I have previously tried. It gives halfwave phase control virtually from 0° to 180° of the mains cycle, it has independently adjustable speed and stability controls, operation is independent of SCR characteristics and it provides stable operation even at low motor speeds with good speed/torque characteristics.

This circuit controls the speed of 240 V universal (ac/dc) motors. On no account must the circuit be used for appliances which are suitable only for ac operation, such as induction motors.

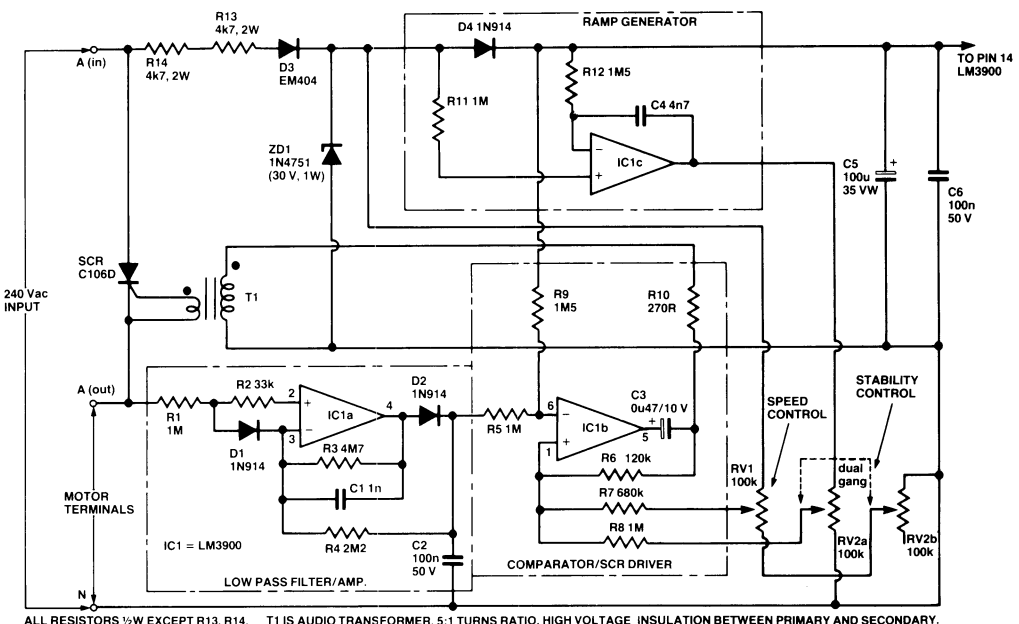An SCR connected between input and output terminals of the circuit conducts on positive half-cycles of the ac supply. Triggering of the SCR is phase controlled. The triggering phase angle is variable over nearly a full 0° to 180° of each positive



half-cycle. The back-emf generated by the motor during the intervals between conduction cycles of the SCR is used as a feedback signal to compensate for varying load conditions imposed upon the motor.

There are two variable control functions, one of which provides the 'speed' setting and the other of which is a 'stability' (or 'gain') control. The latter determines the feedback characteristics of the circuit and can be adjusted to obtain optimum performance from a motor with which the circuit is to be used.

This is an unusual and extremely useful feature as it can be used to programme the speed/torque characteristics of a given motor over a wide operating range and to adjust for an optimum balance between feedback control and motor stability under given operating conditions.

This is especially useful at low speed settings at which the back-emf of any motor is low and it is difficult otherwise to achieve both good torque characteristics and stable motor running.

The circuit uses 3/4 of an LM3900 quad op-amp IC to control the phase triggering of the SCR. The voltage across the motor terminals is converted into a current signal which is applied to the non-inverting input of IC1a.

During the intervals between conducting cycles of the SCR this signal, which is proportional to the back-emf (and hence speed) of

the motor, is amplified by IC1a.

The amplified signal is applied to capacitor C2 via diode D2. The capacitor C2 holds its charge sufficiently long each cycle to present a relatively clean dc signal to comparator IC1b. That is, a signal which is relatively free of spikes and other spurious noise components which could cause erratic phase triggering of the SCR. Capacitor C1 helps by filtering out most of these components before the signal is applied to C2.

Diode D1 ensures that the output of IC1a goes low when the SCR conducts as otherwise C2 would be charged up to a voltage proportional to the applied mains voltage rather than to the back-emf of the motor. In this regard, the ratio of resistors R1 and R2 is chosen so that diode D1 conducts when the input voltage exceeds the maximum (typical) back-emf of the motor (about 15 V).

An integrator, IC1c, provides a ramp signal which is synchronised to the phase of the supply. The amplitude of the ramp signal is varied by potentiometer RV2a and applied to an input of comparator IC1b. Potentiometer RV2a forms the 'stability' control. An adjustable bias signal is obtained from potentiometer RV1 and applied to the same input as the ramp signal. Potentiometer RV1 forms the 'speed' control.

The feedback performance of the circuit is determined by the amplitude of the ramp signal

applied to the comparator relative to the amplitude of the signal from IC1a. Adjustment of RV2, since it varies the signal applied to IC1b also affects the speed. To minimise this effect, a compensating variable resistor, potentiometer RV2b is connected in series with RV1 and ganged with RV2a.

The SCR is triggered by a pulse output produced by IC2, via a transformer. In this case an ordinary transistor output transformer taken out of the 'junk-box' was used. This transformer happened to have a turns ratio of about 5:1 and works well but other ratios may also be satisfactory.

Before it was used however, the pulse response of the transformer was checked with a signal generator and CRO. Most importantly, the insulation between primary and secondary windings was checked to make sure that it would withstand the peak mains voltage.

The power requirements for the IC are modest and thus a simple voltage dropping resistor arrangement was used in preference to a more expensive step-down transformer. The zener diode ensures a stable operating voltage which is virtually immune to mains voltage variations. The diode D3 is optional but has the advantage that it halves the power dissipated in resistors R12 and R13. Apart from these resistors, all resistors may be standard 1/2 watt, 5% types.

READ THIS-

**STOP**

**important notice**

**GO**

**FOR**

**COMPUTERS  
AT REALISTIC  
PRICES**

**ALL QT COMPUTER PRODUCTS NOW  
AVAILABLE ONLY FROM PRE-PAK**

FOLLOWING A RECENT AGREEMENT BETWEEN MR BOB STEIN, OF QT COMPUTER SYSTEMS (AUST) AND MR I. RALPH, OF PRE-PAK ELECTRONICS PTY. LTD, ALL COMPUTER PRODUCTS PREVIOUSLY SOLD BY QT COMPUTER SYSTEMS DIRECTLY, WILL NOW BE SOLD BY PRE-PAK ELECTRONICS AT THEIR SYDNEY STORE. "THIS WILL ALLOW US TO DEVOTE MORE TIME TO MANUFACTURING AND SYSTEMS DEVELOPMENT", SAID MR STEIN, "HOWEVER, WE WISH TO KEEP FAITH WITH OUR MANY 'BUILD-IT-YOURSELF' CUSTOMERS". MR RALPH STATED THAT "MOST QT PRODUCTS ARE CURRENTLY EX-STOCK AND PRICES ARE SUBSTANTIALLY THE SAME AS LAST YEAR'S". "OUR EXTENDED TRADING (6 DAYS), IS A BIG ADVANTAGE", HE ADDED.



COMPUTER  
SYSTEMS

**Z80 SINGLE BOARD \$100  
COMPUTER SBC 2/4**

**\$239**

\$199 NO S/TAX  
KIT PRICE.

BUILT **\$299.00**

& TESTED. \$249 no Tax


BARE BOARD **\$79.20**

PLUS MANUAL. \$66 no Tax

ADD FREIGHT: \$4.00 ONLY

FEATURES:

The QT Computer SBC 2/4 Processor Board may be used as a stand-alone computer or as the host CPU of a large system. It works reliably with dynamic RAM boards and more importantly with soft sector disk controllers, and hence standard versions of CP/M. This gives access to the largest software base for microcomputers. 2 or 4 MHz switch selectable. ● 1K RAM (can be located at any 1K boundary) ● One each serial and parallel I/O ports ● Power on jump to on board EPROM (2708 or 2716) addressable on any 1K or 2K boundary ● Full 64K use of RAM in shadow mode ● Programmable timers available for use by programs ● DMA capability allows MMT signal generation on CPU board or elsewhere in system under DMA or from panel control ● Programmable baud rate 110-9600

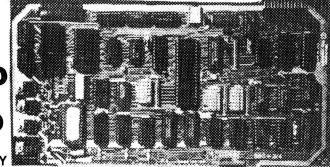

**A LARGE RANGE OF KITS, PARTS, METALWORK**

**QT SILENCE+ MOTHERBOARDS**

The SILENCE+ has become one of the most tried and proven motherboards on the market. Using a unique grounding matrix, each line is completely surrounded with ground shielding which eliminates necessity for termination and gives the unit a very high cross-talk rejection. Has been used as high as 14MHz w/o term.

PRICES:	no Tax	incl Tax
6 slot bare board.....	\$ 31.00	\$ 37.20
6 slot A&T.....	\$ 81.00	\$ 87.20
8 slot bare board.....	\$ 33.00	\$ 39.60
8 slot A&T.....	\$104.00	\$110.60
12 slot bare board.....	\$ 39.00	\$ 46.80
12 slot A&T.....	\$138.00	\$145.80
18 slot bare board.....	\$ 61.00	\$ 73.20
18 slot A&T.....	\$178.00	\$190.20

**DUAL 5 1/4" DRIVES**


432mmLx178mmHx508mmD

**DUAL 8" DRIVES**

432mmLx244mmHx532mmD

- Power and Reset switches on front
- Fully professional

**MAINFRAMES**

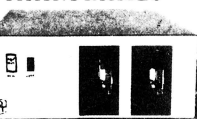

The QT Mainframes are, we believe, the most versatile models on the market. They will accommodate 6, 8 or 12 slot card cages using the Silence+ Motherboards. Any 5 1/4 inch, 8 inch standard or slimline disk drives can be fitted. Adequate space is available for a fan and power supply (these are included in assembled and tested versions). Just add a CPU, memoryboard, disk controller and terminal and you have an inexpensive, high quality computer system. The finish is beige with brown cover.

Prices are for 5 1/4" or 8" sizes. No Tax Incl Tax  
Bare cabinet.....\$198.00 \$237.60  
incl 6 slot M/board (A&T).....\$552.00 \$662.40  
incl 8 slot M/board (A&T).....\$581.00 \$697.20  
incl 12 slot M/board (A&T).....\$612.00 \$734.40  
All parts available separately, let us quote!

**DISK DRIVE CABINETS**

The QT cabinets are professionally designed and finished and are ready to accept power supplies and disk drives.

PRICES:	no Tax	incl. Tax
5 1/4" Mini Single cabinet.....	\$ 35.00	\$ 42.00
incl. power supply (A&T).....	\$129.00	\$154.80
5 1/4" Dual Mini Cabinet.....	\$ 39.00	\$ 46.80
incl. power supply (A&T).....	\$159.00	\$190.80
8" Single Cabinet.....	\$ 89.00	\$106.80
8" Single standard drive or dual slim-line cabinet incl. power supply	\$295.00	\$354.00

(Assembled and Tested)



**QT CARD CAGES**

QT card cages are strong, cadmium-plated steel frames, punched ready-to-accept card-guides and motherboard. Perfectly suited for industrial control applications with the addition of CPU and memory card with the Silence+ Motherboard.

PRICES:	no Tax	incl Tax
6 slot Card Cage.....	\$ 30.00	\$ 36.00
incl motherboard, etc	\$117.00	\$140.40
8 slot Card Cage.....	\$ 33.00	\$ 39.60
incl motherboard, etc	\$145.00	\$174.00
12 slot Card Cage.....	\$ 39.00	\$ 46.80
incl motherboard, etc	\$189.00	\$226.80

**\$100 CONNECTORS**

100 pin standard connector for S100 bus. Specially plated contacts for maximum efficiency. Made in USA.

**\$7.45**

TAX FREE \$6.20 EA. INCL. TAX

**EDGE CONNECTOR**

0.1" inch  
35 Way  
LAST FEW Pcs 0.1" pitch PCB edge connectors with 70 Gold-plated contacts at about HALF the usual price! BUY 10-\$3.90ea, 100-\$3.50  
23 WAY EDGE CONNECTOR 0.1" INCH GOLD-PLATED **\$3**

**DC MOTORS**

6-12V  
LARGE SIZE!  
IDEAL FOR TOYS, MODEL BOATS, CARS, HOBBY ETC.  
OPERATES FROM 4.5V TO 12V, POWERFUL AND RUGGED, SIZE 47MM DIAM X 60MM 10 for \$25 **\$3 ea**

**\*Power Transformers**

Bulk purchase of new, best quality MAINS TRANSFORMERS used in H and K chassis AMA-Thorn colour TV sets.  
H Primary: 0,120V,125V plus 0,120, 125V for 240V, 250V operation.  
H Secondary: 0,120V 1 Amp +6V 1 Amp  
K Primary: 0,240V,250V  
K Secondary: 0,105V 1.3 Amp plus 6V 0.9 Amp plus 12V 0.25 Amp.  
PLUS \$2 EXTRA POST. LAST FEW AVAILABLE!

**PARTY STROBE**

**\$12.50**  
NORMAL PRICE \$29.95  
SAVE NEARLY \$17.50  
"Freeze" the action at your next party or theatrical show! Mains operated with a continually variable flash rate, housed in an attractive black vinyl box 150mm




**VALU ASSORTMENTS**

LUCKY-DIP PACKS \$2ea  
500 1/2WATT RESISTORS  
200 1WATT RESISTORS  
50 1/4 HI-STAB RESISTORS  
20 MIXED POTENTIOMETERS  
20 PRESET POTS ASST.  
30 POLY. GREENCAPS  
100 CERAMIC CAPACITORS  
45 ELECTROLYTIC CAPS  
12 VARIOUS SWITCHES  
40 RADIO/TV KNOBS  
50 ASST TAGSTRIPS  
**\$2** EA CH PACK

**VIDEO IMPROVERS  
DETAIL ENHANCER**

Specially designed to rectify loss in detail derived from VCR tapes and picture impairments. Ideal for off-air recording, dubbing from VCR to VCR etc. Outputs for up to 3 separate VCR's for multi-machine recording.


**\$84.95**

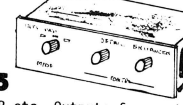

**IMAGE STABILIZER**

Stability control immediately stabilises picture of pre-recorded tapes, removing the copyguard signal. Also ensures no vertical roll or blackout will occur. Offers 2 video inputs (A or B), output for 1 VCR only. Limited quantity available at these fantastic prices.


**\$74.95**

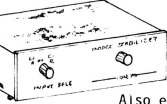

**RF-VIDEO SWITCHER**

Multi-purpose use, very low loss, RF inputs for aerial, home computer, video games, VCR, etc.

**\$39.50**

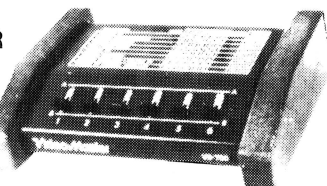

Output: 75 ohms to TV set. beautifully styled, timber ends.

**LEDs**

3mm Round  
RED...10¢  
GREEN...15¢  
YELLOW...15¢  
5mm Round  
RED...10¢  
GREEN...15¢  
YELLOW...15¢  
5x2mm Rect  
RED...20¢  
GREEN...25¢  
from 10¢

Z80A PIO \$9.60  
Z80A SIO \$10.60  
Z80A CTC \$9.60  
8255 \$11.95  
8253 \$17.40

**PACK & POST**  
\$2.00 PLUS 5% OF ORDER VALUE

**BNC PLUGS**

High Quality **\$2**

**COMMUNICATIONS  
POWER MICROPHONE**

Leson high quality with compression. LOW NOISE **\$19**

**SOCKETS**

HIGH QUALITY LOW PROFILE  
8 or 14p... 5 for \$1  
16 PIN... 4 for \$1  
18 PIN... 3 for \$1  
24, 28p... 2 for \$1  
40PIN... 1 for \$1

**ASSORTED POTS**

20 MIXED VALUES Linear, log, our choice!  
100 MIXED VALUES Dual, switched, all new  
250 MIXED VALUES Bonza bulk package!  
**\$3 \$10 \$20**

**IC's**

"SWEEPINGS OFF THE FACTORY FLOOR"  
Approx 100 ASST. FOR **\$11.50** 1000 for \$100



**PRE-PAK electronics p/l**

**1a WEST ST, LEWISHAM, NSW**

**569-9797**  
24 HR PHONE ORDER SERVICE


**SEE THE HUGE RANGE IN-STORE!**  
IF YOU THINK WE PACK A LOT INTO OUR ADS, YOU SHOULD SEE WHAT'S IN OUR SHOP!


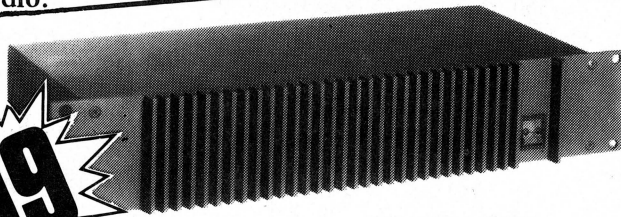
# SO PURE, IT'S WICKED

The ETI 5000 System. Pristine. Pure. Cocaine for the ears.

And to think that they are Australian made and designed. They can stand comparison with any kit or ready-built available — anywhere. In fact we still think that they are the world's best amplifiers. We should be justifiably proud of this achievement in Audio.



## SPECIFICATIONS

### POWER OUTPUT FREQUENCY RESPONSE

Around 100W RMS into 8 ohms  
8Hz to 20kHz, +0 - 0.4dB  
2.8Hz to 65kHz, +0 - 3dB

Note: these figures are determined solely by passive filters

### INPUT SENSITIVITY HUM NOISE 2nd HARMONIC DISTORTION

1V RMS for 100W output  
- 100dB below full output (flat)  
- 116dB below full output (flat, 20kHz bandwidth)  
< 0.001% at 1kHz (0.0007% on prototypes) at 100W output using a +56V supply rated at 4A continuous  
< 0.003% at 10kHz and 100W  
< 0.0003% for all frequencies less than 10kHz and all powers below clipping  
Determined by 2nd harmonic distortion (see above)

< 0.003% at 100W (50Hz and 7kHz mixed 4:1)


Unconditional

### 3rd HARMONIC DISTORTION TOTAL HARMONIC DISTORTION INTERMODULATION DISTORTION STABILITY

We regret to advise that among other things, metalwork and sales tax increases have forced us to increase our prices slightly. Whilst we could have kept our costs down by using inferior components, we refused to take this course of action.
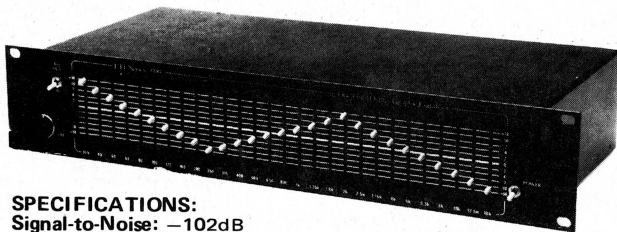
## 5000 SERIES GRAPHIC EQUALISERS

Latest addition to the thoroughbred 5000 Series stable! David Tillbrook has once again produced a 'No Compromise' design. This new component, a 1/3 octave equaliser, gives you ABSOLUTE CONTROL over the acoustics of your particular listening environment. You get 3 SEPARATE CONTROLS for every octave of audio bandwidth to virtually eliminate the subtle nuances that are particular to your listening area. 1/3 octave equalisers have been used by professional engineers in Recording Studios and Live Concerts for over a decade now. It is no accident that the advent of the 1/3 octave equaliser and studio quality live sound have gone hand-in-hand. BUT THERE'S A CATCH. One of these equalisers is not enough. You will have to buy 2 (for stereo). Quite a lot of money — but worth it if you want the best. The Jaycar kit includes a fully pre-punched plated chassis, pre-punched heavy gauge front panel with silkscreened front panel to match the other 5000 components. It is absolutely original. You can purchase the kits one at a time for \$199 each or, for two, \$389 — a \$10 saving. If you are one of the hundreds of happy 5000 users we are convinced that you will be just delighted with this unit.



### SPECIFICATIONS:

Signal-to-Noise: -102dB

with respect to 1 Volt

Frequency Response:

12Hz - 105kHz to -1dB

Boost/Cut: 14dB (28dB total)

Distortion: 100Hz-0.007%

1kHz-0.007%

10kHz-0.008%

(essentially irrespective of cut or boost)

Current consumption (DC)

Approx 100mA @ ±15V

(Requires 30V AC CT)

Output short-circuit proof.

**\$199**

BUY 2 AND SAVE \$10

— ONLY \$389

AUSTRALIAN (NOT HONG KONG)  
MADE — SPECIAL BUILT RACK  
CABINET — QUALITY!!!

ALL IC  
SOCKETS  
PROVIDED

Cat. KE4204

## "BLACK MONOLITH"

REF: ETI JAN/MARCH 1981

Cat. KE4200


The ultimate Hi-Fi power amplifier. We call our model the "Black Monolith" because we feel that the name symbolises the intelligence that went into the design.

The Jaycar "Black Monolith" is without doubt the best kit of the project available. If you have doubts ring our Managing Director, Gary Johnston and he will tell you! (Be prepared for a long conversation).

Several kit suppliers now have 'versions' of the original 5000 P.A. which claim to be similar to ours. This is simply not the case. Space does not allow us to show EVERY refinement that has been made to the 5000 but notable ones are:
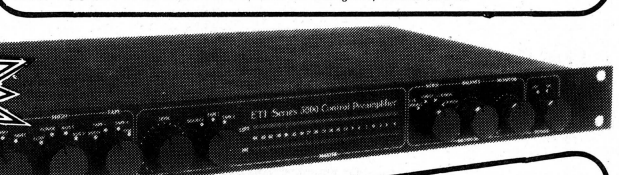
### EXCLUSIVE FEATURES:

- Rear panel mains fuseholder
  - 1% METAL FILM resistors used
  - Flux-shorting strap on power transformers
  - Original chassis bar design
  - Beryllium Oxide (Space Age Ceramic) TO-3 washers. (NOT flimsy Mica)
  - Jig drilled and extruded heavy gauge, anodised heatsink bracket
  - SUPERFINISH front panel. STILL THE BEST now with blind tapped holes
  - New heavy duty heatsinks for the driver transistors. 100% extra heatsink area and black anodised for greater efficiency (NOT in original design)
  - Ventilation holes in metalwork at critical points (NOT in original design)
  - Extra 3 pin DIN socket on rear panel (total 2) to power new 5000 components
- IF YOU THINK THAT YOU CAN SAVE MONEY ON THESE KITS ASK YOUR SUPPLIER IF HE WILL GIVE YOU ALL OF THESE FEATURES AT THE PRICE. MAKE SURE THAT YOU GET IT IN WRITING!! (Write for new glossy leaflet (SAE))



Cat. KE4202

## "BLUEPRINT"

"One Swallow does not make a spring"

— Neither does a few gold RCA sockets!

Several of our competitors are imitating our "Blueprint" preamp by adding a few bits and pieces, notably gold plated RCA sockets to their standard kits. Unfortunately they have missed the point. We supply gold plated sockets in our "Blueprint" preamp but only where it makes sense to do this, i.e. on the inputs — NOT the outputs. 16 gold sockets are provided by us. This, however, does not make a "Blueprint". THIS DOES:

- Low capacitance screened cable - 12 metres of it. NOT Taiwanese cable as supplied in other kits. Our cable costs us NEARLY 5 TIMES MORE than the Taiwanese stuff.
- Original ETI designed front panel. Not an "ADAPTION". Our front panel is by far the nicest.
- Factory annealed PCB's to reduce chances of dry or noisy solder joints.
- Quality LEDs, polished finish, multicoloured display.
- IC sockets on line amp board.
- Special rear panel.
- Special low noise selection LM394H NOT CH device in M.C. preamp.
- Thermalloy (U.S. made) heatsink on 7805 regulator.
- English Lorlin selector switches.
- Apart from the 16 gold RCA's we throw in a pair of gold plated line RCA plugs — worth \$5.
- Special Nylon rear panel grommets.

So don't "Swallow" the facts before they are properly digested!!

You can't make a silk purse out of a sow's ear. Send SAE for full specs.

### FUNCTIONS

- MOVING COIL INPUT
- MOVING MAGNET (DYNAMIC CART)
- INPUTS (2 OFF)
- TUNER INPUT
- AUX INPUTS (2 OFF)
- TAPE INPUTS (2 OFF)
- INPUT LEVEL CONTROL
- TAPE OUTPUTS (2 OFF)
- 400Hz CALIBRATION OSCILLATOR
- LED AVERAGE (VU) & PEAK
- LEVEL METERS -48dB TO +9dB

- MODE SWITCH, STEREO BALANCE CONTROL
- LINE OUT, MONITOR OUT, MONITOR VOLUME CONTROL

### FEATURES

- EXTREMELY CLOSE TRACKING TO RIAA PHONO EQ.
- GOLD PLATED CONNECTORS ON ALL INPUTS
- ENGLISH 'LORLIN' LOW NOISE SELECTOR SWITCHES

- LOW NOISE 1% 50ppm METAL FILM RESISTORS USED
- TINNED FIBREGLASS PCB'S
- LOW CAPACITANCE SCREENED CABLE USED THROUGHOUT
- QUALITY IC SOCKETS
- SPECIAL REAR PANEL
- MULTICOLOURED RECTANGULAR LEDS USED

## Jaycar NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000  
PHONE: 264 6688 TELE: 72293

"NEVILLES CORNER"

Cnr. CARLINGFORD & PENNANT HILLS ROAD,

CARLINGFORD

PHONE: 872 4444

MAIL ORDERS TO: BOX K-39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES

\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)

\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)

\$100 up (\$8.00)

NEW SHOP HOURS

Mon. Fri. 8.30 to 5.30pm

Sat. 8.30 to 12.00pm

Thurs. night to 8.30pm

Mail Order By **BANKCARD**  
Via Your Phone



# SHOPAROUND

This page is to assist readers in the continual search for components, kits, printed circuit boards and other parts for ETI projects and circuits. If you are looking for a particular item or project and it is not mentioned here, check with our advertisers.

## ETI-268 Float charger

Be kind to your NiCads and give them proper charging treatment. This project will look after them, never overcharging, ensuring they have a long life of many charge-discharge cycles. At time of going to press, the following firms indicated they would be stocking kits: **Altronics** (Perth), **Dick Smith Electronics** (stores all over), **Jaycar** (Sydney), **Rod Irving Electronics** (Melbourne). Also try **All Electronic Components** in Melbourne.

If you're making your own pc board and taking the components from your stockpile, you probably won't have the LM336 on hand. We obtained ours from **Radio Despatch Service** in Broadway, Sydney. Any supplier stocking National Semiconductor devices and worth his salt will either have it in stock or order it in for you. It's an under-\$2 item.

## ETI-654 interface

Despite its apparent complexity, this project is relatively simple to

construct and get going. The pc board is a double-sided, plated-through hole type so you won't be able to make your own — unless you have the right facilities! If you don't need the analogue facilities (or would like to leave that till a later date), then you can leave out IC1 (741), IC2 (AD7524) and IC6 (AD570). This will save you some money as the A-D and D-A converters are relatively expensive devices.

Kits in one form or another will be available from **Rod Irving Electronics** in Melbourne and **Jaycar** in Sydney.

The AD7524 DAC and AD570 ADC are distributed by **Parameters Pty Ltd**, Sydney (02) 439-3288 and Melbourne (03)580-7444.

## ETI-335 wiper controller

Despite the relative complexity of the circuit of this project (relative to previous wiper controllers, that is) it's quite simple to put together. All the com-

ponents are widely available 'off the shelf', so constructors should have no difficulty getting it together.

Kits will be available from **Altronics** in Perth, **Rod Irving** and **All Electronic Components** in Melbourne and **Dick Smith** stores in all states.

## Printed circuit board and panel suppliers

Almost every pc board ever published by ETI may be obtained from the following suppliers:

**All Electronic Components**  
118 Lonsdale St  
Melbourne Vic. 3000

**RCS Radio**  
651 Forest Rd  
Bexley NSW 2207

Panels, meter scales and dial faces for almost every ETI project published may also be obtained from the above two firms.

For pc boards produced over the past three to five years, the following suppliers generally keep stocks on hand:

**Electronic Agencies**  
115-117 Parramatta Rd  
Concord NSW 2137  
and  
117 York St  
Sydney NSW 2000

**Radio Despatch Service**  
869 George St  
Sydney NSW 2000

**Rod Irving Electronics**  
425 High St  
Northcote Vic. 3070

**James Photonics**  
522 Grange Rd  
Fulham Gardens SA 5024

**Jamal Products**  
P.O. Box 168  
Victoria Park WA 6100

**Sunbury Printed Circuits**  
Lot 14, Factory 3,  
McDougall Rd  
Sunbury Vic. 3429

**Mini Tech**  
P.O. Box 9194  
Auckland N.Z.

## MOSS COMPONENTS

PO BOX 324, FAIRFIELD, NSW 2165.

Capacitors & Resistors  
Integrated Circuits  
Wires & Cables  
Semiconductors  
Hirose Connectors  
Ribbon Cable  
Plugs & Sockets

MAIL ORDER SUPPLY  
SPECIALISTS

FOR YOUR  
ELECTRONIC  
NEEDS

Write for  
FREE  
Catalogue

## ELECTRONIC HOBBYIST!

DO YOU LIVE IN ...

Ringwood      Lilydale  
Boronia      Wantirna  
Bayswater      Croydon  
Mooroolbark etc....

We carry a comprehensive  
range of electronic  
components at very keen  
prices.

Ian J. TRUSCOTT  
ELECTRONICS

CNR EASTFIELD  
& BAYSWATER ROADS,  
SOUTH CROYDON, VIC.  
TELEPHONE (03) 723 3860

Australians  
are dying  
younger  
from heart  
disease.



National Heart Foundation.

# ETI BOOK SALES

*Save time and trouble with mail order. Just fill out the coupon on page 58*

## electronics textbooks

**ELECTRONICS — IT'S EASY VOL. 1** \$5.95  
Meters, resistance, capacitance and inductance, emitter followers, op amps, power supplies and electronic filters.

**ELECTRONICS — IT'S EASY VOL. 1** \$12.95  
Same content in a hard-cover form.

**ELECTRONICS — IT'S EASY VOL. 2** \$5.95  
Digital sub-systems counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes.

**ELECTRONICS — IT'S EASY VOL. 2** \$12.95  
Same content in a hard-cover form.

**ELEMENTS OF ELECTRONICS**  
This series is an introduction to modern electronics. All the maths is taught as the reader progresses. The course concentrates on the understanding of concepts central to electronics, rather than digressing over the whole field. The author anticipates where difficulties lie and guides the reader through them.

**BOOK 1**  
**BP62** \$7.52  
All fundamental theory necessary to full understanding of simple electronic circuits and components.

**BOOK 2**  
**BP63** \$7.52  
Alternating current theory.

**BOOK 3**  
**BP64** \$7.52  
Semiconductors technology leading to transistors and ICs.

**BOOK 4**  
**BP77** \$9.76  
Microprocessing systems and circuits.

**BOOK 5**  
**BP89** \$9.76  
Communications.

**ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST**  
**228B** \$4.32  
This book supplies the electronics hobbyist with the background knowledge which will exactly suit their specific requirements. Minimum maths.

**BEGINNER'S GUIDE TO DIGITAL ELECTRONICS**  
**BP61** \$3.36  
Covers all essential areas including number systems codes, constructional and sequential logic, analogue/digital/analogue conversion.

**A MICROPROCESSOR PRIMER**  
**BP72** \$5.92  
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

## reference and data handbooks

**AUDIO CYCLOPEDIA**  
**20675P** \$66.00

A complete, in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. Over 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

**REFERENCE DATA FOR RADIO ENGINEERS**  
**21218P** \$21.95

The largest and most comprehensive collection of equations, graphs, tables, and other reference data needed in general radio engineering and design. Contains hundreds of charts, monographs, diagrams, curves, tables and illustrations.

**TUBE SUBSTITUTION HANDBOOK**  
**21746P** \$8.75

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

**CONTEMPORARY MATHEMATICS FOR ELECTRONICS**  
**70274P** \$29.75

This book is split into three sections. Direct current maths introduces the student to the calculator, fractions and dimensional analysis. Alternating current maths covers phasors, quadratics and RMS in both sine and digital waveforms. Active device maths introduces number systems and boolean.

**AUSTRALIAN MICROCOMPUTER HANDBOOK**  
**72505** NOW \$15.00

Normally \$25.00. A detailed buyer's guide to micro-computer systems and application packages in commercial, industrial, scientific, educational and home/hobby areas.

**TRANSISTOR SUBSTITUTION HANDBOOK**  
**21515P** \$8.75

17th edition — Accurate transistor substitution in a matter of seconds with this replacement listing of over 19 000 American and foreign bipolar transistors.

**THE CP/M HANDBOOK WITH MP/M**  
**88048A** \$19.95

Shows you how to use CP/M (control program for microprocessors) and its resources. No prior knowledge of computers is assumed. CP/M is available on nearly all computers using the 8080, 8085 or Z80 microprocessors.

**HANDBOOK OF ICS EQUIVALENTS AND SUBSTITUTES**  
**202B** \$5.76

Contains full interchangeability data on more than 9500 ICs with possible alternatives and equivalents shown. Covers many types of digital and linear ICs.

**HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS**  
**BP2** \$2.25

Equivalents book for amateurs and servicemen. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.

**RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART**  
**BP7** \$1.60

This large wall chart covers all colour codes in use throughout the world. For all radio and electronic components made in UK, USA, Europe and Japan.

## FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

**BP1** \$3.36  
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in UK, Japan, USA, Germany, France, Europe, Hong Kong and includes types produced by more than 120 different manufacturers.

## SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

**BP14** \$5.92  
Interchangeability data covers semiconductors manufactured all over the world. Immediate equivalents are shown and possible substitutes are included.

## GIANT CHART — RADIO, ELECTRONICS, SEMI-CONDUCTORS & LOGIC SYMBOLS

**BP27** \$1.92  
Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks!

## RESISTOR SELECTION HANDBOOK

**BP28** \$2.24  
Shows how to combine two preferred values of resistor to obtain virtually any required value of resistance. Includes information about fixed resistors, standard ranges, colour codes and markings, power ratings and resistor calculations.

## ELECTRONIC CALCULATOR USERS' HANDBOOK

**BP33** \$5.12  
Presents formulae, data, methods of calculation, conversion factors, etc, for use with the simplest or most sophisticated calculators. Includes the way to calculate using only a simple four-function calculator: trigonometric functions, hyperbolic functions, logarithms, square roots and powers.

## DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS

**BP40** \$12.32  
Revised edition showing Japanese, American and European equivalents and pin connections of a popular user-orientated selection of digital ICs (available mid 1983).

## LINEAR EQUIVALENTS AND PIN CONNECTIONS

**BP41** \$9.12  
Shows equivalents and pin connections of a selection of popular linear ICs, with details of families, functions, country of origin and manufacture. Includes devices from Analog Devices, Advance Micro Devices, Fairchild, Harris, ITT, Motorola, Philips, RCA, Raytheon, Signetics, Sescocrem, SGS-ATES, Siemens, AEG-Telefunken, Teledyne, Texas Instruments.

## PRACTICAL ELECTRONIC CALCULATIONS & FORMULAE

**BP53** \$9.76  
For the practical person's workbench. Bridges gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths avoided where possible.

## INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

**BP85** \$9.76  
Companion to BP1 and BP14 equivalents books, but contains a huge amount of information on modern transistors produced by over 100 manufacturers. Wherever possible, equivalents are subdivided into European, American and Japanese types. Also shown are the material type, polarity, manufacturer and indication of use or application.

## HOW TO IDENTIFY UNMARKED ICs

**BP101** \$2.46  
This chart shows the reader how, with just a test-meter, to go about recording the particular 'signature' of an unmarked IC which should enable the IC to be identified with reference to manufacturers or other data.

# electronics for beginners

## BEGINNERS HANDBOOK OF IC PROJECTS

**74286P \$19.25**  
The novice is guided in mastering the fundamentals of building, troubleshooting and testing electronic projects. In addition to many elementary projects, more advanced ones are included concerning bipolar integrated circuits and medium and large-scale integrated circuits.

## HI-FI LOUDSPEAKER ENCLOSURES

**205B \$3.36**  
Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

## SOLID STATE NOVELTY PROJECTS

**219B \$3.04**  
A number of novelty projects using modern ICs and transistors. Includes 'Optomin' — a musical instrument played by reflecting a light beam with your hand, water warbler for pot plants, music tone generator, LEDs and ladders game, touch switch, electronic roulette wheel, etc.

## SOLID STATE SHORTWAVE RECEIVERS FOR BEGINNERS

**222B \$4.32**  
Design and construction of several solid-state shortwave receivers giving high level of performance yet utilising relatively few inexpensive components.

## BEGINNERS' GUIDE TO BUILDING ELECTRONIC PROJECTS

**227B \$5.12**  
Enables total beginners to tackle electronic projects. Includes component identification, tools, soldering, building methods, cases, legends, etc. Practical basic projects are included.

## ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

**228B \$4.32**  
This book supplies the electronics hobbyist with the background knowledge which will exactly suit their specific requirements. Minimum maths.

## RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

**BP7 \$1.60**  
This large wall chart covers all colour codes in use throughout the world. For all radio and electronic components made in UK, USA, Europe and Japan.

## FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

**BP23 \$2.72**  
Full constructional data, circuits, components lists for many practical projects including audio distortion meter, superFET receiver, guitar amp, metronome, etc.

## RESISTOR SELECTION HANDBOOK

**BP28 \$2.24**  
Shows how to combine two preferred values of resistor to obtain virtually any required value of resistance. Includes information about fixed resistors, standard ranges, colour codes and markings, power ratings and resistor calculations.

## HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS

**BP32 \$5.92**  
Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

## ELECTRONIC PROJECTS FOR BEGINNERS

**BP48 \$4.64**  
This book gives the newcomer to electronics a wide range of easily built projects. Actual components and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.

## POPULAR ELECTRONIC PROJECTS

**BP49 \$4.96**  
A collection of the most popular types of circuits and projects to interest most electronics constructors. The projects cover a wide range and are divided into four basic types: radio, audio, household and test equipment.

## BEGINNERS GUIDE TO DIGITAL ELECTRONICS

**BP61 \$3.36**  
Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

## ELECTRONIC GAMES

**BP69 \$5.92**  
How to build many interesting electronic games using modern ICs. Covers both simple and complex circuits for beginner and advanced builder alike.

## RADIO CONTROL FOR BEGINNERS

**BP79 \$5.92**  
How complete systems work with constructional details of solid state transmitters and receivers. Also included — antennas, field strength meter, crystal controlled superhet, electro-mechanical controls. Section dealing with licensing etc. not applicable to Australia.

## EASY ELECTRONICS-CRYSTAL SET CONSTRUCTION

**BP92 \$6.56**  
For those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. The circuits are based on those from earlier publications but have been modified to use modern inexpensive components and home wound coils.

## IC PROJECTS FOR BEGINNERS

**BP97 \$6.56**  
Especially written for the less experienced hobbyist, and offers a range of fairly simple projects based around a number of popular and inexpensive linear and digital ICs. Complete layout and point-to-point wiring diagrams included.

## ELECTRONICS — IT'S EASY VOL. 1

**\$5.95**  
Meters, resistance, capacitance and inductance, emitter followers, op amps, power supplies and electronic filters.

## ELECTRONICS — IT'S EASY VOL. 1

**\$12.95**  
Same content in a hard-cover form.

## ELECTRONICS — IT'S EASY VOL. 2

**\$5.95**  
Digital sub-systems counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes.

## ELECTRONICS — IT'S EASY VOL. 2

**\$12.95**  
Same content in a hard-cover form.

## SIMPLE PROJECTS FROM ETI

**\$2.95**  
Two volumes containing easy projects plus chapters on construction techniques and useful information on components.

## HOBBY ELECTRONICS PROJECT BOOK

**\$4.95**  
Fifty projects ranging from very simple ones for complete beginners to more elaborate ones for those with more experience. There's a complete guide to soldering and instructions on how to make your own pc boards.

## HOW TO BUILD ELECTRONIC GAMES

**\$3.95**  
Alien invaders, electronic die, sound effects, two slot car controllers, electronic poker machine, the family ferry and lots more.

## HOW TO BUILD GOLD AND TREASURE DETECTORS

**\$3.95**  
Tells you how metal detectors work and how to construct the different types of detectors: discriminating, BFO, induction balance and a professional deep-seeking unit. How to build a geiger counter.

# constructional projects general

## DESIGN OF TRANSISTOR CIRCUITS, WITH EXPERIMENTS

**21626P \$20.75**  
A self-teaching course in transistor circuits — seven chapters explore the fundamentals of active semiconductor and their operating principles and procedures. Experiments in design and semiconductor testing provide hands-on experience.

## UNIQUE ELECTRONIC WEATHER PROJECTS

**21484P \$13.25**  
Fun and easy-to-build projects include an IC barometer to serve as a tornado warning and a 'thermostat with a brain' to help conserve energy.

## BUILD YOUR OWN HI-FI & AUDIO ACCESSORIES

**220B \$3.04**  
Essential for keen hi-fi and audio enthusiasts. Projects include stereo decoder, three-channel mixer, FET preamp for ceramic pick-ups, mic preamp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, voice-operated relay, etc.

## 28 TESTED TRANSISTOR PROJECTS

**221B \$4.32**  
Some circuits are new, others are familiar designs. Projects can be split and/or combined for specialised needs.

## 50 CMOS PROJECTS

**224B \$4.64**  
Many interesting and useful projects — multivibrators, amplifiers and oscillators; trigger devices; special devices.

## MAJOR SOLID STATE AUDIO HI-FI PROJECTS

**BP29 \$3.04**  
Three projects for the more experienced constructor: 12.5 W/ch stereo amplifier, eight input stereo/mono mixer and 4x14 W quadrasonic amplifier. Full constructional details provided.

## HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS

**BP32 \$5.92**  
Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

## HOW TO MAKE WALKIE-TALKIES

**BP43 \$5.12**  
This treatise on low power transmitter-receivers (walkie-talkies) covers many aspects from licensing requirements and bands, through practical circuitry and construction to the various types of aerials that may be used.

## PROJECTS IN OPTO-ELECTRONICS

**BP45 \$5.92**  
Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra red transmitters and detectors, modulated light transmission and also photographic projects etc.

## RADIO CIRCUITS USING ICs

**BP46 \$4.64**  
This book describes ICs and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. Also discussed are stereo decoder circuits, quadrasonic circuits and voltage regulator devices.

## POPULAR ELECTRONIC PROJECTS

**BP49 \$4.96**  
Includes a collection of the most popular types of circuits and projects which cover radio, audio, household projects and test equipment.

## HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE

**BP57 \$5.12**  
Project divided into sections for builder individually to construct and test — then assemble into complete instrument. Includes short section on scope usage.

## SINGLE IC PROJECTS

**BP65 \$5.12**  
Simple to build projects based on a single IC. A few projects use one or two transistors as well. A strip board layout is given for each project plus special constructional and setting up info. Contents include low level audio circuits, audio power amps, timers, op-amps and miscellaneous circuits.

## ELECTRONIC GAMES

**BP69 \$5.92**  
A number of interesting electronic games projects using ICs for both the beginner and advanced enthusiast.

## ELECTRONIC HOUSEHOLD PROJECTS

**BP71 \$5.92**  
Most useful and popular projects for use around the home. Includes two-tone buzzer, intercom, smoke and gas detectors, baby alarm, freezer alarm etc. etc.

## REMOTE CONTROL PROJECTS

**BP73 \$6.56**  
Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial as well as model use.

## POWER SUPPLY PROJECTS

**BP76 \$5.92**  
This book gives a number of power supply designs, including simple unregulated types, fixed voltage regulated types and variable voltage stabilised designs. The designs are all low voltage types for semiconductor circuits.

## POPULAR ELECTRONIC CIRCUITS — BOOK 1

**BP80 \$6.56**  
Yet more circuits from Mr. Penfold! Includes audio, radio, test gear, music projects, household projects and many more. An extremely useful book for all hobbyists, offering remarkable value for the designs it contains.

## ELECTRONIC PROJECTS USING SOLAR CELLS

**BP82 \$6.56**  
Includes a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

## DIGITAL IC PROJECTS

**BP84 \$6.56**  
Companion to No. 225 Practical Introduction to Digital ICs and BP61 Beginner's Guide to Digital Electronics. The projects included in this book range from simple to more advanced projects — some board layouts and wiring diagrams are included.

## AUDIO PROJECTS

**BP90 \$6.56**  
Covers a wide range of audio projects including pre-amplifiers and mixers, power amplifiers, tone controls and matching etc. A number of board layouts and wiring diagrams are included.

# LOOK! More books!

mail order coupon on page 58

## ELECTRONIC TIMER PROJECTS

**BP93** \$6.56  
These may have a high degree of accuracy with quartz control or they may be quite simple designs, using only a few components. A number of specialist timer projects are car windscreen wiper delay unit, darkroom timer, metronome etc.

## ELECTRONIC PROJECTS FOR CARS AND BOATS

**BP94** \$6.56  
Fifteen fairly simple projects designed for use with 12 V electrical systems but in some cases can also be employed with 6 V and/or positive earth systems as well.

## MODEL RAILWAY PROJECTS

**BP95** \$6.56  
Projects include such things as controllers, signals and sound effects units. Construction stripboard layouts are provided for each project.

## CB PROJECTS

**BP96** \$6.56  
A number of useful designs include a speech processor, interference filters and a simple CB radio receiver. Stripboard layouts, wiring diagrams and notes on construction are provided.

## POPULAR ELECTRONICS CIRCUITS — BOOK 2

**BP98** \$7.52  
A companion for BP80, this book provides a wide range of designs for electronics enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed constructional information.

## MINI-MATRIX BOARD PROJECTS

**BP99** \$6.56  
This book provides a selection of 20 useful circuits which can all be built on a mini-matrix board which is just 24 holes by 10 copper strips in size. Simple and easy for those with not much experience in electronics.

## MULTI-CIRCUIT BOARD PROJECTS

**BP103** \$6.56  
All circuits are based on one specially designed pc board. Recommended to the less experienced hobbyist.

## ELECTRONIC SCIENCE PROJECTS

**BP104** \$7.52  
These projects range in complexity from a simple colour temperature meter to an infra-red laser. There is an electronic clock regulated by a resonating spring and an oscilloscope with a solid-state display. How to build them and use them is fully explained.

## AERIAL PROJECTS

**BP105** \$6.56  
Practical aerial designs including active, loop and ferrite which are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

## MODERN OP-AMP CIRCUITS

**BP106** \$6.56  
A collection of widely varying circuits and projects based on the op-amp ICs.

## HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

**BP110** \$6.56  
Helps you to overcome the problems of a circuit that doesn't work by indicating how and where to start looking for many of the common faults that can occur when building up a project.

## circuit techniques and design

## TTL COOKBOOK

**21035P** \$17.50  
A complete look at TTL logic circuits — what TTL is, how it works, and how to use it. Many kinds of practical TTL are included, such as digital counters, electronic stopwatches, digital voltmeters, etc.

## ACTIVE-FILTER COOKBOOK

**21168P** \$21.95  
Learn how to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

## ELECTRONIC CIRCUITBOOK 1: PROJECT CONSTRUCTION

**21241P** \$7.50  
Your basic guide to project construction, covering component identification, power supplies, proper tool selection, troubleshooting techniques, oscilloscope use, custom-made enclosures, and more.

## CMOS COOKBOOK

**21398P** \$19.25  
This book explains CMOS technology and its application to 'real world' circuitry. A mini-catalogue is included, which lists over 100 devices, giving their pinouts and application notes.

## IC TIMER COOKBOOK

**21416P** \$15.95  
Gives you a look at the hundreds of ways IC timers are used in electronic instrumentation.

## IC CONVERTER COOKBOOK

**21527P** \$20.75  
Written for the practising engineer, technician, hobbyist or student, this book will be an invaluable working guide to the understanding and use of IC analogue/digital and digital/analogue converters.

## DESIGN OF OP-AMP CIRCUITS, WITH EXPERIMENTS

**21537P** \$16.50  
The design of the fundamental circuits that are the basic building blocks of more sophisticated systems. A series of 35 experiments illustrates the design and operation of linear amps, differentiators and integrators, voltage and current converters, active filters, and lots more.

## 555 TIMER APPLICATIONS SOURCE BOOK, WITH EXPERIMENTS

**21538P** \$11.25  
This book describes the construction of the 555 timer and gives numerous practical examples of its applications in all areas of electrical and computer engineering, including 17 simple experiments.

## DESIGN OF ACTIVE FILTERS WITH EXPERIMENTS

**21539P** \$15.95  
Introduction to the theory, implementation and design of active filters using the 741 op-amp.

## DESIGN OF PHASE-LOCKED LOOP CIRCUITS, WITH EXPERIMENTS

**21545P** \$15.95  
An excellent introduction to the theory, design and implementation of phase-locked loop circuits using various TTL and CMOS devices. Includes manufacturers' data sheets and describes the use of breadboarding aids in the wide range of laboratory-type experiments.

## AUDIO IC OP-AMP APPLICATIONS

**21558P** \$13.25  
This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including small spatial needs, low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

## UNDERSTANDING CMOS INTEGRATED CIRCUITS

**21598P** \$9.95  
This book tells you what CMOS ICs are, how they work, and how they can be used in electronic circuit designs. Many practical circuits, complete with parts values, are included.

## DESIGN OF TRANSISTOR CIRCUITS WITH EXPERIMENTS

**21626P** \$20.75  
A self-teaching course to provide the background and explanations necessary to teach the reader the art of designing transistor circuits.

## GUIDE TO CMOS BASICS, CIRCUITS, AND EXPERIMENTS

**21654P** \$14.95  
If you are already familiar with TTL devices and are ready to examine the benefits of CMOS, this book is your complete source. It tells you what CMOS devices are, their characteristics and design rules. 22 experiments demonstrate the concepts discussed.

## PRACTICAL TRANSFORMER DESIGN HANDBOOK

**21657P** \$35.50  
An easy to understand, illustration-filled guide to designing and constructing transformers. Reviews the fundamentals of electricity, magnetism and algebra needed to understand transformer theory, and covers general design considerations, transformer types, power losses and transformer use in converters and inverters.

## Z80 MICROCOMPUTER DESIGN PROJECTS

**21682P** \$20.75  
This book provides a complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

## DESIGN OF VMOS CIRCUITS, WITH EXPERIMENTS

**21686P** \$17.50  
The authors look at the technology which makes dramatic advancements possible with VMOS, and show how these components can easily and effectively be integrated into common circuit designs to enhance their responses.

## IC OP-AMP COOKBOOK

**21695P** \$23.75  
Basic op-amp theory in detail, with 200 practical, illustrated circuit applications: JFET and MOSFET units are featured, plus manufacturers' data sheets and company addresses.

## EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

**21785P** \$13.25  
Artificial intelligence is the capability of a device to perform functions normally associated with human intelligence. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct interesting and exciting experiments in artificial intelligence.

## PRACTICAL SOLID-STATE CIRCUIT DESIGN

**21787P** \$14.95  
An introductory course in practical solid-state circuit design for the experimenter, designer or technician who is interested in constructing tailor-made circuits.

## SCRS AND RELATED THYRISTOR DEVICES

**21806P** \$19.25  
Written for experimenters, technicians and engineers, this book is a practical and comprehensive guide to theory, operation, specifications and applications of silicon-controlled rectifiers (SCRs) and related thyristor devices.

## REGULATED POWER SUPPLIES

**21808P** \$29.75  
Comprehensive discussion of the internal architecture and operation of the latest solid-state regulators. Explains when regulated supplies are needed and how to incorporate them in your projects, and discusses modern circuitry including linear and switching circuits and late ICs.

## ANALOG INSTRUMENTATION FUNDAMENTALS

**21835P** \$29.75  
Numerous practical, hands-on lab experiments and solved problems are included, plus discussions of movements, dc ammeters, voltmeters, ohmmeters, bridges, filters and attenuators. No calculus is required.

## RF CIRCUIT DESIGN

**21868P** \$33.95  
A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

## SOLAR CELLS

**22270P** \$37.95  
In-depth description of the basic operating principles and design of solar cells. It also covers the techniques currently used to produce solar cells and reviews system applications.

## ELECTRONIC DESIGN WITH OFF-THE-SHELF ICs

**50274P** \$14.70  
It contains virtually all the information you need to design and build electronic circuits, systems and subsystems with readily available ICs. Shows how to interface them into highly complex systems.

## MODERN FILTER DESIGN

**94663P** \$49.95  
This book details the advances in active RC filters, both from a practical standpoint and from a state-of-the-art point of view. It is the first book that gives detailed analysis and design procedures for switched capacitor filters.

## COIL DESIGN AND CONSTRUCTION MANUAL

**160B** \$6.56  
How to make RF, IF, audio and power coils, chokes and transformers. Maths is simplified.

## 50 PROJECTS USING CA3130 ICs

**223B** \$4.32  
The CA3130 is an advanced operational amplifier capable of higher performance than many others: circuits often need fewer ancillary components. Audio projects, RF projects. Test equipment. Household projects. Misc. projects.

## PRACTICAL INTRO TO DIGITAL ICs

**225B** \$4.32  
Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

## 50 CIRCUITS USING GERMANIUM, SILICON AND ZENER DIODES

**BP36** \$3.36  
50 interesting and useful circuits and applications using the germanium and silicon signal diodes, silicon rectifier diodes and zener diodes etc.

**50 PROJECTS USING RELAYS, SCRS AND TRIACS**  
**BP37 \$5.92**  
 Practical working circuits using silicon controlled rectifiers, relays and bi-directional triodes. With a minimum of difficulty you can use them in motor control, dimming and heating control, timing and light sensitive circuits, warning devices and many others.

**50 FET PROJECTS**  
**BP39 \$5.92**  
 Projects include amplifiers and converters, test equipment, tuners, receivers and receiver aids, mixers and tone controls etc etc. The FET used is not critical. This book is of interest and value to SW listeners, radio amateurs, hi-fi enthusiasts and general experimenters.

**50 SIMPLE LED CIRCUITS**  
**BP42 \$3.36**  
 50 interesting and useful circuits and applications using the LED. Also includes circuits for the 707 Common Anode Display for the beginner and advanced enthusiast.

**IC555 PROJECTS**  
**BP44 \$6.56**  
 One wonders how life went on before the 555! Included are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus section on subsequent 556, 558 and 559s.

**PROJECTS IN OPTO-ELECTRONICS**  
**BP45 \$5.92**  
 Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and detectors, modulated light transmission and also photographic projects etc.

**RADIO CIRCUITS USING ICs**  
**BP46 \$4.64**  
 This book describes ICs and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. Also discussed are stereo decoder circuits, quadrophonic circuits and voltage regulator devices.

**LM 3900 IC PROJECTS**  
**BP50 \$4.64**  
 Unlike conventional op-amps, the LM 3900 can be used for all the usual applications as well as many new ones. It's one of the most versatile, freely obtainable and inexpensive devices around. This book provides the groundwork for simple and advanced uses — it's much more than a collection of projects. Very thoroughly recommended.

**50 CIRCUITS USING 7400 SERIES ICs**  
**BP58 \$5.12**  
 50 interesting and useful circuits and applications using these inexpensive and versatile devices.

**50 CMOS IC PROJECTS**  
**224B \$4.64**  
 Projects include multivibrators, amplifiers and oscillators, trigger devices and other special devices.

**SECOND BOOK OF CMOS IC PROJECTS**  
**BP59 \$5.12**  
 Leading on from book number 224 '50 CMOS IC PROJECTS', this second book provides a further selection of useful circuits mainly of a fairly simple nature. Contents have been selected to ensure minimum overlap between the two books.

**COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS**  
**BP67 \$5.92**  
 Well-known author F.G. Rayer features applications and projects using various types of numerical displays, popular counter and driver ICs, etc.

**VMOS PROJECTS**  
**BP83 \$6.56**  
 Though primarily concerned with VMOS power FETs and their applications, power MOSFETs are dealt with too, in a chapter on audio circuits. Projects include audio circuits, sound generator circuits, dc control circuits and signal circuits.

**DIGITAL IC PROJECTS**  
**BP84 \$6.56**  
 Helps the reader to develop a knowledge of the workings of digital circuits. Board layouts and wiring diagrams are included.

**HOW TO USE OP-AMPS**  
**BP88 \$7.52**  
 Design notes and applications on many topics including basic theory, amplifiers, power supplies, audio circuits, oscillators, filters, computers and control engineering. It's written around the 741 IC but includes design notes for most of the common op-amps.

**ELECTRONIC TIMER PROJECTS**  
**BP93 \$6.56**  
 These may have a high degree of accuracy with quartz control or they may be quite simple designs, using only a few components. A number of specialist timer projects are car windscreen wiper delay unit, darkroom timer, metronome etc.

**ETI CIRCUITS BOOKS 1/2/3 \$2.95 ea**  
 Many of these circuits have been published in the 'Ideas for Experimenters' section in ETI.

**ETI CIRCUIT TECHNIQUES VOLS 1/2 \$4.75 ea**  
 The how, what, which, where, why and how much anthology of electronic components, circuits and techniques.

## test equipment and fault finding

### AUTOMOTIVE TUNE-UP AND EMISSION CONTROL SERVICE

**21712P \$20.75**  
 Car owners who wish to save money and maintain their cars at peak performance will learn from this book how to adjust, repair and maintain the systems that ensure best operation.

### TROUBLESHOOTING WITH THE OSCILLOSCOPE

**21738P \$15.95**  
 Excellent for the professional service technician or the serious hobbyist, as it combines step-by-step procedures for using the scope with the specific nuts and bolts of TV receiver troubleshooting.

### EFFECTIVELY USING THE OSCILLOSCOPE

**21794P \$14.95**  
 Excellent for the professional service technician or the serious do-it-yourself, as it combines the correct step-by-step procedures for using a scope with the specific nuts and bolts of TV receiver troubleshooting.

### MICROCOMPUTER DESIGN AND TROUBLESHOOTING

**21819P \$26.75**  
 Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. The author also provides a complete description of two popular microprocessors — the 8085 and the 6502.

### USE OF THE DUAL-TRACE OSCILLOSCOPE

**40023P \$23.75**  
 This programmed text breaks down the process of operating a scope into a series of logical steps starting with the deflection of the electron beam and continuing through proper use of the triggering controls to measure the phase difference between two waveforms.

### ELECTRONIC TROUBLESHOOTING HANDBOOK

**52585P \$10.50**  
 This workbench guide shows you how to pinpoint transistor troubles in minutes, how to test almost everything electronic and how to get the most out of low cost test equipment.

### PRACTICAL REPAIR AND RENOVATION OF COLOUR TVs

**BP34 \$4.32**  
 This book shows how to obtain a working colour TV for very little outlay by repairing and renovating a set that has been 'written off' by a dealer. Includes practical details of how to construct your own CRT tester/rejuvenator and cross hatch generator.

### HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE

**BP57 \$5.12**  
 The oscilloscope is divided into various sections which can be individually constructed and tested and then assembled together to complete the whole instrument. Also tells you how to use the instrument.

### TRANSISTOR RADIO FAULT-FINDING CHART

**BP70 \$1.92**  
 Used properly, this chart should enable the reader to trace most common faults quickly. Across the top of the chart are four rectangles containing brief descriptions of the faults. Selecting the appropriate fault, the reader simply follows the arrows and carries out the suggested checks in sequence until the fault is cleared.

### ELECTRONIC TEST EQUIPMENT CONSTRUCTION

**BP75 \$5.92**  
 Describes construction of wide range of test gear including FET amplified voltmeter, resistance bridge, field strength indicator, heterodyne frequency meter etc.

### POWER SUPPLY PROJECTS

**BP76 \$5.92**  
 Includes simple unregulated types, fixed voltage regulator types and variable voltage stabilised designs. The designs are all low voltage types for semiconductor circuits.

### HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

**BP110 \$6.56**  
 Helps you to overcome the problems of a circuit that doesn't work by indicating how and where to start looking for many of the common faults that can occur when building up a project.

### TEST GEAR — METERING AND POWER SUPPLY PROJECTS

**\$3.00**  
 Includes many types of meters, audio noise and signal generators, simple CMOS tester, oscilloscope calibrator etc.

### TEST GEAR — VOL. 2

**\$3.95**  
 Projects include audio oscillator, transistor tester, true RMS voltmeter, RF signal generator, versatile logic test probe, microwave oven leak detector etc.

### ELECTRONIC PROJECTS FOR YOUNG SCIENTISTS

**\$3.95**  
 PH meter, geiger counter, helium-neon laser, sound level meter, solar cells, negative ion generator and much more.

## electronic music/audio/video

### AUDIO CYCLOPEDIA

**20675P \$66.00**  
 A complete in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. Over 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

### ELECTRONIC MUSIC CIRCUITS

**21833P \$24.95**  
 How to build a custom electronic music synthesiser, outlines numerous other circuit designs and then shows you how to modify them to achieve particular responses. Many of the circuits can be used as special-effects boxes for guitars and other musical instruments.

### INTRODUCTION TO ELECTRO-ACOUSTIC MUSIC

**81515P \$15.95**  
 This book assumes no previous technical knowledge. It discusses the relationship between the technology and the composition of electro-acoustic music.

### MODERN RECORDING TECHNIQUES

**21037P \$19.25**  
 Explains the equipment controls and techniques found in a modern recording studio and how to use them creatively and correctly to produce a desired result. Numerous photographs, diagrams and charts.

### SOUND SYSTEM ENGINEERING

**21156P \$32.50**  
 Dealing with audio systems as a whole, it includes installing and equalising the sound system and interfacing the electrical and acoustic systems. Instrumentation, the acoustic environment and designing for acoustic gain are covered.

### TUBE SUBSTITUTION HANDBOOK

**21746P \$8.75**  
 Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

### HOW TO BUILD SPEAKER ENCLOSURES

**20520P \$8.75**  
 A practical guide to the 'whys' and 'hows' of constructing high-quality top-performance loudspeaker enclosures.

### ACTIVE-FILTER COOKBOOK

**21168P \$21.95**  
 Learn how to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

### DESIGN OF ACTIVE FILTERS WITH EXPERIMENTS

**21539P \$15.95**  
 Introduction to the theory, implementation and design of active filters using the 741 op-amp.

### AUDIO IC OP-AMP APPLICATIONS

**21558P \$13.25**  
 This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including small spatial needs, low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

### VIDEO TAPE RECORDERS

**21521P \$17.50**  
 In this completely revised second edition, the author tells in simple language how helical VTRs work and how to operate and service them. Includes numerous examples of circuits and mechanical systems.

# OOPS! More books!

mail order coupon on page 58

## CHEAP VIDEO COOKBOOK

**21524P \$11.75**  
Complete discussion of a new, low-cost way to get words, pictures and opcode out of your computer and onto any ordinary TV screen, using a seven-IC easy-to-build circuit which you can build for less than \$20.

## AN INTRODUCTION TO VIDEO

**BP100 \$6.56**  
This book is written in layman's language and is for anyone who is thinking about buying or renting or who has just bought or rented a video recorder and wants to get the best out of the machine.

## MOBILE DISCO HANDBOOK

**BP47 \$4.64**  
Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.

## ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING

**BP51 \$5.92**  
Shows how electronic music can be made at home with the simplest and most inexpensive of equipment. Describes how the sounds are generated and how these may be recorded to build up the final composition.

## PRACTICAL CONSTRUCTION OR PREAMPS, TONE CONTROLS, FILTERS, ATTENUATORS

**BP60 \$4.96**  
This book shows the enthusiast how to construct a variety of magnetic tape recording, microphone and disc pre-amplifiers, and also a number of tone control circuits, rumble and scratch filters, attenuators and pads.

## ELECTRONIC SYNTHESIZER PROJECTS

**BP81 \$5.92**  
For the electronic music enthusiast, an invaluable reference. This book is full of circuits and information on how to build analogue delay lines, sequencers, VCOs, envelope shapers, etc. etc. The author takes a clear and logical approach to the subject that should enable the average enthusiast to understand and build up what appears to be a quite complex instrument.

## AUDIO PROJECTS

**BP90 \$6.56**  
Covers a wide range of audio projects including preamplifiers and mixers, power amplifiers, tone controls and matching etc. A number of board layouts and wiring diagrams are included.

## ELECTRONIC MUSIC PROJECTS

**BP74 \$5.92**  
Provides constructors with practical circuits for the less complex music equipment including fuzz box, waa-waa pedal, sustain unit, reverb and phaser, tremolo generator etc. Text covers guitar effects, general effects, sound generators, accessories.

## SONICS 1982 YEARBOOK

**\$5.35**  
An interview with Kraftwerk, how to cope with recording, lighting, rock acoustics, guitars, equipment reviews and more.

## SONICS MAGAZINE

**\$2.35 ea**  
The Australian music magazine dedicated to the art and craft of sound. Published April, July, October, Yearbook in December. \$15 for one year subscription. Please indicate starting issue.

## computers for beginners

### COBOL FOR BEGINNERS

**39378P \$21.95**  
It is a solid text for introductory programming courses in Cobol, using a format that is easy to understand, yet comprehensive enough to make supplementary readings unnecessary.

### THE PET PERSONAL COMPUTER FOR BEGINNERS

**61827P \$20.95**  
This handy guide is written for use with all varieties of PET computer, from the original 2001 to the new 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

### BIG THINGS FROM LITTLE COMPUTERS

**77859P \$19.25**  
A layperson's guide to personal computing with all the basic information and lots of examples of how personal computers can be used.

### BEGINNER'S GUIDE TO DIGITAL ELECTRONICS

**BP61 \$3.36**  
Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

### BEGINNER'S GUIDE TO MICROPROCESSORS & COMPUTING

**BP66 \$5.92**  
Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

### A MICROPROCESSOR PRIMER

**BP72 \$5.92**  
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

### AN INTRO TO BASIC PROGRAMMING TECHNIQUES

**BP86 \$6.56**  
Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

### BEGINNING BASIC

**39806A \$19.95**  
Intended for beginners with no computing experience, one should be able to intelligently program in BASIC in a short time.

### BEGINNING FORTRAN

**46011A \$19.95**  
Starts with simple elementary examples and proceeds to intermediate level programs. Also includes references, tutorials, flow charts, deck set-ups and matrix algebra.

### UNDERSTANDING COMPUTERS

**39815A \$17.95**  
This book describes how computers work. For people who use small computers, it starts with the most elementary gates and works up to the complete computer. Gives an understanding of languages and how they operate in the computer.

### NAILING JELLY TO A TREE

**39842A \$24.95**  
This guide to software teaches you about machine language, assembly language programming and BASIC. The emphasis is not on learning to write programs but on learning to use the thousands of available programs that have already been written.

### PEANUT BUTTER AND JELLY GUIDE TO COMPUTERS

**39813A \$14.95**  
A simple, easy-to-digest source of information on personal computing for the potential buyer who is less than an expert in the field.

### INTRODUCTION TO WORD PROCESSING

**88076A \$17.95**  
Written for the non-technical reader, this book tells about the concepts common to all word processing systems, then analyses all features in detail.

### YOUR FIRST COMPUTER

**88045A \$12.50**  
An easy-to-understand beginner's book to small computers. Understanding them, buying them and using them for personal and business applications.

### FROM CHIPS TO SYSTEMS: AN INTRODUCTION TO MICROPROCESSORS

**88063A \$19.95**  
Explains exactly what a microcomputer system is and how it works. Introduces fundamental concepts and covers all aspects of microprocessors and related components: internal operation, memories, interfacing and system development etc.

### COMPUTERS FOR EVERYBODY

**39849A \$8.95**  
In this easy-to-understand book it is explained how a computer can be used at home, in the office or at school. Includes a consumer's guide to computer equipment that will help the reader decide what to buy and who to buy it from.

## computers hardware & techniques

### USING THE 6800 MICROPROCESSOR

**21512P \$13.25**  
This will guide the reader through the conception, configuration, writing and running of a variety of programs that demonstrate practical use of a 6800 system.

### Z80 MICROCOMPUTER DESIGN PROJECTS

**21682P \$20.75**  
This book provides a complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

### MICROPROCESSOR CIRCUITS VOL. 1

**21877P \$14.75**  
Presents basic microprocessor concepts in simple language for beginners and teaches you to construct a useful microcontroller system. Offers 30 demo circuits which take you through assembly, operation and programming of a microcontroller.

### INTERFACE PROJECTS FOR THE APPLE II

**69387P \$15.95**  
A series of interface projects that are easily built and enable the user to realise the computer's potential through project construction. Projects are primarily hardware-orientated, with some software supporting the hardware.

### PET INTERFACING

**21795P \$25.25**  
Demonstrates how to build numerous interfacing devices for PET hardware. BASIC language programs are used throughout, and the book includes a discussion of the microprocessor's internal architecture and general hardware/software interfacing.

### 6809 MICROCOMPUTER PROGRAMMING AND INTERFACING, WITH EXPERIMENTS

**21798P \$21.95**  
Gives a solid understanding of how to program and interface the high-performance 6809 microprocessor. The author completely explores internal structure, addressing modes, data movement instructions, registers, arithmetic logic and test instructions for the 6809.

### Z80 MICROCOMPUTER HANDBOOK

**21500P \$17.50**  
This thorough handbook covers hardware, software and microcomputers built around the Z80.

### THE \$100 AND OTHER MICRO BUSES

**21810P \$13.25**  
The key to successful computer expansion is a complete understanding of the bus system, through which the computer communicates with peripherals. This book will give you that understanding.

### MICROCOMPUTER DESIGN AND TROUBLESHOOTING

**21819P \$26.75**  
Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. The author also provides a complete description of two popular microprocessors—the 8085 and the 6502.

### DON LANCASTER'S MICRO COOKBOOK, VOLUME 1

**21828P \$20.75**  
This 'cookbook' starts with the very fundamentals of microprocessors and microcomputers and takes you through number systems, codes, memory, etc, until you can work intelligently with micros.

### DON LANCASTER'S MICRO COOKBOOK, VOLUME 2

**21829P \$20.75**  
Carries on where Volume 1 left off.

### APPLE INTERFACING

**21862P \$15.95**  
Using this book, you will be able to perform useful experiments which will provide a much clearer understanding of the fundamentals of computer interfacing and computer electronics. A better understanding of interactions between hardware and software will enable you to communicate more effectively with your Apple.

### MICROPROCESSOR CIRCUITS VOL. 1

**21877P \$14.75**  
Presents basic microprocessor concepts in straightforward language for beginners. Teaches you to construct a useful microcontroller system through progressive demonstration circuits.

### 8080 MICROCOMPUTER EXPERIMENTS

**39808A \$29.50**  
This 'hands on' book includes 105 experiments presenting programs and diagrams as required for clarification.

### A STEP-BY-STEP INTRODUCTION TO 8080 MICROPROCESSOR SYSTEMS

**39804A \$16.95**  
Doesn't require any electronics or computer background. This book describes the 8080 architecture and instruction set through simple examples. Some basic software is introduced.

## DIGITAL CIRCUITS WITH MICROPROCESSOR APPLICATIONS

**46032A** \$39.50  
An introductory text, this book provides readers with the basic ideas and tools needed to analyse and design digital circuits and computer systems. Discusses microprocessor computer organisation, machine language number systems and gate circuits.

## MICROPROCESSOR INTERFACING TECHNIQUES

**88029A** \$24.95  
Teaches you how to interconnect a complete microprocessor system and interface it to the usual peripherals. The hardware and software skills needed to effectively interface peripheral devices are covered along with various buss standards and A/D conversion.

## PRACTICAL INTRO TO DIGITAL ICs

**225B** \$4.32  
Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

## BEGINNER'S GUIDE TO MICROPROCESSORS & COMPUTING

**BP66** \$5.92  
Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

## A MICROPROCESSOR PRIMER

**BP72** \$5.92  
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

## PRACTICAL COMPUTER EXPERIMENTS

**BP78** \$5.92  
How to build typical computer circuits using discrete logic. This book is a useful intro to devices such as adders and storers as well as a general source book of logic circuits.

## THE 6809 COMPANION

**BP102** \$6.56  
It is not a beginners introduction to microprocessors in general but a discussion of the features of the 6809 and a reference work for the 6809 programmer in particular.

## COMPUTERS & COMPUTING YEARBOOK 1980

**BP102** \$4.95  
Includes beginners buying guide, the Apple, Tandy's TRS-80, the Vector MZ, introducing BASIC, \$100 VDU, EPROM programmer, microcomputer power supply and lots more.

## COMPUTERS & COMPUTING YEARBOOK 1982

**BP102** \$4.95  
Includes disks, CP/M and your computer, learners microcomputer, programming in CHIP-8, alphasort, fast plotter, PET talk, the System 80 etc.

## computing software

### CP/M PRIMER

**21791P** \$21.95  
A complete one-stop course on CP/M, the very popular operating system for 8080, 8085 and Z80-based microcomputers. Complete terminology, hardware and software concepts, startup of a CP/M system, and a complete list of CP/M-compatible software.

### THE CP/M HANDBOOK (WITH MP/M)

**88048A** \$19.95  
Contains a step-by-step description of all the CP/M command features. Designed for the beginner, the book progresses to detailed explanations of the file transfer program, the debugging program and CP/M's text editing program.

### HOW TO GET STARTED WITH CP/M

**39832A** \$19.95  
This practical book eases the reader into the essentials of the system, giving an overview of the operating system, an idea of what it will be like to use and what it can do for the reader.

### AUSTRALIAN MICROCOMPUTER HANDBOOK

**72505** NOW \$15.00  
Normally \$25.00. A detailed buyer's guide to microcomputer systems and application packages in commercial, industrial, scientific, educational and home/hobby areas.

### THE C PROGRAMMING LANGUAGE

**10163P** \$21.95  
C is a general purpose 'low-level' programming language. It is not specialised to any particular area of application, but its absence of restrictions make it convenient and effective for many tasks.

## THE 68000: PRINCIPLES AND PROGRAMMING

**21853P** \$19.95  
An easy-to-read, systematic approach to the 68000 advanced 16-bit microprocessor. The book guides you through the complex architecture, instruction set, pinouts and interfacing techniques. Written for design engineers, programmers and students.

## PROGRAMMING IN BASIC FOR PERSONAL COMPUTERS

**30739P** \$14.75  
Simple instructions show how to give BASIC commands and statements a wide range of applications, from programming video games to developing business or scientific programs.

## PROGRAMMABLE CALCULATORS

**46008A** \$24.95  
This book suggests which calculators to buy, their possibilities and limitations, and the how-tos of programming them.

## TAKE A CHANCE WITH YOUR CALCULATOR

**39807A** \$14.95  
An introduction to modern mathematics, this book deals with programming of programmable calculators and includes probability problems.

## AN INTRO TO BASIC PROGRAMMING TECHNIQUES

**BP86** \$6.56  
Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

## BASIC FOR EVERYONE

**61481P** \$19.75  
349 pages of BASIC information for all purposes.

## BEGINNING BASIC

**39806A** \$19.95  
Intended for beginners, this book discusses how a programmer and a basic computer interact with the computer, problems likely to be met by the beginner, the need for and uses of documentation etc.

## FIFTY BASIC EXERCISES

**88056A** \$17.95  
Designed to teach BASIC through actual practice, this book contains graduated exercises in math, business, operations research, games and statistics. The programs were designed to run directly on a TRS-80 and will run with minor or no changes on any system with Microsoft BASIC.

## INSIDE BASIC GAMES

**88055A** \$19.95  
The medium of games teaches readers how to design error-free, interactive BASIC programs. Rules, algorithms and coding differences for the PET, APPLE II and TRS-80 are also included.

## MICROSOFT BASIC

**39823A** \$19.95  
Includes branching and loops, arithmetic in BASIC, strings, editing, arrays and files, the disk and a description of the Radio Shack Level II BASIC.

## INTRODUCTION TO FORTH

**21842P** \$14.95  
The most complete book available on the MMS FORTH version of FORTH, but also a fundamental approach to programming in all versions of FORTH. Many programming examples are provided, with direct comparisons to the Microsoft Level II BASIC version of these programs.

## STARTING FORTH

**42922P** \$23.75  
A clear and complete guide to FORTH, this book covers fundamental principles and then a full set of high-level FORTH commands. It concludes with advanced techniques and style.

## A FORTRAN PRIMER

**80454P** \$6.95  
Assumes no previous knowledge of program writing. It covers the fundamentals of the FORTRAN language, enables extensive program writing and concentrates on programming style.

## INTRODUCTION TO STRUCTURED FORTRAN

**46007A** \$19.95  
Written for the beginner, the text incorporates the new FORTRAN 77 with a discussion of structural programming. Includes a discussion of time-sharing, pseudo language programming and WATFIV statements.

## MICROSOFT FORTRAN

**39846A** \$24.95  
An introductory text on FORTRAN in general and Microsoft FORTRAN in particular. The latter is exceptionally well suited for use on microcomputers using CP/M and others of the 8080/8075/Z-80 family.

## BEGINNING FORTRAN

**46011A** \$19.95  
Introduces readers to FORTRAN. Included are references for further study, brief tutorials on key punching, flow charting, deck set-ups and matrix algebra.

## QWIKTRAN

**39824A** \$19.95  
Quick FORTRAN for Micros, Minis and Main Frames. Starts with the basic concepts of computing and Qwiktran, a fundamental subset of FORTRAN IV. Lots of examples to increase the reader's proficiency.

## THE UCSD PASCAL HANDBOOK

**35536P** \$23.75  
Language descriptions organised in a quick and easy reference are given in this book for readers with no prior experience of Pascal programming.

## INTRODUCTION TO PASCAL

**91522P** \$19.95  
The second edition of this popular book has been updated to conform to the new international standard of Pascal. The contents illustrate the design and construction of Pascal programs, involving a wide range of basic computer algorithms in a practical context.

## PASCAL

**46028A** \$19.95  
For people with little or no programming experience, this book gives lots of examples that clearly explain proper usage of language features. Discusses top-down programming, debugging, self-documentation etc.

## THE PASCAL HANDBOOK

**88053A** \$23.50  
This book summarises the entire Pascal vocabulary, including the variations introduced by different commercial versions of Pascal. All in dictionary format.

## PASCAL PROGRAMS FOR SCIENTISTS AND ENGINEERS

**88058A** \$23.50  
Over 60 of the most frequently used scientific algorithms, along with their program implementation in Pascal, are in this book.

## COBOL FOR BEGINNERS

**39378P** \$21.95  
It is a solid text for introductory programming courses in Cobol, using a format that is easy to understand, yet comprehensive enough to make supplementary readings unnecessary.

## STARSHIP SIMULATION

**39810A** \$11.95  
This book offers both a specific simulation which can be implemented, modified and played, and a complete look at how to put together a simulation on almost any subject.

## BASIC PROGRAMS FOR SCIENTISTS AND ENGINEERS

**88073A** \$19.95  
This book contains scientific and engineering application programs written in BASIC.

## COMPUTER GRAPHICS PRIMER

**21650P** \$21.95  
Almost every page has a colour drawing, photograph, picture or a schematic to help you learn computer graphics quickly and easily. Programming concepts apply to all microcomputers, and examples are given in BASIC for the Apple II.

## INTRODUCTION TO TRS-80 GRAPHICS

**39818A** \$17.95  
It begins with the basic concepts of line drawing and leads the reader on to geometric shapes, moving figure animation and other more advanced topics.

## CIRCUIT DESIGN PROGRAMS FOR THE TRS-80

**21741P** \$21.75  
A number of programs written to aid you in using your TRS-80 and Level II BASIC for the design and analysis of many electronic circuits. The programs analyse information on ms values, periodic waveforms, integrated circuit timers and bipolar transistor circuits.

## MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80 — BOOK 1

**21788P** \$19.25  
28 ready-to-use BASIC programs which have been completely tested and debugged. Programs include a telephone dialler, digital stop-watch, spelling test, house buying guide, gas mileage calculator, and others. Complete with explanations of each program, sample runs, and complete program listing.

## MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80 — BOOK 2

**21865P** \$19.25  
32 ready-to-run BASIC programs, including two to test your ability in history and maths, a Dungeon of Danger that's strictly for fun, eleven household programs, seven on money and investment, two to test your ESP level, and more. Complete with explanations, sample run and listing for each program.

## INTERMEDIATE PROGRAMMING FOR THE TRS-80 MODEL I

**21809P** \$14.95  
Step-by-step instructions for the TRS-80 user who wants to progress from BASIC to machine and assembly language programming with the TRS-80 Model I system. A complete how-to guide with numerous examples.

# ...and for good measure...

## TRS-80 — MORE THAN BASIC

**21813P** \$15.95  
Learn to program in Z80 mnemonics by using the book's error-tolerant interactive monitor program. Over 26 commands available, with total documentation that helps you change the commands to meet specific applications.

## TRS-80 ASSEMBLY LANGUAGE MADE SIMPLE

**21851P** \$19.25  
If you have an understanding of BASIC programming, this book will help you learn to plan, write and hand-assemble your own assembly language programs in memory, using the T-bug and Level II BASIC ROM subroutines.

## PROGRAMMING THE TRS-80 POCKET COMPUTER

**30531P** \$13.25  
This book explains all aspects of problem-solving in BASIC, and covers cassette machine interfacing and how to make the best use of the system's keyboard and display.

## TRS-80 ASSEMBLY LANGUAGE SUBROUTINES

**31188P** \$19.25  
A wide spectrum of applications is discussed in this book, which provides easy-to-use routines that can be used as they stand or modified.

## 32 BASIC PROGRAMS FOR THE TRS-80 COMPUTER

**39827A** \$29.50  
Programs for the TRS-80 Level II or Model III BASIC (with 16K or more user memory).

## APPLE BASIC

**39099P** \$19.25  
This book gives the beginner a thorough introduction to BASIC programming on an Apple computer, and covers all areas of programming, including graphics, games, mathematical programs, and a great deal more.

## CIRCUIT DESIGN PROGRAMS FOR THE APPLE II

**21863P** \$23.75  
A series of ready-to-run Apple II programs ideal for electronics design engineers and others faced with solving problems related to plotting and verification of experimental data. The programs may be used as subroutines in larger programs, and many can be translated to run on other microcomputer systems.

## APPLESOFT LANGUAGE

**21811P** \$13.95  
Written for Apple II micros that use the Microsoft language, this introduction covers each aspect of programming in non-technical language, from elementary concepts to advanced techniques.

## APPLE MACHINE LANGUAGE

**90230P** \$21.95  
This straightforward book teaches machine language programming through BASIC, the transition being made step-by-step. Many sketches of video displays are provided, as well as exercises with answers.

## APPLE PASCAL GAMES

**88074A** \$19.95  
Explore all the essential elements of UCSD Pascal and learn the important Apple Pascal extensions.

## PASCAL PROGRAMMING FOR THE APPLE

**95454P** \$18.95  
This book teaches UCSD Pascal on the Apple II. Many examples, programs for financial applications, graphics, file structures and sound reproduction are supplied.

## 32 BASIC PROGRAMS FOR THE APPLE COMPUTER

**38834A** \$29.50  
Full of programs with practical applications, educational uses, games and graphics.

## PET/CBM BASIC

**61751P** \$19.25  
This book provides a thorough introduction to BASIC programming on a PET computer, explaining programming concepts for graphics, including three-dimensional letters, bar graphs and the use of sound effects in PET programs.

## THE PET PERSONAL COMPUTER FOR BEGINNERS

**61827P** \$20.95  
This handy guide is written for use with all varieties of PET computer, from the original 2001 to the new 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

## PET BASIC 1

**95524P** \$19.25  
For users of the PET computer, this book covers such topics as creative graphics, humour and interesting small programs.

## PET GAMES AND RECREATIONS

**95529P** \$18.85  
Presenting an interesting mixture of diversions guaranteed to entertain and educate. Ideal for beginners, yet also challenging to computer veterans, the book features progressive levels of difficulty and five different types of games.

## 32 BASIC PROGRAMS FOR THE PET COMPUTER

**39825A** \$29.50  
Each chapter fully documents a different bug-free program. If readers have a good working knowledge of BASIC, they can devise and implement their own program changes.

## THE ATARI ASSEMBLER

**90236P** \$19.25  
This practical book gives detailed instructions for using the Atari Assembler cartridge for novices with some knowledge of BASIC programming. Fundamental information programming in assembly language is given.

## ATARI GAMES AND RECREATIONS

**90242P** \$19.25  
Beginners and advanced users can use the preprogrammed games in this book to improve their skill. Charts, flash cards, an error dictionary and graph paper designs are among the features.

## EXPLORE COMPUTING WITH THE TRS-80 (AND COMMON SENSE)

**96137P** \$17.95  
This introduction to microcomputers and the BASIC language is suitable for novices and users of the TRS-80. Among the topics covered are creating tables, arts and graphics, games and simulation.

## 32 BASIC GAMES FOR THE EXIDY SORCERER

**39835A** \$29.50  
Full of programs with practical applications, educational uses, games and graphics. Each chapter documents a different bug-free program.

## THE ART OF PROGRAMMING THE 1K ZX81

**BP109** \$6.56  
This book explains how to use the features of the ZX81 including its random number generator, graphics and timer. PEEK and POKE are explained and you should learn enough to develop programs of your own.

## PROGRAMMING THE 6502

**88046A** \$18.95  
Principles of assembly language programming for the 6502 microprocessor are taught in this introductory text. Includes a discussion of trade-offs between hardware and software and detailed explanations of the 6502's internal registers and bus operation.

## 6502 APPLICATIONS BOOK

**88015A** \$17.95  
Use this book and a few low-cost components to build a complete home alarm system, an electric piano, a motor speed-regulator, a time-of-day clock, a simulated traffic control system and a Morse code generator, etc.

## 6502 GAMES

**88023A** \$17.95  
You learn how to play ten sophisticated games and also learn assembly language programming. Also learn the techniques of algorithm design and data structures.

## 8080 MACHINE LANGUAGE PROGRAMMING FOR BEGINNERS

**39814A** \$12.95  
The book will take the reader step-by-step through the most common 8080 op codes and it will do so at a level anyone can understand.

## PROGRAMMING THE Z80

**88047A** \$19.95  
This book will enable every reader to write complete application programs for Z80-based computer systems. Includes exercises to measure progress and comprehension at each level of programming.

## PROGRAMMING THE Z8000

**88072A** \$19.95  
A complete introduction to programming concepts and techniques for use with the 16-bit, Z8000 microprocessor. Presents detailed descriptions of the architecture and functions of this 'super chip'.

## START WITH BASIC ON THE COMMODORE VIC 20

**97070P** \$14.75  
Helpful exercises and step-by-step instructions show you how to program in BASIC utilising all the graphic functions on the Vic 20.

## computing for business

### BASIC FOR ACCOUNTANTS

**80098P** \$9.95  
Shows accountancy students and accountants how to use a computer to perform the repetitive tasks associated with record keeping, calculating and report writing. Using the BASIC language attention is concentrated on debtors, inventory and general ledger systems.

### COMPUTER BASED BUSINESS SYSTEMS

**80192P** \$10.95  
A short introduction to the sorts of systems used by a typical business to handle its typical activities. The book aims at providing a general understanding and therefore avoids technological detail.

### THE COMPUTER SOLUTION

**80195P** \$13.50  
It should be of interest to business people contemplating, implementing or already using computer data processing or to any non-technical person curious to know why and how computers are used in Australian businesses and organisations.

### SMALL BUSINESS COMPUTERS: A GUIDE TO EVALUATION AND SELECTION

**81134P** \$14.95  
Ideal for the inexperienced user, this text emphasises management considerations in determining the feasibility, economics, evaluation, selection, contracts and practicality of installing a computer.

### SMALL BUSINESS COMPUTER SYSTEMS

**81136P** \$14.95  
This book provides a bridge between the accountant and the DP professional by explaining every step of the trading and reporting process in DP terms. It is especially useful to people engaged in the specification process or in auditing DP accounting systems.

### THE VISICALC BOOK — APPLE EDITION

**98397P** \$22.25  
If you are using Visicalc on your Apple II and want to learn more about its expanded uses then this book will show you how to build a model, enter your data and solve problems about profit/loss projections, pricing/costing estimates etc.

### THE CP/M HANDBOOK (WITH MP/M)

**88048A** \$19.95  
Containing a step-by-step description of all the CP/M command features, the book progresses to detailed explanations of the file transfer program, the debugging program and CP/M's text editing program.

### YOUR FIRST COMPUTER

**88045A** \$12.50  
A beginner's guide to small computers, understanding them, buying them and using them for personal and business applications. Includes peripherals, languages and application packages.

### DON'T (OR HOW TO CARE FOR YOUR COMPUTER)

**88065A** \$16.95  
A guide to computer and peripheral preservation. Specific advice for the computer, floppy disks, hard disks, the CRT terminal, the printer, tape units, the computer room, software and documentation are included.

### INTRODUCTION TO WORD PROCESSING

**88076A** \$17.95  
Written for the non-technical reader, this book tells about concepts common to all word processing systems, then analyses all features in detail, from screens to scrolling and formatting.

### SMALL COMPUTERS FOR THE SMALL BUSINESSMAN

**39831A** \$24.95  
The book tells readers how and where to shop for a computer successfully; what to expect their computer to do for them; how to select software; whether or not to use a consultant; how to introduce the computer to the staff and how much computer is necessary.

### INVENTORY MANAGEMENT FOR SMALL COMPUTERS

**39848A** \$24.95  
Owners of retail businesses and their employees need this book. The program provides an inventory control system so that you know what stock is on hand, where it is located, what price was paid for it and the selling price.

### BASIC FOR BUSINESS FOR THE TRS-80

**90352P** \$22.25  
This book covers the application of BASIC language to business uses on the TRS-80 models II and III.

### FROM THE COUNTER TO THE BOTTOM LINE

**39811A** \$24.95  
A demystifying guide to basic accounting needs and computer use. Includes inventory and purchasing, billing, accounts receivable, accounts payable and general ledger.

## amateur radio, DX, communications

### INTRODUCTION TO RADIO ASTRONOMY

**21246P** \$8.75  
It gives background information on the structure of the universe, classification of galaxies and radio-wave propagation. It covers in detail reception of extraterrestrial radio signals and their sources and the types of antennas. It also explains how to construct several practical, low-cost radio telescopes.

### TUBE SUBSTITUTION HANDBOOK

**21746P** \$8.75  
Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

### RF CIRCUIT DESIGN

**21868P** \$33.95  
A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

### COMPUTERS AND THE RADIO AMATEUR

**66306P** \$28.00  
For the radio operator who wants to know how computers function and how they can be used with other equipment.

### SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS

**222B** \$4.32  
Design and construction of several solid-state shortwave receivers giving high level of performance yet utilising relatively few inexpensive components. See also 226.

### HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS

**BP2** \$2.25  
Equivalents book for amateurs and servicemen. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.

### RADIO CIRCUITS USING ICs

**BP46** \$4.64  
Describes how ICs can be employed in receivers for the reception of either amplitude or frequency modulated signals. Stereo decoder circuits and the devices available at present for quadrophonic circuits are discussed.

### LONG DISTANCE TV RECEPTION (TV-DX)

**BP52** \$6.56  
Written by UK authority, the book includes many units and devices made by active enthusiasts. A practical and authoritative intro to this unusual aspect of electronics.

### RADIO STATIONS GUIDE

**BP55** \$5.92  
This is an aid for all those who have a radio receiver. Shows the station site, country, frequency and/or wavelength, as well as Effective Radiation Power of the transmitter and in some cases, the station's call sign as well.

### AN INTRODUCTION TO RADIO DXING

**BP91** \$6.56  
One section is devoted to amateur band reception and the other section covers broadcast band reception, with advice on suitable equipment and the techniques employed when using that equipment. The construction of a number of useful accessories is described.

### AERIAL PROJECTS

**BP105** \$6.56  
Practical aerial designs including active, loop and ferrite which are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

## general

### AUTOMOTIVE TUNE-UP AND EMISSION CONTROL SERVICE

**21712P** \$20.75  
Car owners who wish to save money and maintain their cars at peak performance will learn from this book how to adjust, repair and maintain the systems that ensure best operation.

### INTRODUCTION TO AUTOMOTIVE SOLID-STATE ELECTRONICS

**21825P** \$14.95  
For the professional as well as the home mechanic — explains the functions of most on-board automotive black boxes and logic systems, including anti-skid braking, electronic spark control, diagnostic systems and trip computers.

### SECURITY ELECTRONICS

**21419P** \$11.25  
The principles of operation of the electronic devices used in the various types of security systems are described. Intrusion detection and alarms, object detectors, bugging and debugging devices, computer protection, as well as the planning of systems.

### ELECTRONIC SECURITY DEVICES

**BP56** \$5.92  
Besides including both simple and more sophisticated burglar alarm circuits using light, infrared and ultra-sonics, this book also gives circuits for gas and smoke detectors, flood alarms, fire alarms, doorphones, baby alarms, etc.

### EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

**21785P** \$13.25  
Artificial intelligence is the capability of a device to perform functions normally associated with human intelligence. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct interesting and exciting experiments in artificial intelligence.

### TELEMATIC SOCIETY

**02460P** \$17.50  
An extensive update of 'The Wired Society', this book demonstrates how developments in telecommunications will affect the way we live.

### ELECTRONIC CALCULATOR USERS' HANDBOOK

**BP33** \$5.12  
Presents formulae, data, methods of calculation, conversion factors, etc. for use with the simplest or most sophisticated calculators. Includes the way to calculate using only a simple four-function calculator: trigonometric functions; hyperbolic functions; logarithms; square roots and powers.

### YOUR ELECTRONIC CALCULATOR AND YOUR MONEY

**BP54** \$4.64  
Starts with a basic revision of percentages and decimals, then deals with mortgages, cars, insurance, fuel, shopping, tax etc. There's a section on investment and the last section deals with the calculator in a small business.

## ORDER FORM

Send to ETI Book Sales, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011.  
Allow 4-5 weeks for delivery. Post & Handling \$1 per book. Effective until April 30, 1983.

Please supply:

BOOK TITLE	BOOK NO.	QTY	TOTAL PRICE
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....
.....	.....	.....	.....

Post and handling .....

I enclose TOTAL \$ .....

Name: .....

Please debit my ☐ Bankcard


Expiry Date .....

Address: .....

☐ American Express Card

Number .....

Postcode ..... Signature .....

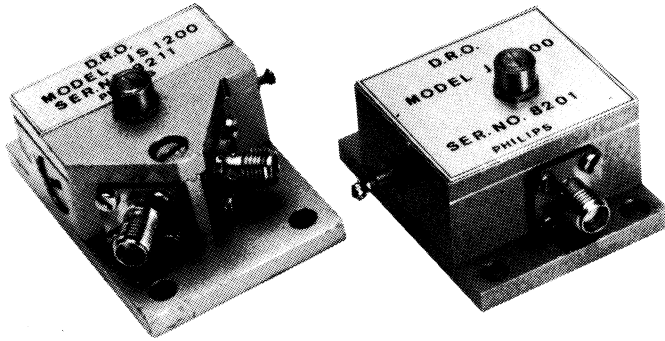

## Low-cost stable microwave oscillators

The Philips JS1200 series of low-cost microwave oscillators feature a claimed stability of better than  $-4 \times 10^{-6}/K$ .

The oscillators have a size of only 34 x 48 x 44 mm, and are suitable for telecommunications systems, radar beacons, ECM receivers and weather radar.

A Gunn diode is used as the active element in these dielectric resonator-stabilised oscillators (DROs). The high stability, small size and low FM noise (quoted as typically 0.15 Hz in a 1 Hz band at 100 kHz off the carrier) are obtained by using a small, high-Q ceramic resonator as the frequency determining element.

The JS1200 series consists of oscillators with centre frequencies of 9 to 12 GHz; each oscillator can be tuned up to 5% from its centre frequency. The nominal output power is 30 mW and other output powers are available on request.

Versions of the oscillators with two outputs are also available for use with transmitters/receivers needing a common frequency source.

For further information contact **Elcoma, 67 Mars Road, Lane Cove NSW 2066. (02)427-0888.**

## Hideaway transceiver suits non-CBers

**Tandy Electronics has released a new kind of 'emergency' CB radio to suit people who don't like CB radios!**

The Realistic TRC-411 is a 40-channel transceiver that needs no installation so there are no holes to be drilled in your car's bodywork.

The unit fits in a small carrying case which stores in the glove box or under the seat until required for a breakdown or other emergency.

The unit employs a telescopic magnet-base antenna which attaches to the bonnet or roof of the car and has a power cord which plugs directly into the car's cigarette lighter socket.

A single switch is used to place the user on the CB emergency frequency, which is monitored 24 hours a day in most areas by volunteer radio operators belonging to organisations such as CREST who give assistance to motorists.

The monitors can obtain breakdown service from the motoring organisations or fetch the emergency services if you report an accident.

The Tandy emergency radio can also function as a regular



40-channel CB, and be used to talk to other CB-equipped motorists near you.

More than just a practical piece of safety equipment, the Realistic TRC-411 is also ideal for people who wish to have CB communications in a rented or company vehicle, Tandy say. The unit retails for \$149.95.

For information, contact David Harvey at **Tandy, P.O. Box 229, Rydalmere NSW 2116. (02) 638-6633.**

## Phase 3B Oscar close to launch

**Launch of the Phase 3B Oscar satellite looks better and better for April this year, according to overseas' sources.**

A firm launch date had not been finalised as we went to press (mid-January) but the launch is mooted to take place in the latter half of the month, probably after the 20th.

The Phase 3B Oscar will be launched from a European Space Agency Ariane L-6 booster, initially going into a 'parking'

orbit from where it will be 'kicked' into its final, highly elliptical, orbit by an on-board apogee kick motor.

The highly elliptical orbit is expected to provide inter-continental communications via the VHF and UHF translators to be carried by the satellite.


## New VHF FM marine radiotelephone

**GFS Electronic Imports, the Australian distributors for Standard Communications of Japan, have announced the release of a new VHF Marine Radiotelephone.**

Known as the Standard Model C-855A, it is a 55-channel marine transceiver designed to operate on the international VHF FM Seaphone band.

With OTC's Seaphone service a boat operator is able to obtain weather forecasts, talk with any telephone in Australia, communicate with other boats or just, keep in touch with a shore base.

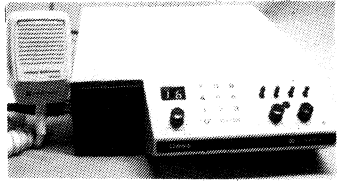The transceiver incorporates keyboard entry of the channels with automatic scanning for up to 10 channels. High priority is given to the emergency channel (Ch. 16) by incorporating a 'dual-watch' facility. Transmitter power output is 25 watts.



The standard C-855A is approved for operation in Australian waters by the department of Communications. Priced at \$689 it is claimed to offer small boat owners an economical alternative to other \$1000-plus FM and SSB radiotelephones.

For further details contact **GFS Electronic Imports, 15 McKeown Road, Mitcham Vic. 3132. (03)873-3939.**

## Largest solar flare in 10 years

**The largest solar flare recorded in the past 10 years occurred on December 14 last, bringing a magnetic storm and disrupting communications here on earth the following day.**

The flare was given an 'X-12' rating by solar-terrestrial scientists in Boulder, Colorado.

The virtual explosion on the Sun's surface released atomic particles and vast amounts of energy into space — more energy

than the Earth uses in an entire year.

'X' is the largest of the three 'classes' of solar flares and a flare of this magnitude has not been noted since the last sunspot peak decline in the early '70s.

## Scanner whips

**Do you 'follow the action' with a portable scanner?**


**To pull in those signals from near and far, you need a Benelec mini flexible scanner whip.**

Benelec's mini flexible scanner whip is 205 mm long and comes in four base styles to suit most applications. The 2-112 has

a push-on sleeve fitting, the 2-113 has a male BNC base, the 2-114 has a PL259 base and the 2-115, a lockcrew base.

The whip is shrouded in black plastic, with a plastic cap on the top, to prevent atmospheric deterioration and physical damage from handling.

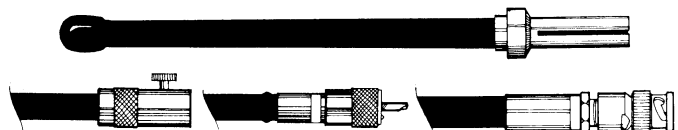Details are available from **Benelec Pty Ltd, P.O. Box 21, Bondi Beach NSW 2026. (02) 665-8211.**



## Power FET device delivers 40 W at 400 MHz

FETs have many advantages over bipolar devices, but RF power FETs have been slow to appear and bandwidths have been limited. A new process looks set to change that.

Many designers of power amplifiers choose to incorporate field-effect transistors instead of bipolar devices because the FETs are easier to use. FETs have a large safe-operating area; their negative temperature coefficient means they are not prone to thermal runaway; and they are voltage-operated instead of current-driven, so they are easier to bias and modulate.

Their limitation has been frequency range — power FETs have not been able to manage more than about 200 MHz.

But a new process developed by Acrian Inc. has pushed the FET bandwidth frontier outward, and the company has come out with what is said to be the first commercially available UHF power FET, the UMIL40FT.

Built with a process called Isofet, the new device is actually two transistors connected in a push-pull configuration.

Acrian claim it delivers 40 W with 20 dB gain, flat within  $\pm 0.5$  dB over the octave from 200 to 400 MHz. Greater bandwidths are achieved at lower power levels: at a 30 W output, the output is flat within  $\pm 1.5$  dB from 20 to 500 MHz, Acrian claim.


Applications for the UMIL40FT include communications systems operating in bands covering 2 to 30 MHz, up to 400 MHz, plus broadband instrumentation etc in the 200 to 500 MHz range.

In high-efficiency AM and FM power amplifier and transmitter applications, the device, operating in class B, will put out 40 W with about 800 mW of drive — a gain of 17 dB.

For low-distortion applications it can be operated in a true class-A amplifier configuration without the need for stabilising networks or feedback circuits. In this set-up, it is capable of delivering a 40 W output with 400 mW of drive, or a gain of 20 dB, Acrian say.

Input coupling is also simple — all that is required is a transformer, instead of the complex matching networks employed in bipolar designs, and biasing is accomplished with a resistor. Priced at US\$105 in small quantities, the UMIL40FT has a maximum power dissipation of 100 W.

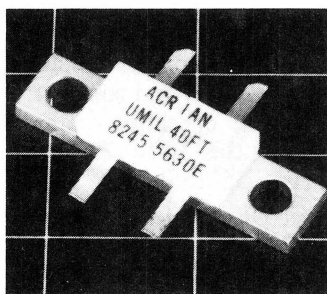Enquiries to Acrian Inc, 10131 Bubb Rd, Cupertino, California 95014 USA.



## New grid parabolas from AEA

Antenna Engineering Australia is currently manufacturing a new range of grid parabolic antennas that they claim are lighter in weight than their previous series, offer superior performance and are very competitively priced.


A feature of these antennas is that they are not just unpresurised, but have void-free feeds for greater reliability.

Models are available for operation in the bands 400-500 MHz, 820-960 MHz, 1427-1535 MHz and 1700-1900 MHz. Antenna sizes are 1.8 m, 2.4 m, 3.0 m, 3.7 m and 4.6 m.

All antennas are rated at 200 km/hr calculated in accordance with Australian Standard AS1170. Higher wind ratings are available. Construction is welded corrosion resistant aluminium of the 6000 series.

The antennas are manufactured in two halves to reduce transportation costs and handling difficulties.

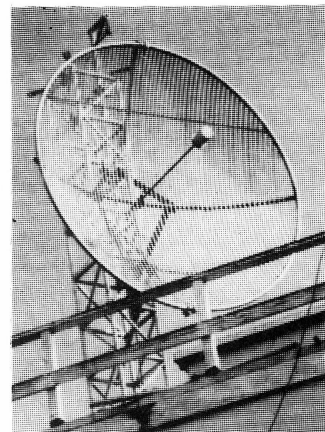AEA has a full parabolic 'GRIDKIT' type parabolic antenna going into production shortly, designed for field assembly.



For further information contact Antenna Engineering Australia Pty Ltd, P.O. Box 191, Croydon Vic. 3136. (03)728-1777.

## Russian ISKRA 3 satellite active

Like the ill-fated ISKRA 2 satellite launched last May (see ETI, July '82, page 67), ISKRA 3 was launched from the orbiting Solyut 7 space station by pushing it through the airlock.

The launch took place on 18 November last year. Approximate orbital parameters are:

period — 92 minutes, inclination —  $52^\circ$ , apogee — 365 km, perigee — 350 km.

The callsign on its 29.583 MHz beacon is RK-03. ISKRA 3 carries a 15m-to-10m transponder, as did ISKRA 2. Life expectancy of this new satellite is believed to be between two and three months in orbit.

## JIL SX-200 A BETTER SCANNING MONITOR RECEIVER.

COVERS 26-88 MHz & 108-180 MHz & 380-514 MHz



Monitors over 33,000 frequencies from 26 to 88 MHz, 108 to 180 MHz and 380 to 514 MHz. Bands included within this range are HF and UHF CB, 27 and 155 MHz MARINE, Australian LOW BAND, AIRCRAFT band, VHF SATELLITE band, 10 Mx, 6 Mx, 2 Mx and 70CMx AMATEUR BANDS, VHF High BAND as well as UHF two-way band.

Mechanically rugged the SX-200 uses high quality double-side Epoxy-Glass printed circuit boards throughout. Some of its other outstanding features include 3 MODE SQUELCH circuitry which allows the lockout of spurious and carrier only signals, extremely low spurious count, AM and FM detection on all bands, FINE TUNING control for off channel stations, 240 VAC or 12 Volt DC operation, Accurate QUARTZ CLOCK, Squelch operated OUTPUT for switching a tape recorder etc, 16 Memory channels, MEMORY BACKUP, which lasts up to two years, high SENSITIVITY and SIGNAL-TO-NOISE ratio on all bands, CRYSTAL FILTER for excellent SELECTIVITY and easy serviceability due to component layout as well as a 90 day warranty.

Its high quality and performance is testified by the fact that it is in use by a large number of State government and Federal bodies including most state and federal police departments. Contact GFS, the Australian Distributors, or our interstate outlets for full technical specifications. We also market a range of pocket scanning receivers and transceivers. Contact us for full details.

PRICE \$525 INC. S.T. + \$8 P&P; SERVICE MANUAL \$10 + \$1 P&P; SCAN-X BASE ANTENNA \$5/ + \$8 P&P. EXP-32—32 CHANNEL MEMORY EXPANDER KIT \$49 + \$4 P&P. A4-AM AUTO AM KIT FOR AIRBAND \$30 + \$4 P&P.

INTERSTATE DEALERS:

WA: (09) 387 4966; NSW: (02) 211 0531; QLD: (07) 397 0808; SA: (08) 269 4744

**GFS Electronic Imports**

15 McKeon Road, Mitcham, 3132, Vic.  
Telex 38053 GFS Phone: (03) 873 3939

# JAYCAR NUMBER 1 FOR VIDEO

WE HAVE THE BIGGEST RANGE OF VIDEO ACCESSORIES!

Check out our great range of video connector cables! Ideal for video - to - video dubs!

BNC plug - BNC plug 1.5m coax Part No. VC-1 \$6.95  
BNC plug - PL259 1.5m coax Part No. VC-2 \$6.95  
PL259 - PL259 1.5m coax Part No. VC-3 \$4.95  
PL259 - RCA plug (metal) 1.5m of coax Part No. VC-4 \$5.95  
RCA plug - RCA plug (metal) 1.5 metre coax Part No. VC-5 \$4.95  
BNC plug - RCA plug (metal) 1.5 metre coax Part No. VC-6 \$5.95  
Sanyo (6 pin DIN plug) to 2.5 & 3.5 RCA plug Part No. VC-8 \$8.95  
(all coax 75 ohms)

## PLUG ADAPTORS

PA21 PL259 plug to RCA socket \$2.95  
PA22 PL259 plug to BNC socket \$3.95  
PA23 BNC plug to RCA socket \$3.95  
PA24 SO239 socket to BNC plug \$3.95

## TV ACCESSORIES

FL-1 Coax (75 ohms) fly lead Belling Lee coax plug to B/L coax plug 1.8 metres \$2.95  
FL-4 As above but 4.5m long \$4.95  
FL-2 Coax lead 1.8m B/L line plug to B/L socket. \$3.45



## VIDEO SWITCHING BOX



**\$49.50**

Cat. AV6504

## LOW LOSS RF SWITCHING

- Allows inputs for; VCR, Video Disc (etc); Antenna, Cable TV, Video Games and Home Computer.  
**WOW!!!**

## KEEP YOUR PRECIOUS TAPES IN SAFETY

We now stock the Video Cassette tape cases that you see in the video stores. You know, the ones they give you when they hire out the tapes. Take care of your tapes with these quality cases. Each case is precision moulded with a stiff spine. They feature a sleeve on the spine to enable you to insert recording information in an easily seen way.

VHS Cat. AV6592  
BETA Cat. AV6590

\$2.95  
\$2.95

VJ-104-CY

## MORE VIDEO ACCESSORIES

VP-8 8 pin square video connector line plug \$7.95

VS-8 8 pin square video line socket \$7.95


PA-25 5 pin 180 degree dubbing adaptor. Reverse pins for video use \$5.95

VC-15 6 pin DIN plug to 6 pin DIN plug 1.5 metres \$4.95

VC-17 5 pin DIN plug to 5 pin DIN plug (reverse pins for video) The plugs are moulded in red to indicate that it is a video connector, 1.5m \$4.95

VJ.104CY Video camera cable (bulk) 2 x 75 ohm video, 2 x shielded microphone, 6 other carriers. Designed for BETA but perfectly suitable for VHS. Up to 30 metre lengths. \$3.95/metre

VS-8

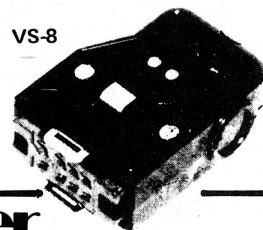

## VIDEO STABILISER

Cat. AV6502

As many of you know, many video tapes, - especially from the USA have the sync pulses suppressed to prevent unauthorised copying of the original dub. This process is fine because it hinders unauthorised re-recording (dubbing) of material. It is annoying though when you hire the original and find that the "Copyguard" is causing problems with your TV. The AV6502 re-inserts the sync pulses automatically and restores stability.

**WARNING!** The AV6502 is intended solely for the use above. Whilst the AV6502 will virtually remove copyguard on a tape copy (and hence restore the picture) it is against the law to unlawfully copy copyright material.

The AV6502 looks almost identical to the AV6500 shown to the right.

**ONLY \$79.95**

## Video Enhancer


NOT A KIT -  
BUILT AND  
TESTED....

**\$89**

Cat. AV6500

Unbelievable but true. This unit enables you to actually IMPROVE a copy of a recorded video tape. How? By amplifying the top end of the video signal by a small amount. This sharpens up the detail of the picture. Dubs can actually look better than the original. Works as a video distribution amplifier as well. Will drive up to 4 VCR's from one VCR input.

**magnificent!**

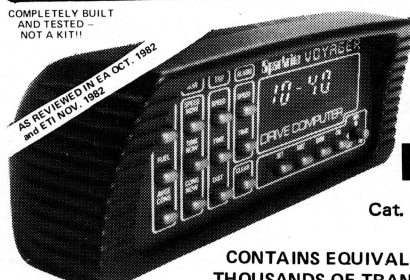

**THE BEST  
CAR  
COMPUTER  
BELOW \$200**

Cat. XC2010

CONTAINS EQUIVALENT OF  
THOUSANDS OF TRANSISTORS  
- USES MASSIVE CUSTOM  
LSI CHIP TO ACHIEVE  
LOW PRICE

## FEATURES

- INSTANT FUEL CONSUMPTION IN LITRES/100KM AND MPG!! (MOST OTHERS HAVE ONLY ONE OF THE ABOVE) JUST SWITCH FROM ONE TO THE OTHER AS YOU DRIVE ALONG.
- INSTANT SPEED, TIME AND OTHER FUEL DATA.
- VISUAL AND AUDIBLE EXCESS SPEED ALARM.

**IDEAL  
RALLY  
COMPUTER!**

Send SAE for more information.

**Jaycar** NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000  
PHONE: 264 6688 TELEX: 72293  
"NEVILLES CORNER"  
Cnr. CARLINGFORD & PENNANT HILLS ROAD,  
CARLINGFORD  
PHONE: 872 4444

MAIL ORDERS TO: BOX K 39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 up (\$8.00)

NEW SHOP HOURS  
Mon Fri 8.30 to 5.30pm  
Sat 8.30 to 12.00pm  
Thurs night to 8.30pm

Mail Order By **BANKCARD**  
Via Your Phone



# THE BEST KIT LINE

YOUR WAGES ARE FROZEN, OURS ARE TOO. SO ARE OUR KIT PRICES – QUALITY FOR NO MORE!

## LOW COST DIGITAL MULTIMETER KIT

BY POPULAR DEMAND

Ref: EA March 1983 (This month)  
Almost everyday we are asked for a multimeter kit. Up until now we thought that it was just not worth it considering the fine low-cost built-up units available. The DP2010 changed all that.  
This kit, fully imported from the UK uses the famous DPM-05 custom LCD/Voltmeter to achieve phenomenal accuracy at very modest cost!  
All parts are included to complete the meter including an attractive and colourful front panel.  
(a 9V battery is required)

Set of test probes to suit \$2.95  
Probe to suit Cat. WT5312 ONLY \$2.50  
Eveready 216 (red) 9V Battery Cat. SB2370 ONLY \$1.40



### SPECIFICATIONS

Function	f.s.d.	Resolution	Accuracy	Protection
Volts (d.c.)	2V	1mV	1%:1 digit	500V for one minute
	20V	10mV	1%:1 digit	
	200V	100mV	1%:1 digit	
	500V	1V	1%:1 digit	
Current (d.c.)	2mA	1uA	1%:1 digit	1A/250V
	20mA	10uA	1%:1 digit	
	200mA	100uA	3%:1 digit	
	2000mA	1mA	5%:1 digit	
Volts (a.c.)	2V	1mV	2%:5 digit	500V for one minute
	20V	10mV	2%:5 digit	
	200V	100mV	2%:5 digit	
	500V	1V	2%:5 digit	
Current (a.c.)	2mA	1uA	2%:5 digit	1A/250V
	20mA	10uA	2%:5 digit	
	200mA	100uA	4%:5 digit	
	2000mA	1mA	7%:5 digit	
Resistance	2K	1	1%:1 digit	260V
	20K	10	1%:1 digit	r.m.s.
	200K	100	1%:1 digit	
	2000K	1K	1%:1 digit	
Diode Test	2V	1mV	1%:1 digit	260V r.m.s.


DP2010 kit Cat. KJ7010  
ONLY \$45

### AC VOLTAGE AND CURRENT RANGES

When S3a selects a.c. functions the output from either the voltage attenuator or current shunts is fed through C1 to remove any d.c. component.

## 500MHz Digital Frequency Period Meter

REF: EA Dec '81 – Feb '82

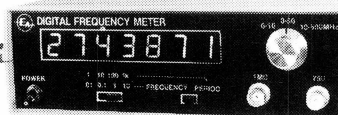


EXCLUSIVE  
Gold plated BNC Input Connectors  
500MHz option only \$26 extra KA1392  
50MHz version \$119 Cat. KA1390  
Tilting bail to suit ONLY \$4.95

Other people may appear to be selling this kit for less. But you GET less!!!  
Exclusive Jaycar features:  
\* Heavy gauge front panel. Pre-punched and silkscreened. (NOT Scotchcal). \* Low aging rate 10.000MHz crystal \* Quality IC sockets provided (A MUST) \* All metal film resistors used (1% 50ppm) \* Thermalloy heatsink for +5V reg.  
Beware of advertised units that do not conform to the original design. They may have inferior performance.

ONLY \$119

## EA dual tracking P/S

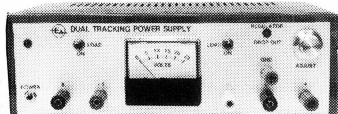

Ref: EA March '82  
Cat. KA1410

\$89.50

Extremely versatile power supply: Will give plus & minus 1.3V to 22V at up to 2 amps PLUS A FIXED +5V@0.9A. The supply is completely protected against short circuits, overloads and thermal runaway. A large meter with voltage calibration is supplied as well as IC sockets. A quality kit.

## STEREO STEREO STEREO STEREO

## Synthesiser

Short Form Version Only  
\$39.50  
Cat. KA1476


Creates a very realistic stereo sound from mono sources i.e. AM tuners, TV or video units  
Very easy to build and comes complete.

Ref: EA September 1982

COMPLETE ONLY


\$49.50

Cat. KA1478

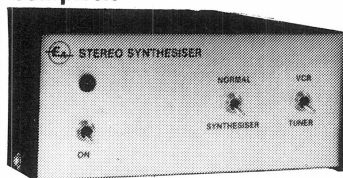

## HEART RATE MONITOR

Ref: EA 7/82

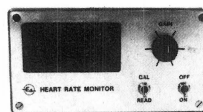

Cat. KA1466

This unit enables you to measure your own pulse instantly and accurately. It is light enough even for joggers to carry. A must for people who may have heart problems.  
Complete kit including LCD Display.

WAS \$79  
SAVE \$10  
NOW \$69

\$69

# UP IN '83-JAYCAR★


CAN AM SOUND LIKE FM? WE THINK SO! ☆ ☆ ☆ ☆ ☆ ☆ ☆

## magnificent! NEW EA Wide-band AM Tuner ☆



AM Tuner alignment kit ref: EA March 83  
This simple project enables you to accurately align your EA wideband tuner.  
Cat. KA1515 \$7.99

Ref: EA Dec-Jan 82-83

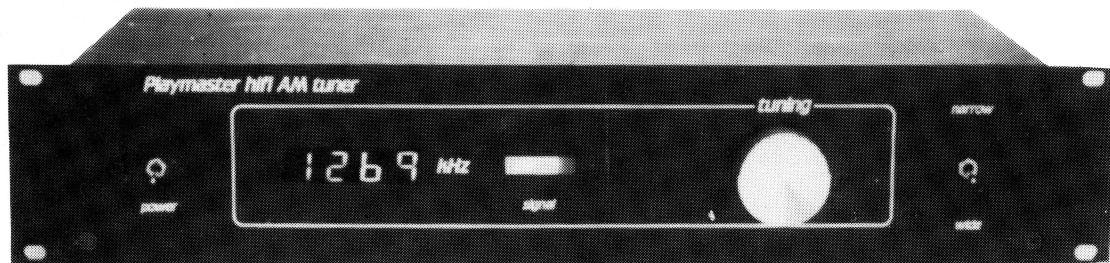

Australia is one of the few countries in the world where wideband AM is transmitted. In fact a good quality AM signal can be much better than its FM counterpart!! Anyone who has suffered from FM multipath distortion will know what we mean. The Playmaster AM tuner is a true broad-bandwidth superhet design. See the frequency response graph in November EA 1982. Once again, the Jaycar kit is a high quality approach. Jaycar supplies an exclusive front panel design that differs from the original EA design. The Jaycar kit provides all components to complete the project INCLUDING a completely pre-punched cabinet.

FANTASTIC VALUE  
AT ONLY

**\$249**


Cat. KA1498

## NEW FUEL CONSUMPTION METER ☆ ☆ ☆

Ref: EA March 1983

Now you have NO EXCUSE to monitor the excesses of your driving habits! At this price your fuel cost savings will pay for the unit very quickly!  
Kit including all electronics and pre-punched case —

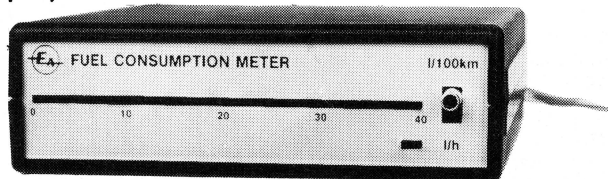Cat. KA1518 \$49.50  
GENUINE MORAY FUEL SENSOR Cat. XC2020 \$69.50  
TAILSHAFT SENSOR TO SUIT Cat. XC2026 \$14.50



## TRANSISTOR ASSISTED IGNITION

Ref: EA January 1983. Latest version of this fantastically popular kit!! The Jaycar kit comes with a genuine DIE CAST box — as used in the EA prototype. Beware of others that use flimsy sheet metal boxes!! Ask us about the OPTO option.

Cat. KA1506



**ONLY \$35**

## NEW EPROM programmer for the MicroBee REF: ET1 2/83


Fantastic little accessory for the popular "MicroBee" computer. The Jaycar kit contains all components including the following SPECIAL features:

- 28 pin IC socket included!
- 3 x 16 pin "PERSONALITY PLUG" HEADERS
- 15 pin PARALLEL CONNECTOR
- IC sockets for all logic devices including personality socket.

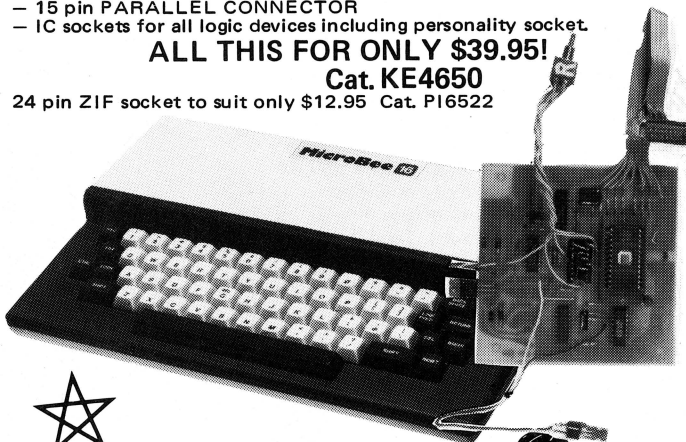**ALL THIS FOR ONLY \$39.95!**

Cat. KE4650

24 pin ZIF socket to suit only \$12.95 Cat. PI6522



## Jaycar NUMBER 1 FOR KITS

125 YORK STREET, SYDNEY 2000  
PHONE: 264 6688 TELEX: 72293  
"NEVILLES CORNER"  
Cnr. CARLINGFORD & PENNANT HILLS ROAD,  
CARLINGFORD  
PHONE: 872 4444

MAIL ORDERS TO: BOX K-39 HAYMARKET, SYDNEY 2000

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 up (\$8.00)


NEW SHOP HOURS  
Mon - Fri 8.30 to 5.30pm  
Sat 8.30 to 12.00pm  
Thurs night to 8.30pm

Mail Order By **BANKCARD**  
Via Your Phone




## Micro Professor

### MPF-I

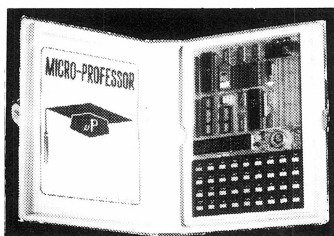

**\$115 + S.T.**

### MPF-II

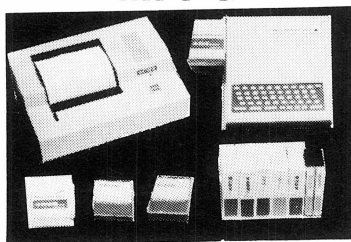

**\$499 + S.T.**

**MPF-II, LOW-COST/HIGH-PERFORMANCE PERSONAL COMPUTER.** R6502 based, 64KRAM, 16KROM, 49 Keyboard, powerful BASIC (APPLESOFT compatible), extended Color and High-Resolution Graphics (280x192 dots), PAL-color TV, B/W monitor, cassette, Remote-control and Printer interfaces and connectors are standard; expansion socket for programme-cartridges, additional peripherals, Disk-Drives.

**OPTIONS:** Green-screen High-Resolution Monitor; Thermal Printer, Fullsize Keyboard; Disk-Drives with controller; RS 232 interface; Programme Cassettes, Cartridges, Disks.

**MPF-I MICROCOMPUTER.** Z-80 based, inexpensive, for learning microprocessors and prototyping, 4KROM, 2KRAM (expandable), cassette interface, expansion / interface sockets.

**OPTIONS:** Thermal Printer; EPROM Programmer; Speech Synthesizer; Sound Generator;




### EMONA COMPUTERS

A division of Emona Enterprises Pty Ltd  
CBC Bank Bldg. 661 George St.  
Haymarket, Sydney. (02) 212 4815

**1** The 1st Australian  
**Personal  
Computer Show**  
Centrepoint Sydney  
10-12 March 1983

**Stand 2016**

## Get AppleMate™ for your Apple

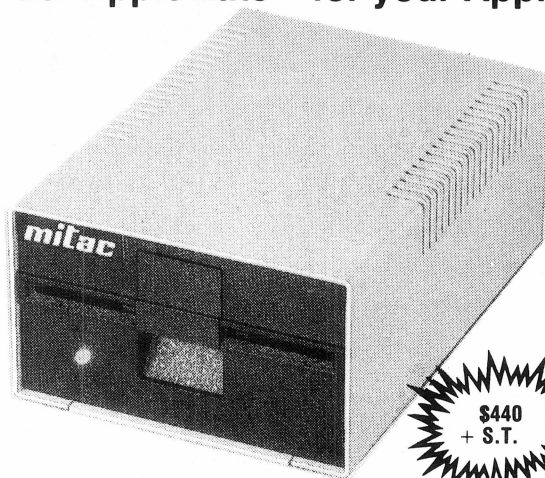

**\$440  
+ S.T.**

AppleMate 5 1/4 inch disk drive will mate your Apple II perfectly. You can mix AppleMate and Apple drives as Drive 1 to Drive 6 on either an Apple or its compatible Disk Interface (Controller) card. AppleMate installs instantly, is software transparent, reliable, and less expensive

### Also available

**MITAC MIS-5000 series SMALL BUSINESS COMPUTERS.** Z-80 based, 64KRAM, CP/M OpSystem, Dual 5 1/4" Single/Double Sided Disk-Drives, up to 2x640KBytes Storage Capacity.

**MIS-900** 12" Video-Terminal, 80x24 Characters, 90 Keyboard (15 editing/cursor-control), RS232C.

**APPLEMATE™** Low-cost 5 1/4" Disk-Drive, totally compatible with APPLE II®, perfect first or second Disk-Drive.

**PAX** Dual Mini Floppy-Disk-Drives; 5/10 Mbyte, Winchester-type, Hard-Disk-Drives and Controllers, all APPLE II® compatible.

**High-Resolution** 12" and 9" Monitors;

**Dot-Matrix Impact and Daisy-wheel Printers;**

**IEEE488 (GPIB) Interfaced, Computer Controlled Instruments.**

# AS NEAR AS YOU'LL GET TO A SMALL VARIABLE TRANSFORMER

## The Ferguson PL1.5-18/20VA Multi-tap Low Profile Transformer

Ideal for development situations or where the secondary voltage needs to be easily adjustable. Takes you from 1.5V to 18V in 1.5V steps. Simply plug and unplug the pinlok connectors till you get the voltage you want. Twin secondaries provide up to 2.2A. Numerous centre-tap configurations.

### •SERIES CONNECTION (1.11A)

1.5V, 3V, 4.5V, 6V, 7.5V, 9V, 10.5V, 12V, 13.5V, 15V, 16.5V, 18V

### Additional Series

#### Configurations (1.11A)

9V-6V-1.5V-0-1.5V-6V-9V or

9V-7.5V-3V-0-3V-7.5V-9V


#### Centre Tap Configurations (1.11A)

1.5V-0-1.5V, 3V-0-3V, 4.5V-0-4.5V,

6V-0-6V, 7.5V-0-7.5V, 9V-0-9V

### •PARALLEL CONNECTION (2.22A)

1.5V, 3V, 4.5V, 6V, 7.5V, 9V

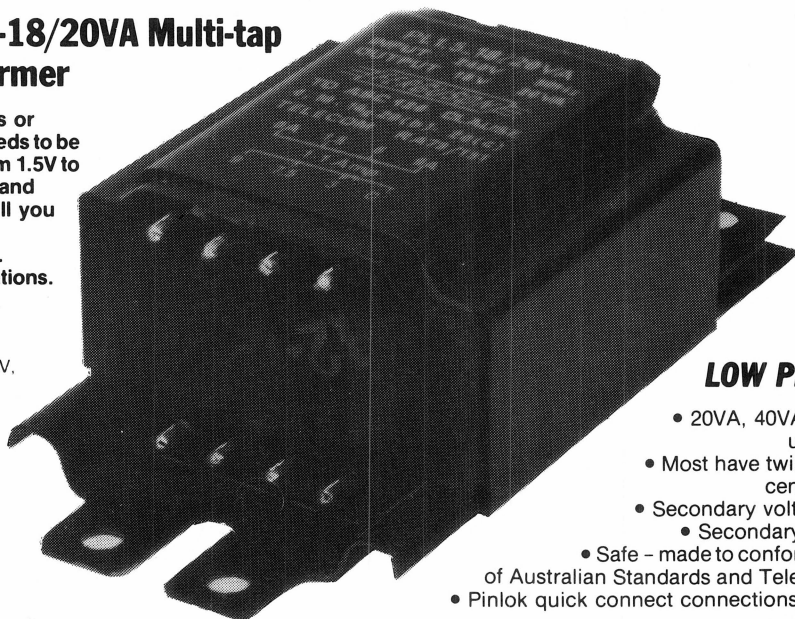

## CHECK THE WHOLE FERGUSON LOW PROFILE RANGE

- 20VA, 40VA and 60VA ratings – use two to get 120VA
- Most have twin secondaries to give centre-taps if necessary
- Secondary voltages from 6V to 40V
  - Secondary currents up to 6.6A
- Safe – made to conform to relevant clauses of Australian Standards and Telecom Australia specs.
- Pinlok quick connect connections • Made in Australia




## FERGUSON TRANSFORMERS PTY LTD

331 High Street, Chatswood N.S.W. 2067. Tel: (02) 407 0261. Telex: AA25728

Branch Office: 181-183 Hawke Street, West Melbourne Vic. 3003.

Tel: (03) 328 2843 Telex: AA33510

# LETTERS

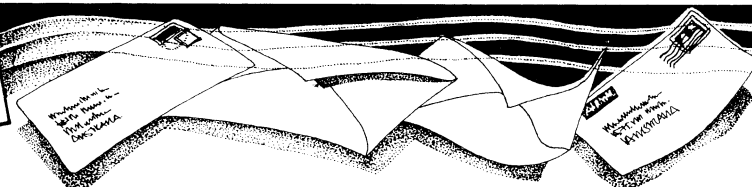

Dear Sir,

I write to you re your 'Dregs' column of the November '82 issue of ETI. In this column a cartoon appeared in which the following phrase was significant, "Ying tong, ying tong, ying tong, ying tong, ying tong yiddle di po."

As was pointed out by the columnist, followers of the 'legendary' Goon Show will recognise this phrase. I am a devout fan of the Goon Show and did, of course, recognise the phrase you printed as a travesty, a living mockery of the Goons. You see the phrase has been misquoted to such a hideous extent that it can only be seen as a direct insult to the small group of individuals who love the Goon Show.

You see, the actual title of this song which is being referred to is the 'Ying Tong Song' and I have just spent ten minutes listening to my copy of this record and can assure you that the phrase you have printed occurs *nowhere* in the song. The correct form of the lines which are quoted in Dregs is, "Ying tong, ying tong, ying tong, ying tong, ying tong yiddle I po."

It is obvious that the words 'iddle I' have been misquoted — nay butchered — to give 'yiddle di'. This disgusting oversight can only be seen as a deliberate slight at the lyrical and poetic brilliance of Spike Milligan.

In today's world we are blasted with so much inferior, classless and totally tasteless humour that to *misquote* the work of probably the greatest comedians of our time can only be seen as criminal. Now we are so saturated with the work of immature and mindless talents (such as Monty Python or 'Not the Nine O'Clock News') that to ignore the work of the great thespians of our past is a crying shame.

I should hope that you will act to correct this disastrous mistake, lest the youth should see such actions continue unbridled and themselves take part. Good God! — you don't go to press with the cover reading 'Electronics Tidly Internuptual', so please don't misquote the Goons. This last comment is expressed with pleading, relish and mustard.

C. Tinney  
Beverly Hills, NSW

We fail to be convinced of two things, namely: whether you're the truly devout Goons fan you claim to be, and whether the Ying Tong song goes "yiddle di po" or "iddle I po".

Firstly, a *truly* devout fan of the Goons would have opened with "... you rotten swine!", and threatened to send us an exploding rancid porridge bomb through the mail.

Secondly, the week after your letter arrived, by happenstance 2BL's famous breakfast announcer, the inimitable Clive Robertson, played the Ying Tong song immediately following the 7 am news one morning. I turned it up

and listened intently. I distinctly heard "... ying tong yiddle di po". Further, Clive replayed the falsetto bit at the end of the track at 33 rpm (the record is a 45 rpm EP). The song *definitely* goes "... yiddle di po"!

May the string that supports your knickerbockers turn into rotten twine and let your trousers down!

Bluebottle Harrison  
Dregs Correspondent  
(by appointment)

Dear Sir,

With respect to improving ETI slightly, I would like to see a brief explanation, with each project you publish, of why you used such and such an op-amp or transistor instead of another. Sometimes I look at one of your circuits and ask myself why a BD.. or a BF.. (a bit hard to get) was used when a common old 2N2222 would do as well. And then I try it and it does work. And you like 301s, when perhaps a TL081 might be better.

You have probably been asked this before but in 'How it works' couldn't you add a sentence or two like this 'there are dozens of transistors which will carry 200 mA and have an  $h_{fe}$  of 250, but we decided to use ... because X had a sale recently'. You know, the overseas magazine that specifies a TUN or a TUP and elsewhere gives a ruddy great list of such.

Your magazine sells to all sorts of people and I can't answer for others, but I would like to see a bit more analysis and more explanation of your circuits; after all, they are usually your designs and you know why you used a 20k resistor on a back-biased photodiode when my references say a 100k. I conclude, of course, that you know something I don't but maybe it was just a misprint.

N. Hobson  
Canterbury, NSW.

Your various points are well taken. We do explain, as often as possible, why we have used certain components or designed a circuit a particular way. For example, in the Series 5000 graphic equaliser, published in the November '82 issue, under the section headed 'Design', David Tilbrook explains the choice of the NE5534 and uA774/TL074 op-amps.

In general, when selecting components, particularly semiconductors, we ask ourselves (1) "What will do the job?", (2) "Is it commonly available?", (3) "If not commonly available, is there a reasonable source of supply (and who?)" and (4) "Is it cost effective?". We specify BD and BF transistors because they meet these criteria, 2N2222s would rarely do so (on an Australia-wide basis). We "like" 301s because they too, meet these criteria, particularly with regard to price — 301s cost 50-60 cents and are really widely available, TL081s cost more than that and are nowhere near as widely available. In any case, the Shoparound page serves to indicate com-

ponent kit suppliers for current projects. We don't like suggesting 'substitutes' unless they are *tried and known*. Semiconductor tolerances can be so broad between supposedly equivalent types that, from bitter experience, it is either impossible to design for, negates the point or degrades the performance of a circuit. We do not specify a particular device "... because X had a sale recently". Projects have a lifetime longer than the life of 'special sales'. We are aware of the practice *Elektor* uses when specifying components — the TUP (transistor-universal-pnp), TUN (transistor-universal-npn) etc. We looked into this very carefully but, for the reasons stated above, and from long experience, we consider the practice unwise. For example, with the ETI-330 Car Alarm (July '81), the 4093B specified for IC3 would not perform in the reset mode as described in the article because *some* devices of *some* manufacturers had distinctly differing performance parameters from those specified for the device of a particular manufacturer we used in the prototypes. (The cure, incidentally, is to change R6 to 100k and C2 to 10n). That's one hell of a trap! Surely a 4093 is a 4093 is a 4093 ... ? Apparently not. ▶

## Riston 3000

### Sensitized P.C. Board

(Fibreglass Base)

	SINGLE	DOUBLE
36x24	\$45.00	\$57.00
24x18	\$22.00	\$30.00
18x12	\$12.50	\$16.00
12x12	\$ 7.90	\$10.75
12x 6	\$ 4.50	\$ 5.85

### Quantity Discounts

\$100+	10%
\$250+	12½%
\$1000+	15%

All plus sales tax if applicable.

## RISTON DEVELOPER PROMOTION SPECIAL


Concentrate (1 = 4) \$4.25 litre  
— 5 litre \$19.50 —

**3M SCOTCHCAL**  
(Photo sensitive label material)  
**3M Image 'N' Transfer**  
(Graphic Transfer Material)  
**MAJOR STOCKISTS**

**KALEX**

101 Burgundy St,  
Heidelberg 3084  
(03) 458 2976  
Telex AA37678  
MELTON  
(03) 743 1011

# LETTERS

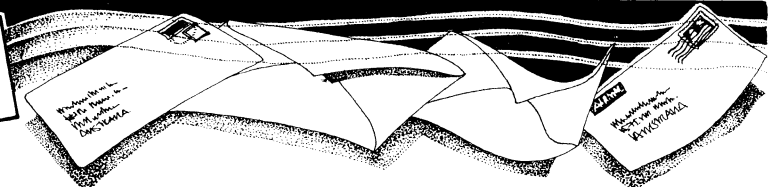

Dear Sir,

I write to you re your 'Dregs' column of the November '82 issue of ETI. In this column a cartoon appeared in which the following phrase was significant, "Ying tong, ying tong, ying tong, ying tong, ying tong yiddle di po."

As was pointed out by the columnist, followers of the 'legendary' Goon Show will recognise this phrase. I am a devout fan of the Goon Show and did, of course, recognise the phrase you printed as a travesty, a living mockery of the Goons. You see the phrase has been misquoted to such a hideous extent that it can only be seen as a direct insult to the small group of individuals who love the Goon Show.

You see, the actual title of this song which is being referred to is the 'Ying Tong Song' and I have just spent ten minutes listening to my copy of this record and can assure you that the phrase you have printed occurs *nowhere* in the song. The correct form of the lines which are quoted in Dregs is, "Ying tong, ying tong, ying tong, ying tong, ying tong yiddle I po."

It is obvious that the words 'iddle I' have been misquoted — nay butchered — to give 'yiddle di'. This disgusting oversight can only be seen as a deliberate slight at the lyrical and poetic brilliance of Spike Milligan.

In today's world we are blasted with so much inferior, classless and totally tasteless humour that to *misquote* the work of probably the greatest comedians of our time can only be seen as criminal. Now we are so saturated with the work of immature and mindless talents (such as Monty Python or 'Not the Nine O'Clock News') that to ignore the work of the great thespians of our past is a crying shame.

I should hope that you will act to correct this disastrous mistake, lest the youth should see such actions continue unbridled and themselves take part. Good God! — you don't go to press with the cover reading 'Electronics Tidily Internuptual', so please don't misquote the Goons. This last comment is expressed with pleading, relish and mustard.

C. Tinney  
Beverly Hills, NSW

We fail to be convinced of two things, namely: whether you're the truly devout Goons fan you claim to be, and whether the Ying Tong song goes "yiddle di po" or "iddle I po".

Firstly, a *truly* devout fan of the Goons would have opened with "... you rotten swine!", and threatened to send us an exploding rancid porridge bomb through the mail.

Secondly, the week after your letter arrived, by happenstance 2BL's famous breakfast announcer, the inimitable Clive Robertson, played the Ying Tong song immediately following the 7 am news one morning. I turned it up

and listened intently. I distinctly heard "... ying tong yiddle di po". Further, Clive replayed the falsetto bit at the end of the track at 33 rpm (the record is a 45 rpm EP). The song *definitely* goes "... yiddle di po!"

May the string that supports your knickerbockers turn into rotten twine and let your trousers down!

Bluebottle Harrison  
Dregs Correspondent  
(by appointment)

Dear Sir,

With respect to improving ETI slightly, I would like to see a brief explanation, with each project you publish, of why you used such and such an op-amp or transistor instead of another. Sometimes I look at one of your circuits and ask myself why a BD.. or a BF.. (a bit hard to get) was used when a common old 2N2222 would do as well. And then I try it and it does work. And you like 301s, when perhaps a TL081 might be better.

You have probably been asked this before but in 'How it works' couldn't you add a sentence or two like this 'there are dozens of transistors which will carry 200 mA and have an  $h_{fe}$  of 250, but we decided to use ... because X had a sale recently'. You know, the overseas magazine that specifies a TUN or a TUP and elsewhere gives a ruddy great list of such.

Your magazine sells to all sorts of people and I can't answer for others, but I would like to see a bit more analysis and more explanation of your circuits; after all, they are usually your designs and you know why you used a 20k resistor on a back-biased photodiode when my references say a 100k. I conclude, of course, that you know something I don't but maybe it was just a misprint.

N. Hobson  
Canterbury, NSW.

Your various points are well taken. We do explain, as often as possible, why we have used certain components or designed a circuit a particular way. For example, in the Series 5000 graphic equaliser, published in the November '82 issue, under the section headed 'Design', David Tillbrook explains the choice of the NE5534 and uA774/TL074 op-amps.

In general, when selecting components, particularly semiconductors, we ask ourselves (1) "What will do the job?", (2) "Is it commonly available?", (3) "If not commonly available, is there a reasonable source of supply (and who?)", and (4) "Is it cost effective?". We specify BD and BF transistors because they meet these criteria, 2N2222s would rarely do so (on an Australia-wide basis). We "like" 301s because they too, meet these criteria, particularly with regard to price — 301s cost 50-60 cents and are really widely available, TL081s cost more than that and are nowhere near as widely available. In any case, the Shoparound page serves to indicate com-

ponent kit suppliers for current projects. We don't like suggesting 'substitutes' unless they are *tried and known*. Semiconductor tolerances can be so broad between supposedly equivalent types that, from bitter experience, it is either impossible to design for, negates the point or degrades the performance of a circuit. We do not specify a particular device "... because X had a sale recently". Projects have a lifetime longer than the life of 'special sales'. We are aware of the practice *Elektor* uses when specifying components — the TUP (transistor-universal-ppn), TUN (transistor-universal-npn) etc. We looked into this very carefully but, for the reasons stated above, and from long experience, we consider the practice unwise. For example, with the ETI-330 Car Alarm (July '81), the 4093B specified for IC3 would not perform in the reset mode as described in the article because *some* devices of *some* manufacturers had distinctly differing performance parameters from those specified for the device of a particular manufacturer we used in the prototypes. (The cure, incidentally, is to change R6 to 100k and C2 to 10n). That's one hell of a trap! Surely a 4093 is a 4093 is a 4093 ... ? Apparently not. ▶

## Riston 3000

### Sensitized P.C. Board

(Fibreglass Base)

	SINGLE	DOUBLE
36x24	\$45.00	\$57.00
24x18	\$22.00	\$30.00
18x12	\$12.50	\$16.00
12x12	\$ 7.90	\$10.75
12x 6	\$ 4.50	\$ 5.85

### Quantity Discounts

\$100+	10%
\$250+	12½%
\$1000+	15%

All plus sales tax if applicable.

## RISTON DEVELOPER PROMOTION SPECIAL

Concentrate (1 = 4) \$4.25 litre  
— 5 litre \$19.50—

**3M SCOTCHCAL**  
(Photo sensitive label material)  
**3M Image 'N' Transfer**  
(Graphic Transfer Material)  
**MAJOR STOCKISTS**

**KALEX**

101 Burgundy St,  
Heidelberg 3084  
(03) 458 2976  
Telex AA37678  
MELTON  
(03) 743 1011

# LETTERS

If you *must* search out component equivalents, then best arm yourself with a stack of different manufacturers' data books and some knowledge of circuit analysis. For transistors and FETs, one of the best books is National Semiconductor's *Transistors/FETs, small signal, power*. This lists devices in familiar tabular form, and the rear section has the characteristics of devices listed by *Process Number*. 'Equivalents' can be found by matching process numbers. The 2N2222, for example, is a process 20 (npn medium power) transistor, described as a "non-overlay double diffused, gold doped, silicon epitaxial device. Complement to Process 63." Other process 20 devices are MPS3642, 2N3641/42/43. That's all very well, but in some circumstances, the circuit may not tolerate a different tolerance range on some parameter or another — some of which may be due to the particular package.

As for more circuit analysis and why we used 20k where your reference shows 100k, we include such things where it seems warranted, but I'm afraid project descriptions would get very lengthy, if not tedious, if we did it all the time covering every minute detail. Besides, it's almost impossible to predict exactly all the detail points you will want to know about. Hence, we often include a discussion on general design details and principles (see Project 461, Balanced Input Differential Preamp, in the December '82 issue, for example).

We would welcome other readers' views on this subject. Do you want even more design detail included in projects (remember, there's a practical limit on space)? Do you want less?

**Roger Harrison**  
Editor, ETI.

Dear Sir,

I have just completed the ETI-5000 pre and power amps which I purchased as kits from Jaycar. The result is an amplifier that performs better than anything I have listened to. It took me six weeks of discussing and listening to amplifiers and reading about them before I made up my mind and invested \$600. It certainly suits the classical/folk

music I listen to.

Although I have very little electronic experience I built these amps entirely from the information in your articles. I am still trying to grasp the logic and theory of the 'workings' of these amplifiers. I appreciated your articles as they are helping me to understand things more and I can share this knowledge with my 13 year old son.

Thank you ETI, for this project which enables people with limited budgets and expensive tastes to satisfy their needs.

I would appreciate some advice on whether it is possible to fit a headphone socket direct to the speaker outputs.

Thanks again for a superb project.

**W. Rath**  
Kambah ACT.

Headphones can be driven directly from the speaker terminals of the Series 5000 amplifier. It would be a wise idea, if doing so, to connect a series resistor between each output terminal and each headphone (right and left). The value would depend on the impedance of the 'phones. For low impedance types 330R/1W resistors are recommended. If you wish, medium to high impedance headphones may be driven directly from the output of the preamp.

**Roger Harrison**  
Editor, ETI

Dear Sir,

After reading about the problem of people pirating audio, video and computer software, I have come to the conclusion that one way to stop it, or at least stem the flow, is to reduce the cost of the original material to bring it more in line with the cost of the blank medium.

Let's say, for example, that the cost of a video movie is \$70. If I can buy a blank tape for less than \$20 and borrow another video recorder, then it's well worth the effort. But if the original tape costs less, say \$30, then it wouldn't be worth the trouble.

Who is he kidding, they all say. But just think how many times a movie is pirated. A calculated guess would be at least once.

Therefore each person is obtaining your movie for \$35, only \$5 more than my suggested price. No matter how much you reduce the cost you will still get the pirates, but most people would rather have an original in the box with the associated printed material.

This includes video, audio and computer software. So how about the marketing people having a go at selling material at a price we can all afford. Not everybody can pay \$70, in these times, for movies, music or software.

The above prices are quoted as examples only.

**Gary Osborn**  
Blackburn Sth, Vic.

Dear Sir,

I received my first prize from ETI/Minitools contest and I am very impressed with the performance and quality of these miniature tools.

I am writing to express my sincerest thanks to all those who made the contest possible. It really is a fantastic prize and I am thrilled to own such high performance gear.


Many thanks to all at ETI and Minitools Australia.

**Peter Mann**  
Robinvale Vic.

Dear Sir,

Many people seem to think that those of us who are interested in electronics live in a world of our own, separated from the real world and divorced from what's happening in it. I disagree, as would most of us, but I will admit that we often view it from a different perspective as this 'circuit' drawn by a friend of mine shows.

**John Windle**  
Penrith NSW

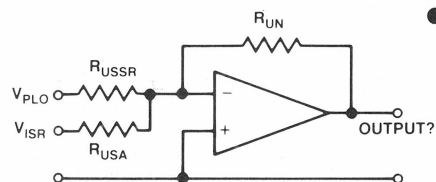



## If Athlete's Foot has got your toes in a shocking state...


### Try Tinacidin. Pull the plug on the burning, itching, prickly pain of Athlete's Foot... fast!

At pharmacies everywhere.

SCHERING CORPORATION U.S.A., AUSTRALIAN SUBSIDIARY  
 — ESSEX LABORATORIES PTY. LTD., BAULKHAM HILLS, N.S.W.

Health Care is our business

PM6067/82 SX 8914/3

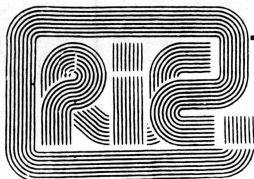

# Rod Irving's

# ZIP OUT

## catalogue

## ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131.


TO ORDER: Heavy items sent Skyroad Freight on Mail Order Phone 481-1436. Wholesale Customers

Phone: 489-7099. Mail Orders to P.O. Box 235, Northcote Vic. 3070.

Minimum P&P \$2. Ad extra for heavy items, registration and certified mail.

Prices subject to change without notice.


ICL7106	12.50	74S157	3.10	74H04	.90	74C150	6.50	74LS12	30	74LS155	1.20	74LS354	3.95	6522	10.00	LM301H	1.50	UA710CN	1.00
ICL7107	15.50	74S158	3.10	74H05	.90	74C151	4.20	74LS13	50	74LS156	1.20	74LS365	.60	6522A	11.00	LM302H	6.50	LM711	1.20
ICL7109	27.50	74S160	5.90	74H08	1.10	74C154	6.00	74LS14	.60	74LS157	.60	74LS366	.60	6532	12.50	LM305H	1.50	LM723	.75
ICL7116	21.50	74S161	5.90	74H10	.80	74C157	3.75	74LS15	.30	74LS158	.80	74LS367	.60	6545	22.50	LM307CN	1.00	LM723CH	1.50
ICL7117	21.50	74S162	7.90	74H11	.80	74C160	1.90	74LS18	.45	74LS160	.80	74LS368	.60	6551	12.90	LM307H	1.60	LM725	4.75
ICL7660	4.90	74S163	7.90	74H12	.80	74C161	1.90	74LS19	.45	74LS161	.70	74LS373	1.50	2650	21.00	LM308	1.00	LM733	1.50
ICL7663	4.90	74S168	11.50	74H15	.80	74C162	2.00	74LS20	.30	74LS162	1.10	74LS374	1.75	2651	23.00	LM308H	1.80	UA739	2.75
ICL7664	4.90	74S169	11.50	74H20	.80	74C163	2.00	74LS21	.30	74LS163	.90	74LS375	.85	6800	8.00	LM309K	1.90	741	.50
ICM7211	12.50	74S174	4.50	74H21	.90	74C164	1.90	74LS22	.30	74LS164	1.40	74LS377	2.15	6802	10.00	LM310N	3.20	UA747	1.30
ICM7261A	47.50	74S175	4.50	74H22	.80	74C165	1.90	74LS24	.55	74LS165	.60	74LS378	1.20	6808	12.50	LM310H	3.20	UA748	.80
ICM7216B	42.50	74S181	8.50	74H30	.90	74C173	1.50	74LS26	.30	74LS166	2.55	74LS379	1.90	6809	17.00	LM311	.80	MC1310	9.50
ICM7217A	18.50	74S182	3.40	74H40	.90	74C174	1.50	74LS27	.35	74LS170	2.45	74LS386	.50	6810	3.50	LM311H	1.80	MC1312	6.90
ICM7218A	18.50	74S188AN	4.10	74H50	.90	74C175	1.50	74LS28	.35	74LS173	.90	74LS390	1.80	6820	5.50	LM317T	2.50	MC1314	6.90
ICM7224A	18.50	74S189	8.50	74H51	.90	74C192	1.90	74LS30	.30	74LS174	.80	74LS393	1.80	6821	3.50	LM317K	4.50	MC1315	7.50
ICM7226A	48.50	74S194	3.30	74H52	.90	74C193	1.90	74LS32	.30	74LS175	.80	74LS395	2.00	6840	6.50	LM318	3.50	MC1327	6.50
ICM7227A	48.50	74S195	2.90	74H53	.90	74C195	1.90	74LS33	.35	74LS181	2.80	74LS396	2.50	6844	15.00	LM319	3.50	MC1350	1.30
ICM7231A	15.50	74S196/82590	4.90	74H54	.90	74C200	14.00	74LS37	.35	74LS183	4.00	74LS398	3.00	6845	32.00	LM324	1.20	MC1408L8	7.50
ICM7240	7.50	74S197/82591	4.90	74H55	.90	74C221	2.40	74LS38	.40	74LS190	1.20	74LS399	1.90	6847	7.50	LM325	4.50	MC1437	3.50
ICM7242	3.90	74S201	9.90	74H60	.90	74C240	2.60	74LS40	.40	74LS191	.80	74LS424	5.50	6850	3.50	LM326	4.50	MC1445	3.75
ICM7250	7.90	74S214AN	P.O.A.	74H61	.90	74C244	2.60	74LS42	.80	74LS192	.80	74LS440	5.50	6860	10.00	LM329DZ	.90	MC1456	1.50
ICM7260	7.90	74S225	10.90	74H62	.90	74C245	3.00	74LS47	1.80	74LS193	.80	74LS441	5.50	6875	13.50	LM344Z	1.70	MC1458	1.20
ICM7555	1.90	74S226	7.90	74H64	.90	74C374	3.00	74LS48	1.80	74LS194	.80	74LS442	5.50	Z800CPU	7.00	LM335Z	2.20	MC1466L	14.50
ICM7556	2.50	74S240	6.90	74H65	.90	74C901	1.50	74LS49	1.80	74LS195	1.25	74LS443	5.50	Z800CPU	8.00	LM339	.90	MC1469R	6.90
		74S241	6.90	74H71	1.40	74C902	1.00	74LS51	.35	74LS196	1.25	74LS445	2.20	Z800CPU	16.00	LM348	1.60	MC1488	1.20
		74S244	9.90	74H72	1.20	74C903	1.00	74LS54	.40	74LS197	1.20	74LS446	5.50	Z80P10	4.50	LM349	1.60	MC1489	1.20
74S		74S251	9.90	74H73	1.80	74C904	1.00	74LS55	.40	74LS221	1.20	74LS447	1.90	Z80AP10	6.50	LM350	6.50	MC1494	7.50
74S00	.80	74S253	4.90	74H74	1.80	74C905	15.00	74LS63	2.80	74LS240	1.20	74LS448	5.50	Z80CTC	6.50	LF351-N	.80	MC1495	6.90
74S02	.80	74S257	3.30	74H76	1.90	74C906	1.00	74LS73	.50	74LS241	1.20	74LS449	5.50	Z80ADMA	8.50	LF356N	1.40	MC1496	1.90
74S03	.80	74S258	3.30	74H78	1.90	74C907	1.00	74LS74	.40	74LS242	1.50	74LS490	3.20	Z80DMA	16.00	LF357	1.40	LM1596	2.30
74S04	.85	74S260	2.90	74H87	7.90	74C908	1.70	74LS75	.50	74LS243	1.50	74LS540	11.95	Z80ADMA	19.00	LM358	1.00	MC1648	4.90
74S05	1.10	74S274	P.O.A.	74H101	1.80	74C910	14.00	74LS76	.55	74LS244	1.20	74LS541	11.95	Z80AS10	19.00	LM361	3.50	LM1812	10.50
74S08	.80	74S275	P.O.A.	74H102	1.80	74C911	12.50	74LS77	.65	74LS245	1.50	74LS621	2.75	Z80S10	16.00	LM377	4.90	LM1830	3.90
74S09	1.10	74S280	5.90	74H103	2.50	74C912	12.50	74LS78	.55	74LS247	1.20	74LS622	2.75	AY-3-8910	14.50	LM378	3.95	LM2907	3.50
74S10	.80	74S281	P.O.A.	74H106	2.50	74C914	2.50	74LS83	1.00	74LS248	1.40	74LS623	2.75	AY-3-2513	14.50	LM379-S	7.95	LM2917 8 pin	3.40
74S11	.80	74S283	7.90	74H108	2.50	74C915	2.00	74LS85	1.30	74LS249	1.30	74LS629	2.95	MM5303	7.50	LM380 8 pin	1.40	LM2917 14 pin	3.40
74S15	1.30	74S287	3.30	74H113	1.10	74C917	12.50	74LS86	.40	74LS251	1.00	74LS640	2.95	S1883	8.50	LM380 14 pin	1.50	MN3001	17.50
74S20	1.00	74S288	3.60	74H114	1.10	74C918	1.90	74LS90	.70	74LS253	.90	74LS641	2.75	MM5303	7.50	LM381	2.00	CA3028	2.00
74S22	1.20	74S299	13.90	74H183	7.90	74C920	12.50	74LS91	.70	74LS257	.75	74LS642	2.75	LH0002	9.50	LM382	2.20	CA3046	1.90
74S30	.80	74S301	12.90			74C921	12.50	74LS92	.70	74LS258	.90	74LS643	2.75	LH0042CH	7.50	LM383	2.95	CA3056	6.50
74S32	.80	74S314	P.O.A.	74C		74C922	6.50	74LS93	.60	74LS259	2.25	74LS644	2.75	LH0071	7.50	LM384	2.75	CA3059	5.95
74S37	1.70	74S330	P.O.A.	74C00	.60	74C923	6.50	74LS95	.75	74LS261	2.50	74LS645	2.75	LH0071	7.50	LM386	1.95	CA3080	1.50
74S38	1.70	74S331	P.O.A.	74C02	.60	74C925	7.90	74LS96	1.00	74LS266	.70	74LS668	1.75	TL061	1.00	LM387	2.00	CA3086	1.80
74S40	1.20	74S373	9.90	74C04	.60	74C926	7.90	74LS107	.60	74LS273	1.55	74LS669	1.75	TL062	2.90	LM390	2.95	CA3089	3.90
74S51	.80	74S374	9.90	74C08	.60	74C927	7.90	74LS109	.60	74LS275	6.80	74LS670	2.75	TL064	2.90	LM391	2.90	CA3130E	1.60
74S64	1.20	74S381	9.90	74C10	.60	74C928	8.00	74LS112	.60	74LS279	.80	74LS673	12.55	TL074	1.20	LM393	1.00	CA3130T	1.90
74S65	1.20	74S387	3.30	74C14	1.00	74C929	9.50	74LS113	.60	74LS280	2.60	74LS674	12.55	TL072	1.60	LM394	4.95	CA3140E	1.60
74S74	1.30	74S412/8212	5.90	74C20	.60	74C930	2.75	74LS114	.60	74LS283	1.20	74LS690	3.95	TL073	3.20	LM395T	1.90	CA3140T	1.90
74S86	1.60	74S428/8228	7.90	74C30	.60	74C932	2.50	74LS122	.90	74LS290	1.20	74LS691	3.95	TL074	2.90	LM396K	19.50	LM3401	1.00
74S109	2.50	74S470	9.90	74C32	.60	74C941	2.50	74LS123	.90	74LS293	1.10	74LS692	3.95	TL081	1.90	LF398	5.90	LM3900	1.20
74S112	1.30	74S471	9.90	74C42	1.60	74C989	8.90	74LS125	.60	74LS295	1.50	74LS693	3.95	TL082	1.80	NE544	6.50	LM3905	1.75
74S113	1.30	74S472	P.O.A.	74C48	2.50			74LS126	.65	74LS297	1.20	74LS696	3.95	TL083	2.90	NE555	.50	LM3909	1.30
74S114	2.50	74S473	P.O.A.	74C73	1.20	74LS		74LS132	.80	74LS298	1.20	74LS699	16.50	TL084	2.90	NE556	1.20	LM3911	1.95
74S124	5.90	74S474	P.O.A.	74C74	1.20	74LS00	.25	74LS136	.60	74LS299	3.90			TL494	4.90	NE558	4.90	LM3914	4.90
74S132	3.50	74S475	P.O.A.	74C76	1.20	74LS01	.30	74LS138	.70	74LS320	3.95	CPU		TCA220	2.20	NE560	4.60	LM3915	4.90
74S133	1.20	74S482	11.90	74C83	2.30	74LS02	.25	74LS139	.70	74LS321	3.95	6502	11.00	TCA280	4.50	NE561	4.60	LM3916	4.90
74S134	1.40	74S289	7.90	74C85	2.30	74LS03	.30	74LS145	2.10	74LS322	6.75	6502A	12.00	TDA1024	2.90	NE565	1.60	LM3999Z	2.60
74S135	2.30			74C86	1.20	74LS04	.30	74LS147	2.50	74LS323	6.50	6503	11.00	TA7205P	3.90	NE566	2.90	RL4136	1.50
74S138	3.30	74H		74C89	6.90	74LS05	.35	74LS148	1.20	74LS324	2.20	6504	11.00	TA1002	17.50	NE567	2.00	RC4145	2090
74S139	3.30	74H00	.80	74C90	1.60	74LS08	.30	74LS151	.90	74LS326	2.20	6505	11.00	UA170	3.75	NE570	5.90	RC4194	3.90
74S140	1.90	74H01	.80	74C93	1.50	74LS09	.30	74LS152	1.95	74LS327	2.20	6507	11.00	UA180	3.75	NE571	5.90		
74S151	3.10	74H02	.80	74C95	1.80	74LS10	.30	74LS153	.70	74LS352	2.20	6520	5.50	LM10CH	7.50	NE594	9.50	SCR & TMCAS	
74S153	2.90	74H03	.80	74C107	2.20	74LS11	.30	74LS154	1.75	74LS353	2.20	6521	5.90	LM301	.50	LM709-14	1.00	SC141D	1.50</

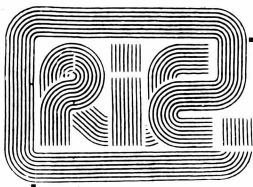


SC141E	1.95	BF458	1.00	TIP122	3.45	2N5656	2.50	74109	.60	9305	2.40	8379	8.50	OPTO	OM350	9.50	4096	2.40	
SC142D	2.95	BF459	1.00	TIP125	2.90	2N5770	.30	74110	.80	9307	3.80	8282	6.90	4N25	1.20	IM65X08CPE	5.00	4097	6.50
SC146D	2.85	BF469	.90	TIP127	3.40	2N5777	1.50	74111	.80	9308	3.60	8283	6.50	4N26	1.20	XR2206	5.00	4098	2.90
SC146M	2.95	BF470	.90	TIP145	3.40	2N5830	.30	74112	.80	9309	2.40	8284	6.50	4N27	1.20	XR2207	6.50	4099	3.90
SC150D	4.95	BF494	.90	TIP2955	1.90	2N5831	.30	74113	.80	9310	1.50	8286	6.50	4N28	1.20	XR2208	4.90	4104	6.90
SC151D	2.95	BF495	.90	TIP3055	1.90	2N5873	1.40	74114	.80	9311	2.50	8287	6.50	4N29	1.50	XR2209	5.90	4160	1.25
C103YY	.90	BFW10	1.50	2N301	4.00	2N5874	1.70	74120	1.65	9312	2.50	8288	25.00	4N30	1.60	XR2211	6.90	4161	1.25
C103B	.90	BFW11	1.50	2N697	1.00	2N5944	15.50	74121	.65	9313	6.00	8289	73.00	4N32	2.50	XR2216	4.90	4162	1.25
C106B	.90	BFW16	1.50	2N918	1.00	2N5945	15.50	74122	.65	9314	2.40	8291	43.00	4N33	2.50	XR2240	4.90	4163	1.25
C106D	.90	BFY50	1.20	2N1304	1.00	2N5946	19.50	74123	.60	9316	1.90	8292	34.50	4N35	2.50	XR2242	4.90	4174	1.25
C122D	2.50	BFY90	1.50	2N1613	1.20	2N5961	1.90	74125	.55	9317	4.20	8293-10	26.50	4N37	2.00	XR2243	5.90	4175	1.60
C122E	2.95	BU126	2.50	2N2102	1.90	2N6027	1.00	74126	.60	9318	4.60	8741	57.50	MCT6	2.50	XR8038	6.50	4194	1.95
SC260D	8.50	BU208	3.90	2N2219	.90	2N6049	1.90	74128	1.80	9319	2.00	8748	23.50	MCT66	6.90	ICG7660	12.50	4402	1.00
SC260F	9.90	BU326	3.00	2N2222A	1.00	2N6080	8.50	74132	.80	9320	6.90	8749	58.50	MCT2	5.90	95H90	8.50	4404	1.15
2N2646	1.20	BUX80	4.90	2N2369	1.00	2N6083	17.90	74136	.55	9321	2.40	8755	33.50	1LD74	5.90	11C90	16.50	4408	6.90
2N2647	2.50	MFE131	2.90	2N2484	1.00	2N6084	22.50	74138	1.80	9322	1.90	2911	26.50	1LD74	6.50	LM7555	1.90	4409	13.50
2N6027	.90	MFE3001	9.90	2N2647	1.20	2N6124	1.90	74139	1.00	9324	1.40	2912	27.50	FND357	1.80	MC10116L	1.50	4410	11.50
TRANSISTORS																			12.60
AC125	1.20	MJ802	7.50	2N2904	1.10	2N6133	1.90	74142	1.10	9328	4.90	2920	239.00	FND500	1.80	LF13741-H	1.50	4412	.45
AC126	1.20	MJ901	4.50	2N2905	1.10	2N6256	13.50	74143	1.45	9338	5.90	3242	17.50	FND507	3.50	DS75451	.60	4415	10.15
AC127	1.20	MJ1001	3.90	2N2906	1.10	2N6259	13.50	74144	3.90	9340	9.90	3245	10.90	T1L31A	2.95	DS75452	.60	4416	.60
AC128	1.20	MJ11011	9.90	2N2907	1.10	2N6274	29.50	74145	1.45	9342	5.90	3628	18.50	T1L81C	2.95	DS75491	2.00	4419	3.45
AC187	1.50	MJ11015	14.50	2N3019	1.90	2N6378	4.90	74148	1.95	9368	2.20	8008-1	62.50	T1L306	14.50	DS75492	2.00	4422	9.50
AC188	1.50	MJ11016	14.50	2N3053	.90	2N6425	4.50	74150	1.40	9374	3.30	8031-3	29.50	BPW50	2.25	7216A	41.50	4426	2.35
AC149	3.40	MJ15003	6.50	2N3054	1.90	2N6578	5.90	74151	1.15	9386	2.40	8035	6.90	CQY89	1.50	7216B	42.50	4428	1.75
AC161	2.90	MJ15004	6.50	2N3055	1.20	2N6578	5.90	74153	.65	75107	2.50	8039	7.90	MOC3011	2.95	DM2502	10.00	4433	2.25
AC162	2.90	MJ15024	10.00	2N3096	1.20	2SJ49	7.50	74154	1.15	75154	2.50	F01771	19.00	MOC3020	2.50	ADC0800	16.00	MC14433	13.90
AF118	2.90	MJ2955	1.50	2N3109	1.90	2SK134	7.50	74155	.85	75450	1.50	F01793	35.00	MOC3021	2.95	ADC0808	17.00	4435	7.95
AF126	2.90	MJ3002	6.90	2N3251	1.90	7400	.25	74156	1.45	75451	.60	F01795	35.00	DAC0800	4.50	4441	1.50		
AF127	1.50	MJ4032	12.50	2N3302	1.90	7401	.30	74157	.60	75452	.60	F01797	35.00	DAC0808	3.50	4443	3.90		
BC107	.50	MJ4035	1.90	2N3440	1.80	7402	.25	74158	.85	75453	.60	WD1691	16.50	SAK140	.25	ZN414	1.95	4446	3.55
BC108	.50	MJ4502	6.90	2N3441	2.90	7403	.35	74160	.85	75461	1.50	WD2143	12.50	3mm YELLOW	.15	4000	.40	4449	1.00
BC109	.50	MJ3440	2.00	2N3442	3.50	7404	.30	74161	1.00	75462	1.50	WD1931	22.50	5mm RED	.15	4001	.40	4450	3.75
BC159	.50	MJ3550	2.50	2N3563	.30	7405	.35	74162	1.00	75471	3.00	WD1933	34.00	5mm GREEN	.30	4002	.40	4451	3.75
BC177	.60	MJ3731	2.90	2N3564	.30	7406	.40	74163	1.00	75472	3.00	WD1983	14.75	5mm YELLOW	.30	4006	1.60	4457	5.90
BC178	.60	MJ5521	2.50	2N3565	.30	7407	.40	74164	.60	75491	2.00	WD1993	59.00	5mm ORANGE	.30	4007	.50	4458	9.90
BC179	.60	MJ5700	3.90	2N3566	.30	7408	.35	74165	.60	75492	2.00	WD2123	26.50	RED RECT	.30	4008	1.40	4469	14.90
BC212	.30	MJ8000	2.50	2N3567	.30	7409	.35	74166	1.35	75493	3.00	WD8250	16.50	GREEN RECT	.30	4009	.60	4490	5.90
BC318	.30	MJ2801	3.95	2N3568	.30	7410	.30	74167	2.20	75494	3.00	TR1602	8.50	YELLOW RECT	.30	4010	.70	4495	3.95
BC320	.40	MJ2955	4.90	2N3569	.30	7411	.35	74174	1.45	8121	4.00	TR1863	8.90	RED CHROME	.30	4011	.40	4500	8.90
BC327	.30	MJ3055	3.90	2N3638	.30	7412	.35	74175	.85	8123	4.00	COM8116	24.00	BEZEL	1.20	4012	.50	4501	.50
BC328	.30	MJ13005	5.90	2N3640	.30	7413	.50	74176	1.10	8130	6.00	BR1941	12.50	YELLOW CHROME	1.20	4013	.75	4502	1.80
BC338	.30	MJ13007	7.90	2N3641	.30	7414	.70	74177	1.10	8131	3.95			BEZEL	1.20	4014	1.50	4503	.90
BC546	.40	MJ13009	12.50	2N3642	.30	7415	.35	74178	2.15	8135	4.25	74F SERIES		GREEN CHROME	1.20	4015	.95	4504	2.00
BC547	.20	MPF121	2.50	2N3643	.30	7416	.60	74179	2.15	8136	4.25	74F00	.79	BEZEL	1.20	4016	.65	4506	.75
BC548	.20	MPF131	2.50	2N3644	.30	7417	.55	74180	.90	8303	5.50	74F02	.79			4017	1.20	4507	.40
BC549	.20	MPSA05	1.00	2N3645	.30	7420	.25	74182	.90	8304	5.50	74F04	.92	VOLTAGE REGS		4018	1.50	4508	4.50
BC550	.40	MPSA06	1.00	2N3646	.30	7421	.40	74184	1.20	82523	4.50	74F08	.79	7805UC	.90	4019	.60	4510	1.50
BC556	.40	MPSA09	1.00	2N3702	1.20	7422	.40	74190	1.00	825123	3.90	74F10	.79	7805KC	2.00	4020	1.35	4511	1.50
BC557	.20	MPSA10	1.00	2N3704	1.40	7423	.45	74191	1.45	8311	4.87	74F11	.79	7812UC	.90	4021	1.10	4512	1.10
BC558	.20	MPSA12	1.00	2N3739	4.50	7425	.45	74192	1.65	8641	3.83	74F20	.79	7812KC	2.00	4022	1.15	4513	2.65
BC559	.20	MPSA13	1.00	2N3771	5.50	7426	.35	74193	.80	8820	4.95	74F32	.79	7815UC	.90	4023	.40	4514	2.90
BC635	.80	MPSA14	1.00	2N3772	5.70	7427	.40	74194	1.10	8830	5.00	74F64	.79	7815KC	2.20	4024	1.00	4515	2.90
BC636	.80	MPSA20	1.00	2N3773	5.90	7428	.40	74195	.65	8831	5.00	74F74	.89	7818UC	1.00	4025	.40	4516	1.45
BC637	.80	MPSA42	1.00	2N3792	6.00	7430	.35	74196	.85	8832	5.00	74F86	1.19	7818KC	2.20	4026	2.00	4517	8.75
BC638	.80	MPSA43	1.20	2N3819	1.20	7432	.35	74197	1.10	8833	4.90	74F109	.99	7824UC	1.00	4027	.60	4518	1.50
BC639	.50	MPSA55	1.00	2N3866	2.95	7433	.55	74198	1.10	8834	5.90	74F138	1.79	7824KC	2.40	4028	.90	4519	.90
BC640	.50	MPSA56	1.00	2N3904	1.00	7437	.40	74199	1.30	8835	4.00	74F139	1.79	7905UC	1.40	4029	1.20	4520	1.55
BCY70	1.90	MPSA63	1.00	2N3906	1.00	7438	.45	74221	.90	8836	2.00	74F151	1.79	7905KC	3.00	4030	.60	4521	3.90
BCY71	1.90	MPSA65	1.00	2N4032	2.20	7439	.70	74240	1.50	1488	1.20	74F153	1.79	7912UC	1.40	4031	2.50	4522	1.90
BD135	1.00	MPSA92	1.00	2N4033	2.20	7440	.45	74241	.50	1489	1.20	74F157	1.79	7912KC	3.00	4032	2.25	4526	1.85
BD136	.90	MPSA93	1.20	2N4036	2.50	7442	.50	74242	1.50	81LS95	2.20	74F158	1.79	7915UC	1.50	4033	2.25	4527	2.65
BD137	.90	MPF102	.90	2N4121	1.50	7443	1.30	74243	1.50	81LS96	2.20	74F175	2.78	7915KC	3.00	4034	3.00	4528	1.15
BD138	.90	MPF103	.90	2N4123	1.50	7444	1.10	74244	1.75	81LS97	2.20	74F181	5.98	7918UC	1.50	4035	1.30	4529	1.80
BD139	.60	MPF105	.90	2N4236	1.90	7445	1.10	74245	1.75	81LS98	2.20	74F182	7.23	7924UC	1.50	4038	2.75	4530	1.60
BD140	.90	MPF106	.90	2N4237	1.90	7446	1.00	74246	2.25	8126	3.00	74F189	7.44	78L05	.50	4040	1.40	4531	1.65
BD201	.90	MPF109	.90	2N4248	.40	7447	.95	74247	2.25	8128	3.00	74F190	4.86	78L12	.50	4041	1.50		
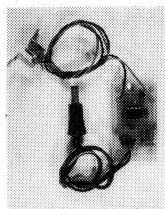
# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA. Ph (03) 489 8131. Telex No. 38897



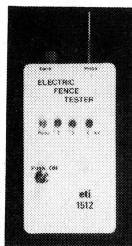**ETI-268 NICAD  
FLOAT CHARGER**  
Keep your NiCad batteries  
in tip-top condition with this  
cheap, simple charger.





**ETI-1512  
ELECTRIC FENCE  
TESTER**

Electric fence **\$17.50**

Check  
our  
prices

SEPTEMBER EA 1982

**ETI-488 60 W AMP USING  
TWO NDFLs**

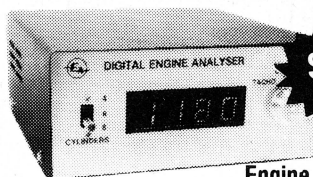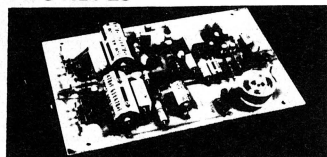

**\$48.50**


Engine Analyser Kit

12/240 volt Inverter



MAY EA 1982


Dual Tracking Power Supply

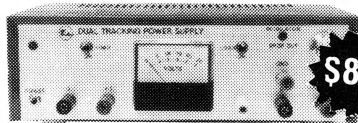

**\$83.50**

**\$79.50**


Function Generator

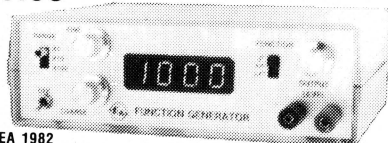

APRIL EA 1982

**EA DIGITAL READOUT FOR  
SW RECIEVERS**

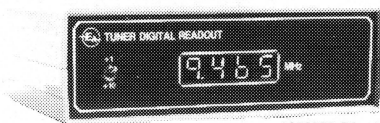
Short form without case **\$49.50** **\$70**



OCTOBER EA 1982
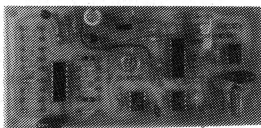
## THIS MONTHS KITS

**ETI-335 PUSHBUTTON-PROGRAMMABLE  
WIPER CONTROLLER**




No more fiddling with knobs and not getting the delay  
between wipes that you want — this windscreen wiper  
controller is simply 'programmed' with two pushbuttons  
to provide the wiping delay you need.

**ETI-1511  
TEMPERATURE  
CONTROLLER**




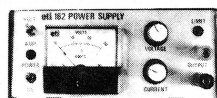**ETI-162 30 V/1 A FULLY PROTECTED  
POWER SUPPLY**




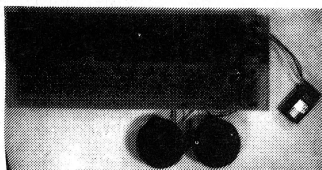**\$47.50**

**ETI-905 POLYPHONIC TOUCH  
SENSOR ORGAN**




Tacho/dwell meter with digital display

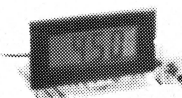

MAY EA 1982

**\$62**

Eprom  
Programmer

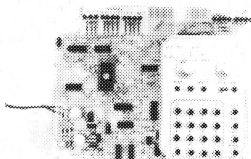

JANUARY EA 1982

**\$55.00**




**\$55.00**

SEPTEMBER EA 1982

**Portable 3½ Digit Heart Rate Monitor**

JULY EA 1982

**\$79.00**

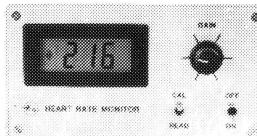


**EA EASY-TO-BUILD  
FREEZER ALARM**

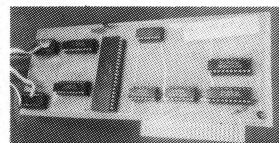**\$21**

OCTOBER EA 1982




**ETI-654 APPLE II ANALOGUE/DIGITAL  
INTERFACE**



This project will give your Apple a set of 8-bit digital  
inputs and outputs plus one analogue input and  
one analogue output. Applications include: driving a  
robot, recording science experiment results, etc. (digital  
only shown)

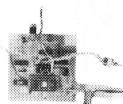
**ETI-668  
MICROBEE EPROM  
PROGRAMMER**



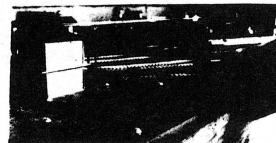
**ETI-334 AUTO TESTER**



**ETI-1510 MODEL TRAIN POINTS  
CONTROLLER AND INDICATORS**




Ultrasonic Rule

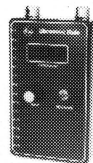

AUGUST EA 1982

**\$49.00**

Car Computer

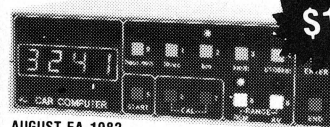

AUGUST EA 1982


**\$109**



**\$189.00**

Analogue and Digital Storage CRO Kit

**100w Sub-Woofer  
Amplifier**

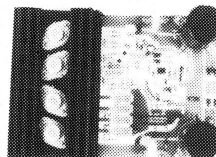

JULY EA 1982

**\$85.00**

**EA ELECTRONIC STARTER  
FOR  
FLUORESCENT  
LAMPS**

**\$5**

OCTOBER EA 1982




**64K SS50 STATIC NOW AVAILABLE \$399 + TAX**  
**64K S100 STATIC NOW AVAILABLE \$399 + TAX**  
**DON'T FORGET TO CHECK WITH US BEFORE YOU BUY A COMPUTER OR OTHER PRODUCTS**

# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA

## 16K EPROM CARD-S 100 BUSS

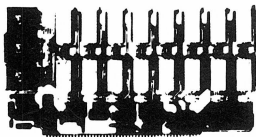

\$109.00

BLANK PC BOARD \$69.00

USES 2708's!

Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.

OUR 450 NS 2708'S ARE \$5.90EA. WITH PURCHASE OF KIT

ASSEMBLED AND FULLY TESTED ADD \$36

## 16K STATIC RAM KIT-S 100 BUSS

KIT \$179  
A&T \$199



### KIT FEATURES

1. Addressable as four separate 4K Blocks
2. ON BOARD BANK SELECT circuitry (Cromemco Standard) Allows up to 512K on line
3. Uses 2114 (45NS) 4K Static Rams
4. ON BOARD SELECTABLE WAIT STATES
5. Double sided PC Board with solder mask and silk screened layout. Gold plated contact fingers
6. All address and data lines fully buffered
7. Kit includes ALL parts and sockets
8. PHANTOM is jumpered to PIN 67
9. LOW POWER under 1.5 amps TYPICAL from the +8 Volt Bus
10. Blank PC Board can be populated as any multiple of 4K

BLANK PC BOARD W DATA \$69.00

LOW PROFILE SOCKET SET \$22

SUPPORT IC'S & CAPS \$29


ASSEMBLED & TESTED ADD \$30

OUR #1 SELLING RAM BOARD!

## S100 COMPUTER PRODUCTS

### 32K S-100 EPROM CARD

NEW!

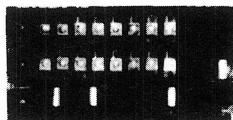

\$109.00

### KIT


USES 2716's  
Blank PC Board - \$69  
ASSEMBLED & TESTED  
ADD \$30

SPECIAL: 2716 EPROM's (450 NS) Are \$5.90 EA. With Above Kit.

### KIT FEATURES

1. Uses +5V only 2716 (2Kx8) EPROM's
2. Allows up to 32K of software on line!
3. IEEE S-100 Compatible
4. Addressable as two independent 16K blocks
5. Cromemco extended or Northstar bank select
6. On board wait state circuitry if needed
7. Any of all EPROM locations can be disabled
8. Double sided PC board: solder-masked, silk-screened
9. Gold plated contact fingers
10. Unselected EPROM's automatically powered down for low power
11. Fully buffered and bypassed
12. Easy and quick to assemble

## \*\*\* AVAILABLE AGAIN \*\*\*

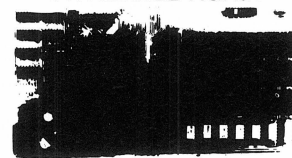

- 16K Dynamic Ram Board
- Fully Expandable to 64K
- Assembled, tested and guaranteed
- S100 Compatible

16K Dynamic RAM Board assembled and tested: Special \$289 plus tax (4mHz) \$299 plus tax (4mHz) This must be the best offer available on quality tested dynamic RAM boards.

32K Assembled and tested \$289 plus tax (4mHz)

48K Assembled and tested \$329 plus tax (4mHz)

## 16K STATIC RAM SS-50 BUSS

PRICE CUT!

\$199 KIT  
A&T \$219

FULLY STATIC  
AT DYNAMIC  
PRICES



32K STATIC ALSO AVAILABLE

### KIT FEATURES


1. Addressable on 16K Boundaries
2. Uses 2114 Static Ram
3. Runs at Full Speed
4. Double sided PC Board Solder mask and silk screened layout Gold fingers
5. All Parts and Sockets included
6. Low Power Under 1.5 Amps Typical

BLANK PC BOARD - \$69 COMPLETE SOCKET SET - \$22 SUPPORT IC'S AND CAPS - \$49

## ETI 660 THE \$99 COMPUTER!
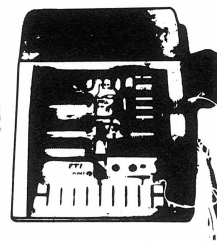
### FEATURES INCLUDE:


Colour capability, operates from optional 9V plugpack. 1K memory expandable to 3K on-board, single-board construction, cassette interface, audio output, simple to program (uses Chip 8). Expansion projects coming up include ASCII keyboard, light pen, games software, etc. Starter Kit (1K RAM, 8K Video) \$99.00. 9V, 1 amp plug pack to suit \$12.50. Colour video option \$13.50. RAM Expansion (add to PCB) \$16.00.


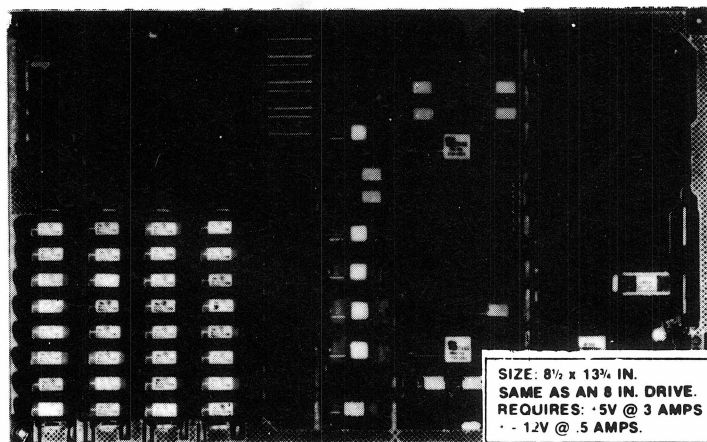
### ETI660 7 SLOT MOTHERBOARD WITH ACTIVE TERMINATION

Kit of Parts \$89.00. Assembled and tested \$115.00, inc tax. RITRON COMPUTER GRADE POWER SUPPLY, +5V Reg. 10A, ±16V Unreg. Kit of parts \$89.90 inc tax A&T \$109.00 inc tax.

Write for list of other power supplies. Tax free prices also available.



## SINGLE BOARD COMPUTER KIT NOW ONLY \$475 Including tax (\$435 tax exempt)

Also available: Blank PCB's with Roms \$275 + Tax.  
Assembled & Tested \$599 inc. tax.

THE FERGUSON PROJECT: Three years in the works, and maybe too good to be true. A tribute to hard headed, no compromise, high performance, American engineering! The Big Board gives you all the most needed computing features on one board at a very reasonable cost. The Big Board was designed from scratch to run the latest version of CP/M\*. Just imagine all the off-the-shelf software that can be run on the Big Board without any modifications needed! Take a Big Board, add a couple of 8 inch disc drives, power supply, and an enclosure, and you have a total Business System for about 1/3 the cost you might expect to pay.

**FEATURES: (Remember, all this on one board!)**

### 64K RAM

Uses industry standard 4116 RAM's. All 64K is available to the user, our VIDEO and EPROM sections do not make holes in system RAM. Also, very special care was taken in the RAM array PC layout to eliminate potential noise and glitches.

### Z-80 CPU

Running at 2.5 MHZ. Handles all 4116 RAM refresh and supports Mode 2 INTERRUPTS. Fully buffered and runs 8080 software

### SERIAL I/O (OPTIONAL)

Full 2 channels using the Z80 SIO and the SMC 8116 Baud Rate Generator. FULL RS232C! For synchronous or asynchronous communication. In synchronous mode, the clocks can be transmitted or received by a modem. Both channels can be set up for either data-communication or data-terminals. Supports mode 2 Int. Price for all parts and connectors: \$49

### BASIC I/O

Consists of a separate parallel port (Z80 PIO) for use with an ASCII encoded keyboard for input. Output would be on the 80 x 24 Video Display.

### REAL TIME CLOCK (OPTIONAL)

Uses Z-80 CTC. Can be configured as a Counter on Real Time Clock. Set of all parts: \$15

### 24 x 80 CHARACTER VIDEO

With a crisp, flicker-free display that looks extremely sharp even on small monitors. Hardware scroll and full cursor control. Composite video or split video and sync. Character set is supplied on a 2716 style ROM, making customized fonts easy. Sync pulses can be any desired length or polarity. Video may be inverted or true.

### FLOPPY DISC CONTROLLER


Uses WD1771 controller chip with a TTL Data Separator for enhanced reliability. IBM 3740 compatible. Supports up to four 8 inch disc drives. Directly compatible with standard Shugart drives such as the SA800 or SA801. Drives can be configured for remote AC off-on. Runs CP/M\* 2.2.

### FOUR PORT PARALLEL I/O (OPTIONAL)

Uses Z-80 PIO. Full 16 bits, fully buffered, bi-directional. User selectable hand shake polarity. Set of all parts and connectors for parallel I/O: \$21
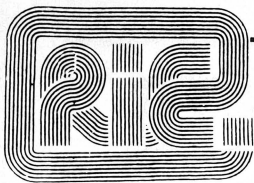
### PFM 3.0 2K SYSTEM MONITOR

The real power of the Big Board lies in its PFM 3.0 on board monitor. PFM commands include: Dump Memory, Boot CP/M\*, Copy, Examine, Fill Memory, Test Memory, Go To, Read and Write I/O Ports, Disc Read (Drive, Track, Sector), and Search. PFM occupies one of the four 2716 EPROM locations provided. It does not occupy any of the 64K of system RAM!



## FERGUSON TRANSFORMERS

### PRINTED CIRCUIT BOARD MOUNTING TRANSFORMERS

PL9/5VA	\$7.95	PL24/5VA	\$7.95	PL18/12VA	\$10.50
PL12/5VA	\$7.95	PL30/5VA	\$7.95	PL24/12VA	\$10.50
PL15/5VA	\$7.95	PL40/5VA	\$7.95	PL30/12VA	\$10.50
PL18/5VA	\$7.95	PL161/5VA	\$10.50		

### LOW PROFILE CHASSIS MOUNTING TRANSFORMERS

PL12/20VA	\$14.75	PL12/60VA	\$19.50	PL24/40VA	\$16.50
PL15/20VA	\$14.75	PL15/60VA	\$19.50	PL30/40VA	\$16.50
PL18/20VA	\$14.75	PL18/60VA	\$21.50	PL40/40VA	\$16.50
PL24/20VA	\$14.75	PL24/60VA	\$21.50	PL30-9/40VA	\$23.50
PL30/20VA	\$14.75	PL12/40VA	\$16.50		
PL40/20VA	\$14.75	PL15/40VA	\$16.50	PL30/60VA	\$21.50
PL1.5-18/20VA	\$23.50	PL18/40VA	\$16.50	PL30-9/60VA	\$25.50

### CONVENTIONAL CHASSIS MOUNTING TRANSFORMERS

PF3577	\$33.90	PF3993	\$23.90	PF4362	\$57.90
PF3783	\$79.50	PF4244	\$46.50	PF4363	\$57.90
PF3787	\$21.50	PF4354	\$49.50	PF4405	\$44.50
PF3788	\$43.50	PF4361/1	\$49.50		

### BELL TRANSFORMERS

PPB4/1000	\$15.50	PPB8/1000	\$15.50	PPB12/500	\$15.50
-----------	---------	-----------	---------	-----------	---------

### AUDIO TRANSFORMERS

MT552	\$28.50	OP590	\$46.50	OP592	\$36.90
-------	---------	-------	---------	-------	---------

### D.C. POWER SUPPLIES

PPA30C	\$12.90	PPA60C	\$12.90	PPA90C	\$12.90
PPA45C	\$12.90	PPA75C	\$12.90		

## INTERSIL LCD \$38.50 3 1/2 DIGIT PANEL METER KITS

Build a working DPM in 1/2-hour with these complete evaluation kits.

Test these new parts for yourself with Intersil's low cost prototyping kits complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter ICL7106EV (LCD).

### P.C. EDGE CONNECTORS



S100 gold plated wire wrap	\$8.50
S100 solder tail	\$7.90
D2 Motorola bus	
43 B6 solder tail	\$8.50
43 B6 gold plated wire wrap	\$11.50

### 10 TURN POTENTIOMETERS


Stock resistance values

50R 100R 200R	
500R 1K 2K 5K	
10K 20K 50K	
100K	

Spectrol model 534 + shaft	
Price 1 9	\$10.90
10 + values may be mixed	\$10.00
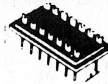
### DIP PLUGS

Ideal for use with flat ribbon cable or to mount components on 14 pin \$1.50  
16 pin \$1.90



24 pin \$2.90  
40 pins \$5

### POWER TRANSFORMERS

SPECIALLY DESIGNED FOR MICROCOMPUTERS

- Good regulation electrostatic shield
- RI 810 8V @ 10A x 15V @ 1A \$31.00
- RI 820 8V @ 20A 15V @ 1A 15V @ 3A \$37.50

### 20 TURN CERMET TRIM POT



### SPECTROL 43P ACTUAL SIZE

STOCK RESISTANCE VALUES					
10R 20R 50R 100R 200R 500R 1K 2K 5K 10K 20K 50K 100K 200K 500K 1M 2M					
1 9				\$1.80	
10 99				\$1.60	
100				\$1.30	

Values may be mixed.

### Hexadecimal Keypad \$36.50



19 key pad includes 1-10 keys ABCDEF and 2 optional keys and a shift key

Ideal for dream project

### MULTIDIALS



Dials to suit 10 T Pots	
Model 21 1 8" dia	\$18.50
Model 16 9" dia	\$13.50
Model 18 1" x 1 75" dia	\$21.50



### cermet single TURN TRIM POT

Spectrol model 63P ACTUAL SIZE


STOCK VALUES		
10R 20R 50R 100R 200R 500R 1K 2K 5K 10K 20K 50K 200K 500K 1M 2M		
1 9		\$1.20
10 99		\$1.00
100		\$0.90

Values may be mixed.

### DIP SWITCHES SPST

P N	No of Switches	Price
SD3	3	\$1.60
SD4	4	1.70
SD5	5	1.90
SD6	6	2.30
SD7	7	2.40
SD8	8	2.50
SD9	9	2.70
SD10	10	3.00

### DIP SWITCHES SPST

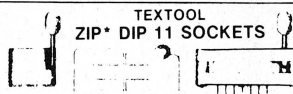

16 Pin Zip* Dip 11	\$11.50
24 Pin Zip* Dip 11	12.50
40 Pin Zip* Dip 11	17.50

\*Zero Insertion Pressure

### INCREDIBLE MEMORY AND DISC DRIVE PRICES

2708	1.9 10.25 25+
2716	4.90 4.00 3.90
2732	4.90 4.20 3.90
2732	8.00 7.50 7.00
4116 (200nS)	1.95 1.80 1.75
4164 64K Dynamic	11.00 10.00 9.50
M58725P (2K x 8)	10.00 9.00 8.50
Static	
(As used in new 64K Static \$100 PCB)	
ALL PRICES INCLUDE SALES TAX	

### DISK DRIVES

MPI 51 \$275.00 + 17.5% ST
MPI 52 \$385.00 + 17.5% ST
MPI 91 \$415.00 + 17.5% ST
MPI 92 \$515.00 + 17.5% ST

Mitsubishi 8" \$625 including tax.  
Microline 80 \$499 inc tax

### RS232 & "D" TYPE CONNECTORS

PART NO	DESCRIPTION	1 9	10 25	25+
DE 9P	9 PIN MALE	\$3.50	\$3.50	\$3.10
DE 9S	9 PIN F MALE	4.50	4.20	3.90
DE 9C	9 PIN COVER	2.20	2.10	1.90
DA 15P	15 PIN MALE	4.50	4.20	3.90
DA 15S	15 PIN F MALE	5.10	4.90	4.70
DA 15C	15 PIN COVER	2.30	2.10	2.00
DB 25P	25 PIN MALE	5.90	5.60	5.10
DB 25S	25 PIN F MALE	6.90	6.60	6.10
DB 25C	1 pc Grey Hood	2.40	2.20	2.00
DB 25C2B	2 pc Black Hood	2.80	2.70	2.50
DB 25C2G	2 pc Grey Hood	2.70	2.50	2.40
DC 37P	37 PIN MALE	7.90	7.50	7.10
DC 37S	37 PIN F MALE	10.90	9.90	9.10
DC 37C	37 PIN COVER	4.90	4.50	4.10
DH S	Hardware set (2 Pairs)	2.10	1.90	1.80

### BUILD YOUR OWN SPEAKERS WITH PHILLIPS

PART No	PRICE
AD0140T8	\$11.86
AD01610T8	\$16.95
AD01605-TB	\$16.54
AD0162-T15	\$18.78
AD0162-T15	\$13.03
AD0162-TB	\$13.77
AD0210-SQ8	\$42.00
AD02160-SQ8	\$45.00
AD02161-SQ8	\$33.46
AD010100-W8	\$52.72
AD012100-HP8	\$85.10
AD012100-M15	\$79.11
AD012100-M8	\$79.11
AD012100-W8	\$53.99
AD012200-W8	\$73.12
AD012250-W8	\$83.00
AD012650-W8	\$59.00
AD02273-T8	\$5.03
AD04060-W8	\$19.06
AD05060-SQ4	\$22.05
AD05060-SQ8	\$22.05
AD05060-W8	\$17.59
AD05061-MB	\$17.08
AD070601-W8	\$22.00
AD070620-M8	\$21.54
AD07063-M8	\$20.78
AD070630-M8	\$20.78
AD070650-W8	\$26.96
AD07066-W8	\$26.96
AD080601-W8	\$20.24
AD08061-W8	\$20.24
AD080652-W8	\$26.20
AD08066-W4	\$27.66
AD08081-M8	\$9.81
AD0910-M8	\$41.11
ADF1600-8	\$19.44
ADF500-4500-8	\$19.44

### DIODES

	10-99	100+
IN4001	6c	5c
IN4002	6c	5c
IN4004	7c	6c
IN4148	5c	4c
IN5404	30c	25c
IN5408	35c	30c
IN4007	12c	11c

### HEATSINKS

#### High Thermal Capacity Black Anodised

	1-4	5-9	10-49	50-99	100-499	500 plus
HST - 38mm	\$	\$	\$	\$	\$	\$
185	1.75	1.50	1.35	1.00	0.90	
HS2 - 75mm						
300	2.90	2.50	2.00	2.00	1.50	
HS3 - 150mm						
580	5.40	4.90	3.80	2.90	2.70	
HS4 - 225mm						
810	7.60	7.10	5.90	4.50	4.30	
HS5 - 300mm						
890	8.40	7.90	6.50	4.90	4.60	
Unanodised						
HS11 - 38mm						
140	1.20	1.00	0.90	0.80	0.70	
HS12 - 75mm						
250	2.20	1.90	1.60	1.25	1.20	
HS13 - 150mm						
490	4.50	4.00	3.20	2.45	2.40	

### BLANK CASSETTES T.D.K.

TDK ADC60	1 for \$3.60	10 for \$26.00
TDK DC60	1 for \$2.10	10 for \$18.00
TDK ODC60	1 for \$3.50	10 for \$31.00
TDK SAC60	1 for \$3.50	10 for \$31.00
TDK SAXC60	1 for \$5.70	10 for \$46.00
TDK DC90	1 for \$2.40	10 for \$21.00
TDK ADC 90	1 for \$3.50	10 for \$30.00
TDK SAC 90	1 for \$4.20	10 for \$39.00
TDK ODC90	1 for \$4.70	10 for \$45.00
TDK SAXC90	1 for \$5.50	10 for \$49.00
TDK DC120	1 for \$4.50	10 for \$37.00
TDK ADC120	1 for \$5.40	10 for \$46.50



Please debit my Bankcard.  
Bankcard No. ....  
Expiry Date ....  
Name ....  
Signature .....

Post & Pack \$2.50 small kits, heavier kits add extra postage.  
Prices subject to change without notice. Send 60c and SAE for free price list and inclusion on all future mailing lists.

MAIL ORDERS: PO Box 235, Northcote, Vic 3070. Min P & P \$1.00.  
Ph: (03) 489 8131. ERRORS AND OMISSIONS EXCEPTED

# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA. Ph (03) 489 8131 Telex No. 38897  
48-50 A'BECKETT STREET, MELBOURNE (03) 347-9251

# RITRONICS WHOLESALE PTY LTD

425 HIGH STREET NORTHCOTE 3070 MELBOURNE (03) 489-8131  
48-50 A'BECKETT STREET MELBOURNE (03) 347-9251

## "BIG BOARD II"


PARALLEL  
KEYBOARD  
PORT

SERIAL PORT NO. 1

SERIAL PORT NO. 2

DISK DRIVE CONNECTORS: ONE  
50 PIN FOR 8" DRIVE, THE OTHER  
34 PIN FOR 5 1/4" DRIVE

SASI INTERFACE

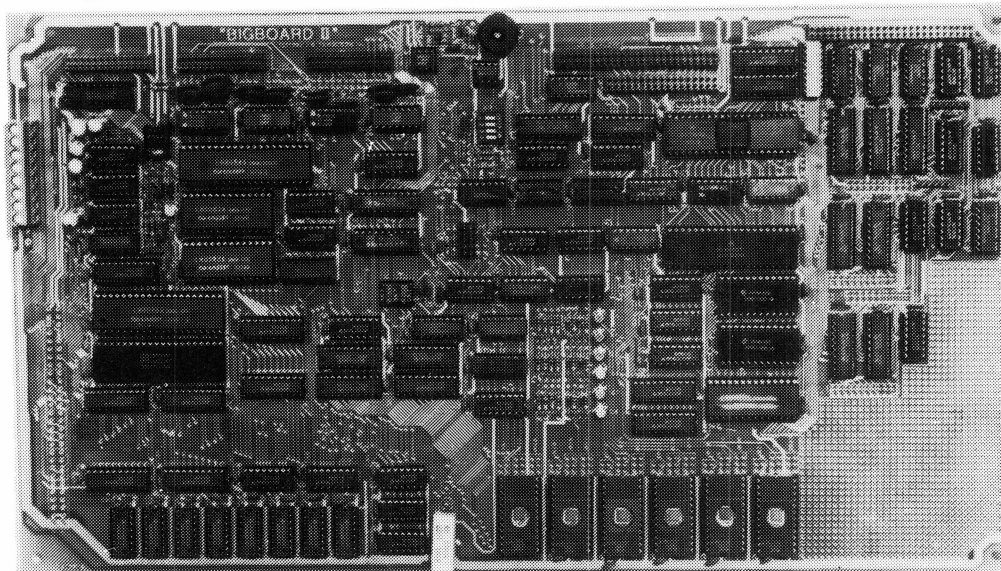

**STD  
Bus  
Connector**

**EPROMs  
shown only  
for clarity.**

**Prototyping  
Area**

**Jim Ferguson, the designer of the "Big Board" distributed by Digital Research: Computers, has produced a stunning new computer that we will begin shipping in November called "Big Board II", it has the following features:**

### **4 MHz Z80 — CPU AND PERIPHERAL CHIPS**

The Ferguson computer runs at 4 MHz. Its monitor code is lean, uses Mode 2 interrupts, and makes good use of the Z80-A DMA chip.

### **64K DYNAMIC RAM + 4K STATIC CRT RAM + 24K E(P)ROM OR STATIC RAM**

"Big Board II" has the three memory banks. The first memory bank has eight 4164 RAMs that provide 60K of user space and 4K of monitor space. The second memory bank has two 2Kx8 SRAMs for the memory-mapped CRT display and space for six 2732 As, 2Kx8 static RAMs, or pin-compatible E(P)ROMs. The third memory bank is for RAM or ROM added to the board via the STD bus. Whether bought as a bare board, a full kit, or assembled and tested, it comes with a 350 nS2732 EPROM containing the monitor.

### **MULTIPLE-DENSITY CONTROLLER FOR SS/DS FLOPPY DISKS**

The new Ferguson single-board computer has a multiple-density disk controller. It can use 1793, 1797, or 8877 controller chips since it generated the signal with TTL parts. The board has two connectors for disk signal with 34 pins for 5.25" drives, the other with 50 pins 8" drives.

### **VASTLY IMPROVED CRT DISPLAY**

The new Ferguson SBC uses a 6845 CRT controller and 8002 Video Attributed controller to produce a display that will rival the display of quality terminals. Characters are formed by a 5x7 dot matrix on 15.75 KHz monitors and 7x9 dot matrix on 18.60 KHz monitors. The display is user programmable with the default display 24 lines of 80 characters. 8002a chip supplied for 18 to 60 kHz monitors.

### **STD BUS CONNECTOR**

The Ferguson computer brings its bus signals to a convenient place on the PC board where users can solder an DSTD, bus cards can be plugged directly into it, and it can as well be connected by bus cable to industry-standard card cages.

### **DMA**

The new Ferguson computer has a Z80-A DMA chip that will allow byte-wise data transfers at 500K bytes per second and bit serial transfers via the Z80-A S10 at 880K bytes per second with serial processor overhead, though the monitor for the new computer uses the DMA chip mainly for transferring data to and from disk, the chip can readily be used for other things since its "wait/ready" pin can be connected under software control to some half a dozen signal lines. When a hard-disk subsystem is connected to the "Big Board II" via its "SASI" interface, the DMA chip makes breathtaking disk performance possible.

### **"SASI" INTERFACE FOR WINCHESTER DISKS**

The "Big Board II" implements the Host portion of the "Shugart Associates Systems Interface". Adding a Winchester disk drive is no harder than attaching a floppy-disk drive. A user simply 1: Runs a 50-conductor ribbon cable from a header on the board to any of several inexpensive controller cards for Winchester drives that implement the controller portion of the SASI interface. 2: Cables the controller to an appropriate drive, and 3: Provides power for the controller-card and drive. Since our CBIOS contains code for communication with hard-disk, that's all a user has to do to add a Winchester to a system!

### **A Z80-A S10/0 = TWO ASYNCHRONOUS/SYNCHRONOUS SERIAL PORTS**

### **A PARALLEL KEYBOARD PORT = FOUR OTHER PARALLEL PORTS USER I/O**

The new Ferguson single-board computer has one parallel port for an ASCII keyboard and four others for user-defined I/O. When the computer is powered-up or reset, the monitor looks for a carriage-return at the keyboard and serial ports. If the first carriage-return the monitor gets comes from the parallel keyboard, the monitor uses the board's video display circuitry to communicate with the user via a CRT. If the first carriage-return is typed at an ASCII terminal attached to a serial port, the monitor autobauds and makes the terminal the system console.

### **TWO Z80-A CTCs = EIGHT PROGRAMMABLE COUNTERS/TIMERS**

The new Ferguson computer has two Z80-A CTCs. One is used to clock data into and out of the Z80-A S10/0, while the other is for systems and application use.

### **PROM PROGRAMMING CIRCUITRY AND SOFTWARE**

The new Ferguson SBC has circuitry and drivers for programming 2716s, 2732(A)s, or pin-compatible E(P)ROMs. Software \$25 extra.

### **CP/M**

CP/M with Russell Smith's CBIOS for the new Ferguson computer is available for \$220. The CBIOS is available separately for \$65. Actual board size: 39.6cm x 22.2cm. 5 inch BIOS being developed. Approx price \$95.

### **Pricing and Availability:**

Availability: 2 weeks delivery.

In single quantities, full kits cost \$750.00 + tax, and A&T'd computers cost \$895. There are attractive discounts that range to 35% for OEM's and dealers. For details about them please call Rod Irving on (03) 489 7099. ie: 3 Ferguson II "Big Board" are less 20% off the one-off price, hard disks disk controllers, boxes and power supply to suit both 8" & 5 1/4" systems will be available.

Errors and omissions excepted

NOW OPEN AT 48-50 A'BECKETT STREET, MELBOURNE



# C. Itoh PRINTERS

FROM ROD IRVING ELECTRONICS

## Pro/Writer Printer 8510

**Print Features:** Number of columns—136 col. max. Print Speed—120 CPS. Print Direction—Single-directional and Bidirectional, Switch Selectable. Throughput Speed—From 44 to 152 lpm. Character spacing (max. number of columns per line)—Pica 10 CPI (80), Double Width 5 CPI (40), Compressed Font 17 CPI (136), Double Width 8.5 CPI (68), Elite 12 CPI (96), Double Width 6 CPI (48), Proportional Double Width Proportional. Line Spacing—Variable to 1/144". Print Width—203 mm (8") max.

**Forms Type: Fan Fold Roll or Cut Sheet:** Width—113 mm to 254 mm (4.5" to 10.0"). Total Thickness—0.05 to 0.28 mm (0.002" to 0.011"). Number of Copies—Original + 3 copies nominal.

**Form Feed:** Method—Tractor or Friction. Form Loading—Either rear or top.

**Interface—Serial:** Method—EIA RS232-C and 20mA (40 & 60mA switchable option) Current Loop Serial Interface. Baud Rate (BPS)—110, 300, 600, 1200, 2400, 4800, 9600. Transmitting Method—Half Duplex. Synchronization—Asynchronous.

**Interface—Parallel:** Method—TTL compatible, 7-bit, parallel interface. Control Signals—ACK, BUSY, SELECT, DATA STB, INPUT PRIME FAULT, INPUT BUSY, PAPER EMPTY. Instruction Codes—(ASCII): CR, LF, VT, FF, CAN, SO, SI, DEL, DC1, DC2, DC3, DC4, GS, RS, US, FS, EM; GRAPHIC SYMBOLS: BIT GRAPHICS.

**Error Detection:** (1) Parity (VRC)—Odd, Even, No-parity. Switch selectable. (2) Framing Error—Stop bit check. (3) Overrun Error—Error is detected when data are received before the previous data have been processed.

**Physical dimensions:** 398 mm W x 120 mm H x 285 mm D (15.7" W x 4.7" H x 11.2" D).

**Weight:** 8.5 kg (18 lbs., 12 oz.)

P\*\$855 (\$755 ex)

S\*\*\$895 (\$810 ex)

## Model 1550

The Model 1550 is a compact desk-top dot matrix serial impact printer used for data communication terminals, hardcopy of CRT displays, peripheral terminals for minicomputers and microcomputers, and small-sized business systems.

The character format is a dot matrix of 7(H) x 9(V), or 8(H) x 8(V).

Print speed is 120 characters/second. Up to 136 characters can be printed per line at 10 CPI.

Its main features are: • Compact desk-top dot matrix printer • 136-column print • Lightweight • Low power-consumption • High-quality print • Bit image graphics • Graphic Symbols • Prints in six different languages • High reliability • Low cost.

P\* \$1225 (\$1050 ex)

S\*\* \$1275 (\$1195 ex)

## F-10 Printmaster Daisy Wheel Printer

**Print Speed:** 40 CPS. **Print Method:** Static Print Impact. **Number of Printable Columns:** 136, 163, Variable. **Character Spacing:** 1/120 Inch (minimum). **Line Spacing:** 1/48.

**Return Time:** 900 msec. **Line Feed Time:** 40 msec. **Paper Width:** 406 mm (maximum).

**Print Characters:** 96. **Printwheel:** Industry Standard 96 Character Wheel. **Interface:**

Industry Standard 8-bit Parallel, RS232-C Compatible, X-ON, X-OFF, 12-bit Qume and Diablo Compatible. **Dimensions:** 574 mm W x 405 mm d x 153.5 mm H (22.5" W x 15.9" D x 6" H). **Weight:** 14 kg (30.8 lbs.) with cover and power supply. **Noise:** Less than 65 Db (1M from Platen, A Scale).

P\* \$1600 (\$1450 ex) \* Parallel Interface \*\* Serial Interface

S\*\* \$1750 (\$1510 ex)

ERRORS AND OMISSIONS EXCEPTED

Extra Special Microline 80  
\$499 incl. tax \$435 tax exempt  
While stocks last

# RITRONICS WHOLESALE

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131.

NOW OPEN AT 48-50 A'BECKETT STREET, MELBOURNE (03) 347 9251

TO ORDER: Heavy items sent Skyroad Freight on Mail Order Phone 481-1436. Wholesale Customers Phone: 489-7099. Mail Orders to RITRONICS WHOLESALE, P.O. Box 235, Northcote 3070. Minimum P&P \$2. Add extra for heavy items, registration and certified mail. Prices and specifications subject to change without notice.

Bankcard mail orders welcome  
**ORDER FORM**  
Please Debit my Bankcard  
No. ....  
Expiry Date .....  
Name .....  
Signature .....

WE NOW HAVE 2 LOCATIONS IN MELBOURNE



# SERIES 5000

As designed by ETI

## PREAMPLIFIER

### SPECIFICATIONS

Frequency response:

High-level input: 15Hz-130 kHz, +0, -1 dB Low-level input — conforms to RIAA equalisation,  $\pm 0.2$  dB

Distortion:

1kHz <0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation).

S/N noise:


High-level input, master full, with respect to 300 mV input signal at full output (1.2V): >92 dB flat >100 dB A-weighted.

MM input, master full, with respect to full output (1.2V) at 5 mV input, 50 ohm source resistance connected: >86 dB flat >92 dB A-weighted.

MC input, master full, with respect to full output (1.2V) and 200  $\mu$ V input signal: >71 dB flat >75 dB A-weighted.



## POWER AMPLIFIER

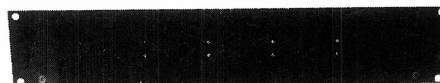

Please note that the "Superb Quality" Heatsink for the power amp was designed and developed by Rod Irving Electronics and is being supplied to other kit suppliers. This product cost \$1,200 to develop so that your amplifier kit would have a professional finish as well as sound. We also have a new range of rack mounting boxes which will be released soon.

### SPECIFICATIONS

Power output:

100W RMS into 8 ohms ( $\pm 55$  V supply).

Frequency response:

8 Hz to 20 kHz, +0 -0.4 dB 2.8-Hz to 65 kHz, +0 -3 dB. NOTE: These figures are determined solely by passive filters.

Input sensitivity:

1V RMS for 100W output.

Hum:

-100dB below full output (flat).

Noise:

-116 dB below full output (flat, 20 kHz bandwidth).

2nd harmonic distortion:

<0.001% at 1 kHz (0.0007% on prototypes) at 100 W output using a  $\pm 56$  V supply rated at 4 A continuous. <0.003% at 10 kHz and 100 W.

3rd harmonic distortion:

<0.0003% for all frequencies less than 10 kHz and all powers below clipping.

Total harmonic distortion:


Determined by 2nd harmonic distortion (see above).

Intermodulation distortion:

<0.003% at 100 W. (50 Hz and 7 kHz mixed 4:1).

Stability:

Unconditional

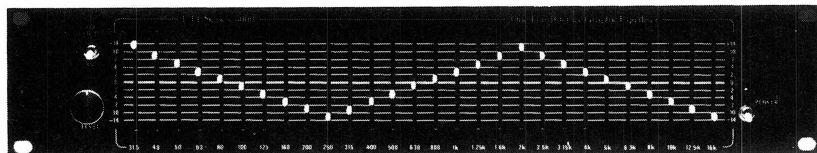

### EXTRA FEATURES OF OUR KITS POWER AMPLIFIER

KIT PRICE \$299 P&P \$8.00

- 1% Metal Film Resistors are used where possible
- Prewound Coils are supplied
- Aluminium case as per the original article
- All components are top quality
- Over 200 Kits now sold
- We have built this unit and so know what needs to go into every kit.
- SUPER FINISH Front panel supplied with every kit at no extra cost to you.
- We are so confident of this kit that we can now offer it assembled and tested so that people who do not have the time can appreciate the sound that this amplifier puts out. This is done on a per order basis delivery approx. two weeks after placement.

only \$425

\*All parts available separately for both kits.

### PREAMPLIFIER

KIT PRICE \$259 P&P \$8.00

- 1% Metal Film Resistors are supplied
- 14 metres of Low Capacitance Shielded are supplied (a bit extra in case of mistakes)
- English "Lorlin" Switches are supplied no substitutes as others supply
- We have built and tested this unit and so know what needs to go into every kit
- Specially imported black anodised aluminium knobs
- Again as with the power amp we are offering this kit A & T at a price which we do not believe there is a commercial unit available that sounds as good. Same delivery as the P.A.

only \$425

## THIRD-OCTAVE GRAPHIC EQUALISER

### SPECIFICATIONS

Bands:

28 Bands from 31.5 Hz to 16 kHz

Noise:

<0.008 mV, sliders at 0, gain at 0 (-102 dB),

20 kHz bandwidth

Distortion:

0.007% at 300 mV signal, sliders at 0, gain at 0; max. 0.01%, sliders at minimum.

Frequency Response:

12 Hz-105 kHz, +0, -1 dB, all controls flat.

Boost & Cut:

14 dB

1 UNIT \$189

2 UNITS \$359

ERRORS AND OMISSIONS EXCEPTED.

# ROD IRVING ELECTRONICS

425 HIGH STREET NORTHCOTE 3070 MELBOURNE (03) 489-8131  
48-50 A'BECKETT STREET MELBOURNE (03) 347-9251

# COMPUTING TODAY

## 'Dazzling' growth predictions for modems and interfaces

Only about 15% of today's personal computer users are equipping them with modems or other data interface devices, but this will soon go to 100%, according to a new report from International Resource Development Inc, a specialised US market research firm.

The report projects 'dazzling' growth in markets for local network interfaces, 1200 bps modems and other interface devices for the 'new generation' of personal computers and office workstations.

Demand in the US market will more than double in the next two years, according to the report, with 'spectacular action' in the full-duplex 1200 bps sector as personal computer users move up to 1200 bps from the 300 bps which most of them use today. The IRD researchers expect this demand to be satisfied by 212-A-compatible modems which provide full-duplex 1200 bps operation over a two-wire telephone loop. However, the report points to developments in Europe, related to demand for videotex modems, which could result in the availability of low-priced chips which are not compatible with the 212-A protocols popular in the US.

Major factors in stimulating the consumer market for modems and interfaces will be the increasing attractiveness of consumer orientated information and transaction services, such as bank-at-home and tele-shopping services. According to IRD, by the end of the decade more than half of all routine banking transactions will be conducted either from the home or from variously-located automatic teller machines. Tests during the past two years, conducted by more than twenty banks in the US, have shown that the convenience of paying bills, switching deposits etc, from home is a major attraction to the upper-income banking customer

who hates standing in line for a teller.

With today's telebanking services being operated from home computers, and tomorrow's perhaps using videotex/TV terminals, the position of specialty terminal suppliers has become 'tenuous', according to IRD. Banking-orientated terminals may lose out to low-cost personal computers from Timex/Sinclair, Atari, Texas Instruments and, eventually, IBM.

IRD says that, in the US, there will be three million personal computers in place by the end of 1983, with about two million of them in the hands of consumers and the other million in businesses and schools.

In the office automation market it will be access to electronic filing systems which will be a major stimulant to the use of modems and local network interfaces, including the Ethernet protocol and the emerging TI/IBM baseband network technique. One of the factors leading to the rapid introduction of electronic filing will be the continued trend towards rapid increases in the storage capacity of magnetic disc systems, and the possible introduction of optical-disc-based electronic filing systems as soon as 1984.

Pointing to the continued development of digital networks, such as the packet-switching networks from GTE Telenet and Tymnet and the value-added Net/1000 soon to be introduced by AT&T's American Bell unit, the IRD report points out that these networks still required interface devices.



### HP's 16-bit personal computer

A personal technical computer, the HP Series 200 Model 16, is Hewlett-Packard's first 16-bit personal computer.

Its 16/32-bit processor, 8 MHz system clock and software power provide very fast program execution.

It consists of a 229 mm diagonal CRT, a detached ASCII keyboard and a choice of single or twin 3½-inch microfloppy drives, each with 270K memory. A single

microfloppy is also available with a 4.6M Winchester hard disk.

The Model 16 has a standard 128K memory, built-in graphics and is available with BASIC, HPL and Pascal language systems. Numerous HP applications software packs are available.

For further information contact Hewlett-Packard, 31-41 Joseph St, Blackburn Vic. 3130. (03)890-6351.

### IBM to purchase 12% stake in Intel

The computer firm IBM Corp., one of Intel's largest customers, will acquire a 12 per cent stake in Intel Corp. for US\$250 million.

The sale will make IBM Intel's largest single shareholder, surpassing Intel board chairman Gordon Moore, whose shares currently represent 9.8% of the company.

Under the terms of a deal, which is subject to review by the Justice Department or Federal Trade Commission, IBM will purchase 6 250 000 unregistered shares of stock at US\$40 a share and will have the option to extend its position to 30% in future private buys. The upper limit, however, can be renegotiated by mutual agreement eight years after the stock sale takes place.

As part of the agreement,

Intel's ten-member board of directors will be expanded by a single seat to be filled by a representative of IBM. According to the two firms, the IBM director will be 'excused from deliberations in which there is a potential conflict of interest as judged by the director or Intel'.

Industry observers see IBM's unprecedented move as an opportunity for Intel to resolve a cash shortage problem and an opportunity for IBM to assure the continued well-being of a semiconductor firm on which it is becoming increasingly dependent for microprocessors, memory parts and MOS technology. ●

# WHY PAY MORE?

BUY AT DICK SMITH'S  
DIRECT IMPORT  
PRICES - JUST  
LOOK AT THESE



GIVE  
THEM A  
HEAD  
START

SAVE  
HEAPS

## SYSTEM 80 MEANS BUSINESS!

Keep the cash coming in with  
Dick Smith's Invoicing  
System

**\$99**  
WAS \$199

This package runs either as a stand alone or interactively with your Stock Control & Pricing system. It provides full invoicing session summary reports, including sales tax & revenue totals. Allows for credits or returned items & even allows a mix of items being returned for credit with items being sold. Cat. X-3751



### General Ledger

**\$149**  
WAS \$299

Lets you know exactly how your business is running & provide the necessary information to make business decisions based on accurate reports, as to your company's status. Cat. X-3752

### Accounts Receivable

This package gives you the vital information concerning the 'heart' of your business, i.e. cash flow. Produces reports such as the Trial balance, Debtors ledger, & Posting summaries. Cat. X-3756

### Payroll program

Now even small business (up to 100 employees) can 'go computer'! This program produces payslip, coin/cheque analysis, bank deposit advice, payroll tax report and group certificates, as well as catering for different deductions, hourly pay/monthly salary, cash/cheque or deposits, etc. Cat. X-3769

### Stock Control & Pricing

Handles up to 2750 stock lines & offers powerful features like Aust. Sales Tax Option, ability to produce up-to-date price lists at any time, a facility to print out of stock count sheets & compare counts with 'on hand' figures. Cat. X-3750



**\$149**  
WAS \$275



**\$149**

**STOCK  
UP NOW!**

### SPDT Microswitch

this unit is a must where a positive snap action is required. Complete with 16mm actuator paddle. Cat. S-1920  
FEATURES: 240V AC 10A contact rating. Body size: 10.5mm x 28mm. Quick connect terminals

Great for burglar alarms or as machinery limit switches

**\$1.80**  
only  
10 or more \$1.60 each



DICK SMITH'S  
COMPUTERS  
FOR KIDS  
SYSTEM-80 EDITION  
EASY TO LEARN, EASY TO USE

## Dick Smith's Computers for Kids

A basic programming manual written just for kids! Written by an experienced teacher, it talks in a language the kids can understand. Cat. B-6190


**\$4.95**  
only
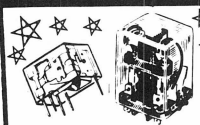
## GIVE YOUR PROJECTS A PROFESSIONAL FINISH! Panel Lettering Set



Each pack contains hundreds of words, letters, numbers & symbols for quick easy labelling of electronic equipment. These are transfer sheets that are easily applied by burnishing.

Size 1 (3.1mm high) Black lettering  
Cat. N-1800 ..... **\$5.95**  
Size 2 (2.3mm high) Black lettering  
Cat. N-1804 ..... **\$5.95**  
Size 2 (2.3mm high) White lettering  
Cat. N-1806 ..... **\$5.95**



### Quality Relays

#### Ultra Miniature PCB Mounting

Low cost miniature relay for projects with little room to spare. Fits standard 2.54mm matrix. Cat. S-7112  
Contact Current (max.): 1A  
Contact Voltage (max.): 100V AC  
Nominal Coil Voltage: 12V  
Coil Resistance: 320 ohm


**STOCK  
UP NOW**

#### High Rating Power Relay

Small high capacity relay ideal for power switching. Great for switching 240V projects from transistor or IC control. Cat. S-7200  
Contact current (max.): 10A  
Contact voltage (max.): 240V  
Nominal coil voltage: 12V  
Coil resistance: 160 ohm

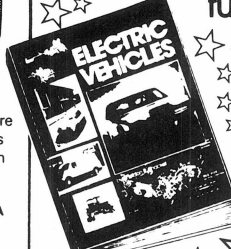**\$9.75**

Electric vehicles viable in the future? Find out in this fascinating book



Understand this new and exciting field! 168 pages, a book about the past, present and future of electric cars, bike etc. Cat. B-2400

**\$9.95**  
only

## SCOOP PURCHASE PCB SPECIAL

Pre-cut quality PC boards with permanently bonded copper on both sides. Double sided 28 gram laminate. 550 x 150mm Cat. H-5561

**\$3.10**  
only

## Transformer Bargain

Model M-0146  
240V AC primary, secondary 20-0-20 @ 1.25A (1.25A @ 40V) Used in the twin 25 Playmaster Amplifier Kit. Cat. M-0146

**\$19.50**  
only



## KEEP YOUR HEADS DEMAGNETISED


Ideal for use with all audio tape recorders. Simply plug into 240V AC and use like a wand to 'sweep' away excess magnetism! Cat. C-7222

ESSENTIAL FOR  
ALL HI FI BUFFS **\$7.75**  
only

## KNOW THE TIME ANYWHERE IN THE WORLD!
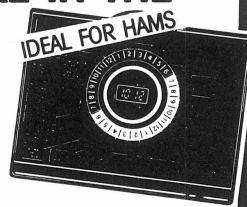
### LCD WORLD CLOCK

Great for radio hams, telephonists, international businessmen or anyone who wants to know the time anywhere in the world! Has LCD & an easy to read scale dial. Cat. Y-1054



**\$14.95**  
Value

## 12V Power Supply

For any equipment requiring 12V DC at a max. of 200mA. Simply plugs into any 240V AC outlet. Suggested uses would be with handheld transceivers when used as base stations & the older type portable radio that worked on 12V DC etc. Cat. M-9550



**FULLY APPROVED**

**\$12.95**  
only

**DON'T BE FOOLED  
BY OUR LOW PRICE!**



**HIGHLY  
ECONOMICAL FOR  
BEGINNERS**

**WAS \$149**

**SAVE  
OVER  
\$50**

This is a  
**genuine discriminating  
detector under \$150**

Highly recommended for beginners, this amazing  
unit separates trash from treasure. Light weight,  
handy and very easy to use. Cat. Y-1066

**FIND YOURSELF A  
FORTUNE FOR \$99  
ONLY**

**BUILD AN  
ALARM  
FROM THIS  
SIREN  
SPEAKER**

A neat horn type speaker  
with electronic siren module  
built-in. It delivers an ear-  
splitting penetrating wail  
that can be heard for blocks.  
It's weatherproof, so it can  
be indoor or outdoor.  
Operates from 12V.  
Cat. L-7026

**only  
\$27<sup>95</sup>**



**WHY PAY MORE?**

**Quality Stainless Steel Tools  
DICK SMITH PRICES!**

Resists rust, spring load return,  
insulated, easy grasp hand grips.

**Transister Nipper**

Ideal for PCB work, long life, cutting  
edge. Cat. T-3205

**Mini Flat Nose Plier**


Great for those small nuts.  
Cat. T-3325

**Mini Needle Nose Plier**

Ideal for small components,  
confined places. Cat. T-3570

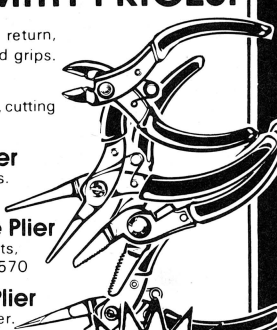**Mini Long Nose Plier**

Long reach in a small plier.  
Cat. T-3565



**DIRECT IMPORT  
YOU REAP  
THE BENEFIT!**

**ALL ONE  
PRICE**

**\$7<sup>75</sup>**

**BUILD YOUR  
OWN MINI-  
SYNTHESIZER**

**The  
Incredible \$45  
Electrochune**

**WAS  
\$75**

The Electrochune is a keyless monophonic organ and  
uses the circuitry of a synthesizer to give variable  
attack/decay times, tremolo and square/sine wave  
output mixing. It even has a built-in amplifier and  
speaker with separate volume control. Complete  
with plugpack and full instructions. Cat. K-3506

**YOU REAP  
THE BENEFIT!**



**FORTAN FOR YOUR  
SYSTEM 80**

**Microsoft Fortran - 80**  
Ideal for science & engineering applications, Fortran  
has become one of the most widely used programming  
languages ever. Fortran code is exceptionally fast,  
compact & modular. Includes full ANSI standard  
Fortran X3.91966, except the COMPLEX data type.  
Requires 32K, disk based. Cat. X-3669

**\$199**

**MMS FORTH V2.0**

You can customize & expand FORTH into virtually any  
language you like - yet it runs from 10 to 20 times  
faster than the ROM BASIC! Comes with excellent  
documentation; on disk, with its own DOS (written in  
FORTH!). Minimum 16K and one disk drive. T1, S1,  
S2. cat. X-3668

**\$199**

**OLD FASHIONED  
QUALITY**

**High  
Impedance  
Mono H' phones**

Magnetic - high impedance. Ideal for  
your crystal set. As used by spies  
everywhere! Cat. C-4000

**only \$7<sup>95</sup>**



**Tag Tantalums  
from only**

**55¢**

These are resin dipped electrolytic type.  
They offer very low leakage and a high  
capacitance in a tiny package. Ideal for  
PC board mounting.

Value in UF	Voltage	Cat. No	Value in UF	Voltage	Cat. No.
0.1	35	R-4700	4.7	35	R-4740
0.22	35	R-4705	6.8	35	R-4745
0.33	35	R-4710	10	25	R-4750
0.47	35	R-4715	15	16	R-4755
1.0	35	R-4720	22	16	R-4760

**STOCK UP  
NOW!**

**ALL ABOVE TANTALUMS:**

From 0.1uF to 6.8uF 60c 10 up 55c  
From 10uF to 100uF 70c 10 up 65c

**20 TIME ZONES**

**WORLD TIME  
DUAL MELODY  
ALARM**

Tell the time anywhere in the  
world! This fantastic watch  
not only displays local time  
but 20 different time zones  
as well.

- Dual melody alarm
- LCD displays date, alarm,  
home time & 20 different  
world times.
- World graphic display
- Night light

Great for the businessman,  
amateur radio operator or  
anyone who wants to know  
the time around the world.




**\$49<sup>50</sup>**

**AUDIO  
ENTHUSIASTS**

**TAPE  
DUB BOX**

An easy way for the tape  
buff to get the results he  
wants without miles of  
cords, plugs & mess!  
Simply switch between the  
inputs & outputs required!  
Cat. C-7220

**only  
\$23<sup>95</sup>**

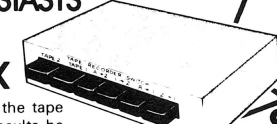

**SYSTEM 80 MAKES  
MUSIC**

**FRED  
SOUND  
SYNTHESIZER**



**only  
\$149**

Give your System 80 the ability to produce  
music with this sound synthesizer, it just  
plugs directly into the expansion connector  
with the audio output connecting directly  
into the AUX, TAPE or TUNER facilities of  
most Hi-Fi amplifiers. Cat. X-3280

**RESISTANCE  
SUBSTITUTION  
WHEEL  
only**

**\$4<sup>95</sup>**

Convenient size with large, easy to read  
value selection that enables you to  
select values from 5 ohms to 1M ohm in  
36 steps using most common divisions.  
Complete with leads & insulated  
crocodile clips. Cat. Q-1410



**Matte Black Spray**

This quick drying matte finish  
spray. Suitable for giving your project  
that professional finish. Ideal for  
spraying heatsinks to increase  
thermal efficiency. Pressure pack can. Cat. N-1070

**\$2<sup>90</sup>**

**DICK SMITH  
Electronics**

**Incorporated  
in NSW**



NSW Auburn 648 0558 - Bankstown Sq. 707 4888 - Blakehurst 546 7744 - Bondi Jct. 387 1444 -  
Broadway 211 3777 - Brookvale 93 0441 - Chullora 642 8922 - Gore Hill 439 5311 - Liverpool  
600 9888 - North Ryde 888 3200 - Parramatta 689 2188 - Sydney (Bridge St) 27 5051 - Sydney (York  
St) 290 3377 - Tamworth 66 1961 - Tighes Hill 61 1896 - Wollongong 28 3800 ACT Fyshwick 80 4944  
VIC Coburg 383 4455 - Frankston 783 9144 - Geelong 78 6766 - Melbourne 67 9834 - Richmond  
428 1614 QLD Brisbane 229 9377 - Buranda 391 6233 - Chermide 59 6255 SA Adelaide 212 1962 -  
Darlington 298 8977 - Enfield 260 6088 WA Perth (William St) 328 6944 - Perth (Hay Street) -  
Cannington 451 8666 TAS Hobart 31 0800

MAIL ORDER CENTRE: PO Box 321, North Ryde, NSW 2133. Phone: (02) 888 3200. Prices correct and stock  
COMPUTER HOT LINE: (02) 888 2002. available at press time

## EPROM memory for HP-41C/CV

An EPROM based ROM emulator, independently manufactured in the USA is now available in Australia.


Known as the HHP-16K it is a ROM emulator device designed for use with the Hewlett-Packard 41C/CV calculator hand-held computer. It offers large scale program storage of 4K, 8K or 16K and when plugged into any port it is directly accessed like any standard ROM.

The HHP-16K is 147 mm x 91 mm x 28 mm and is HP-41C/CV powered having a very low power requirement. On disconnection there is no program loss.

Three ZIF (Zero Insertion Force) sockets are used to hold the EPROMs which are a combination of type 2716, 2732 and 2764. The EPROM box address is DIP switch selectable.

An EPROM burning service is available for the transfer of programs from HP-41C/CV cards or cassette storage systems.

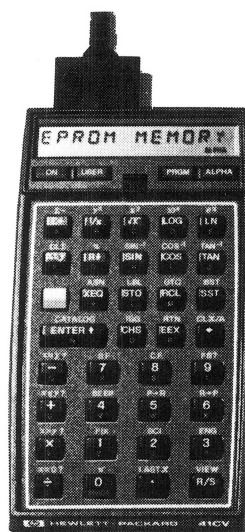Enquiries can be made to Dataprom Pty Ltd, P.O. Box 476, Hurstville NSW 2220. (02)587-9701.



## Atari troubled, to phase out Model 400, introduce 64K Model 1200XL

Despite predictions that the US personal computer industry will crack US\$3 billion turnover this year, Atari seems to have fallen back from the crest of the wave and will restructure its computer lines this year.

Commodore and Texas Instruments cut Atari's lead in the home computer market last year, the VIC-20 being the highest selling unit in the US now. TI's late introduction of the TI 99/4A last year further eroded Atari's hold in the low price end of the market.

In mid-December, Atari's Home Computer Division announced it would open additional manufacturing facilities in the Far East and add more production shifts to its California plant to give it more leverage in the home computer market currently experiencing a round of sharp price reductions.

Competitive strategems being effected include: • price cuts for the models 400 and 800; • phase-out of the 400 in favour of an updated model; • introduction of its anticipated Model 1200XL.

It seems that aggressive pricing by the competition has been a major factor in the demise of Atari's share in the US home

computer market. Atari has held back from dropping the price of the 400 in order to avoid infringing on its video games market and to help recoup comparatively high costs.

The Model 400 now sells for US\$200, directly against the TI 99/4A and VIC-20. The 400 is expected to be phased out later this year, but no details of an 'upgraded' replacement are available at present.

The Model 1200XL commenced shipping in January and was expected to retail around the US\$900 mark. It is a 6502-based machine with 64K of RAM, a full keyboard plus 12 user-function keys and a self-diagnostic program.

The 1200XL has one-touch cursor control, 256-colour availability, four 'voices' that cover 3½-octaves plus two controller ports for joysticks, paddles and a numeric keypad. Australian release was not known at press time.

## QT Computer Systems 16-bit computer

QT Computer Systems has released its first 16-bit microcomputer system with the 8086 microprocessor.

This system comprises 128K to 256K of RAM, two RS232 communication ports with selectable baud rates of 75-19.2K bps, one parallel printer port, floppy disk controller and hard disk controller.

It features a fully integrated

380 mm green phosphor CRT with anti-glare filter, 66 lines x 80 characters per line and includes BASIC, CIS COBOL and CBASIC 86. WordStar and various other application programs are also available.

For more information on this system contact QT Computer Systems, 41 Sydney St, Marrickville NSW 2204. (02)519-2680.

## New agent for Ye-Data floppy disk drives


Software Australia has been appointed as an agent for Ye-Data products and is marketing 125 mm (five inch) and 200 mm (eight inch) drive ranges.

The company will concentrate sales on the YD-180 eight inch slimline and YD-174 normal size eight inch drives. Both drives have a three millisecond track-to-track stepping rate and will support single and double-density, single and double-sided operation using the latest technology steel band positioner.

Software Australia says that it has developed an attractive price schedule for all end users, from OEMs to single purchasers.

Ye-Data will also market, through Software Australia, the YD-274 5¼" double-sided, double-density floppy disk drive this year. The larger capacity 80 track YD-280 and the YD-380T will follow soon.

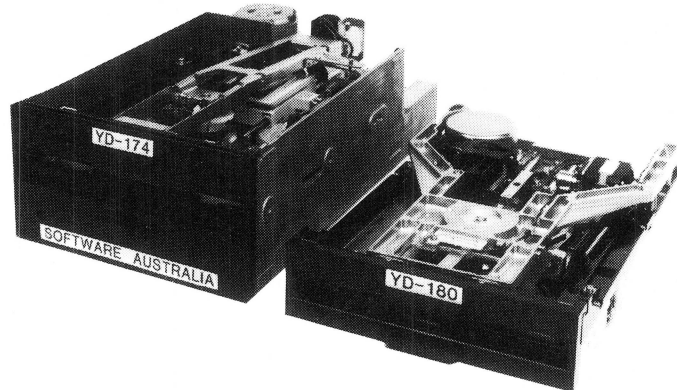Any company interested in Ye-Data products should contact Software Australia, 2 Somerfield St, Mt Gravatt Qld 4122. (07)349-9122.



## Floppy disk controller kit

The SYM-1 Users Group in the US have released an economical floppy disk controller kit for the SYM-1 and AIM-65.

Designed by Synertek Systems, the kit features quality through-plated holes, solder mask, silk screened pcb with sockets for all ICs and a disk drive cable.

Called the PER-SYM-ONE it is capable of supporting two

double-sided density 5¼" disk drives for a total of 640K bytes. It connects directly to the SYM-1 Econnector or may be installed in a motherboard under the SYM. A 2K SYM DOS on EPROM is provided with a complete source listing. The DOS allows saving and loading of programs using SUPERMON, BASIC and RAE. Additional utilities are provided.

These kits are available from Energy Control, P.O. Box 6502, Goodna Qld 4300. (07)288-2757.

# JUNK SALE

The Boss has a weird sense of humour, as you'll see when you look through the list of boards and equipment below.

One of our suppliers, SME Systems, has just finished a major upgrade on 200 Government installations and we've got hold of this good gear for a song.

Don't be fooled by the prices. It's good quality gear most systems engineers would give their eye-teeth to have.

Look at this .....

## TEAC DIGITAL TAPE DRIVES T-2-24\*

We have 50 brand new 2-track drive + controller units with 760K bytes, 15" ips read write, 45 ips search mode, 75 ips rewind. 24bps data transfer rate. On-board LSI, intelligent controller. Needs parallel port interface, +5v/+12v power supply. New price \$600 + tax. Our Price \$490.

## SHUGART SA 400 FLOPPY DRIVES\*

We have 60 of these 5 1/4" drive in excellent condition for a magic price. \$250 each.

## DRC-II\*

The state-of-the-art S-100 memory card, with bank select, supports 64K to 256K bytes of Dynamic memory. Operates up to 4MHz. We have 30. Save \$\$\$\$\$. New price \$600. OUR PRICE \$297.

## GP-100 CARDS\*

General Purpose S100 card. Has 2/16 channel multiplexed inputs for use in keyboard encoding etc., on-board Real Time Clock Calander, buzzer, driver, 4 on-board sockets for 2K CMOS RAM or 4K Eproms; power-fail detect, on-board Ni-cad battery & recharge circuitry; 8-way switch on parallel port for option selections. Software write/protect. Our bargain price \$150.

## S100 EXTENDER/TERMINATOR CARDS

We have 17 of these at the steal price of \$40 ea.

## 16-KEY KEYPADS\*

20 units unencoded with pin-out to suit GP-100. \$30ea.

## 4" MUFFIN FANS\*

We have 60 of these 240v fans for the steal price of \$10 ea.

## S-100 HEAVY DUTY POWER SUPPLIES\*

8v @ 5amps, 15v @ 2amps, -18v @ 2amps, +12v @ 5amps. Complete with extruded heat sink, regulators, capacitors and connectors. Our unbeatable price \$75 ea.

11-Slot S-100 Mother Board  
Our Price \$30  
SD Systems 2708/2716 Eprom Card 16/32K, fully address selectable. (1 only). Our Price \$80.

## SME 2708 16K EPROM CARDS

Switch selectable for 8K, full address decodable. Our Price \$40.

## SD SYSTEMS MPB-100

Z80 CPU Card  
4MHz, 2k Eprom on board, front panel interface.

A steal for \$135

## CCS 16K STATIC RAM CARDS

S-100, bank select. Our Price \$195

## FDC-I

Single-density floppy disk controller. Suits single/double-sided 5 1/4 or 8" drives. Handles up to four drives. Our Price \$185

MEE/T Eprom Eraser, inbuilt timer takes 9 chips. Erases in 20/30 mins. Our Price \$95.

## S100 WIRE WRAP CARD.

Double-sided & reflow soldered and gold-plated edge connectors. Buy and save. \$32.

## S-100 11-SLOT CARD CAGE & POWER SUPPLY

19" Bench mount \$425  
Rack Mount \$385  
Mini 5-card \$130

## SD SYSTEMS MPC-41/O CARDS

On-board processors, 4 serial ports. Manual supplied. New \$700. Supplied 'as is' condition. Price \$150

## CENTRAL DATA S.B.C. KIT

Features 2650 Microprocessor, video display 80x16 lines, 2K on-board. RAM; 4K ROM, Kansas City standard cassette Interface.

Keyboard Port, Cassette Control Port, Monitor in ROM. All lines buffered & expandable to S-100 bus. Includes software on tape — ED/ASM, ALP,

Basic, Debugger, includes h/ware & s/ware manuals, and software sources. Package price \$200.00

K-NAR also stock a full range of the latests S-100 boards. Write to us today for a full list of product data sheets.

Items marked with \* are sales tax exempt. For other items add 20% sales tax were applicable. All prices plus freight (\$3.50 minimum).

# K-NAR

## COMPUTER CARDS

PO Box 412, Dandenong, 3175 Phone (03) 795 5858  
Authorised distributor of SME System products.

### To K-NAR Computer Cards

Please send me product data sheets.  
(I enclose 4 stamps).

I wish to order

My cheque/order form is enclosed

Please debit my Bankcard No.

Name

Address

Signature

Please include me on your new product mailing list. I am mainly interested in systems for ☐ Hobby, ☐ Industrial use ☐ Education ☐ Business ☐ Process control ☐ Other

## The Sun comes up in Australia

It was no coincidence that the TCG Group announced it had been awarded the Australian distribution rights for the Sun computer graphics workstation at the same time the movie 'E.T.' began screening in Australia.

'E.T.', the latest box office success from Steven Spielberg, used the facilities of Lucas Films in the creation of special effects, for video editing, previewing and control of video equipment, editing machines and video disks. Lucas Films has 18 Sun systems which it uses for production and control work. Filmmaker George Lucas and Spielberg, in collabor-

ation, have produced some of the world's highest grossing and most successful films.

The Sun system provides individual users with the power of a mini on their own desks. Networking means there is no degradation or downgrading of performance in a multiple user situation because each has his own processor.

The system has powerful graphics capabilities with high quality resolution. The system can be upgraded at a relatively low cost with additional workstations, as disk based units or networked together. It offers a network system to support such diverse applications as CAD/CAM, engineering and robotics as well as the graphics arts, typesetting, office automation and executive administration.

An integral Ethernet local area network connection provides a high speed interface (one million characters per second) and an advanced user interface

includes high resolution bitmap graphics capability, a 'mouse' pointing device for graphic input and a powerful Motorola 68000 microprocessor which operates at 10 MHz with no wait states. It is claimed to be as powerful as a VAX II/780 for non-floating point work.

Using the Intel Multibus as the I/O bus, the Sun workstation is expandable with a variety of peripheral controllers and off-the-shelf board level components.

For more information contact the TCG Group, 30 Balfour St, Chippendale NSW 2008. (02) 699-8300.

## Sinclair ZX software

Gloster Software has added to the range of software available for the ZX81 and ZX80 8K computers.

The 'Household Management Pack' features a budget system which not only allows for inflation and other changes in income and expenditure over time, but makes possible introduction of irregular variations, seasonal items and once-only items. It can handle up to 255 entries. After simulating transactions over a given period, the user is told how to maximise investments in common maturity terms based on the resultant cash flow.

The system is readily expandable as the data used is saved separately from the programs. Also included in the pack is a planner diary generator which enables the family to keep track

of each other's activities and avoid engagement clashes, allowing three time periods per day. It requires 16K RAM and a printer is helpful but not essential.

Gloster Software has also expanded its 'Data Pack'. Besides allowing data manipulation and taped data files, program merging, line re-numbering and bulk line deletion, the system now features a command to verify program saving.

Other new items include 'ZX Space Trek' (ZX81 only) and 'Casino' (four game pack).

Enquiries should be made to Gloster Software, P.O. Box 5460CC, Melbourne Vic. 3001. (03)232-2398 ah.

## Atari gets bar on Commodore stick

In the US, Commodore Business Machines, manufacturer of the Vic-20 computer, have been barred from making and distributing joystick controllers which imitate the controller developed by Atari for its Video Computer Systems and home computers.

So Atari has won the first round in its patent infringement suit against Commodore. Shortly before the US District Judge handed down his decision Atari and Commodore reached an agreement that Commodore would temporarily suspend manufacturing and wholesale sales of its Vic-20 joystick controllers. Commodore did not

admit to any wrongdoing in signing the agreement.


Commodore said that it has redesigned its Model 1311 joystick and has been marketing the altered version with adjustments. But Atari considers that this is also a patent violation and is seeking action against Commodore for making and marketing it.

## 32K BYTES FOR THE ZX81

### SPECIAL RAM PACK FOR THE ZX81

This board uses dynamic RAM chips for lower cost and lower power consumption. Simply plugs into the ZX 81 expansion port offering 32K BYTES for basic programmes and data handling. No extra PSU required. Extra memory to help you build your ZX81 into a powerful microprocessor system at an affordable price. Compare the price with other RAM PACKS available on the market!

# VENDALE

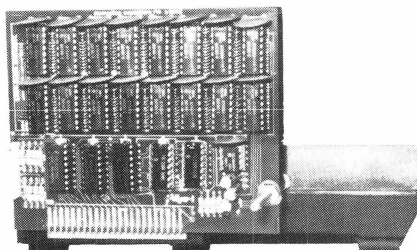

**Price for 32K RAM Pack (RP32)**  
**Was only: \$165.00 incl. P & P (Aust)**  
**Now only: \$125.00 incl. P & P (Aust)**

Free cases available soon.

Please send order or S A E for further information to:  
 VENDALE PTY. LTD., Dept T7, Box 456,  
 Glen Waverley, Victoria 3150.  
 36 Plymouth St., Glen Waverley.  
 (03) 232 0444.



## ZX80/81 PROGRAMMABLE CHARACTER GENERATOR

Using simple BASIC programs you can create your own unique character sets and graphic symbols for games, High Res graphs and charts and interesting patterns. Program symbols normally available only on more expensive microprocessors and you are not limited to preprogrammed graphic sets.

**Fully assembled price \$95.00 incl. P & P (Australia)**  
 Uses the 8K ROM from Sinclair (not incl.).

## UPGRADE YOUR ZX80 GRAPHICS

Now you can upgrade your ZX80 to the full animated graphics of the ZX81. Your ZX80 will now run in SLOW mode.

**Fully assembled price only \$38.50 incl. P & P (Australia)**

Works only in conjunction with 8K ROM from Sinclair (not incl.)

## Club Call

**A MicroBee Owners Club** would be a great idea. If you cannot find a club or you are interested in starting a club then send a SSAE to Colin Johns, 6 Tunks St, Waverton NSW 2060 and he will send you the latest information.

ZX81 users can now contact the ZX81 **Software Exchange** by sending a SSAE to ZSE, c/o Chris Tuono, 5 Muir St, Mt Waverley Vic. 3149.

The **Australian Sirius Users Group** is being formed to look after the needs of Sirius One and Victor 9000 computer users. This national group, founded by microcomputer enthusiast, Stephen Page, will issue a newsletter containing programming tips and information about new products, and will develop a software library.

Membership in the group will be free of charge. For a membership form write to the Australian Sirius Users Group, P.O. Box 204, Chermside Qld 4032. (07)350-2611.

## lassifieds : Classifieds

### CLASSIFIED RATES

15¢ per character

Minimum of 32 characters

CHARGES: Cash with order only

**BUSINESS** for sale. Thriving electronics sales & service business selling due to ill health. Good returns. Room for expansion. Books available for inspection to interested buyers only. Further details apply The Manager, P.O. Box 244, BOOVAL 4304.

**COMPUTER CLINIC** repairs & services Sorcerer, Pet, Apple, System 80, Super 80, Tandy & others. (07)269 8573, P.O. Box 68, Aspley, Qld.

**PCB's** and **SCREEN PRINTING** at the best prices. Short runs, long runs from your own artwork. Contact Peninsula Circuits, 7 Portrush Gr., Mornington 3931. (059) 75 5568.

**REPAIRS** to all home, hobby and small business microcomputer systems and peripherals, also all EA & ETI projects. CAE Electronics, 1/27 Forge St, Blacktown 2148. (02)621 4242.

**HP41C/CV** owners. Increase program capacity of your machine. Load up to 16K of program into EPROM (ROM emulator) which plugs into any port. Compact size, powered by calculator. Dataprom Pty Ltd, P.O. Box 476, Hurstville NSW 2220.

**COMPUTERS:** call us for the best price on full range of Commodore & Osborne computers. Inc. software and component parts. See our add this issue. Data Parts, Shepparton. Phone (058) 21 7155, 21 0240.

**SORCERER** Disk Upgrade Kit with manual. Many Pro features. MICRO-POLIS \$44.95. EXIDY FDS \$39.95. A must! Also free Soft. catalogues. PJB Box 252, Forestville 2087.

**COMPUTER** Clinic repairs and services Sorcerer, Pet, Apple, System 80, Super 80, Tandy and others. (07) 269 8573, P.O. Box 68, Aspley, Qld.

magmedia magmedia magmedia

## Here's to longer life with Datalife from Verbatim.



Verbatim is committed to offering customers the very best removable magnetic storage media. Our line of highest quality magnetic storage products extends to virtually all removable media forms and includes Datalife TM flexible disks and minidisks, data cartridges, data cassettes and Datalife TM head cleaning diskettes. Verbatim is intent on keeping their products at the forefront of technology, going above industry standards, setting a new standard for excellence.



**magmedia**

MAGMEDIA SERVICE PUTS THE CUSTOMER FIRST

**SYDNEY**  
(02) 428 1100  
**CANBERRA**  
(062) 48 6751

**BRISBANE**  
(07) 229 1600  
**HOBART**  
(002) 34 4522

**MELBOURNE**  
(03) 699 9688  
**PERTH**  
(09) 328 3311

**ADELAIDE**  
(08) 223 6261

magmedia magmedia magmedia

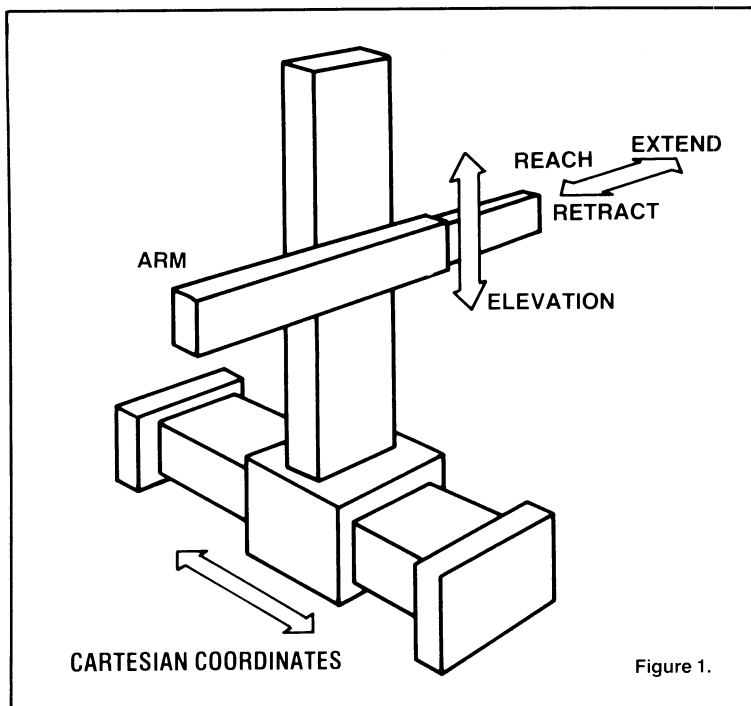


Figure 1.

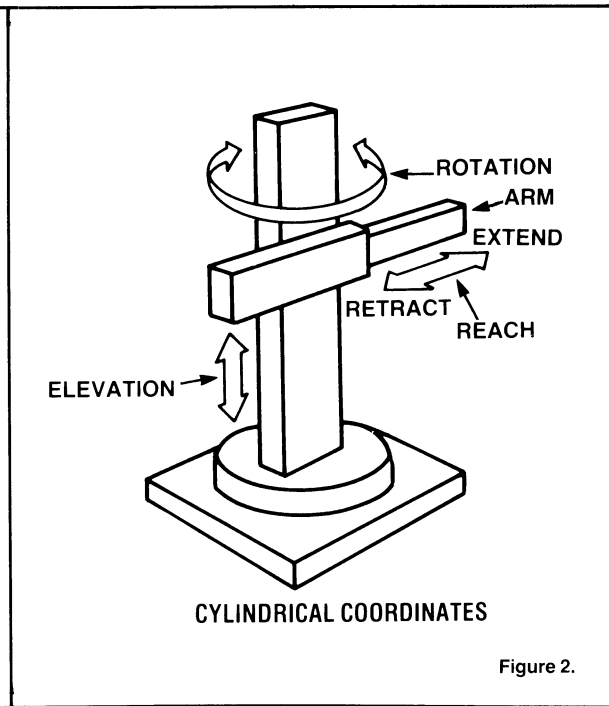


Figure 2.

# Robotic arm techniques

The problems surrounding the remote manipulation of objects under the control of a computer have long been a topic of discussion between and among mechanical and electronic engineers and scientists. This article takes a brief look at the four fundamental systems that have been evolved and suggests an approach for hobbyists interested in robotics.

**Roger Harrison**

MANIPULATING OBJECTS by means of a robotic arm requires a 'marriage' between mechanical engineering and electrical engineering if one is to arrive at an effective system. Four basic coordinate systems for moving an 'arm' have been evolved. Each has its merits and disadvantages. The four systems are:

1. The cartesian coordinate system.
2. The cylindrical coordinate system.
3. The polar coordinate system.
4. The revolute coordinate system.

The number of fundamental motions that a robotic arm can perform is determined by the number of axes employed in the system. The number of axes are often referred to as the 'degrees of freedom'. Thus, a robotic arm that can move on four axes is said to have 'four degrees of freedom'. The number of axes, and thus the degrees of freedom, endemic to a particular arm are important when considering the tasks it may have to perform. Another important consideration is the 'work envelope'. If you put a paint brush on the end of a robotic arm and then had the arm describe its complete area of movement (with the arm fully extended), the brush would 'paint' a surface in the air — that surface would be its work envelope.

The four basic systems illustrated have only three degrees of movement but vastly

different capabilities.

The cartesian coordinate system is illustrated in Figure 1. Here, a pillar can move back and forth along a base. The arm is mounted on the pillar and can move up and down it (elevation). The arm is in two pieces, one piece being capable of extension and retraction.

As all movements are linear, the cartesian system has a work envelope shaped like a cube.

By fixing the pillar of the cartesian system and making it rotate, we make the cylindrical coordinate system, so called because it has a cylindrical work envelope. Two linear movements are left and an angular movement added. Somewhat more complex movement is possible with this system, over and above the cartesian system.

By pivoting the arm around a rotating pillar, one produces the polar coordinate system. This has a work envelope shaped like a half-sphere and the complexity of motion is another step better than the previous system.

The revolute system, Figure 4, emulates the human arm. It is pivoted in two places and can rotate on its base. All movements are angular and, for a three degrees of movement system, it is capable of very complex motion. The work envelope approximates a

major portion of a sphere as the arm can be made to reach below the plane of the base.

A really complex system having ten degrees of freedom is illustrated in Figure 5. This is a combination of the cylindrical, polar and revolute systems mounted on a mobile platform.

## Gripping

An arm is useless without some mechanism to grip the 'work objects'. For hobbyists, a simple jaw grip system is probably the easiest to implement. Hinged tongs with a spring system to hold them open and a solenoid or motor to pull them shut are simply constructed and controlled. The general principle is shown in Figure 6.



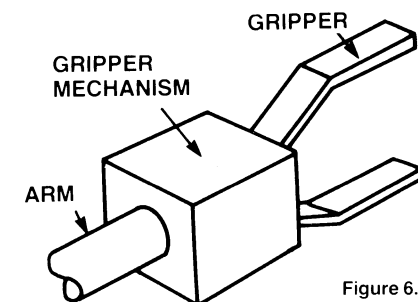


Figure 6.

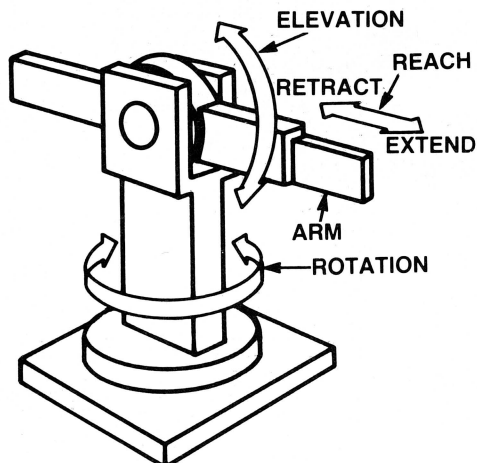

POLAR COORDINATES

Figure 3.

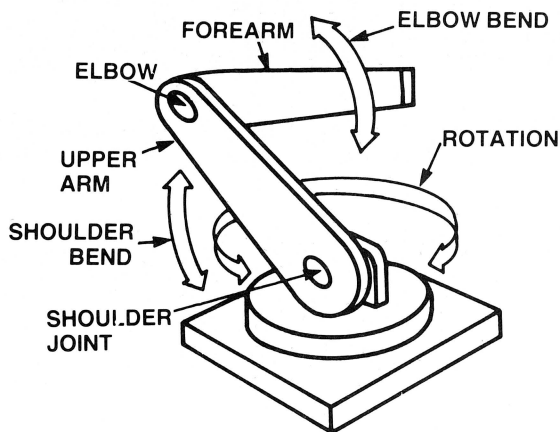

REVOLUTE COORDINATES

Figure 4.

## Drive systems

Industrial robots require physical strength and thus use large, multiple-horsepower electric motors and/or pneumatic or hydraulic drives. Even in relatively small industrial robot arms, hydraulic systems have many advantages. At present, such systems have distinct disadvantages for the hobbyist, not the least of which is cost.

Small electric motors are the most cost-effective drives for small arms and electric/electronic control is readily implemented and interfaced to a computer system.

## Grasp the nettle


'Personal robotics' is following in the footsteps of personal computing. In fact, they're related in many ways — via the microprocessor.

In early-1982 we published the construction details for an Australian-designed and manufactured 'turtle-style' robot — the

Tasman Turtle, that was controlled by a microcomputer system via an interface. It created a great deal of interest. Since then we have searched for other robotics projects of wide appeal and within the means of enthusiastic constructors.

Late in 1982 we found a British firm who had designed and was manufacturing a reasonably-priced robotic arm kit employing the revolute coordinate system, called 'The Micro-Grasp'. The firm was Powertran. Local kit and component supplier, Jaycar, sought and obtained the agency for Powertran kits — which have a much-envied reputation for quality in Britain — and we sought the rights to publish the project here.

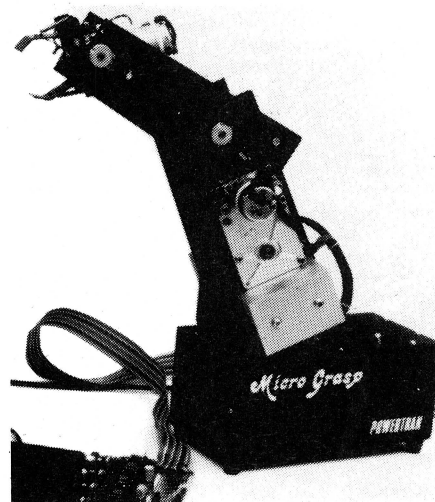The Micro-Grasp is an articulated arm jointed at shoulder, elbow and wrist positions. The entire arm rotates about the base and there is a motor driven gripper. Each of the arm movements is servo-controlled i.e. there are position sensors feeding back inform-



**This'll grab you!** The Micro-Grasp, a computer controlled robot arm project, scheduled to be described in April ETI, features four degrees of freedom, a motorised gripper and simple interfacing.

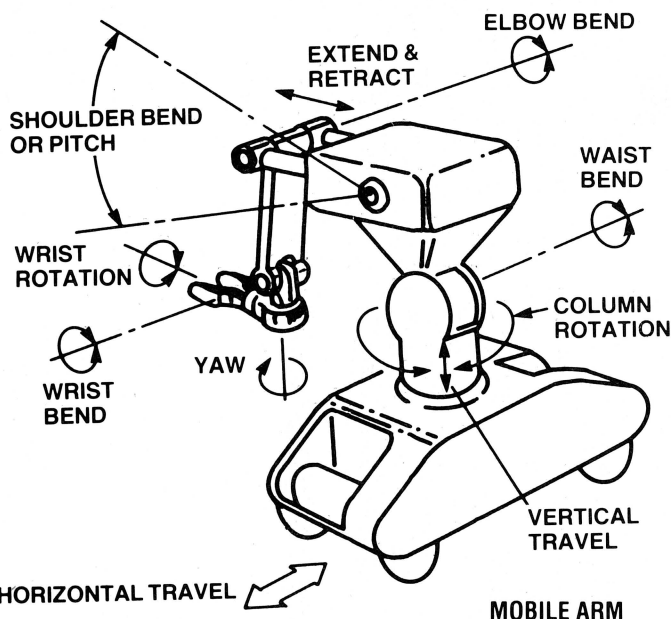


Figure 5.

ation to the interface board where it is compared with the programmed intended position and automatically takes corrective action.

This servo action is independent of the computer, greatly simplifying the software to drive the robot and all programming is carried out with a small number of BASIC commands.

The interface board is memory mapped using only 64 bytes at any of 1024 switch selectable locations. The control signals required are the address buss, data buss, write and memory request or alternatively I/O request if it is preferred to operate the robot as an I/O device.

The edge connector format could be arbitrary as the board is suitable for almost any computer.

The newly-formed Cybernetics division of Jaycar will be importing and marketing the Powertran Micro-Grasp in Australia.

The Micro-Grasp project is scheduled to be published in the April issue of ETI — don't miss it!

# The SME Systems 'Unicorn' computer

Do all Z80 systems look alike to the user? In some ways yes, and in other ways no. They'll all run CP/M, Wordstar and other useful utility programs, but monitor stunts vary from system to system. With the Unicorn our reviewer found himself on the horn of a dilemma . . .

**Mort Street**

RECENT ADVERTISEMENTS for small computers have featured such eye-catching shots as a small child holding the machine up with one hand. This is definitely not possible with the 'Unicorn'. In fact, I came within about 1.5 Newtons of getting a hernia just lifting *part* of the system.

The monster comes in four parts — first, a terminal. This is a pretty standard Televideo model 925, with an SME Systems sticker on the front of it. So far, so good. Next is the printer. This is a Microline u84, again with an SME sticker on it. Then comes the guts of the system — the CPU box. This is a very well-built unit (if the weight of it is any guide) with a keyswitch and a reset button on the front, and the usual socketry on the back. There is one socket for the disk drive, one for a 9600 baud terminal (RS-232), one for a 1200 baud printer (also RS-232), and one for a Centronics-type printer. There are also two power output sockets, which presumably are for the printer and the disk drive unit.

The disk drive is a dual eight-inch unit, built into the same sort of cabinet as the CPU.

Getting the computer onto a table was my first problem. That required a lot of sweating and swearing, and also a short prayer that the table would hold. Fine. Now I had the unit where I wanted it. I decided to plug it all together. Then my problems really began.

Like any conscientious reviewer, I first looked through all of the manuals. There was a SuperCalc user's guide. Fine. I would need that later. There was a Microsoft BASIC reference manual. That I would need later, too. There was a Wordstar training manual, and a set of Wordstar reference manuals. Good. Then there was a CP/M manual. Great.

Up to this time, I had seen nothing to tell me how to turn the machine on. Picking up the last manual (which advertises itself as the 'SME Systems Technical Manual'), I settled down to read all about the system. Page 3 says "SME SYSTEMS MONBIOS". I assume that by that they mean their monitor and I/O system? Turning the page, I was confronted by an assembly listing of the complete monitor.

Aghast, I turned pages till I came to the end of that — then I was given an I/O port map, followed by a photocopy of the Zilog specs on the Z80 and associated chip set. Wading through this, past the specs for various other chips inside the machine, I



**Slim.** The 'Unicorn' is a specially-built slimline S100 buss system. The CPU unit (top right) employs a 10-slot vertical motherboard with off-set slots to achieve the low height. The twin 8" disk drive unit sits beneath it. The Unicorn can be used as a single terminal multi-purpose machine or built up to a 15-user system employing a range of SME system cards.

came at last to a piece of blue cardboard. This was, in fact, the end of the book!

Amazed, I looked again through the other volumes. Was there anything I had missed? Perhaps even a manual for the monitor? No such luck.

I realised then that reviewing the system was going to be a difficult task — with no documentation to tell me how to operate the thing, never mind describing what hardware was in it, reviewing the 'Unicorn' was not going to be simple\*.

The system documentation consists of four documents:

1. The manual I just described, giving monitor listing and chip technical data.
2. A piece of paper in each disk drive box that told me to "REMOVE HEAD PROTECTION SHEET BEFORE APPLYING POWER".
3. A six-page document describing the extra CP/M files supplied with the system.
4. Hand-written sticky labels beside the sockets on the back of the CPU unit.

. . . and that is it. Oh well, I thought, what you get is what you get. So I plugged the right plugs into the right sockets (I know they were the right ones because it worked), put a CP/M disk into the left-hand disk drive, and turned on the power.

Nothing happened. Well, the RESET button lit up, and the fans on the two units started up. The cursor even appeared on the monitor. But nothing else happened.

Well then, I thought, SME have obviously decided not to provide power-up reset. So I pressed the RESET button.

The monitor came up with the message:

SME SBC800 Monitor V 2.0  
M>

. . . great. But the disk hadn't started up, so I was obviously still in monitor. And the monitor documentation consisted of an assembly listing . . .

No, I thought, these guys have got to be joking.

Taking an inspired guess, I entered a C (for CP/M — haven't you read 'Zen and the Art of Motorcycle Maintenance', about inspiration and engineering?) and pressed RETURN.

Sure enough, the disk started to move, and I got the message:


64K 2:1 Double Density CP/M 2.2,  
By SME Systems  
A>

From then on in, it was plain sailing. I assume by the message that the machine has 64K of memory, that the disk drives are double density, and that CP/M 2.2 is supplied with the system.

— continued on page 89. ►




#### Business Graphics

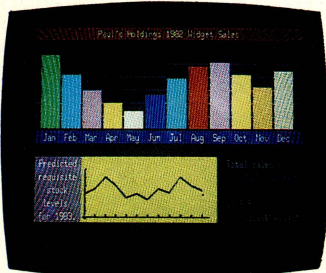

#### Arcade Games



#### Educational Programmes

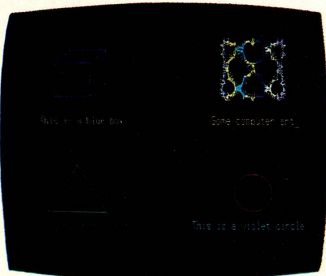

**Microbee — Australia's own educational and personal computer!**  
(Approved by NSW and WA schools.)



**Designed and manufactured in Australia.**



**Over 7,000 sold.** (Over 2,500 in schools in Australia and New Zealand.)



**Fully expandable from cost-effective 16K and 32K models to a fully featured 64K.**  
(Suitable for networking and disk drives.)




**Wide range of optional peripherals —**  
Printers · Plotters · Monitors · Disk Drives · Colour Adaptors · Modems.



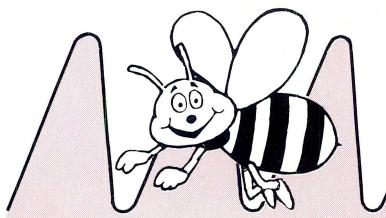**More computer for your money — more software support.**



AVAILABLE FROM DEALERS THROUGHOUT AUSTRALIA AND NEW ZEALAND.



# MICRO WORLD UPDATE

## NEW 'PLUS' SERIES WITH EXTRA FEATURES

### 16K PLUS

The 16K PLUS with features such as built in music generation, high and low resolution graphics, with a screen display of 16 lines each containing 64 upper and lower case characters. When you also consider all of the standard extras like continuous memory, built in printer and input/output interfaces and parallel port, 4.5 volt battery back-up and self testing BASIC in ROM, the MicroBee 16K PLUS is unbeatable in its class.

### 32K PLUS

All of the standard features of the 16K PLUS with twice as much usable RAM. When you add the new Word Bee ROM Pack, you have a powerful word processing capability which does a lot more than play the many games available for the MicroBee. Add a printer and maybe even the Tasman Turtle and just see what you and your family can now do with your home computer.



### 64K PLUS



The MicroBee 64K is equipped with 56K of user RAM with Battery backed continuous memory and has built-in 80 x 24 screen format as well as 64 x 16 line. All characters are upper and lower case and powerful graphics are readily available. A value packed exclusive feature of the MicroBee 64K PLUS is that it can double as an ADM3A Terminal operating in serial mode at either 300 or 1200 baud (full or half duplex). You can add a modem and use your MicroBee 64 as your personal information window to the world.

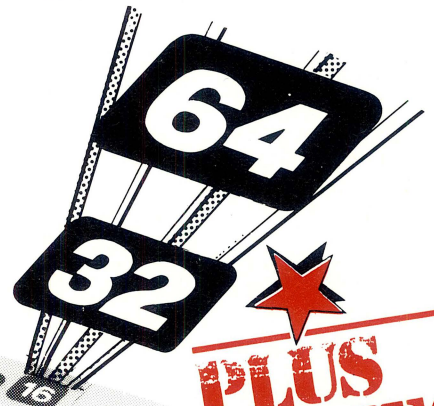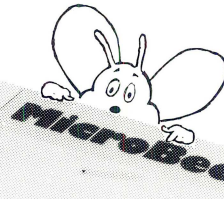**A better Bee for '83**

★ Now with  
★ BATTERY BACK-UP  
★ PARALLEL INTERFACE  
★ SELECTED CONTINUOUS  
★ MEMORY



★  
**PLUS  
SERIES**



Come and see us at

**The Australian Personal Computer Show  
10th - 12th March**

and see the new Colour Bee, 64K Bee  
with low cost disk drives and the Bee  
Modem/Networking.



# More Features . . . More Software . . . More Computer for Your Money!

## ROM PACKS

### WORDBEE — a full featured Wordprocessor.

Convert your MicroBee into a professional quality wordprocessor. Suitable for any 16K or 32K MicroBee. Enables the user to select either BASIC or WORDBEE/MONITOR as required.

**WORDBEE is friendly and easy to use, and has extensive HELP files built into the ROM.** It uses the familiar control key and dot commands from WORDSTAR, the on-line help from WORDMASTER and the on-screen formatting from ELECTRIC PENCIL.

### EDASM — MicroBee monitor and Z80 Editor Assembler.

This ROM pack converts your MicroBee into a combined BASIC/MACHINE CODE/ASSEMBLY LANGUAGE unit and is ideal for those who need to develop programs in machine code. Built in commands include EXAMINE and MODIFY memory, BLOCK MOVE and FILL memory, EXECUTE a program, READ and WRITE to cassette tape, SEARCH and COMPARE code and RETURN to BASIC.

### NETWORK 1


By popular demand we are making this ROM available for networking to other computers over the telephone lines. Contains the software to convert any 16K/32K MicroBee into a 'DUMB TERMINAL'.

### "MICROSPACE INVADERS"

Yes the arcade favourite! This fast-moving version was written especially for the MicroBee by Tim Morris-Yates and has become one of the most popular programs yet released.
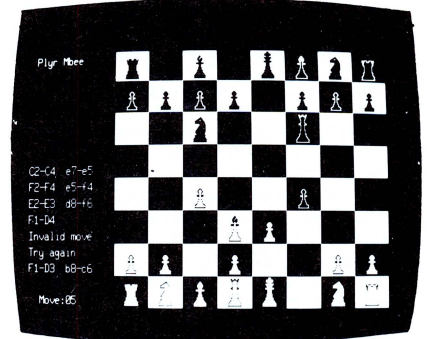
### "MISSILE WARS"

Equipped with radar and ray cannons your mission is to defend your city against the attacking alien invaders. This game is fast moving and very exciting. The graphics and synchronized sound effects will really involve you in the game.



## FAMILY GAMES

### "CHESS"

Match your skills against the MicroBee chess master. You can select from 1 to 6 ply and also analyse any position. A built-in 'HELP' feature enables the computer to play YOUR current move.

### "CONCENTRATION"


A real family favourite for 1 to 4 players to test your memory skills. If you call one player MERLIN, the computer will play that turn so watch out!

### "HOUSE OF FRANKENSTEIN." A New Release

The first adventure game for the MicroBee. Needs a 32K machine and can take weeks to resolve. Has built-in game save facility to re-load the game and resume play from your last session.
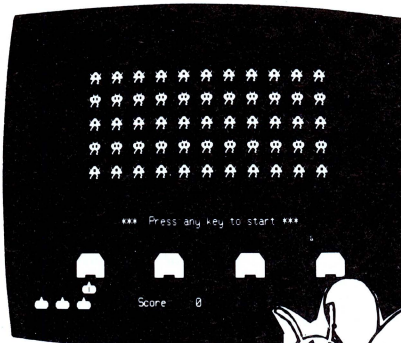
### "BIORHYTHM/CALENDAR MAKER"

Ideal for parties or carnivals. Requires a serial printer. You can print BIORHYTHMS for anyone — just enter their name and birthday!



"BEE Quick the Invaders are coming"

"BEE think it Mazing"

## EDUCATIONAL SOFTWARE


*Because the MICROBEE is recommended for use in Australian schools, considerable software is now being written to match the curriculum in several States. Demonstration programs are available on EDPACK I and EDPACK II. Watch for the release of OZLOGO, PASCAL in the near future!*

### TURTLE GRAPHICS

A very clever program allows the student to use the MICROBEE to draw using high resolution turtle graphics. A booklet of procedures is available from the NSW Department of Education. This is a very powerful graphics program which uses the PCG facility in the MICROBEE to its full extent.
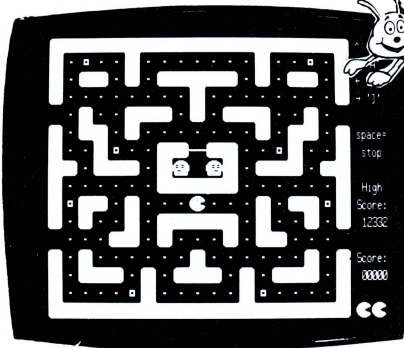
### WORK-A-BEE

A new release. WORK-A-BEE is a program which can actually write educational programs almost automatically! Any teacher with little or almost no knowledge of BASIC can insert details as to question and answer, number of tries, marks per question and other controls. Any CAI program can be saved and reused and subroutines have been included to enable the student to go back over his work, printing answers, avoid error traps etc.




## ARCADE GAMES

*Ideal for parties, these action games make full use of the superb graphics and sound effects of the MicroBee. Your friends and family are set for hours of fun and excitement!*
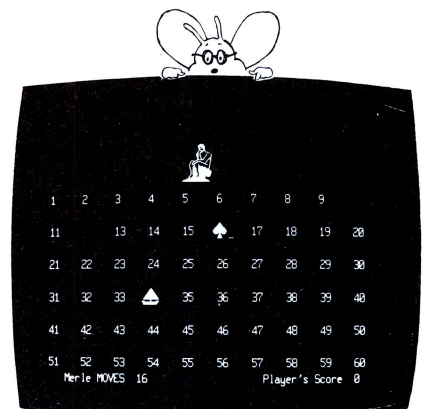
### "ROBOT MAN" — A New Release.

You must move about the maze eating up the power food. Watch out for the Robot Men as they are programmed to destroy you before you complete your mission!




## COMPUTER UTILITIES

*These programs are included as enhancements of the MicroBee computer itself.*

**PCG TUTORIAL — ESCKEY — and DISSEM are three of them.**

# MicroBee PRICE LIST

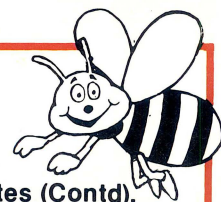

## HARDWARE

### MICROBEE PLUS SERIES

(See features on previous pages)

110.017	MicroBee 16K PLUS	\$449.00
110.032	MicroBee 32K PLUS	\$549.00
110.064	MicroBee 64K PLUS	\$699.00

**MONITORS** — Three to choose from or you can convert your old black and white television. We recommend the KAGA Green Screen with 18 Mhz bandwidth for serious users and the new MicroBee Monitor with built-in power supply for general purpose, but quality Green Screen performance.

150.020	KAGA High Resolution Monitor	\$299.00
150.022	MicroBee Hi-Resolution Green Screen	\$199.00
150.025	B. & W. Monitor (converted television)	\$149.50

### CASSETTE RECORDER —

High reliability cassette recorder such as National or Sanyo is recommended. We will supply with your MicroBee.

150.030	High reliability cassette recorder	\$39.50
---------	------------------------------------	---------

### BLANK DATA CASSETTES —

For saving your own programs. Made in Australia to our specifications.

110.310	C10 Data Cassette	\$1.20
110.311	C20 Data Cassette	\$1.30
110.312	C30 Data Cassette	\$1.40

## CASSETTE BASED SOFTWARE

### NEW RELEASES —

(As featured previous page).

250.042	Robot Man	\$14.75
250.048	Work-A-Bee	\$14.75
250.049	Turtle Graphics	\$14.75
250.045	House of Frankenstein	\$14.75

### OTHER MicroBee Cassettes

(Also featured previous page)

250.020	Microspace Invaders	\$14.95
250.036	Missile Wars	\$9.95
250.022	Chess	\$9.95
250.021	Concentration	\$9.95
250.027	Biorythm Calendar	\$9.95

### MORE MicroBee Cassettes

**Z TREK** — Captain! The warp drives are disabled, the Klingons are closing in on us, what will we do? In Z Trek YOU are the captain of the starship Enterprise, your five year mission to search out the

### MicroBee Cassettes (Contd).

Klingons and destroy them. There are ten levels of difficulty (0 - 9). Beware of this game — it is strangely addictive.

250.032	Z Trek	\$9.95
---------	--------	--------

### WUMPUS — THE ADVENTURE GAME

Have you ever played the game Wumpus? If you liked it then you'll like this! The object is the same as the earlier version except that it's a lot harder. To say any more would spoil the fun. Good Hunting!

250.031	Wumpus	\$14.75
---------	--------	---------

**ESC KEY** — This is a program for all of the two fingered typists in the world. The program allows you to enter BASIC key words in an abbreviated form. For instance, instead of typing "list" the user would type "esc" and then "1". The computer then types out the rest of the word for you. Suitable for 16K and 32K machines only.

250.041	ESC Key	\$9.95
---------	---------	--------

**GRAPHIC GAMES** — This cassette contains five programs, 'Poker', 'Slots', 'Dodgem', 'Picture', 'Richochet'. 'Poker' is the main program on the cassette. In this game the computer is the bank and you have to beat it at Draw Poker.

**Warning** — the computer plays a cunning game and is quite prepared to bluff! 'Slots' is a one armed bandit and for 20c a go you can try your luck. In 'Dodgem' the player must guide his car through a forest to the bottom of the screen. — this game allows you to drive a car without the random breath tester getting you!! 'Picture' is an excellent game for the children. The final program on the cassette is 'Richochet', where the player is to decide when to fire a bullet through a hole in the wall. If you hit the wall you're dead.

250.035	Graphic Games	\$9.95
---------	---------------	--------

**PCG SAMPLER** — The PCG Sampler cassette has eight programs on it. These programs show you how the PCG works and demonstrates its capabilities by way of games etc. The cassette is excellent for both beginners and experts. It allows you to design your characters on the screen, so you can see exactly what you are creating. Suitable for all MicroBees.

250.037	PCG Sampler	\$9.95
---------	-------------	--------

**STARSHOOT/HANGAMAN** — Starshoot is perhaps one of the most deceptive games available on computer. It appears to be very easy: it isn't.

### MicroBee Cassettes (Contd).

**Hangman** is based on the popular school game that everybody knows.

250.026	Starshoot/Hangman	\$7.95
---------	-------------------	--------

**ELIZA** — Want someone to talk to? Eliza is possibly the person for you. (If you can get her to shut-up). Eliza is a program that demonstrates artificial intelligence. Eliza is prepared to talk about life, the universe and everything.

250.028	Eliza	\$9.95
---------	-------	--------

**TYPING DRILL/SOLITAIRE** — Want to become a touch typist? Typing Drill enables you to learn touch typing without paying an exorbitant fee to learn. Solitaire is a game in which the object is to remove all of the "pegs" from the board, leaving one peg in the centre of the board. Sounds simple, but, it requires skill to master it.

250.023	Typing Drill/Solitaire	\$9.95
---------	------------------------	--------

**TARGET** — Target is a game of hit and miss. Your task is to aim the cannon at the bottom of the screen and shoot down the U.F.O.'s (ET watch out). There are nine levels of play to this entertaining game thus making it suitable for any player. Suitable for all MicroBees.

250.024	Target	\$9.95
---------	--------	--------

### LUNAR LANDER/HURKLE —

Crash! This game was probably originally designed by N.A.S.A. scientists — after all it's much cheaper than Apollo. The object of Lunar Lander is to land your space craft on the moon without using up all of your fuel. Don't laugh and say that's easy: it isn't.

For a description of Hit the Hurtle please see the Kids Pack.

250.025	Lunar Lander	\$7.95
---------	--------------	--------

**MASTERMIND/NIM** — The Mastermind on this tape is quite similar to the version on the Kids Pack except for the fact that you can enter up to nine digits as the mystery code. This makes the game extremely interesting and mind bending. Nim is also played in a similar style to the version in the Kids Pack except that you can have up to 9 piles of 'matches'.

250.030	Mastermind/Nim	\$9.95
---------	----------------	--------

## ROM BASED SOFTWARE

(See features on previous page)

250.003	Editor Assembler	\$59.50
250.040	Word Bee ROMPAK	\$89.50



**Make a BeeLine for your MicroBee Computer Shop today!**

#### SYDNEY:

Applied Technology,  
1a Pattison Ave. Waitara.  
Phone: 487 2711.

Electronic Agencies,  
117 York St. Sydney.  
Phone: 29 2098.

Specialty Enterprises,  
6th Floor,  
104 Bathurst St. Sydney.  
Phone: 267 7747.

#### GOSFORD:

Applied Technology,  
1 Debenham Rd. West Gosford.  
Phone: (043) 24 1022.

#### CANBERRA:

MicroBee Computer Shop,  
Level 1, Cooleman Court,  
Weston, ACT.  
Phone: (062) 644 277.

#### MELBOURNE:

Computerland Sth. Melbourne,  
19 - 37 Albert Road,  
(Cnr Kingsway & Albert Rd.),  
Melbourne.  
Phone: 268 6647.

Specialty Enterprises,  
1st Floor,  
305 Latrobe Street, Melbourne.  
Phone: 67 8811.

#### BRISBANE:

Specialty Enterprises,  
6th Floor, 246 Queen Street,  
Brisbane.  
Phone: 229 2450.

#### PERTH:

Altronics  
105 Stirling St, Perth.  
Phone 328 1599

#### NEW ZEALAND

Checkpoint Computers,  
36 Main Road, Tawa,  
New Zealand.  
Phone: (4) 32 6988.

## MicroBee PHONE ORDERS

Save time and order your MicroBee direct on our Beeline number. Just give your Bankcard Number and Name. We will check stocks and get the goods on the way.



**(02) 487 2711**

Now, there is no point in me reviewing CP/M itself, or Wordstar, or Supercalc or any of the other software in the system, because this is a review of the 'Unicorn' itself.

So that leaves the special files that SME give with the system, which were described in their little six-page leaflet.

The first is **MCOPY**, which is a disk copy program. Then there is **BAUD2**, which changes the baud rate for the printer or terminal. **FINDBAD** checks the disk for bad sectors, and creates a file which covers those sectors.

**TOD** gives the day, date and time. I tried it, and it gave the correct answer. By this, I deduced that the 'Unicorn' contained some sort of battery-driven clock. The documentation told me that the clock could be set from the monitor, but did not tell me how.

**DDU** is a 'disk utility for patching/reviewing disk data'. Unfortunately, the documentation did not tell me *anything* else about this piece of software, and its short description made me think that perhaps it was not the sort of program that should be operated by trial and error.

**REMAC** is a disassembler, for producing opcodes from a .COM file, so that they can be used with a macro-assembler. **SSUB** is a type of super-submit utility, that allows you to enter a series of commands and have them executed automatically one after the other. **BMAP** produces a disk allocation map.

As software utilities go (and these are given in addition to the usual CP/M utilities) these look not bad — but the fact that not one of them has more than two paragraphs of documentation makes them less than useless.

All in all, the 'Unicorn' *looks* like quite a nice system. Unfortunately, the total lack of decent documentation makes it about as useful as a horse with a horn sticking out of its back . . .

I would like to suggest to SME that they get their act together and, if they expect a serious user (a small business, for example) to buy and use this machine, get some manuals written for it.

And for those of you reading this review — don't buy *any* system until you have seen the final version of the manual, and are happy that you can find all of the information that you want in it. ●

#### \* EDITOR'S NOTE

I contacted Mike Pratt of SME concerning the documentation questions raised by our reviewer. Apparently, SME market this system to 'educated' users — that is, those with an existing technical background in computers, hospitals, colleges, etc. They deliver and install the system, and get it running. In addition, they give the staff who will be using the machine a short training course and don't leave them alone with it until they feel the staff can cope, according to Mike Pratt.

That softens the blow considerably, but this system is definitely not for a 'first time user', as the computer buzz phrase goes. But what happens if those staff leave the organisation?

If there are any technical writers out there with a knowledge of digital and microprocessing systems who can write clear English and explain technical matters in plain language . . . Mike Pratt would like to have a little chat.

R.H.

# MPI Hi-D Mini Drives

freedom  
of choice

Our  
way..




.. or theirs

Professional, push-button disk eject, or industry standard flip-front . . . Either way, MPI builds the quality in. Head load for media protection, 5mSec track-to-track and a choice between 48, 96 and 100TPI, single or double sided 5 1/4" Floppy Drives.

## TRUE FREEDOM OF CHOICE
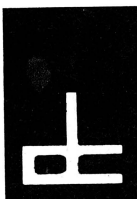
### Authorised Dealers:


**Sydney:** (02) E&M Electronics 51 5880. Applied Technology 487 2711. QT Computers 29 5599. Micro Repair 747 1061. Computer Components 868 3614. **Wollongong:** (042) Macelec 29 1455. **Brisbane:** (07) Baltec 36 5183. **A.C.T.:** (062) Ortex 80 5283. Boulevard 48 5411. **Perth:** (09) Micro Controls 445 2544. Electronic Systems 335 7313. **Adelaide:** (08) DC Electronics 223 6946. Micro '80 211 7244. **Melbourne:** (03) Stewart Electronics 543 3733. Ellitronics 602 3282. Ritronics 489 8131. Pennywise Peripherals 82 2389. Deforest Software 877 6946. Comp Soft 428 5269. **Tasmania:** Coastal Computers (004) 31 3259.



**daneva australia pty ltd.**

66 Bay Road, Sandringham, Vic., 3191. Ph: 598 5622. Telex: AA34439

# Time flies on the TRS-80C

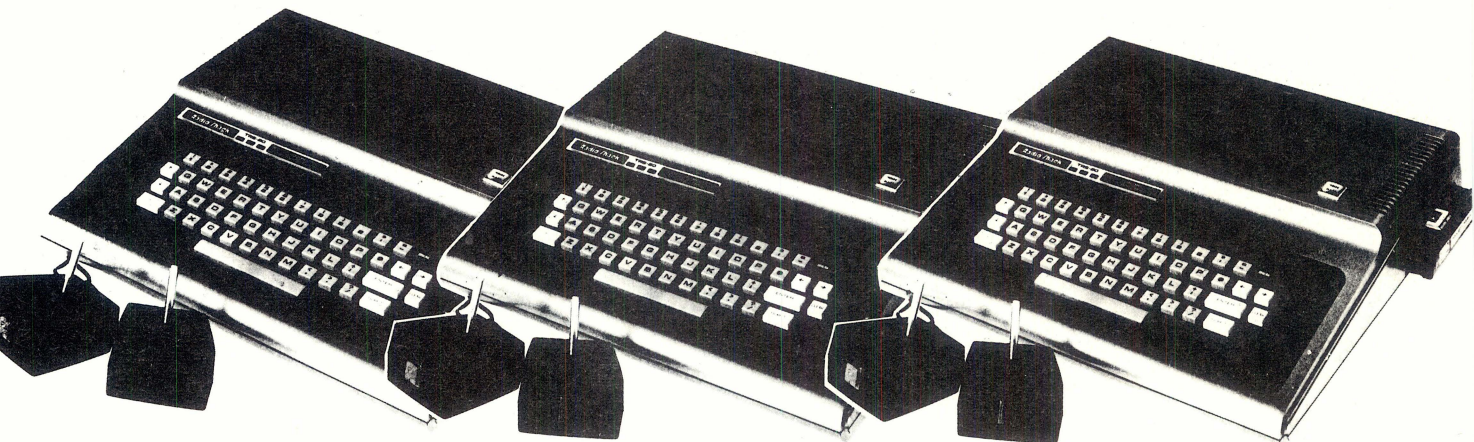

Here are two clock programs for the Tandy TRS-80 Color Computer. They take advantage of the colour graphics capabilities built into the Extended BASIC and there's plenty of scope for further development, like adding comments, reminders, etc. In other words — start here and take them as far as you like!

## Greg Wilson

YOUR EDITOR asked me to write a program for the TRS-80 Color Computer. Beaut! But I wanted to write an automatic program generator for the 4K machine. Computer-illiterate teachers would be able to create cassette data files without having to throw a switch. The program would throw questions to students and feed the teacher's voice response for the chosen answer and . . . and everything! Your Editor said, "Yeah, fine *but* I want a clock program first".

I had never seen a clock program. I shuddered and quickly turned away from one I saw running in a Sydney shop. (I now wish I hadn't.) No teacher ever taught me about radians, I'll swear.

'Twas a weekend when I started, no one to ask, so I forged ahead (well, groggily staggered) to produce the second listing printed here. A brief burst on that one later, it has a few good points.

I was then told by an acquaintance of mine, Dave Gilbert, an educator not a teacher, that "pi converted theta, as in x coordinate of points, on a circumference is given by sine theta, where theta is the angle in degrees". Back to scratch, but it was a breeze.

Because of the TIMER function of the 80C's Extended BASIC, it will give digital time readouts with just one line in a main program. To use the 80C as a graphic clock is silly unless the graphic program is quick enough to give the computer plenty of time to get on with something useful.

The first listing (CLOCKSUB) does its job in one-twentieth of the real time, so you can GOSUB from line 280 to your own more

sensible program. (The second gobbles up a third of the real time. It's pretty, but!) There is plenty of room left on the screen for time updates from your program. You had better brush up on all the DRAW type commands, though. Not the trillion combinations, just the fifty-odd commands. Sorry for writing in Extended BASIC if you haven't got a 16K machine. Complain to your Editor! There are heaps of programs for the 4K machines, anyway.

### Program chunks

The action starts at line 200 in 'CLOCKSUB'. Before line 200, arrays are filled for the sixty screen-points reached out to by the minute hand. The hour hand demanded sixty, too. At 140, the graphics of drawing the clock start. That horrible line 200 draws the little flicks at each minute stop and a larger point every five. I prefer brown on beige (140) to the other one that looks like a blueprint. (A shame that the best of the five 80C Invaders uses it.)

You don't like the beige? Change it then. Ignore those librarians who told you that magazines were not to be written on but kept in racks.

The second timing loop (260-300) displays a 4x4 pixel open box (PSET,B) just inside the clock rim. It turns that box off (PRESET) before leaping to the next. The minute-hand loop (230-340) has to work harder, but less often. It goes through the same on and off carry-on (lines 240 and 320, respectively). It also has to PSET (330) the hour hand if it has lobbed on it and rubbed it out when it did

a PRESET to itself. The hour hand doesn't use a loop but works on updating (250) the variable H set (220) as minus one. Maybe I just like being able to turn out off-normal time. Read on for why, or skip the fine print.

### Fine print

When I began fiddling with micros, memory was valuable so I developed the habit of hoarding variable storage by re-using a variable after it had served its original purpose. Variable 'R' was so easy to remember as a radius (20 & 190), and 'T' (40 & 180) is so generally used for any old loop, that I pulled them off the junk heap to use again.

If there had been only one pair of X-Y (coordinate) arrays, the variables would have been 'X' and 'Y'. The minutes fought the hours for them, and won. The hours pair is 'V' and 'W', which you'll mix up, just as I did. They won 'R' for radius, minutes had to settle for 'S'. 'P' and 'Q' (60) are just to save you typing too many lines (80-110) where it's easy to lose your place. 'CX', the centre X coordinate, is a trifle easier to type than '100'. I hope it will tease you to test different values for 3-D effects — and shocking messes!

The variable 'C' (70) is involved in all that sine-cosine jazz. How can I explain it if I don't understand it? It was easy to work out though. There was no need to worry about sequence for the flicks (200). These work backwards from 29 minutes to 30 minutes. Got it?

The printing, generated by line 120, reassures us that something is happening. The columns give 'C' the minutes, then the X

```

10 REM CLOCKSQR 12/1/82
20 CX=100: R=60: S=80
30 DIM V(59), W(59), X(59), Y(59)
40 FOR I=20 TO 120 STEP 2
50 IF I<62 THEN M=-30 ELSE M=30
60 PI=3.14285714: P=SIN(PI*I/60): Q=COS(PI*I/60)
70 C=60+M-I/2
80 X(C)=INT(CX+S*P+.5)
90 Y(C)=INT(CX+S*Q+.5)
100 W(C)=INT(CX+R*P+.5)
110 V(C)=INT(CX+R*Q+.5)
120 PRINT USING "## ## ## ## ##": C; X(C); Y(C); W(C); V(C): REMember not
#####...
130 NEXT I
140 PMODE 4,1: PCLS: SCREEN 1,1
150 CIRCLE(CX,100),90,1,1
160 CIRCLE(CX,100),84,1,1
170 PAINT(CX,186),1,1
180 FOR I=20 TO 120 STEP 2
190 IF INT(I/5)<I/5 THEN R=86 ELSE R=90
200 LINE(CX,100)-(CX+R*(SIN(PI*I/60)),CX+R*(COS(PI*I/60))),PSET
210 NEXT I
220 H=-1
230 FOR M=0 TO 59
240 LINE(CX,100)-(X(M),Y(M)),PSET
250 IF M/12=INT(M/12) THEN LINE(CX,100)-(V(ABS(H)),W(ABS(H))),PSET:
: LINE(CX,100)-(V(H),W(H)),PSET
260 FOR S=0 TO 59
270 LINE(X(S)-2,Y(S)-2)-(X(S)+2,Y(S)+2),PSET,B
280 REM "FOR D=0 TO 7: NEXT D" to slow
290 LINE(X(S)-2,Y(S)-2)-(X(S)+2,Y(S)+2),PSET,B
300 NEXT S
310 SOUND 5+M*4,1
320 LINE(CX,100)-(X(M),Y(M)),PSET
330 IF M=H THEN LINE(CX,100)-(V(H),W(H)),PSET
340 NEXT M
350 IF H=59 THEN 220 ELSE 230

```

```

10 REM***CLOCKSQR
100 PMODE 4,1: PCLS: SCREEN 1,0
110 X=8: Y=6: XS=8: YS=6
120 CX=X+15*XS: CY=Y+15*YS
130 LINE(X,Y)-(2*CX-X,2*CY-Y),PSET,B
140 CIRCLE(CX,CY),XS*5,1,YS/XS,1: PAINT(CX,CY),1,1150 X=X+8: Y=Y+8: XS=(30*XS-16)/30: YS=(30*YS-16)/30
160 XE=X+30*XS: YE=Y+30*YS
170 LINE(X,Y)-(XE,YE),PSET,B: PAINT(X-2,Y-2),1,1
180 BX=INT(X+(CX-X)*.2): BY=INT(Y+(CY-Y)*.2)
190 XM=1.6*XS: YM=1.6*YS: EX=BX+15*XM: EY=BY+15*YM
200 D=2*XS: R=2*YS: DIM V(D,R)
210 X1=INT(X+(XE-X)/6): X3=INT((X+5*XE)/6)
220 Y1=INT(Y+(YE-Y)/6): Y3=INT((Y+5*YE)/6)
230 DRAW"COBM"+STR$(CX-4)+","+STR$(Y-2)+"R3L2U5G1R2BR2R1E1R2F1G3D1R4U1"
231 DRAW"BM"+STR$(X3-5)+","+STR$(Y-2)+"R3L2U5G1"
232 DRAW"BM"+STR$(XE+3)+","+STR$(Y1+2)+"R4L4U2E3H1L2G1"
233 DRAW"BM"+STR$(XE+3)+","+STR$(CY-2)+"E1R2F1G1F1D2G1L2H1"
234 DRAW"BM"+STR$(XE+3)+","+STR$(Y3-1)+"D4R4L2U3D5"
235 DRAW"BM"+STR$(CX+1)+","+STR$(YE+3)+"H1L1G1D3F1R1E1U1H1G1"
236 DRAW"BM"+STR$(X3+2)+","+STR$(YE+2)+"L3D2R2F1D1G1L3"
237 DRAW"BM"+STR$(X1+1)+","+STR$(YE+2)+"R3D1G3D1"
238 DRAW"BM"+STR$(X-5)+","+STR$(Y3-1)+"R2F1G1L1G1D1F1R1E1U1H1L1H1E1"
239 DRAW"BM"+STR$(X-2)+","+STR$(CY)+L3H1U1E1R1F1D4G1L1H1"
240 DRAW"BM"+STR$(X-3)+","+STR$(Y1+2)+"H1U4E1F1D4G1BL3U6"
241 DRAW"BM"+STR$(X1-1)+","+STR$(Y-2)+"U5BR4D5"
250 SCREEN 1,1: GET(CX=0/2,CY=R/2)-(CX+0/2,CY+R/2),V,G
260 HX=CX-0*X2: HY=Y-R: OX=0: OY=0: DRAW"C1BM1,1"
270 PUT(CHX,HY+4)-(CHX+1,HY+5),V,PSET
280 HX=HX+O: FORS=1 TO 2: PUT(CHX,HY)-(CHX+O,HY+R),V,NOT: NEXTS
290 B=1: MY=BY+1: FOR M=0 TO 7: MX=CX+M*XM: GOT0360
300 B=0: FOR M=1 TO 15: MY=BY+M*YM: IF M<>5 THEN 360 ELSE 350
310 FOR M=1 TO 15: MX=EX-M*XM: 355
320 IF M=8 THEN 580 ELSE IF M<>14 THEN 360 ELSE 350
330 FOR M=1 TO 15: MY=EY-M*YM: IF M<>11 THEN 360 ELSE 350
340 FOR M=1 TO 7: MX=BX+M*XM: GOT0360
350 HX=HX+OX: HY=HY+OY
360 SY=Y+1: FORS=1 TO 15: SX=CX+S*XS: GOT0 410
370 FORS=1 TO 30: SY=Y+S*YS: GOT0 410
380 FORS=1 TO 30: SX=XE-S*XS: GOT0 410
390 FORS=1 TO 30: SY=YE-S*YS: GOT0 410
400 FORS=1 TO 15: SX=X+S*XS
410 LINE(CX,CY)-(SX,SY),PSET
420 LINE(CX,CY)-(SX,SY),PSET
430 LINE(CX,CY)-(MX,MY),PSET
440 PUT(CHX,HY)-(HX+O,HY+R),V,NOT
450 IF SX>XE-1 THEN SX=SX-1: GOT0 370
460 IF SY>YE-1 THEN SY=SY-1: GOT0 380
470 IF SX<X+1 THEN SX=SX+1: GOT0 390
480 IF SY<Y+1 THEN SY=SY+1: GOT0 400
490 NEXT S
500 SOUND(M+1)*10,1: LINE(CX,CY)-(MX,MY),PSET
510 IF M=7 AND B=1 THEN 300
520 IF MY<EY-.9 THEN MY=MY-1: HX=HX+OX: HY=HY+OY: GOT0310
530 IF MX<BX+.9 THEN MX=MX+1: GOT0330
540 IF MY<BY+.9 THEN MY=MY+1: GOT0 340
550 NEXTM
560 PUT(CHX,HY)-(HX+O,HY+R),V,PSET
570 HX=HX+OX: HY=HY+OY: GOT0290

```

and Y coordinates of the minutes, and the equivalents for the hours. The hour hand jumps a minute section for every twelve jumps of the minute hand.

We need sixty flicks, or minutes. You can think of them as 1-60 or 0-59. Think 0-59, else you will start at one minute after one rather than noon, midnight or 12 o'clock. Luckily, computers think the same way. When told to DIM X(59), room is made for an array of sixty, 0-59. Because zero divided by any number ends up as zero, at start, the line 250 test will be met and 'H' incremented. We want 'H' to be zero after that addition of one (250). Line 230 wastes too much time sounding a rising tone.

If you want a stop watch, drop it.

Use an INKEY\$ line to start. In the same way, it's not hard to INKEY\$ a start time. Make up your own mind to drop it or expand it to give tones of longer duration for the minutes. You won't have to look at the clock face after a few weeks. Your body clock will do the conversion of tones to time for you. You'll likely be in a padded cell, so you may as well keep time as do anything else!

## Square clock

The second listing, 'CLOCKSQR', doesn't give a square clock, it gives a rectangular one. It fills the screen. BUT you can easily change X-Y in line 110 to give you a new top left-hand corner. If YS is greater than XS, you'll get a tall skinny grandfather clock. What will happen if you use the same number for YS as for XS? Reduce XS-YS and you can get a small face, leaving you plenty of room for update information.

The face has an oval centre that I think is pretty. Well it looks like antique lace, if you go for that. If you don't, how about the same second hand that draws the lace, tucking out a tiny diagonal of the rim? I reckon that it gives the frame a 3-D effect.

I've looked at that frame so long in testing the program, I suppose I could see anything in it. That frame contains very costly (230-241) numbers. Work out where to place them and you can use them in the first program. It would have been simple to wed hour hands to the second and minute ones. I didn't because I'm a Smart Aleck. Instead, a large blinking block moves around the frame, taking four steps each hour. Work out why the block doesn't erase the numerals when it lands on and moves off them. Instead, they blink too. You can fool the 80C just as easily as any other computer.

I won't waste valuable paper going on about how it works. It's not a trim program. The 6809 in the 80C really moves, even at the normal speed. It's hard not to become sloppy, it loves being kept busy. By the way, if your 80C will run at double speed, forget that stuff about one-twentieth and one-third. Halve them.

## Keying-in

If you have a Master Control program, getting the programs into the 80C won't be too hard. Debugging to find your typing errors will give you the feel of some of the graphics commands. The Microsoft Editor built into the Extended BASIC is a dream for program editing; fixing those errors will be a pleasure.




## SYSTEMS THAT GROW WITHOUT GROWING PAINS

Head Office:  
41 Sydney St,  
Marrickville 2204  
Phone: (02) 519 2680
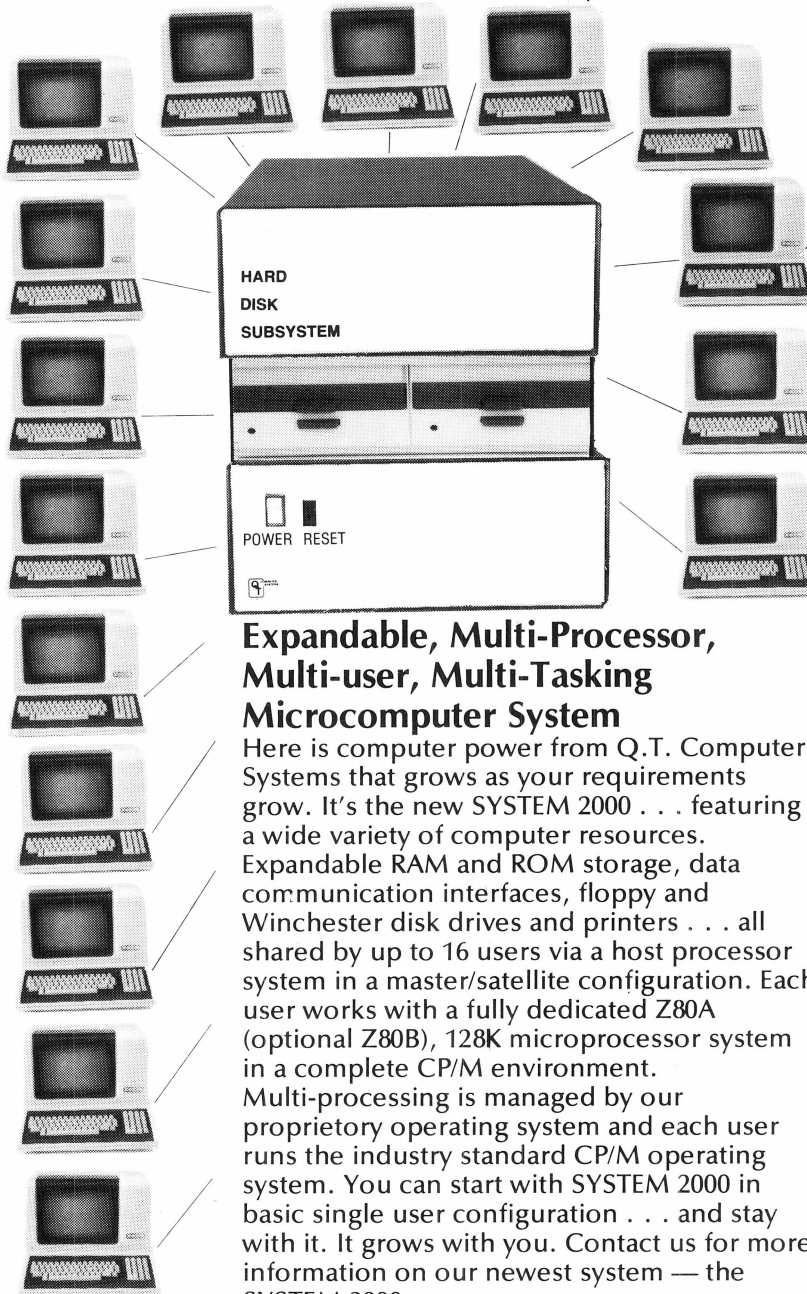
### One Q.T. System 2000 Supports 16 CP/M User Stations

AND NOW AVAILABLE  
as a standard feature with all systems  
**MEMORY DRIVE SOFTWARE**  
for lightning performance  
**SOON TO BE RELEASED**  
16 bit micro based  
on the 8086 processor



### Expandable, Multi-Processor, Multi-user, Multi-Tasking Microcomputer System

Here is computer power from Q.T. Computer Systems that grows as your requirements grow. It's the new SYSTEM 2000 . . . featuring a wide variety of computer resources. Expandable RAM and ROM storage, data communication interfaces, floppy and Winchester disk drives and printers . . . all shared by up to 16 users via a host processor system in a master/satellite configuration. Each user works with a fully dedicated Z80A (optional Z80B), 128K microprocessor system in a complete CP/M environment. Multi-processing is managed by our proprietary operating system and each user runs the industry standard CP/M operating system. You can start with SYSTEM 2000 in basic single user configuration . . . and stay with it. It grows with you. Contact us for more information on our newest system — the SYSTEM 2000.

Typical Applications include — A multi-station word processing network, educational systems, business systems, real time data acquisition etc.

We are actively seeking local and interstate distributors for our new system. OEMs can purchase the system in knocked down form as bare boards, bare metal work, kits etc. Complete systems available from as little as \$2800 + S.T. Bare boards from \$195 + S.T.

Prices and specifications subject to change without notice.

## 660 SOFTWARE

### CHARACTER GENERATOR AND VIDEO MESSAGE MAKER

Frank Rees, 27 King St, Boort Vic. 3537

Here is a subroutine to generate characters and numerals. Two small programs are also presented, one allowing you to display the complete character set generated, the other allowing you to write messages on screen by typing in an appropriate set of 'tokens' or codes for each character required. Combine this with your own programs and you've got a powerful message generator.

The first thing you should do is enter the CHARACTER GENERATOR ROUTINE FROM 073C. Then, you can do one of two things: to examine the complete character set, enter the DISPLAY CHARACTER SET program and run; or enter the VIDEO MESSAGE MAKER program and run.

With the video message maker, a flashing cursor will appear at the top left hand corner of the screen. Think of a word or simple message to type on screen, say 'ETI'. Look at the character code table and work out the codes for each letter. E = 0E, T = 1D, I = 12. The first figure of the code serves two purposes. Press key 0 twice. The first press will cause the cursor to disappear, the second time you press it, the computer will beep at you signifying you've entered the first half of the character code or token. Then press key E and the letter E will appear at the top left hand corner of the screen. The cursor will then appear at the next location on the screen. Then press key 1 twice. At the first press the cursor will disappear, at the second press the computer will beep and the letter T appear on the screen. The cursor will reappear in the next location. Then press: 1 — 1 — 2 and I will appear. Voila — ETI!

When the cursor is on screen, you can move it about by pressing C. A single press will shift the cursor along one character space. If you hold the key down it will move along the spaces from left to right. When it reaches the end of a line it will jump to the start of the next line. Upon reaching the end of the screen it will return to the top left hand corner and start again. Using the cursor, you can position your message where you like on the screen.

You can write up to sixteen characters on a line and you get four lines on the screen.

Back-spacing is done with the D key.

To correct an error, move the cursor over the incorrect character and type the token for the correct character. To erase a character, move the cursor into place and enter the code for the cursor. Move the cursor and the character will disappear.

The characters are generated using the method described in 'Hints for CHIP 8 programmers, part 1' in ETI December 1982, page 110 under the heading of 'Captions-to-screen movers'. Sixteen consecutive bits of data (two bytes) are moved into view on screen in a 3 x 5 matrix, making up the characters. This is very economical of memory space as it uses the least amount of data storage. Diagram 1 shows the general arrangement of the bytes and how the bits are positioned on screen in the 3 x 5 matrix. Note that the least significant bit (LSB) of byte 2 is not used. The most significant bit (MSB) of byte 1 appears in the top left hand corner of the matrix.




To display a character on screen, the data is shifted from its location in memory (07C6-7) to locations 07F4-5-6-7-8. Then, using the AMMM and DXYN instructions, this is shifted into position on screen, stacking the five bytes down the screen. Diagram 2 shows how it happens when you enter the code for the letter P.

c = cursor    d = back space


### CHIP 8 CHARACTER GENERATOR character code table

X	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
code	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0X	G	H	I	J	K	L	M	N	O	P	Q	R	S	T	U	V
1X	W	X	Y	Z	?	<	>	.	+	-	x	/	=	'	!	
2X																

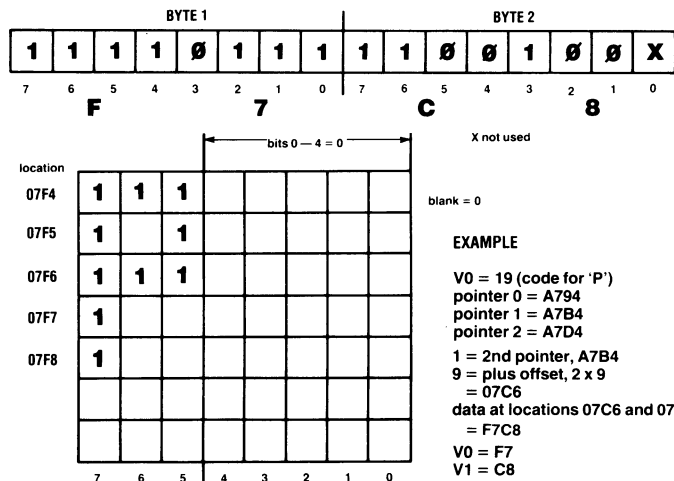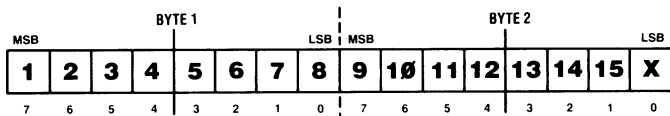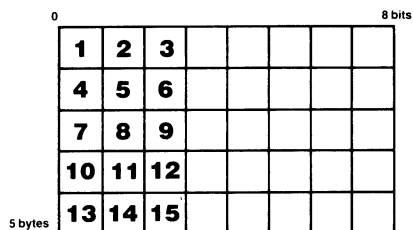X must be a hex number from 0 to F, e.g. a code of 28 gives +; 08 gives 8;  
2 C is the cursor.



VIDEO MESSAGE MAKER	273C do subroutine 073C	8030 V0 = V3	F6DF 0
0600 1602 go to 0602	DAB5 show N @ VX,VY	2786 do subroutine 0786	F7C8 P
6700 V7 = 00	7A04 VA = VA + 4	A7FA I = 07FA	F6F4 Q
6801 V8 = 01	0650 1610 go to 0610	F565 V0:V5 = MI	F7EB R
6902 V9 = 02	(character generator to be entered	0780 A7F4 I = 07F4	711D S
6C0C VC = 0C	from 073C)	00EE return	E925 T
6D0D VD = 0D	CHARACTER GENERATOR	8004 V0 = V0 + V0	07D0 B6DE U
6A00 VA = 00	073C A7FA I = 07FA	8004 " "	B6D5 V
6B00 VB = 00	F555 MI = V0:V5	8004 " "	B7FA W
0610 602C V0 = 2C	0740 630F V3 = 0F	8004 " "	B55A X
273C do subroutine 073C	8302 V3 = V3 AND V0	8042 V0 = V0 AND V2	B7A5 Y
DAB5 show N @ VX,VY	64F0 V4 = F0	0790 F055 MI = V0	E54F Z
273C do subroutine 073C	8402 V4 = V4 AND V0	00FF return	E789 ?
DAB5 show N @ VX,VY	A794 I = 0794	F6DF 0 #character data	2A22 <
ECA1 skip if VC # key	4410 skip if V4 = 10	4925 1 starts here	07E0 88A8 >
7A04 VA = VA + 4	A7B4 I = 07B4	E7CF 2	0003 .
EDA1 skip if VD # key	4420 skip if V4 = 20	E79F 3	0BA0 +
0620 7AFC VA = VA - 4	0750 A7D4 I = 07D4	96F3 4	0380 -
3A40 skip if VA = 40	8334 V3 = V3 + V3	F39F 5	1550 x
162E go to 062E	F31E I = I + V3	07A0 F3DF 6	0540 /
6A00 VA = 00	F165 V0:V1 = MI	E493 7	FFFF cursor
7B06 VB = VB + 6	A7F4 I = 07F4	F7DF 8	1C70 =
4B2A skip if VB # 2A	8200 V2 = V0	F79F 9	07F0 9000 '
160E go to 060E	8310 V3 = V1	F7DB A	4905 ! #character data ends
E7A1 skip if V7 # key	64E0 V4 = E0	D7DD B	4040 store for 5 display bytes
0630 163C go to 063C	0760 6580 V5 = 80	F24F C	4000
E8A1 skip if V8 # key	278E do subroutine 078E	D6DD D	2F80 store for 6 progr. variables
163C go to 063C	8020 V0 = V2	07B0 F3CF E	0BA0
E9A1 skip if V9 # key	2788 do subroutine 0788	F349 F	E080
163C go to 063C	8020 V0 = V2	F2DF G	(note: 07F4 - 07FF can be anything)
1610 go to 0610	8004 V0 = V0 + V0	B7DA H	DISPLAY CHARACTER SET
F00A V0 = key	8152 V1 = V1 AND V5	E92E I	0600 1602 6000 6B06 6A00 160A 273C DAB5
8004 V0 = V0 + V0	3100 skip if V1 = 00	24DF J	7001
0640 8004 V0 = V0 + V0	0770 7001 V0 = V0 + 1	B75A K	0610 7A04 3A40 1608 7B06 3B18 1606 F00A
8004 V0 = V0 + V0	2784 do subroutine 0784	924F L	00E0
F10A V1 = key	8030 V0 = V3	07C0 BFDA M	0620 1602
8014 V0 = V0 + V1	278C do subroutine 078C	F6DA N	then enter Character Generator from 073C.●

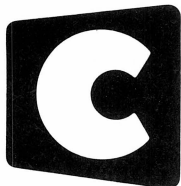

# Cromemco

## SMALL BUSINESS COMPUTERS

The power, speed and expandability needed for business, science, industry and education.

- Word Processing
- Data Processing
- Business Applications Software



FOR  
FURTHER  
DETAILS  
CONTACT:

# AE ADAPTIVE ELECTRONICS P/L

418 ST KILDA ROAD, MELBOURNE 3004. Ph: (03) 267 6800 (4 lines). Telex: AA32565

# THE UNIVERSE —from AED

"AUSTRALIA'S S100 SPECIALIST"

*This advanced system is the second generation of our famous Supercomputer.*

- \*6 MHz 8085 8 Bit CPU and 8 MHz 8088 16 Bit CPU in one computer
- \*20 slot IEEE 696 S100 Bus
- \*DMA floppy and/or hard disk, fixed and removable
- \* Unserial terminal

MORE END APPLICATIONS THROUGH MORE OPERATING SYSTEMS

CP/M \*CP/M + MPS \*CP/M - 86 + MPS \*MULTI/OS + MPS

\*MS - DOS \*MP/M - 86 'ETC'

**MPS** (MULTIPLE PROGRAM SELECTION)

**NO!** IT'S NOT MULTI USER **NO!** IT'S NOT MULTI TASKING

**YES!** IT IS ONE OF THE MOST SIGNIFICANT SINGLE ADVANCES IN OPERATING SYSTEM CONCEPTS EVER MADE IN THE INTEREST OF HELPING YOU, THE ACTUAL USER!

AT LAST YOU CAN LEAP FROM PROGRAM TO PROGRAM TO PROGRAM, AND LEAP BACK AGAIN — RIGHT BACK! EXACTLY TO WHERE YOU LEFT OFF, WITH THE SCREEN RESTORED. NOW YOUR SYSTEM CAN BE A COMPLETE ELECTRONIC OFFICE IN A WAY NOT POSSIBLE BEFORE.

\* SEE REVIEW MARCH ELECTRONICS AUSTRALIA \*

WE ALSO SPECIALISE IN S100 CARD SUPPLY AND CUSTOM BUSINESS AND INDUSTRIAL COMPUTERS.



ACOUSTIC ELECTRONIC DEVELOPMENTS PTY LTD

## MICROCOMPUTER PRODUCTS

130 MILITARY ROAD, GUILDFORD 2161. NSW.

TEL: (02) 681-4966 TLX: AA70664. OPEN 9-6 MON TO SAT.



Advance Australia

THIS MONTH is a potpourri of contributions from readers ('Bee owners all) on a wide variety of topics covering software and hardware.

For those who had difficulty with Tom Moffat's 'Bee-O-Rhythms' printout in the January issue, he's now got a proper printer (the Model 15 teletype has been pensioned off ...) and a better printout is reproduced here. Let's get on with a few hints and tips, then.

## INTEGER ACCURACY

Andrew Allan, Manly Vale NSW

Be careful of the effect of accuracy of functions when working with integers in mixed mode. Here's a good illustration. The following small program was intended to print a natural binary series — but, boy, did it go wrong!

```
FOR N=1 TO 10:Q=INT(2*FLT(N)):LPRINT ":",Q:NEXT N:END
2
3
8
16
32
64
128
256
512
1024
```

That 3 is not what you want. The problem is due to a change in sign of the error in the operator for raising a real to a power. Take a look at this:

```
FOR N=1 TO 10:Q1=2*FLT(N):LPRINT ":",Q1:NEXT N:END
2.0000003
3.9999968
8.0000145
16.0000018
32.0000007
64.0000084
128.000014
256.000041
512.000058
1024.0021
```

The solution is to always use a bias to offset things as INT rounds down. Do it like this:

```
FOR N=1 TO 10:Q=INT(0.01+2*FLT(N)):LPRINT ":",Q:NEXT N:END
2
4
8
16
32
64
128
256
512
1024
```

## CASSETTE BACKUP

Michael Alexander, Balaclava NSW

Here is a short routine that enables you to make backup cassette program copies. Note that, if you're doing this with a program purchased on tape, then the backup should be for your personal use only — resale of a copy or copies is a *breach of the Commonwealth Copyright Act*, which is now a *criminal offence*. You have been warned.

It is obvious that the easiest way to make a copy or backup tape is to simply use two recorders and dub from one to the other. This approach is sort of OK, but reliability can suffer because of the signal shaping circuitry in cassette recorders. They are not designed to handle square waves efficiently.

The approach I used was to employ two recorders still, but send the signal from one recorder to the other via the computer to square up the signal before recording. The routine below is written in BASIC for ease of use but the program only serves to enter a machine language subroutine.

To use it, first play the tape into the computer to check that it will load. While you're doing it, time how long it takes. If it loads OK, get rid of it and then load the program shown below. Type RUN and connect the lead which usually goes to the cassette earphone to the earphone output of the cassette player in which you are playing the tape. The other cassette lead goes to the microphone input of the recorder making the backup tape.

```
00100 REM Biorhythm program by Tom Moffat; 5,9,82
00110 REM To be used with or without printer.
00120 DIM T(12),S1(52)
00130 FN0=(SIN(FRAC(A1/#)*6.28)+1)*25+3
00140 CLS: INPUT "What is your name? ",N1$
00150 INPUT "Do you want a description? (Y or N)",K1$
00160 IF K1$="n" OR K1$="N" THEN 340
00170 CLS: PRINT " Well, ";N1$; ", now is your chance to see if you"
00180 PRINT "will prosper or wither, live or die. The theory of BIORHYTHM"
00190 PRINT "states that life exists in three cycles, all starting at birth."
00200 PRINT " The PHYSICAL cycle has a period of 23 days, the EMOTIONAL"
00210 PRINT "cycle is 28 days, and the INTELLECTUAL cycle is 13 days,"
00220 PRINT " When a cycle is UP the function is operating at peak"
00230 PRINT "efficiency; when it is DOWN the function is resting, storing"
00240 PRINT "energy for the next UP phase. At the zero crossing the"
00250 PRINT "cycle is said to be CRITICAL, a time when caution is"
00260 PRINT "indicated. When two cycles coincide at CRITICAL the day is"
00270 PRINT "said to be 'double-critical'. When all three coincide at"
00280 PRINT "CRITICAL the day will be a total disaster."
00290 PRINT " Now, ";N1$; ", you may say this whole concept is a"
00300 PRINT "load of old codswallop. If so, press BREAK to exit the program."
00310 PRINT "But if you're game, press any other key to continue."
00320 K1$=KEY$
00330 IF K1$="" THEN 320
00340 CLS
00350 INPUT "PLEASE ENTER YOUR BIRTHDAY (DD,MM,YY):" D,M,Y
00360 GOSUB 790
00370 A=Z
00380 INPUT "WHEN DO YOU WANT YOUR CHART TO BEGIN (DD,MM,YY)?" D,M,Y
00390 GOSUB 790
00400 A=Z-A
00410 INPUT "AND FOR HOW MANY DAYS?" L
00420 DATA 31,28,31,30,31,30,31,31,30,31,30,31
00430 FOR I=1 TO 12
00440 READ T(I)
00450 NEXT I
00460 OUT#5 ON
00470 CLS
00480 PRINT TAB(10); "*** PERSONAL BIORHYTHM CHART FOR ";N1$; " ***"
00490 PRINT TAB(10); "Physical = P; Emotional = E; Intellectual = I"
00500 PRINT
00510 PRINT " "; "DATE";
00520 PRINT TAB(13) "DOWN";
00530 PRINT TAB(35) "CRITICAL";
00540 PRINT TAB(62) "UP"
00550 PRINT " ";[A62 45]
00560 A1= FLT(A)
00570 P=INT(FN0(23))
00580 E=INT(FN0(28))
00590 I=INT(FN0(33))
00600 FOR X=0 TO 52
00610 S1$(X)=" "
00620 NEXT X
00630 S1$(28)="."
00640 S1$(P)="P"
00650 S1$(E)="E"
00660 S1$(I)="I"
00670 PRINT STR(D); STR(M); STR(Y); TAB(10);
00680 FOR X=0 TO 51
00690 PRINT S1$(X);
00700 NEXT X
00710 PRINT S1$(52)
00720 IF L=1 THEN OUT#5 OFF: END
00730 L=L-1
00740 A=A+1
00750 D=D+1
00760 IF M=2 AND D=29 AND Y=(Y/4)*4 THEN 560
00770 IF D<=T(M) THEN 560 ELSE LET M=M+1: D=1
00780 IF M<12 THEN 560 ELSE LET M=1: Y=Y+1: GOTO 560
00790 M1=FLT(M): Y1=FLT(Y)
00800 Z=INT(30.57*M1)+INT(365.25*Y1-32537.25)+D
00810 IF M<3 THEN RETURN
00820 IF Y=(Y/4)*4 THEN LET Z=Z-1 ELSE LET Z=Z-2
00830 RETURN
```

Play the original tape into the computer and simultaneously record it with the other recorder. Having already timed how long it takes, let it run the required time plus a few seconds more to be on the safe side.

Having made your backup, load it into the computer in the usual way to test it.

The backup copy is always of inferior quality to the original, you'll find. Always use the backup and put the original in a safe place. If the backup fails for one reason or another, just make another copy from the original.

The program will work on all tapes, even machine language ones.

## THE 64K+ AND ETI-668 EPROM PROGRAMMER

Geoff Nicholls, ETI

If you have the 64K+ MicroBee, like we do, and want to use the ETI-668 EPROM Programmer project with it (February '83 issue), then you'll need to make a small modification to the software. The 64K+ has the monitor residing from E000 hex, so here's what you do:


- change location 0E32 to E0 (was 80)
- change location 0F03 to E0 (was 80)
- change location 0EAB to 76 (was 09).

# AUDIO CRITICS RAVE ABOUT THE V15 TYPE V:

"Our tests show that the Shure V15 Type V not only lives up to the claims made for it, but in virtually every respect OUTPERFORMS the best cartridges we have previously tested . . . It is hard to imagine how the V15 Type V could be improved significantly. It offers the MOST PERFORMANCE in the most areas, plus the most convenience and safety in installation and operation." - **Julian Hirsch, Stereo Review, June, 1982.**

"... (The V15 Type V) is definately the FINEST pickup Shure has ever made, which makes it one of the finest ever made, period." - **High Fidelity, July, 1982.**

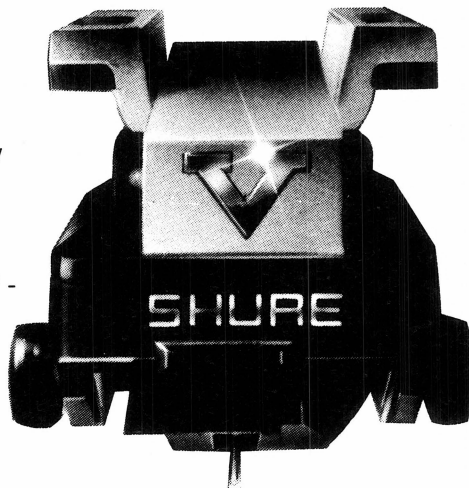"... In a world of audiophile discs with demanding tracking requirements, the Shure V15 Type V



KEEPS AHEAD of the times." - **Rich Warren, Chicago Sun-Times, June 4, 1982.**

"(The V15 Type V) REDEFINES its maker as a pioneer in cartridge design not only from the beginnings of microgroove technology but well into the future of the LP disc." - **FM Guide (Canada), June, 1982.**

"... It may be safe to say that this cartridges excellent tracking ability is NUMBER ONE in the world. Provides exquisite and elaborate sound." **Swing Journal (Japan), May, 1982.**

# SHURE



AUDIO ENGINEERS P/L

342 Kent Street  
Sydney NSW 2000  
(02)29 6731

NOMIS ELECTRONICS (S.A.)  
(08)293 4896

AUDIO ENGINEERS (Qld)  
(07)369 9670

AUDIO ENGINEERS (Vic)  
(03)44 3295

MARKETEC Pty Ltd  
(09) 335 8275

## SUBSCRIPTIONS BACK ISSUES BINDERS PHOTOCOPIES BINDERS

### ORDER FORM

I enclose \$ . . . . . for (tick appropriate box/es). All prices include postage.  
Send orders to: ETI, Federal Publishing, 140 Joynton Ave, Waterloo NSW 2017.

☐ **Subscriptions** \$25.75 per year within Australia \$ . . . . .  
\$39.00 overseas (surface mail) \$ . . . . .  
Airmail rates on application

☐ **Back issues** \$2.50, available from November 1978.

☐ **or photocopies** \$2.50 per article per issue  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .

Please attach a list if more than four required.

☐ **Binders** No. . . . . @ \$6.10 in NSW \$ . . . . .  
No. . . . . @ \$7.50 in other states \$ . . . . .

NAME (Please print)

ADDRESS . . . . .

Please debit my ☐ Bankcard  
☐ American Express card

Number: . . . . .

Signature . . . . .

## Ortofon MC 2000 cartridge

Ortofon claim that the MC 2000 is the world's first ortophase cartridge. The ortophase concept is the optimal interplay between amplitude response and phase response, based on tests which showed that the best sounding cartridges were actually those that had a practically linear phase response together with a frequency response that showed a rise of approximately 2 dB at 20 kHz.

The output voltage of this moving coil cartridge at 1 kHz, 5 cm/s is 0.05 mV. At 1 kHz the channel balance is less than 1 dB and the channel separation is better than 25 dB. The channel separation at 20 kHz is greater than 18 dB.

The frequency range is 5 Hz to 90 kHz and the amplitude response is 5 Hz to 50 kHz, from 5 dB to 1 dB.


The FIM distortion is less than 1% and the tracking ability at 315 Hz, at the recommended tracking force, is better than 100 µm.

The MC 2000 stylus is a

symmetrical contact line diamond with a recommended tracking force of 15 mN/1.5 g.

The equivalent stylus tip mass is 0.27 mg which is achieved by using a light aluminium cantilever of conical shape, a tiny diamond and a very small cross-shaped aluminium armature. The legs of the cross are hollow, reducing the mass by 66% in comparison to traditional armature designs.

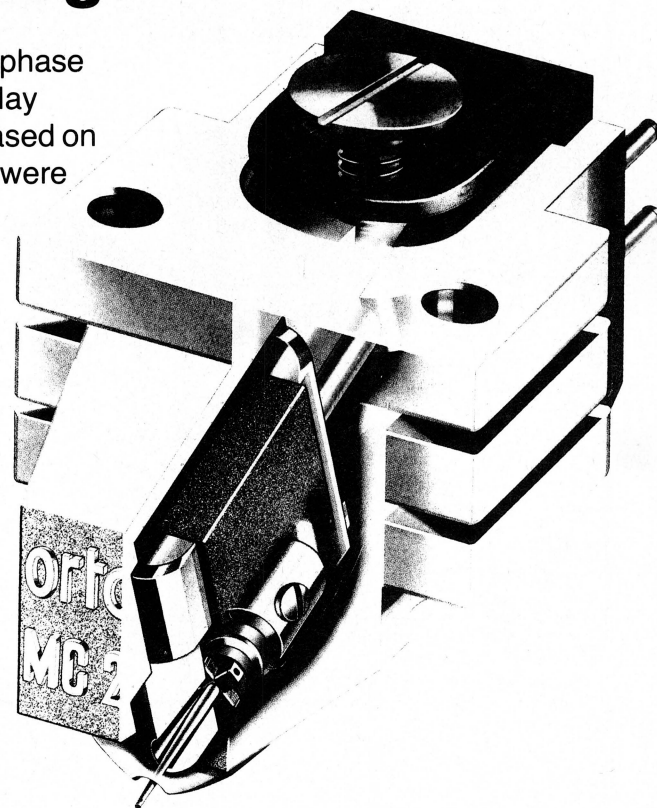The magnesium headshell which was designed for the MC 2000 has a standard Ortofon/SME plug.



## Cut the static in your car radio/cassette player

Noise generated by a vehicle's ignition and other electrical components can ruin your enjoyment of a program on your car radio or tape playing in your cassette player.

Benelec Pty Ltd offer a range of vehicle noise suppressors that can restore peace and quiet to your car radio/cassette player.

Although your vehicle may be fitted with ignition 'suppressor' leads, ignition noises can be conducted along the 12 V battery cables and into your radio/cassette player via its power lead.

Benelec's 'hot line' noise suppressor kit, catalogue no. 11-105, will get rid of that source of noise, in most cases, when inserted in the car radio/cassette player's power lead.

To get rid of persistent noise from your vehicle's alternator/generator, Benelec has no less than four suppressors to tackle the problem.

For cars fitted with alternators,

you can choose from the 11-101, a light duty type, the 11-102, a heavy duty type (for vehicles with batteries from six to 32 volts) and the extra heavy duty type, rated to carry 100 amps, the 11-104.

The 11-103 is a 'tunable' generator filter, rated to carry 25 amps, and is especially suited for suppressing generator whine in CB rigs and HF transceivers.

A feedthrough noise suppressor to get rid of the last vestiges of annoying alternator/generator whine and regulator clicks and plops is also available, catalogue no. 11-110.

Full details can be obtained from Benelec Pty Ltd, P.O. Box 21, Bondi Beach NSW 2026. (02)665-8211.

## RCA plans to release CED Disc System soon in Europe

For the initial launch of its CED Video Disc System RCA will be supplying discs from its disc manufacturing plant in Indianapolis USA.

According to Jay Brandinger, vice-president and general manager of RCA SelectaVision Video Discs operations, "The hardware and software facilities are ready for mass production while marketing and distribution matters are in current negotiations".

European CED players are expected to be offered by a number of brands presently doing business in Europe. Demonstrations have been given showing the compatibility of CED discs with both the PAL and SECAM television systems.

Dr. Brandinger said that while the disc size is the same for both the NTSC and European systems, the latter employs a slower rotational speed of 375 rpm and 50 Hz frequency, compared with 450 rpm and 60 Hz in NTSC

countries. The CED European players feature visual scanning, forward and reverse at four times, 16 times and 120 times normal speed, random search and pause, stereo sound and two-channel bilingual sound.

## New address for Dynaudio

Dynaudio (Aust) Pty Ltd have transferred their facilities to 274 Victoria St, Brunswick Vic. 3056. (03)387-6170. Tlx AA38348.

They are appointing new dealer outlets throughout Australia and have released two new fully imported models of loudspeakers, the DA100 and DA200. ►

# Why Direct

## Don't tangle with Technics.

The majority of audio systems – even the most beautifully designed – have something ugly to hide.

It's that mass of jumbled-up connecting leads that you find, all too easily, at the rear of the equipment. Not only are they ugly, they're inconvenient, too.

And as audio components become smaller, the problem becomes bigger and more unsightly.

To solve this problem, Technics developed their Direct Connector systems, which eliminate all audio connecting leads between the tuner, amplifier, graphic equalizer and cassette deck.

Each of these components features a special flip-up connector to allow them to be literally plugged in to each other!

It's an elegant piece of Technics technology that results in a stylish, neat installation that can be put together or taken down for re-location in a matter of seconds.

## The 315 Series.

But Direct Connector capability is not the only innovative feature in this new and compact series from Technics.

The SL-5 direct-drive, linear-tracking turntable employs its own plug-in connector system for the pickup cartridge.

This unique Technics development has been adopted as a World Standard.

It means you can compare and evaluate cartridges from leading manufacturers like Audio Technica, Ortofon, Shure, Stanton, Empire, Pickering, ADC and, of course, Technics without conventional setting up procedures.



# Technics developed Connector systems.

No adjustment of tracking weight or bias correction is needed.

The innovations continue in the rest of the components: the SU-5 amplifier includes a Super Bass switch to enhance the bass response of a speaker system without inducing bass boom; the ST-5 quartz synthesizer digital tuner provides random access memory for 16 pre-set stations; the SH-E5 graphic equalizer – offers adjustment of 12 audio bands from 16Hz to 32Hz on each channel; whilst the RS-5 cassette deck – has soft touch controls, auto selection of metal, CrO<sub>2</sub> and normal tape settings plus convenient Cue and Review functions.

Finally, a pair of SB-F5 speakers with horn-type tweeters and bass reflex porting turn the high quality electrical signals of the rest of the system into the high quality sound you expect.

**Compact components, full-size warranty.**

All components in this series are perfectly matched in styling and performance.

And all are covered by a full 2-year warranty backed by Technics' reputation. Visit your Technics stockist soon and experience the superb styling and brilliant sound of Technics' compact Series 315 for yourself.



## Technics

National Panasonic (Australia) Pty Ltd


Expanding the music experience.

## Sony chairman awarded the Albert medal

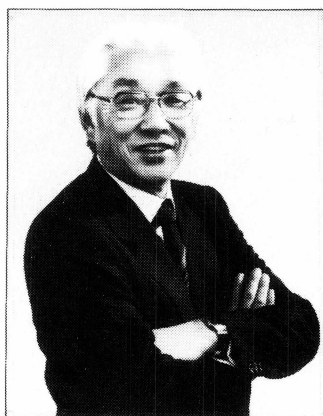**Akio Morita, Chairman and Chief Executive Officer of Sony Corporation, has been awarded the Royal Society of Arts 1982 Albert Medal.**

He received the medal from HRH The Duke of Edinburgh, President of the Royal Society of Arts, for his "Outstanding contributions to technological and industrial innovation and management, industrial design, the development of recording and video systems and the growth of world trade relations".

This is the first time that a person from outside Europe or America has received an Albert



medal.

Sony established Sony (UK) Ltd in 1968, as a wholly-owned subsidiary. In 1980 Sony (UK) received the Queen's Award for export excellence.

## Pioneer develops 'still pictures with sound' for videodisc

**Pioneer Electronics has developed the technology to add sound to still pictures on its laser optical video disc.**

The principle of the 'Still Picture with Sound' system (SWS) involves the compression of soundwaves using a special technique, before they are digitised and recorded on the portion of the disc where picture images would have been recorded.

A still picture associated with the sound is then recorded on the next portion, allowing a still picture with approximately 13 seconds of accompanying sound to be played back.

The standard 30 cm videodisc currently available on the market is capable of storing 54 000 still pictures without sound and will run for about 20 hours. But this will be extended to 50 hours or longer if the clarity of sounds are restricted to the level of telephone quality.

Pioneer plans to introduce the SWS system into the business use market within two or three years for training and education. The disc edited for SWS can be played back with the addition of an adaptor to the current player model.

Pioneer now has four Laserdisc models available, including the LD-600 which is used exclusively for movies and music programmes.

Laserdisc was introduced into the European market late in 1982 at a cost of approximately \$900.

It is expected that Europe will follow the American and Japanese example by using videodiscs as 'records that reproduce pictures', while also taking advantage of features such as random access

which enables instantaneous search for a desired picture and the function to view a still picture for a long time.

20 cm (8") discs, which will enable soft disc makers to meet the needs for less expensive software, will soon be introduced to complement the 30 cm discs currently available. The new discs will be used primarily in the domestic market.

Pioneer is now manufacturing laser videodiscs in a fully-automated factory in Japan. By the middle of 1983 there will be a Pioneer disc pressing plant in California US.

Commercial use of the system is expected to be boosted by the Pioneer Videodisc interface IF 1000 which can be used to connect the Laserdisc system with a personal computer.

This interface will increase the ways in which the Laserdisc can be used with personal computers by allowing the picture and sound of Laserdisc to be programmed freely with the personal computer.

The interface part can be connected to almost any printer board of a personal computer and, by using the display switching function, one monitor can be used for both the personal computer and the Laserdisc.

For more information contact **Mr. Ron Ward, Pioneer Electronics Australia Pty Ltd, 178 Boundary Rd, Braeside Vic. 3195. (03)580-9911.**



## Computerised microphone discussion systems

**The International Congress Service, Microphone Discussion System (Digimic Mini) consists of a standard 19 inch central control unit, operator's console, delegate discussion microphone desk stand and microphone with built-in loudspeaker.**

The built-in loudspeaker allows decentralised sound reinforcement, without the need of large loudspeakers or sound columns, which may cause feedback or echoes. The electret microphone is insensitive to mechanical vibrations and electromagnetic interference.

The individual microphones are centrally controlled by a microprocessor according to the

programmable mode of operation which may be selected on the operator's console.

The Digimic Mini uses single cable technology and has the capacity for 63 microphones.

The system is available for sales or rental from **R.H. Cunningham Pty Ltd, 146 Roden St, West Melbourne Vic. 3003. (03)329-9633.**





## National's new range of video equipment

**National has predicted that in 1983 the demand for portable video cassette recorders and cameras will double that of 1982.**

Their new range of portable video equipment and accessories includes the NV-100A light-weight portable VTR which is one third smaller and is almost 40% lighter than previous models. It features cue and review (x9 speed), insert edit, slow motion playback and up to two hours portable recording.

The NVV-10A compatible deluxe tuner timer features 14 day 4 programme timer, 16 function cordless remote control, auto search tuning for up to 16 different channels and one touch timer recording.

The WVP-50N hand held colour camera weighs 1.7 kg and features auto-focus through an ultra sonic system, advanced picture quality for high resolution, electronic viewfinder, automatic audio video fade in and fade out

and automatic white balance.

The WVP-100N shoulder mount camera has all the features of the WVP-50N plus a special character display facility which allows recording of the filming date, tape counter and memory function, stop watch and camera function check and battery charge level indication.

The WVP-30N hand held colour camera weighs only 1.5 kg and has an electronic viewfinder and one touch slide zoom.

Accessories for the WVP-100N are a remote controller for the camera and the recorder, film slide adaptor and zoom lens.

More information can be obtained from National Panasonic (Aust) Pty Ltd, 95-99 Epping Rd, North Ryde NSW 2113. (02)887-5333.

## AM stereo broadcasting under way in the US

**Station KTSA in San Antonio began stereo broadcasts on the AM band (540-1630 kHz) late in July last year, followed by some 25 other stations in the latter half of 1982.**

Many of the new stereo stations employ the 'Kahn system' of modulation where the carrier is phase-modulated with L-R signal and then amplitude modulated with the L+R signal. Sophisticated circuitry produces the broadcast signal which has the left channel on one sideband and the right channel on the other. The system has the advantage that, when tuned on an ordinary

receiver, it demodulates the signal as R+L, and the listener is unaware that the station is transmitting a different signal.

Stereo reception of the Kahn system requires the receiver to have phase detection as well as AM envelope detection to separate the two channels. (For more information, see ETI, July 1977, pages 12-13.)

## Pioneer unveils digital audio disc player

**At the Brisbane Home and Outdoor Exhibition Pioneer took the wraps off their digital audio disc player and discs which will eventually replace the conventional turntable and long playing records.**

With the Pioneer Digital Audio Disc, the recorded information is encapsulated in a transparent protective coating that is fully accessible to the laser beam optical pick-up. Each 120 mm diameter disc contains over five billion digital sound signals which are laid out in a helical track and are scanned from the centre outwards.

The digital technique provides many significant performance advantages over the conventional audio system. There is no rumble, wow or flutter with a flat frequency response between 5 to 20 kHz.

There is negligible noise or distortion with a dynamic range of 90 dB. Channel separation is over 90 dB against 30 dB for a good conventional record player and there is no sound colouration.

As there is no disc contact with the laser pick-up the skip, index scan, repeat and search functions are very fast.

The digitally recorded information is sealed inside the disc within the transparent plastic coating so it is safe from dust, scratches and fingerprints.

Major record companies in Europe, the United Kingdom and Japan are currently pressing new titles in the digital audio disc format for a progressive worldwide launch this year.

Pioneer expects to launch the digital audio disc and player in Australia sometime this year at a cost of approximately \$750 per player. Discs will be available through conventional record outlets at approximately \$15 each.

For further information contact **Mr. Ron Ward, Pioneer Electronics Australia Pty Ltd, 178 Boundary Rd, Braeside Vic. 3195. (03)580-9911.**



## Video cassette recorder manufacturers warn retailers

**Evidence of possible infringements of Section 52 of the Trade Practices Act has prompted manufacturers of Beta format video cassette recorders to issue a warning to retailers.**

Indications suggest the Beta format manufacturers are totally disenchanted with the dishonest attitude being demonstrated by some video retailers who are making deliberately misleading statements to prospective VCR purchasers regarding the different video formats.

Beta manufacturers have undertaken an Australia wide survey of video dealers and pre-recorded video software resellers in an attempt to determine which retailers are contravening Section 52 of the Trade Practices

Act.

A spokesman for the group, Managing Director of Toshiba (Aust) Pty Ltd said, "Sufficient information in the form of signed statements by the principals of the companies manufacturing Beta format machines has been printed and published to ensure that no doubt exists in the minds of the retailers of Australia as to the future of the Beta format".

For more information contact **Mr. T. Thacker, c/o Toshiba (Aust) Pty Ltd. (02)887-3322.**

# ARE YOU MISSING OUT?

You've spent hundreds or maybe thousands of dollars on your hi-fi. Great amplifier, superb turntable, fantastic speakers. But are you getting all the sound you paid for? Probably not . . . if the vital connections between your hi-fi components aren't made using the Monster Cable system of precision cables, connectors and accessories.

Monster Cable is a proven interconnect system that will dramatically increase audio performance and provide the best acoustic value-for-money improvement you're ever likely to make to your hi-fi.

If you're really serious about your sound system and the listening pleasure you derive from it . . . read on!

## MONSTER CABLE

### AUSTRALIA'S LARGEST SELLING SPEAKER WIRE SYSTEM

The rapid improvements in power amplifiers and loudspeakers have focused attention on a major weakness — the speaker cable system.

By eliminating the problems associated with conventional wire, Monster Cable directly couples your amplifier to your speakers without loss, without distortion.

How? More copper, finer strands, higher purity and a unique winding configuration that lets your amplifier and your speakers make beautiful music together. For sounds that are dynamic and powerful, open and clear. The way real music should be.

And more! Monster Cable provides big performance for little dollars. You can significantly improve the performance of your sound system simply by switching from your conventional speaker wire to Monster Cable — it costs you less than buying better speakers, a better amplifier, or even a better cartridge.

However . . . beware the imitators. They offer price but not quality. Only the finest materials are used in producing Monster Cable. And it is safe to use with all amplifiers, regardless of design.

Monster Cable is available conveniently pre-packed in 3.7 metre (12 ft), 6.1 metre (20 ft) and 9.1 metre (30 ft) pairs, or can be professionally cut and terminated in custom lengths at your local Monster Cable dealer.


## PERFORMANCE STANDARD SERIES

### INTERLINK/PHONOLINK

Designed specifically for transmitting low level audio signals, Interlink sets a new standard of performance and value in interconnect cables — for turntables, pre-amplifiers, tuners and tape decks. (And video equipment as well.)

Interlink features a special ULTRA LITZ conductor — over 100 separately insulated strands of high purity copper. This inner core allows the most accurate signal transfer without high frequency loss.

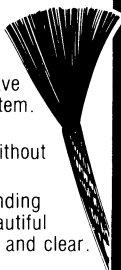Monster Cable has also developed and produced the perfect termination for Interlink cable — Phonolink, a precision gold-plated RCA-type plug.



Phonolink features a split centre shaft for increased contact pressure and materials that reduce interference with the audio signal to an absolute minimum.

Sonically, Interlink/Phonolink combine to maximise your sound system's performance for increased clarity, greater dynamic range, lower distortion and reduced hum and RF interference.

Interlink/Phonolink is available in pre-packaged 1 metre pairs or can be cut and terminated to the exact length you require by your Performance Standard Series dealer.

## POWERLINE

Powerline is a four conductor, controlled impedance speaker cable that has been designed as the ultimate link in the amplifier-speaker interface.

Based on the high purity, fine copper stranding construction of Monster Cable, Powerline utilizes two conductors for each polarity. This results in extremely low resistance and a greater surface area of conductivity for maximum power transfer at all frequencies.

Sonically, Powerline brings you one step closer to the musical event. Startling clarity in the highs, tight well-articulated bass, dynamic impact and the precise localisation of instruments within the sound stage enhance your aural experience.

Powerline is available in custom cut and terminated lengths from your local stockist. He'll also be able to demonstrate the advantages provided by this new technology, which make Powerline a lifetime investment in your listening pleasure.

## AND WHATEVER THE CONNECTION . . . MONSTER CABLE CAN MAKE IT

**Gold Pin.** The smallest and perhaps the most universal of our amplifier-to-speaker connectors.

**Gold Spades.** Beautiful construction with hard gold surfaces to make the ideal connection with many of today's amplifiers and speakers.



**Gold Banana.** An elegantly simple connector, using a crimp-on design with multiple fingers, that can significantly reduce contact distortion.

**X-Terminator.** An expanding solid shaft tip provides both greater contact area and high contact pressure — the ultimate banana-type connector.

**Cramolin.** Oxidation and contamination, which attack every connection point in an audio system, can now be corrected and prevented.

Cramolin Red solution removes distortion-producing oxides and corrosions, while Cramolin Blue solution preserves and protects cleaned contacts from any further deterioration.

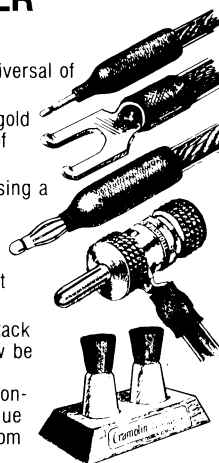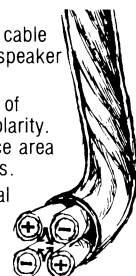*The Monster Cable interconnect systems and accessories are available at all leading hi-fi stores. Happy listening from all of us at Monster Cable.*



## Get all the sound you paid for...

# MONSTER CABLE

Distributed by Convoy Sydney (02) 698 7300

RG/C1594



## Sony Betamovie: top secret

**Sony has made an unofficial announcement about a new product called Betamovie but details of its specifications are classified information until it is due to be launched.**

Betamovie is a combined camera/recorder using standard half inch Beta tape. It is a record only machine. It has no playback facilities but a tape recorded with Betamovie can be played on a conventional Beta VCR.

Betamovie is not a 8 mm video as it has been derived from a totally different concept. And it is not the same as Betacam which

is for professional usage.

It will be approximately half the size of the SL-F1E video recorder, weigh about 2.5 kg and have a recording time of 3.25 hours with L-750 tape.

Betamovie is a PAL system and will be released in Japan in July and in Australia in December. It will sell in Japan for about \$1000.

## The sound that doesn't go round

**There's a lot of talk that the compact disc is the digital audio disc system of the future. But Soundstream, the digital recording company, has developed a digital playback system where the software is in the form of a non-moving card.**

The system, called the AudioFile, is based on a card the size of a conventional 125 x 75 mm index card and has the thickness of a credit card. The card will store up to 45 minutes of audio and can contain up to 600 M of digital data. For non-audio purposes such as video and computer software a larger card can be used.

Unlike the Compact Disc, which is injection moulded from a stamper, rather like a normal LP, the AudioFile is duplicated by a photographic process. This should make it more reliable and less expensive to produce than rotating discs.

The AudioFile also encodes the audio signal as a digital bit stream which is read by a low power laser beam, but the data is stored in a different manner from the CD system. The data is split into discrete traces which are then scanned, raster fashion, by a moving spot of light.

The data is written as a

sequence of spots and spaces on the photographic medium in a series of discrete arcs. To read the data, rather than go in for the complicated servo and speed control of CD, a rotating disc with focusing microscope objective lens mounted on its periphery causes the laser beam to scan an arc on the card surface.

Using simple on-axis optics and clamping to ensure a flat record means that there is no need for a complicated focus servo mechanism.

As the working distance between the record and the scanning disc is so large the entire optical system can be sealed. This should increase reliability and could even reduce costs.

Another positive factor for the AudioFile is that the low cost of mastering/duplicating cards will make it viable for short production runs suitable for specialist musical interests.

## Robust mic connectors

**A range of robust multi-pin microphone plugs and sockets is offered by the Sydney-based importer and distributor, Benelec Pty Ltd.**

The range comprises two in-line plugs, three in-line sockets, two panel mount sockets and a panel mount plug.

Straight and right angle in-line sockets in two-pin, three, four, five, six, seven and eight-pin versions are stocked along with a straight in-line plug in two-to eight-pin versions. A panel mount socket to suit these is

also available. This group of connectors is listed in Benelec's catalogue from number 4-501 to 4-528.

In addition, a set of plugs and sockets that mate with Canon connectors is stocked. There is an in-line plug (4-561), an in-line socket (4-563), a panel mounting plug (4-562) and a panel mounting socket (4-564).

Benelec also carry a range of DIN connectors and 6.5 mm jacks.

For further details contact **Benelec Pty Ltd, P.O. Box 21, Bondi Beach NSW 2026. (02) 665-8211.**

## Denon's dynamic servo tracer tonearm

**High compliance cartridges and lightweight tonearms help improve tracing, but Denon believe that their new dynamic servo tracer tonearm goes further to complete improvements in performance.**


In conventional tonearms the low frequency resonance is a function of the compliance of the cartridge and the effective mass of the tonearm. If the level of this resonance is too high the results are IM distortion, an increase in crosstalk, excessive wear on both the stylus and record and damage to the stylus cantilever.

The dynamic servo tonearm features electronic damping in both the horizontal and vertical planes to minimise and control low frequency resonance. Denon

claims that tracing is improved in even the most abnormal groove conditions, such as those found on hard-to-trace warped or off-centre records.

Originally designed for Denon's top-of-the-line DP-100M turntable, the dynamic servo tracer tonearm can now be found on several medium priced Denon turntables.

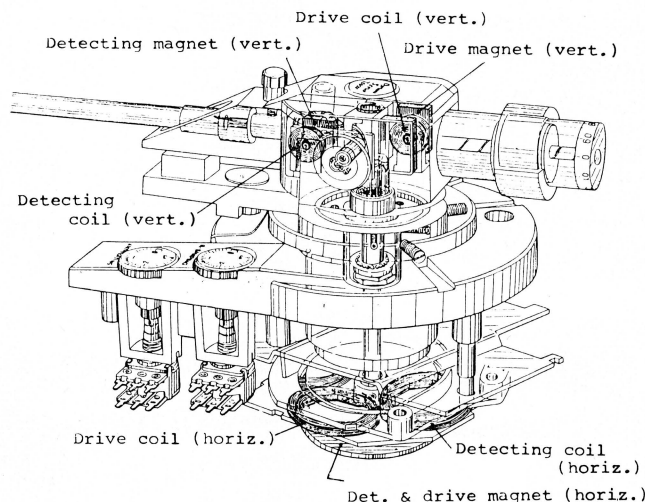For more information contact **AWA-Thorn, 348 Victoria Rd, Rydalmere NSW 2116. (02) 638-9022.**



# trim, taut and terrific

Mini  
&  
Slim

Here, at last, are the portable radio cassette recorders with the really big performance. Tough enough to handle, with sound reproduction you'd expect from a full size stereo.

See and hear one now at your nearest retailer...you may even take one home. But-that's life.



**SANYO**

*That's Life!*



M7880K




M7770K



M-W25F



M7000

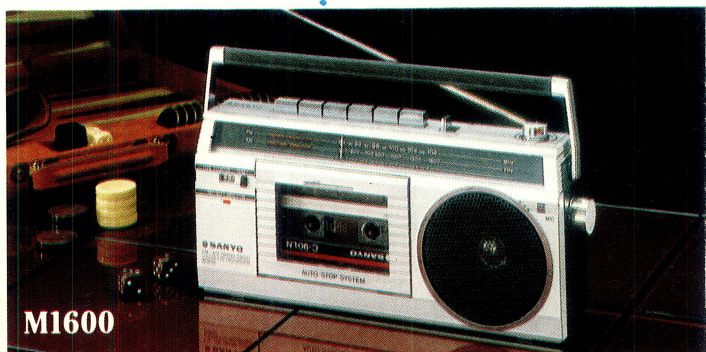

M1600

# Pioneer A-8 amp re-tested

The strange story of a schizoid amplifier and how Pioneer have a 'world beater' on their hands but haven't let the world know about it.

BACK IN JUNE last year we published Louis Challis' review of the Pioneer A-8 stereo amp. Louis said the A-8 had one major virtue: "...the quality of sound it can produce." Performance was very good at low and high power levels. THD at 1 kHz was 0.0036% (36 parts per million) and at 1 kHz/90 W it was 0.0018% (18 ppm). TIM was also very low.

Shortly after the review appeared we were contacted by Edward Cherry, Associate Professor from the Electrical Engineering Department of Monash University, Melbourne. He said he was surprised that the distortion was so high as Pioneer was employing his distortion-lowering technique of nested differentiating feedback loops (NDFLs), and paying royalties to do so.

As it turned out, that particular amplifier we measured did not incorporate Cherry's NDFLs. We subsequently obtained an A-8 through Monash University, purchased at a large Melbourne hi-fi retailer, and ran a second series of distortion tests.

We later learned that Pioneer produced

two 'series' of the A-8, the latter series incorporating the NDFLs, the earlier series without. Pioneer's brochure on 'stereo amps and tuners A-9/A-8/A-7/A-6/A-5/F-9/F-7/F-5' has one paragraph mentioning nested feedback loops, crediting Associate Professor Cherry. According to Pioneer, the A-8, A-7, A-6 and A-5 all incorporate NDFLs or, as the Japanese prefer, NFLs.

Pioneer, to our knowledge, have not publicised the fact that their amplifiers employ the NDFL technique — either in the technical press or in the general media. The only mention we can find is in that one brochure. Pioneer — we think you should make more of it, plus its origin.

Further reading on the subject can be found in *Audio Amplifiers Using Nested Differentiating Feedback Loops*, ETI October and November 1982.

## The re-test


As you can see, the latest version of the A-8 amplifier containing the NDFLs has distortion figures that are an order of magnitude

superior when compared with the original version.

The distortion levels are so low that they really are at the threshold of our ability to measure them — (what do I do now if they develop better amplifiers?). Equally significantly the IEC High Frequency Total Difference Frequency distortion performance is also excellent, particularly at the higher power levels where the performance is almost half an order of magnitude better than the best amplifier we had previously seen (Marantz SM6 in class A mode, which was better at low power level).

The nested feedback circuit has converted what was an excellent amplifier, into what must now be described as a *superb amplifier*. Bravo Associate Professor Cherry! Bravo Pioneer! But why no fanfare? Don't they realise what they have produced? (Next marketing step will obviously be a class A amplifier with nested feedback circuit which will drive us right up the wall if my guess is not wrong.)

**Louis A. Challis**

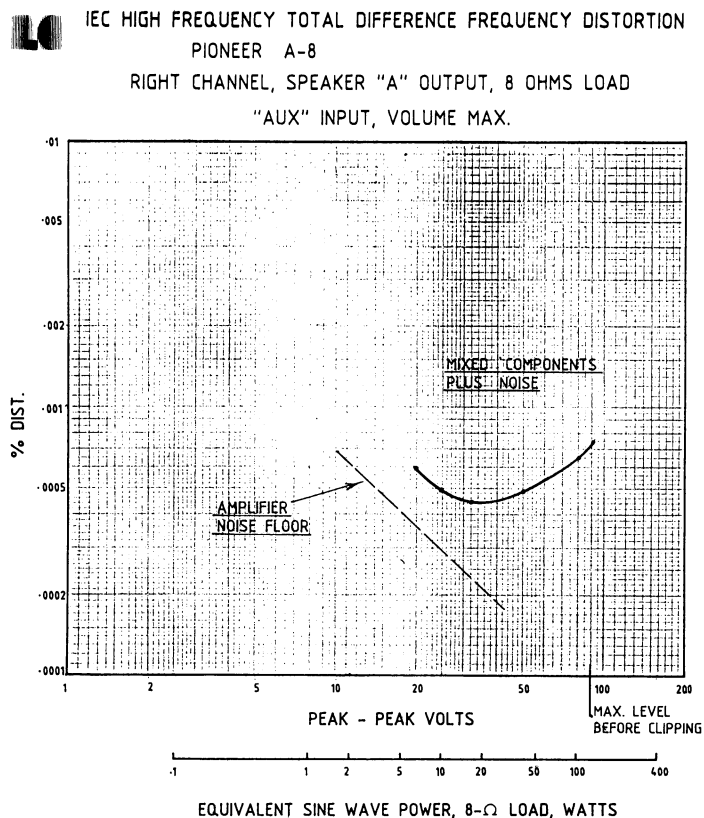

MEASURED PERFORMANCE OF: PIONEER AMPLIFIER MODEL A-8  
SERIAL NO. CC95011955

### HARMONIC DISTORTION:

@ 1 watt into 8 ohms

	100Hz	1kHz	6.3kHz	
2nd	-100.6	-101	97.0	dB
3rd	-85.4	-	-	dB
4th	-107.3	-	-	dB
5th	-	-	-	dB
THD	0.0055	0.00089	0.0014	%

@ 90 watts into 8 ohms

	100Hz	1kHz	6.3kHz	
2nd	-89.8	-111.7	-112.0	dB
3rd	-81.4	-105.2	-112.0	dB
4th	-116.9	-	117.0	dB
5th	-98.6	125.4	-	dB
THD	0.0092	0.0006	0.00038	%
(residual hum in amplifier)				

### LAC Generator and Analyser Threshold Distortion Values

	100Hz	1kHz	6.3kHz	
2nd	-116.4	-	-119.0	dB
3rd	-104.2	-122.8	-121.5	dB
4th	-	-	-	dB
5th	-	-	-	dB
THD	0.00063	0.00007	0.00014	%
(residual hum)				

# Shure V15 type V cartridge



Exciting results. An absolutely stunning performance shows that the conventional microgroove record is still a force to be reckoned with. This excellent cartridge could not be improved upon with the current technology.

WHEN SHURE BROS decided to make cartridges for record players some thirty or more years ago it is doubtful whether they were aware of the impact they would have on the world of home entertainment. But now their industry is threatened by the new and exciting medium of laser discs. These digital discs may well change the future of the recording industry and in particular, the preferences as to which equipment will be used to play our music.

Notwithstanding any threat to the medium, Shure Bros and most of their competitors are actively engaged in developing new cartridges to overcome the performance limitations which are common to all record player cartridges. The areas for concern are, in order of importance, trackability, frequency response, frequency linearity, channel separation and signal-to-noise ratio, together with the one parameter that is seldom discussed in much detail by manufacturers, the life of the cartridge. The life of the cartridge depends on the ability of the stylus assembly to withstand abuse and also depends on the rate of wear on the stylus which is a function of the stylus configuration chosen.


Most of the international reviewers who have spoken on this subject have stated that frequency response is the most important parameter in a phono cartridge. I just don't agree and both Shure Bros and I believe that the most important parameter is track-

ability. 'Trackability' is defined as the ability of the stylus to faithfully follow the path between the sides of the record player grooves. Shure Bros have stressed the trackability feature of their top line cartridges in their literature and ever since 1966 have presented in their 'Audio Obstacle Course' records what have been the industry standards for trackability tests. The release of the V15 type V is no exception to this rule and, for those people fortunate enough to purchase the new cartridge, the manufacturers provide a copy of their new record to assist in assessing the new cartridge's performance.
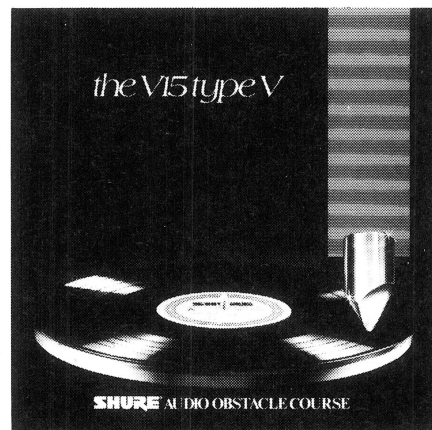
## Features

The V15 type V, like all the other cartridges in the Shure range, is a moving magnet configuration with a hyperelliptical nude diamond tip. This configuration is remarkably similar to that used for the now famous Shibata type CD4 tip. The hyperelliptical stylus was selected because it produced significantly lower tracking distortion than either a conventional spherical tip or a biradial tip. The microwall stylus shank assembly has a diameter of only 0.04 mm and a wall thickness just a shade thicker than 0.01 mm.

Shure decided to use a thin walled beryllium stylus support arm which incorporates a much smaller diamond tip than any



**Obstacle course.** The Shure TTR117 test record, available from Audio Engineers, the Shure distributor.


**Louis Challis**

## SHURE V15 TYPE V CARTRIDGE

Weight:	6.6 g
Price:	Rrp \$299
Manufactured:	In USA by Shure Bros, Illinois
Distributor:	Audio Engineers, 342 Kent St, Sydney NSW 2000 (02)29-6731.

previous Shure cartridge. By using beryllium they achieve very high strength and very low weight. I consider that this is about as far as they can take the current technology and materials without thinking of developing some entirely new esoteric material. Obviously Shure are intent on decreasing the effective moving mass of the cartridge and claim that they have achieved a 40% reduction compared with the type IV model.

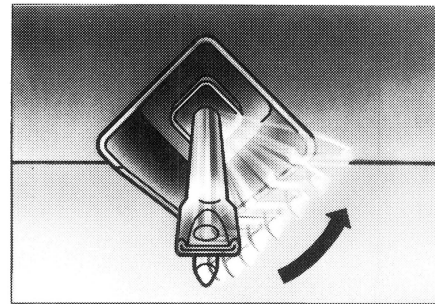The benefits of such a change are obvious. Firstly, they have been able to shift the stylus tip resonance from approximately 22 kHz to almost 33 kHz. This allows them to achieve a flat frequency response within the desired 20 Hz to 20 kHz audio band. More



**Side-guard.** This illustration shows how Shure's 'side-guard' system responds to side thrusts on the stylus by withdrawing the entire stylus shank and tip safely into the stylus housing before the shank can be damaged.

importantly, with a lower mass in the stylus assembly, the ability to cope with higher tracking velocities in the latest generation of digital and 'direct to disc' recordings is now a reality.

Shure claim that the new type V cartridge can track signals at speeds of up to 80 cm/s at 5 kHz and as our measurements have shown, the velocity levels are almost this high in the majority of the best (and most expensive) recordings now being produced in America and Europe.


The cartridge incorporates a number of other features which are designed to protect the cartridge against abuse. The most significant of these features is the 'side guard' stylus assembly which enables the entire assembly and tip to be withdrawn into the housing when exposed to a significant sideways thrust. It also incorporates a 'dynamic stabiliser' which consists of a damped carbon fibre filter brush. This brush, which precedes the stylus on its path around the record, is intended to reduce the effect of the tone arm resonance and simultaneously improves the tone arm's tracking over warped records. This brush also cleans out the dust and debris which may lurk in front of the unsuspecting stylus.

In keeping with the latest research work undertaken in their laboratories, Shure have introduced a new jargon or 'buzz word' which they call the 'Total Trackability Index' (TTI). They define this as the trackability factor  $\times$  the indentation factor. The theory behind this system is described on the associated TTR 117 record cover jacket.

The indentation factor is defined as the relationship between tracking force, the tip geometry and the amount of record wear. Obviously the vinyl or plastic based records deform (indent) as a result of the passage of the stylus through the groove of the record. Provided the indentation is not too severe, the vinyl will go through a plastic mode of deformation, with the extent of restoration being a function of the force applied to the surface of the groove. Different stylus tip characteristics have different areas of contact and so the tracking force is obviously a function of the surface area of the tip which makes contact with the record grooves. The rate of wear of these grooves is a direct function of the indentation depth and is consequently a function of the velocity and the exposed surface area of the stylus tip. The latest generation of hyperelliptical nude tips provides a 25% to 26% improvement in performance over a typical spherical stylus. This means that the record played by this stylus will suffer 26% less wear than that produced by a spherical tip.
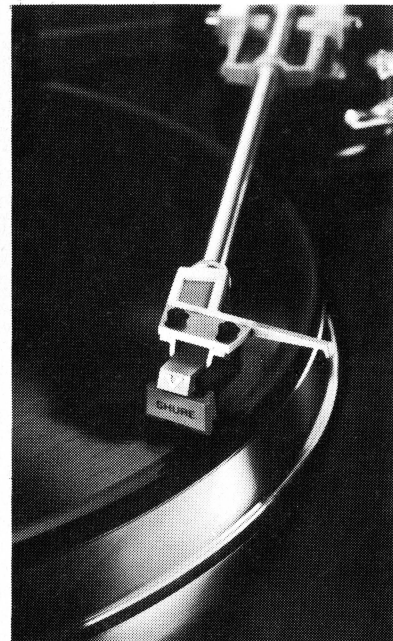
## Aligning the cartridge

The cartridge arrived in an unusual plastic box which I soon discovered doubles as an alignment gauge. They have attached a dummy stylus assembly to the gauge so that you will not damage your new toy as you



**Precision alignment.** To ensure that the V15 type V cartridge's performance is optimised by accurate orientation in the tone arm, precision alignment instrumentation is provided with each cartridge. This includes the Shure-designed Duo-Point Alignment Gauge (left) and Leveling Alignment Stylus (right) which simplify accurate alignment. The Duo-Point gauge accurately establishes correct lateral tracking geometry for minimum distortion during playback. The Leveling Alignment Stylus aids in optimising channel separation by providing a means with which to judge cartridge body orientation relative to the record surface.

enthusiastically position it correctly in the tone arm. The alignment gauge is provided to allow you to check whether your head shell is parallel to the record surface. This is absolutely essential if proper stereo separation is to be achieved. The box also incorporates a series of small plastic self-adhesive shims to allow the cartridge to be tilted and adjusted where rotational geometry is not provided as part of the head shell or tone arm assembly.

A second alignment gauge is provided which allows you to align the cartridge for minimum lateral tracking distortion. By adjusting the cartridge to have the correct overhang, the minimum overall distortion can readily be achieved. This particular alignment gauge is called the duo-point alignment gauge and adjusts the cartridge at the correct distances of 66 mm and 120.7 mm from the record centre.


Each cartridge is supplied with its own individual calibration sheet. This provides specified levels of output at 5 cm/s, the channel balance parameters, channel separation at both 1 kHz and 10 kHz, the trackability at 400 Hz and both left and right channel frequency responses.

It is interesting to note that the V15 type V sold in the United Kingdom is not supplied with as much comprehensive information as those sold in Australia. I presume that the Americans either believe that the Australians are a more sophisticated market or they require more technical information than their United Kingdom counterparts.
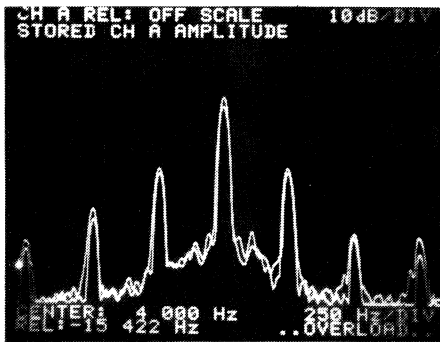
## Test conditions

I asked the local agents if they wanted to supply the cartridge in one of the latest SME arms, which have in the past been the preferred and favoured tone arm assembly recommended by Shure Bros. The local agent assured me that the V15 type V will work in *any* tone arm and would make it perform better than it would with any other cartridge. Taking the agent at his word, I decided to avail myself of the opportunity to assess the V15 type V in the Audio-Technica type AT1010 DTS Universal Tone Arm. This particular tone arm is a j-shaped aluminium unit with an effective length of 241.3 mm from the pivot to the turntable centre and it is mounted with a gymbal based on precision ball bearings. The head shell is machined from die-cast magnesium alloy which is covered by a rubber solution to damp out resonance modes. The tone arm tube is mounted above vertical pivots so that the stylus of the cartridge will be positioned in the plane of the pivots when playing the record. This minimises warp, wow and changes in the vertical stylus angle.

The counter weight at the far end of the tone arm incorporates the tracking force scale calibrated from 0 to 2.5 g in 0.1 intervals and the rear of the arm is vibrationally isolated with rubber from the front portion. The suspended mass can thus supply anti-resonant compensation for the main low frequency resonance between the total



**Trackability test.** Using a 400 Hz and 4 kHz two tone test signal on the Shure TTR 103 test record. The graph shows the difference between the distortion components at the peak tracking signal on the record when superimposed on the base level. The velocity was recorded at 15 cm/s and 24 cm/s on two tracks.

effective arm, cartridge mass and the compliance provided by the cantilever mounts. A small knob on the top of the arm pivot provides adjustable damping so as to vary the stiffness of the elastic coupling between the two sections of the tube. On one side of this arm is a balance weight to compensate for lateral imbalance. This is supplemented by a gyro balance weight that can be shifted vertically to compensate for the vertical period of swing of the tone arm. The effective arm mass, without the cartridge,

is about 18 g which is not low but it does provide a reasonable degree of stability in the system.

I mounted the V15 type V cartridge and the tone arm on the Luxman PD444 direct drive turntable which allows two tone arms and cartridges to be evaluated simultaneously on the same record in the measurement set up.

## Testing

The testing sequence that followed provided a great deal of information on the performance that this cartridge can achieve when correctly mounted in a good tone arm. The testing also provided a great deal of information on the tone arm itself.





The frequency response of the V15 type V is typically  $\pm 0-2$  dB from 20 Hz to 10 kHz with a very smooth frequency response that is less than 3 dB down at 20 kHz. The channel separation is typically 35 dB at midband in the left channel and better than 30 dB in the right channel when measured on either the JVC TRS 1007 or the Bruel & Kjaer 2009 test records. These figures are just about the records' limits so that the indicated results are very good. The frequency response is only 6 dB down at 35 kHz, when measured on the Denon XG-7002 test record, which is an exceptionally good performance.

The indicated cartridge resonance utilising the same test record lies between 30 and 33 kHz which is also excellent. I tested the cartridge with a 1.25 g tracking weight and found that the cartridge would happily track with just the slightest suggestion of distortion at a velocity of 24 cm/s at 400 Hz with a superimposed 4 kHz test tone.

Other audio test records which I used are the Shure TTR 103 and TTR 109, Audio Technica AT 6605 and JVC 1005. Surprisingly Shure do not provide trackability signals in any of their standard test records at the 80 cm/s velocity level that they refer to. So on the straight objective testing, using the material I currently have available such as the orchestral bells and other test signal material, we measured velocities up to 60 cm/s. The conventional test material, especially the two tone test records, provide very good evaluation material for objective tests.

I spent a lot of time analysing these signals on our fast Fourier analyser and although I was able to measure distortion levels and transient intermodulation signals all the way up to 40 cm/s, the cartridge nonetheless has what I would classify as very satisfactory tracking and excellent trackability performance.

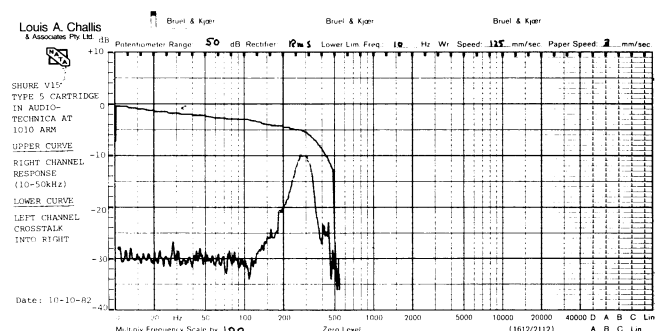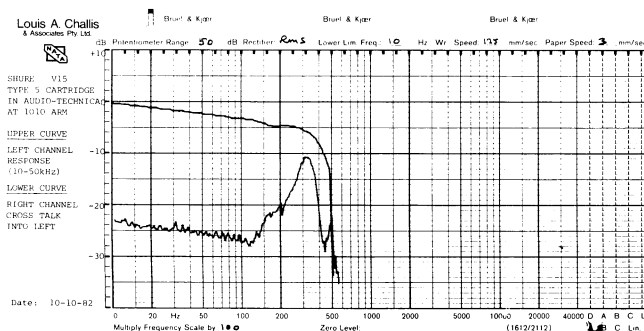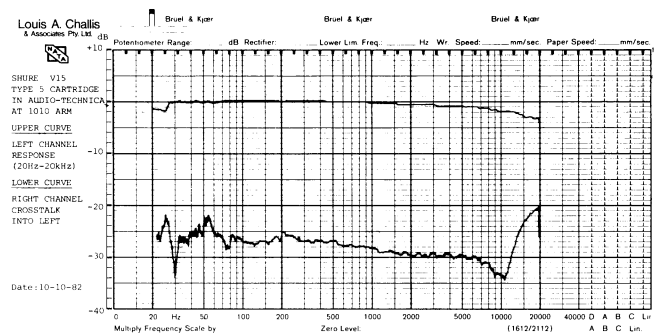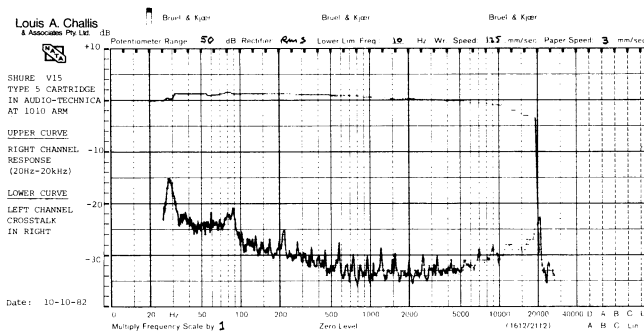Another factor of equal interest is the effect of the dynamic stabiliser on the tone



arm resonance. This is displayed particularly well in the graph below. This shows a 7 dB drop in the resonance peak of the tone arm at 5.5 Hz which is altered to a new resonant peak at 6.5 Hz when the stabiliser brush is used during the resonance playback evaluation. The overall maximum rise at 6.5 Hz, compared with the 20 Hz signal, is only 7 dB. I measured the distortion with and without the stabiliser in use and found that the distortion level rises by a small but measurable amount when the stabiliser is used. The stabiliser thus has a number of attributes and one liability!

## Subjectively

Of course the question is 'how does it perform on *real material*'? The first record I chose for the subjective evaluation was a Sony CBS DR Master Sound Digital Recording 28AC703 with Hiroko Nakamura playing selected pieces from Greig. By a strange quirk of circumstances I received the first laser disc player to reach Australia with exactly the same pieces of music digitally recorded on disc.

Without pre-empting that review I was able to compare the performance of the Shure V15 type V cartridge with the same material replayed digitally. The results were exciting because the V15 type V cartridge performs exceptionally well and shows that the conventional microgroove record is still a force to be reckoned with. The piano playing projected a superlative quality with depth, colour, vitality and warmth being fully displayed.

The second record I chose to play was the Sheffield Track Record (lab 20) which does contain really nasty peak velocities exceeding 70 cm/s at midband and low frequency velocities well above 30 cm/s. The cartridge seemed to revel in its role and I enjoyed listening to the music which it produced. The V15 provides an absolutely stunning performance and is undoubtedly a worthy successor to the V15 type IV.

All in all the V15 type V is an excellent cartridge highlighting a situation in which the designers have now reached the top of the development curve, with no new technology and few new avenues available to them to improve what is already a fine product. ●



## MEASURED PERFORMANCE OF SHURE V15 TYPE V CARTRIDGE

**SERIAL NO :** 007027

**SENSITIVITY :** Right Channel 0.64 mV/cm/sec  
Left Channel 0.62 mV/cm/sec

**CROSSTALK :**

	100Hz	1KHz	6.3KHz	
Left into Right	- 28	- 35	- 32	dB
Right into Left	- 27	- 28	- 29	dB

Left into Right minimum @ 28KHz 5dB  
Right into Left minimum @ 32KHz 5dB

## -tone ARM RESONANCE :

5.5 Hz (see attached graph)


## FREQUENCY RESPONSE

20 Hz  $f_0$  35 KHz (see attached graphs)  
(allowing for arm cable capacity)

## HARMONIC DISTORTION

Left Channel		50Hz		1KHz		6.3KHz	
	Stabiliser	With	Without	With	Without	With	Without
(1st Column using stabilizer with tracking weight to suit)	2nd	-52.0	-53.9	-43.7	-42.9	-33.5	-29.2 dB
	3rd	-55.6	-56.1	-47.8	-49.0	-45.7	-39.6 dB
	4th	-	-	-55.6	-	-44.0	-37.4 dB
	5th	-	-	-	-	-	- dB
	THD	0.3	0.25	0.71	0.80	2.7	3.8%

Right Channel		50Hz		1KHz		6.3KHz	
	Stabiliser	With	Without	With	Without	With	Without
(1st Column using stabilizer with tracking weight to suit)	2nd	-46.9	-49.8	-29.5	-32.3	-31.2	-31.1 dB
	3rd	-53.5	-54.1	-33.9	-35.3	-28.4	-33.1 dB
	4th	-56.3	-	-42.3	-41.2	-34.5	-42.6 dB
	5th	-	-	-48.7	-49.5	-	- dB
	THD	0.52	0.38	4.0	3.1	5.1	3.6%

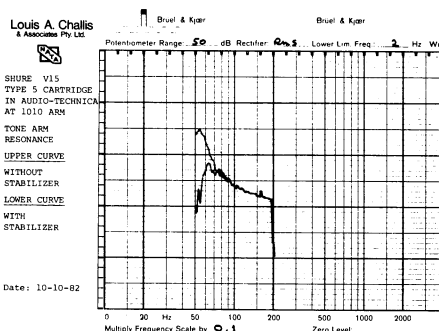

# The slickest way to get car grease out of your hair.

Getting rid of grease from your car engine used to be a headache. Then Kitten came along and invented two magic products that do the whole job quickly and thoroughly.

Simply ask for Degreezo or Jet Spray Degreaser from The Kitten System.

Jet Spray Degreaser eats oil and grease, swallowing the build-up on the engine and chassis.

Jet Spray Degreaser will not harm paint, metal or lacquer. Just spray on, let it work for five to ten minutes, and then hose off. The job's finished.

If you prefer a paint-on application to an aerosol, try Degreezo in the economical 750 ml pack.

Paint it on engines, extra dirty motor parts or your oil-stained driveway and stand back to watch Degreezo lift out the muck.

Degreezo's specially developed formula dissolves oil and grease, so all you have to do is hose it off, leaving your parts as bright as the day you bought them.

So, to get car grease out of your hair permanently, ask for either Jet Spray Degreaser or Degreezo from The Kitten System.




KIW 311/3






## THE KITTEN SYSTEM.

### THE CREAM OF CAR CARE.

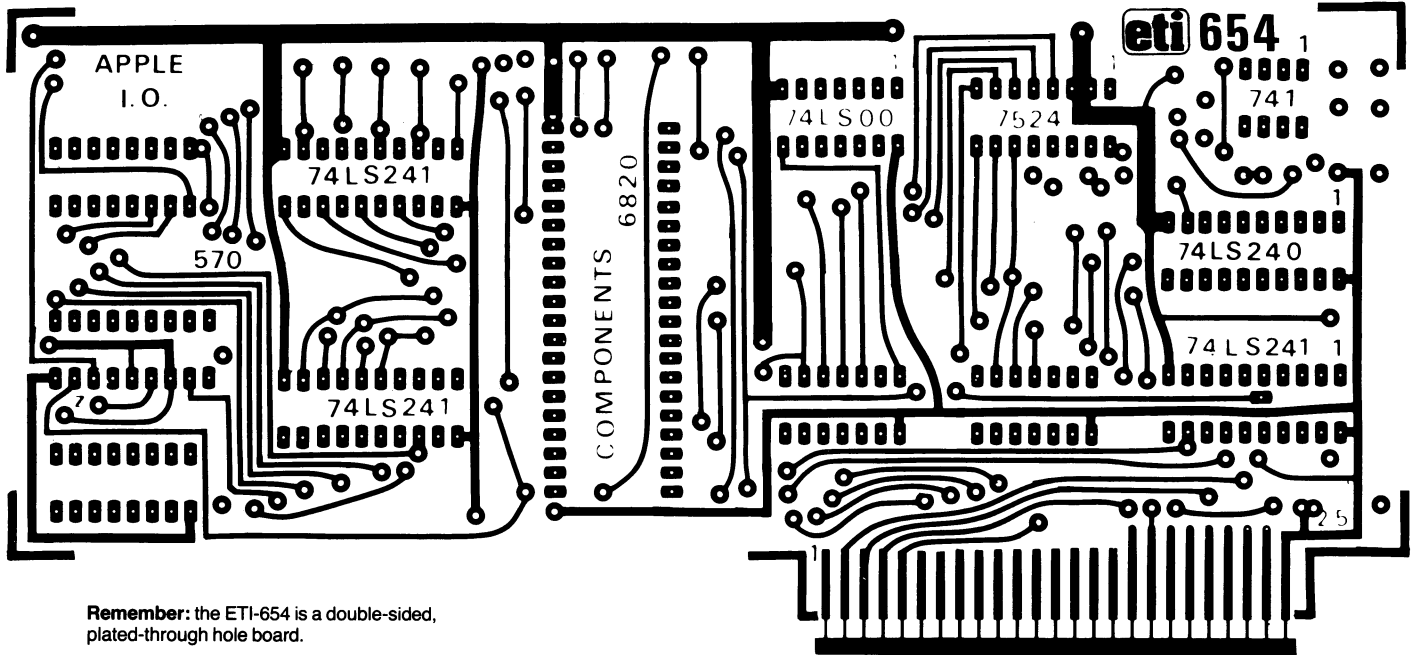

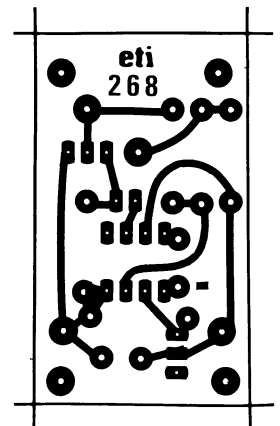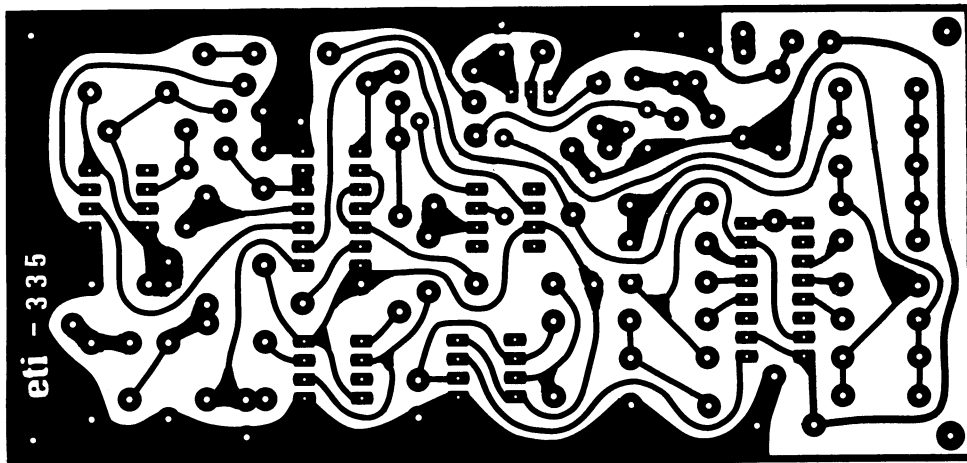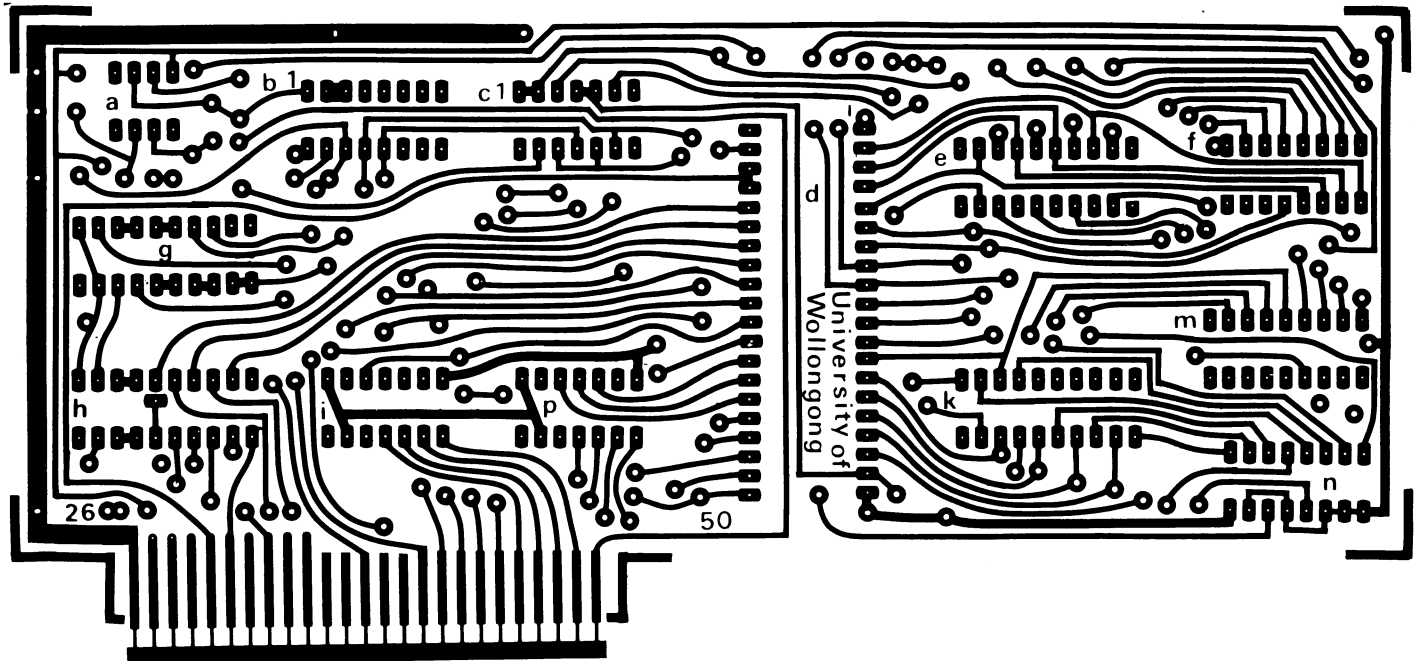**Remember:** the ETI-654 is a double-sided, plated-through hole board.



# MINI-MART

## Where readers can advertise — For Sale/Wanted/Swap/Join

● We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy **must** be with us by the 1st of the month preceding the month of issue. Please — **please** — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received; however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable:

● **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:

**ETI Mini-Mart,**  
4th Floor, 15 Boundary St,  
Rushcutters Bay NSW 2011.

### AUDIO

**NAKAMICHI 1000.** Best offer. Mint condition. Used less than five hours. Reason for sale — cassette format not used. Contact John (02)977-2357 ah.

**SELL: PEAK HI-FI stereo amplifier,** 30 W each channel, Kemstar wide band AM tuner, Silcron belt drive turntable, speakers. The lot \$140. Lower Blue Mts. (047)39-2464.

**SELL: KEYBOARD INSTRUMENT,** Kimber-Allen SKA. Best available. Factory mounted with pads, springs, silver contacts and wipers, 37 keys. Unopened. Half price at \$170. (03)29-1820.

### COMMUNICATIONS

**SIGNAL GENERATOR MARCONI TF801A/1,** AM/CW, 10 to 310 MHz, output calibrated attenuator range 100 dB in 1 dB steps, 0.2 V to 2 uV, fully metered, brand new with handbook, \$250. VK2ASZ, (047)39-4109.

**APX6 1296 MHz trscvr** with 240 V P/S-audio unit, \$40. Copies of conversion articles for APX6 trscvrs, 20 pages, \$9. VK2ASZ, (047)39-4109.

**FOR SALE: COLLINS 32RS1 H/F SSB 100 W base station Trcvr,** 240 Vac, \$400. VK2ASZ, (047)39-4109.

### COMPUTERS

**DISK DRIVES,** dual 8" DS DD REMEX 4001 with power supply, \$1100 ono. Two 5¼" MPI 92 quad density DS drives, \$475 ono. Ring between 6.30 and 9.30 pm (051)34-7836. Morwell Vic.

**Z80 STARTERS KIT** by SD Systems. Fully expanded, 2K RAM, 4K ROM, Hex keypad and display, cassette interface and S100 expansion. Full documentation, \$250. G. Bond, Potts Rd, Cranbourne Sth Vic. 3977. (059)78-2613.

**ETI-640 VIDEO BOARD,** complete and working, \$100 ono. ETI-680 CPU board, requires final assembly, \$175 ono. ASCII keyboard, \$60. ETI-636 terminated motherboard, c/w 3 connectors, \$60. G. Bond, Potts Rd, Cranbourne Sth Vic. 3977. (059)78-2613.

**MEMORY FOR Motorola Exorciser Buss,** 8K RAM, (2114), \$60 ono. 16K RAM (2114), \$90 ono. Ring between 7 pm and 9.30 pm (051)34-7836. Morwell Vic.

**ZX81, 16K, books, manual, tapes, games cassette player.** Complete \$265. Consider swap for pocket computer. (065)83-2679 ah. Ask for Michael.

**FOR SALE: NEW dual 8" floppy disk drives** suitable for double density. \$1000 ono. Suit Cromemco or other S100 microcomputers. (02)376-2830.

**VDU CARDS,** stand alone. 64 x 16 SCVT-100, \$170 ono. 80 x 24 Video Plus II, 6502 based, \$299 ono. Ring between 6.15 and 9.30 pm. (051)22-1157.

**SELL: TRS-80 Model 1,** keyboard and case. Keyboard in working order, \$35. John Peschar, 134 Main Rd, Marks Point NSW 2280. (049)45-3616.

**SELL: SINGLE BOARD 6502 computer,** 48K RAM plus BASIC, full keyboard, graphics etc, \$450. (09)401-4652 ah.

**OSI SUPERBOARD II,** 8K RAM, power supply, monitor and full documentation. Two BASIC games books. Must sell, \$400. Dane Howe (03)350-1646.

**MICROBEE 16K software,** Adventure #1 and Astrofighter (action space game). \$9.95 each + \$1.50 postage. J. Burns, 6 Banksia St, Townsville Qld 4814.

**SUPER 80, 48K RAM,** character gen, EPROM BASIC, custom metal case, power supply mains filter, \$300. Phone Newcastle (049)82-8606.

**SELL: CRAIG M100 translator,** six modules included, only \$115. All in A1 cond. Cost over \$200. Contact Paul, 586 William St, Mt Lawley WA 6050.

**FOR SALE: PDP11, 64K, DEC tapes,** VT50, console emulator, documentation, \$1500. Centronics 101A printer, \$450. 16K DEC memory, \$350. Two Memorex 601 Winchester 50MB drives, \$350. Offers or trade quality hi-fi/photo equipment. Norm (03)534-1192.

**SELL: Z80, S100 microcomputer.** Includes DGZ80 CPU, DG640 VDU, expandoRAM with 32KB, power supply, keyboard, monitor and lots of software, \$650. Gordon (02)587-3449.

**MICROBEE FINANCIAL MANAGER:** a cheque account program with account file SAVE/LOAD. Instructions, listing (8 pages) \$8. With tape \$13. H. Proctor, 27 Roberts Avenue, Mordialue NSW 2223.

**HOBBY COMPUTER:** 2650 CPU, 16K RAM, dual VDU, built-in cas. rec, 110/300/3000 baud, I/O ports, RS232, video and RF outputs, assembler, BASIC, software, CCT diagrams etc. \$225. (08)336-4114.

A MICROBEE OWNERS club would be a great idea. If you can't find a club or you are interested in starting one send a SSAE envelope to Colin Johns, 6 Tunks St, Waverton NSW 2060 and I will send you the latest information.

**FLOPPY DRIVE:** Brand new, unused 8 inch 2S2D Remex RFD4000 and full maintenance manual. Sell \$570. Craig, 110 Greeves St, Fitzroy Vic. 3065. (03)341-8549 bh.

**SELL: MICROBEE 16K plus editor/assembler,** manuals, six cassette programs including chess, ztrek, target. \$395 ono. John Petersson, 15 Robinson St, O'Connor ACT 2601. (062) 72-3711 bh.

**VP111 OWNERS:** get 16K for \$90 not \$450! RAM and EPROM can be mixed and battery backup optional. \$10 for circuit and construction information. D. Hutchinson, 69 Bulla Rd, Bulla Vic. 3047.

**ACT VIC 20 bimonthly newsletter.** Many interesting articles and programs. February issue \$1. Bimonthly \$8 per year. Write to Chris Groenhout, 25 Kerferd St, Watson ACT 2602.

**WANTED: Dr. Dobbs issues or copies.** Nos 33, 34, 35, 40, 41, 45, 48. Phone James (03)534-1272 ah.

### MISCELLANEOUS

**SELL: SCALEXTRIC SLOTCAR set,** 13 m track, two cars, electric transformer, excellent condition, \$150 ono. Use with ETI-824/825 controllers. Robert Roseby, 46 Ham St, Cloncurry Qld 4824.

**GAMES: LED multisport, LCD 'Dr. Dental' watch,** \$10 ea. LCD racer, 'Lion' watch, TV game, Cylon Voice (kit), \$5 ea. As new, some in box. (02)84-6564.

**SELL: 19 inch ALUMINIUM RACK mounting boxes** with extendable sliding mountings, 13 x 43 x 43 cm, some with fans, \$100. Brett Billett, 3/21 Hargrave St, Scullin ACT. (062)54-9508 ah.

**SELL: Train layout, yard type layout,** with turntable, engines, wagons, partially wired, all electric points, \$180 ono. Ring Mr. S. Sidoti after 5.30 pm. (02)660-5120.

**FOR SALE: SB-4-350 AEG impact drill,** 4-speed, good condition, \$60. Ring Mr. S. Sidoti after 5.30 pm. (02)660-5120.

**FOR SALE: ONE 65 metre length of heavy duty,** 25 core, multi strand cable, \$65. (02)456-1604 after 6 pm or (02)239-9472 bh.

**SELL: TTY MODEL 15,** good condition, with SC/MP microcomputer and ASCII baudot converter. SC/MP and TTY manuals included, \$70. (07)208-7247. Slacks Creek Qld.


**WANTED: INTERNATIONAL correspondence school,** electronics course, Phase One texts, notes etc, complete or incomplete. Will pick up anywhere in Sydney. (02)709-1746.

**WANTED: CIRCUIT DIAGRAM/manual** for Simpson model 312 VTVM. G.J. Hill, 64 Robe St, Grange, Brisbane Qld 4051. (07)356-7727 ah.

**SELL: ONE HOBBY-BLOX IC starter pack** (Part No. 921490-R). Good condition, \$15. B. Begg, 18 Sturt Ave, Toorak Gdns SA 5065.

**DIGITAL FREQUENCY meter (EA),** 20 MHz adaptable to 200 MHz, \$80. Audio signal generator 0-30 kHz sine/square, digital synthesised sine wave, \$60. Sinclair DM350 digital multimeter with circuit diagram. Precision instrument when it worked. Consider offers. (062)48-2719 bh.

# THE HOBBYIST'S MANUAL

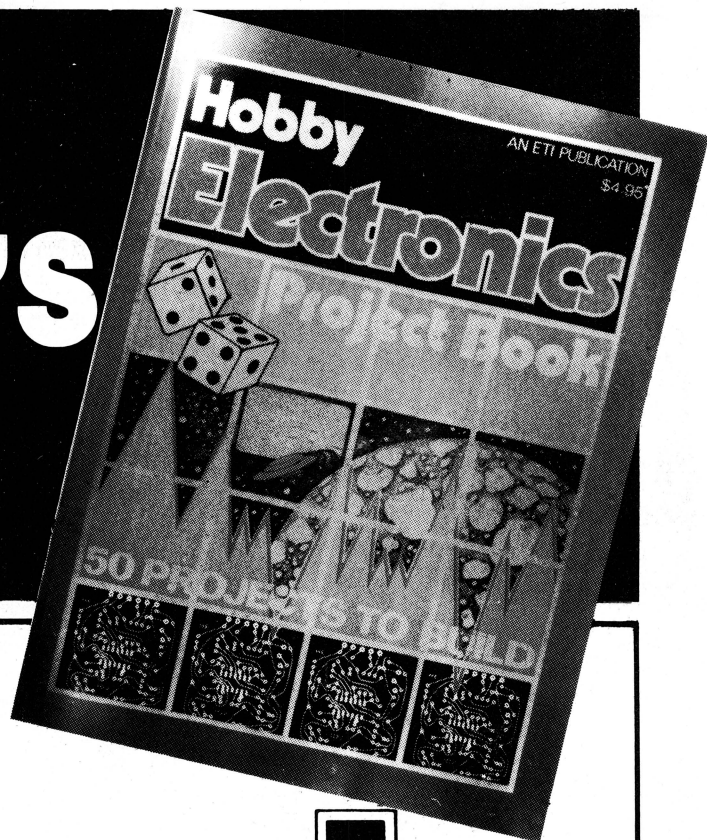

## Hobby Electronics Project Book

### 50 PROJECTS TO BUILD!

Yep — radio projects, audio projects, games, test gear, measuring instruments and miscellaneous devices.

Everything from a radio microphone to a hi-fi amplifier, from an alien invaders game to a frequency meter, from a humidity meter to a negative ion generator.

Plus — all about capacitors and how to read capacitor codes, diodes and how they're used, transistors and transformers, how to read circuit diagrams and understanding components numbering. You can learn all about soldering and how to make printed circuit boards. You never saw an electronics book like this before!

An ETI publication.

# ORGS

## It was just so embarrassing

Life is never dull, especially when there's a party on. And if you're in the mood for people-watching at parties you'll find that it's becoming an even more interesting occupation now.

Eager young man, smoking and drinking, has checked out all the chicks and is making his move. He starts to chat her up but has all his hopes shattered when he hears the strains of that golden-oldie, *Smoke Gets In Your Eyes*, coming from her direction. Just a bit off-putting. Her pendant is giving him a message. He's standing too close and blowing smoke in her face.

Jewellery is no longer only a decorative accessory to the rest of one's outfit, an expensive and pretty item to show off. It can also be practical with a message, thanks to US designer Mary Ann Scherr. Although undoubtedly the embarrassed ones who have been caught out won't be too impressed with her designs.

She makes necklaces, belts and bracelets that double as smoke sensors or bad breath detectors, warn of bad posture and sagging stomachs, let you know how much you fancy that attractive man in the corner and even let you know when you are about to nod off.

Mary Ann's pendant contains a smoke sensor and a music box which, at the first hint of any kind of smoke, gives you a few bars of the song *Smoke Gets In Your Eyes*. Not the sort of thing you'd want to have around if you were lighting up in a dark corner.

But things could be worse. The eager young man has passed the first test and is doing quite well. He's bending low over the lovely young lady, looks deep into her eyes, his lips almost touching hers and then her necklace starts blinking bright red. It's telling her (and him) he stinks of alcohol, onions, garlic or just plain bad breath.

Hullo. I'm John Cleese and this is a film I have made for ETI project builders. In it I describe everything that can possibly ever go wrong with a project and at the end, a bit of advice... a smashing rendition of 'Always Look on the Bright Side of Life'!



Then there's the fancy-scrrolled silver bracelet that buzzes when your heart starts to race and your pulse gets more rapid when that special man you've had your eye on all night makes an obvious move in your direction. This one is for those people who didn't know that they were excited.

For people with poor posture, Mary Ann has come up with a belt that gives off an electronic signal whenever your stomach starts to sag. That could be quite a shock for some people.

The 'no-nod' device is attached to a pair of glasses or a headband and a

beeper goes off when the wearer's head starts to nod down towards his chest. I suppose explaining the 'beep' at a boring dinner party could be less embarrassing than apologising for falling asleep at the table.

This particular device was originally designed for children suffering from cerebral palsy to signal them to keep their heads up. And now the military brass at the Pentagon are interested in it. They feel that a special headset, with a special built-in 'no-nod' capability, would be just the thing for sentries on duty at missile bases.

# The range of Hi-Fi equipment you thought was beyond your means is now within your grasp.

## RECEIVERS

## SEPARATE AMPS

## CASSETTE DECKS

INTEGRATED AMPS  
TUNERS  
CASSETTE DECKS  
TURNTABLES  
RECEIVERS  
SEPARATE AMPS  
SPEAKERS  
CARTRIDGES  
HEADPHONES  
SYSTEM COMPONENTS

A Hundred Years of Musical Experience

# YAMAHA HI-FI



Please send me the latest  
Yamaha Hi-Fi catalogue.

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_



Yamaha Hi-Fi Division, Rose Music Pty. Ltd.,  
17-33 Market St., South Melbourne, Victoria. 3205.

MCR/RM 3861 E/R



# BLACK POWER



Pioneer Black Avante Systems give you the very latest in sound technology. Featured here is the G9 system – SA 930 amplifier with power output of 70 watts RMS and auto input selector, plus a TX 930 tuner with 8 FM/AM pre-set station selectors, auto band search and LED frequency indicator. A PL 930 direct drive turntable features an exclusive quartz lock indicator to give you perfect sound reproduction at all times.

The CT 930 cassette deck has 3 motors that are computer co-ordinated for superb musical accuracy. It also features auto reverse, music search and Dolby® B&C noise reduction circuitry. A pair of Pioneer 3-way speakers with maximum output of 70 watts RMS completes the system. It all adds up to maximum sound performance – that's Pioneer Black Avante power.

**PIONEER®**  
Leads the world in sound.

Pioneer Electronics Australia P/L (Incorp. in Victoria), 178-184 Boundary Road, Braeside 3195. Telephone (03) 580 9911. Branches in all states.

Systems and product specifications subject to change without notice.  
\*Dolby is the registered trademark of Dolby Laboratories.